


6/11

MESH CURRENT ANALYSIS

Mesh

A closed path for the flow of current.

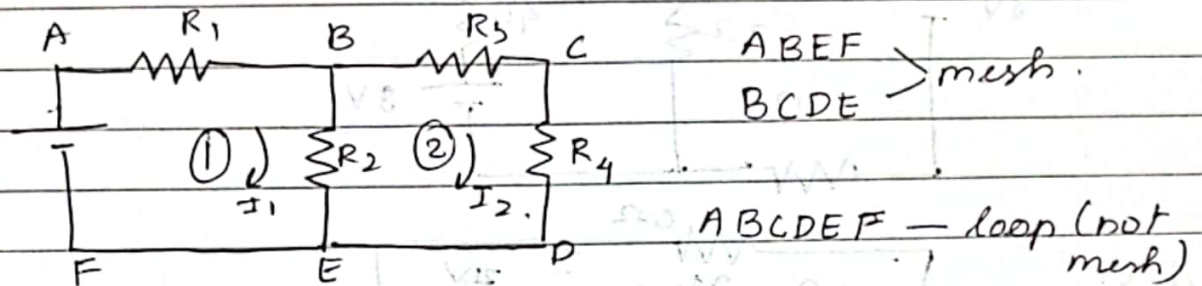KVL - The algebraic sum of voltages in a mesh is 0.



All meshes are loops but not all loops are meshes.

$$V - I_1 R_1 - (I_1 - I_2) R_2 = 0.$$

$$V = I_1 (R_1 + R_2) - I_2 R_2 \quad \text{--- (1)}$$

or


$$-I_2 R_3 - I_2 R_4 - R_2 (I_2 - I_1) = 0 \quad \text{--- (2)}$$

Sign conventions for KVL - refer previous class notes.


METHOD:

- Convert current sources to voltage source.
- Mark different currents in all independent meshes.
- Write KVL equation for meshes.
- Solve for current.

Q. Determine power drawn by 2Ω resistor.

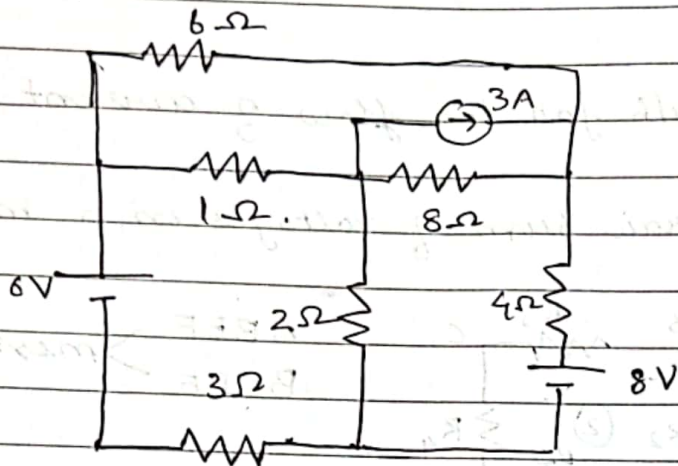

Ans.

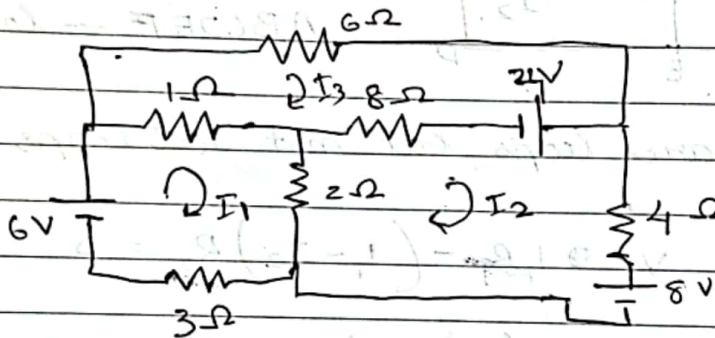

Mesh 1

$$6 - 1 \times (I_1 - I_3) - 2(I_1 - I_2) - 3I_1 = 0.$$

$$6I_1 - 2I_2 - I_3 = 6 \quad \text{--- (1)}$$

Mesh 2

$$-8(I_2 - I_3) + 24 - 4I_2 - 8 - 2(I_2 - I_1) = 0.$$

$$-2I_1 + 14I_2 - 8I_3 = 16 \quad \text{--- (2)}$$

Mesh 3.

$$-6I_3 - 24 - 8(I_3 - I_2) - 1(I_3 - I_1) = 0$$

$$-I_1 - 8I_2 + 15I_3 = -24 \quad \text{--- (3)}$$

Solve: ①, ② & ③.

$$I_1 = 0.99 \text{ A}$$

$$P = I^2 R$$


$$I_2 = 0.587 \text{ A}$$

$$= (0.99 - 0.587)^2 \times 2$$

$$I_3 = -1.22 \text{ A}$$

$$= 0.324 \text{ W}$$

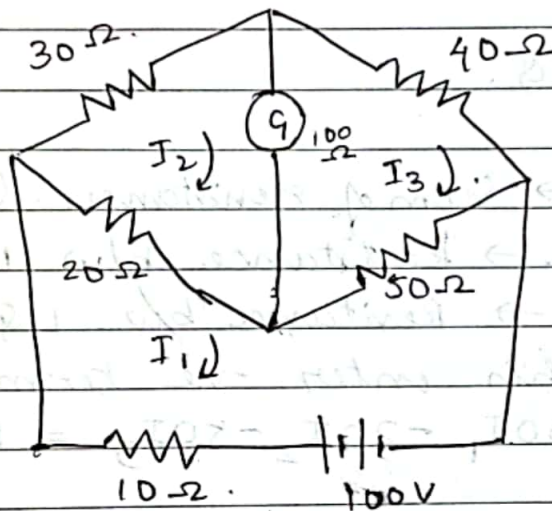9. Determine the current through the galvanometer G.



Ans. Mesh 1

$$100 - 10I_1 - 20(I_1 - I_2) - 50(I_1 - I_3) = 0$$

$$80I_1 - 20I_2 - 50I_3 = 100 \quad \text{--- (1)}$$

Mesh 2

$$-30I_2 - 100(I_2 - I_3) - 20(I_2 - I_1) = 0$$

$$150I_2 - 20I_1 - 100I_3 = 0 \quad \text{--- (2)}$$

Mesh 3

$$-40I_3 - 50(I_3 - I_1) - 100(I_3 - I_2) = 0$$

$$-50I_1 - 100I_2 + 190I_3 = 0 \quad \text{--- (3)}$$

~~$I_1 = 1.678 A$~~

~~$I_1 = 1.678 A$~~

$2.23 A = I_1$

~~$I_2 = 0.262 A$~~

$1.06 A = I_2$

~~$I_3 = 0.589 A$~~

$1.14 A = I_3$

$$I_4 = I_3 - I_2 = 1.14 - 1.06$$

$$= 0.08 A \text{ (upward)}$$

HOW TO WRITE THE EQUATIONS USING INSPECTION

Refer video:

in previous Q.

Mesh 1

For $I_1 \rightarrow$ Sum of resistances $(80 \times I_1)$

(-ve) I_2 b. \rightarrow Resistance b/w 1 & 2 is 20

(-ve) $I_3 \rightarrow$ Resistance b/w 1 & 3 is 50

Wt This enter -ve terminal of 100V

$$\therefore 80I_1 - 20I_2 - 50I_3 = 100.$$

Mesh 2

For $I_2 \rightarrow$ Sum of resistances (150)

(-ve) $I_3 \rightarrow$ on b/w 2 & 3 (100)

(-ve) $I_1 \rightarrow$ b/w 2 & 1 (20)

Mesh 3


For $I_3 \rightarrow$ Sum of resistances (190)

and so on


Q. Draw the mesh.

$$\begin{bmatrix} 30 & -20 & 0 \\ -20 & 50 & -20 \\ 0 & -20 & 20 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ -20 \end{bmatrix}$$

Ans.

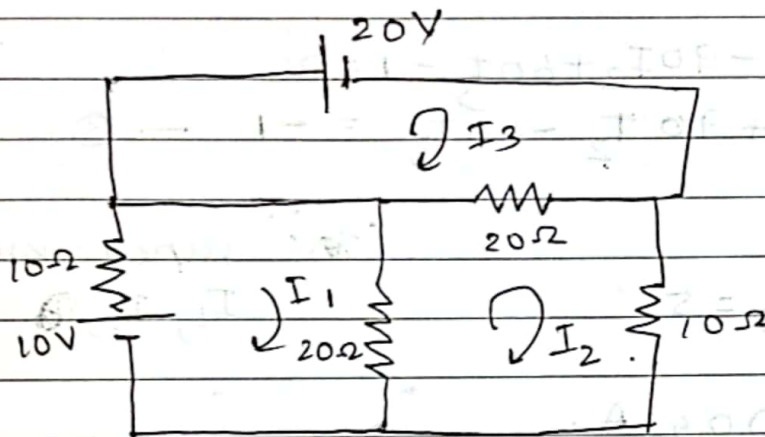

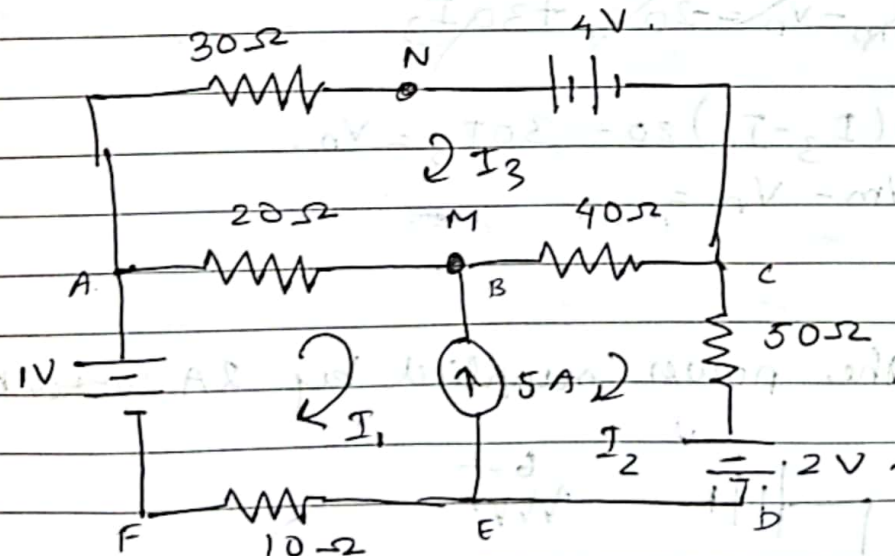Q. Find the power supplied by the 5A current source. also determine the voltage b/w pts M & N.



→ Super Mesh
(due to the
ideal
current
source)

Mesh 3

$$-30 I_3 - 4 - 40(I_3 - I_2) - 20(I_3 - I_1) = 0$$

$$-20 I_1 - 40 I_2 + 90 I_3 = -4 \quad \text{--- (1)}$$

Mesh 1

$$1 - 20(I_1 - I_3) - 40(I_2 - I_3) - 50 I_2 - 2 - 10 I_1 = 0$$

$$-30 I_1 - 90 I_2 + 60 I_3 - 1 = 0$$

$$30 I_1 + 90 I_2 - 60 I_3 = -1 \quad \text{--- (2)}$$

Mesh 2

$$I_2 - I_1 = 5$$

(~~7~~ \therefore super mesh

I_1, I_2, I_3 are +ve)

$$I_1 = -4.004 \text{ A}$$

$$I_2 = +0.9958 \text{ A}$$

$$I_3 = -0.491 \text{ A}$$

$$V_m + 20 I_1 + 30 I_3 = V_n$$

$$V_m - V_n = -20 I_1 + 30 I_3$$

$$V_m = (I_3 - I_1) 20 - 30 I_3 = V_n$$

$$V_m - V_n =$$