
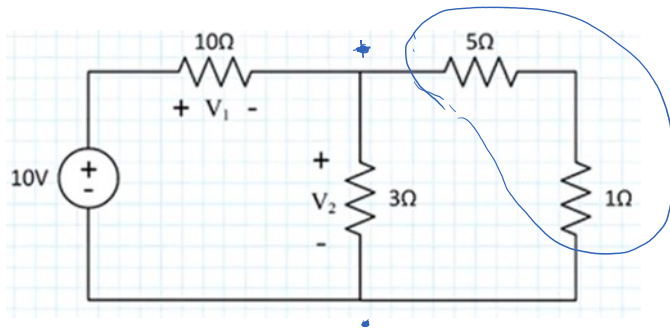


Illustration 1

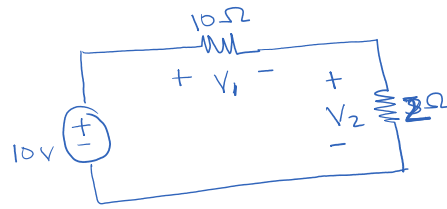Find voltage V_1 and V_2 as marked in the given circuit using voltage division rule.



$$(5+1) \parallel 3 = 2\Omega$$





$$V_1 = V \times \frac{R_1}{R_1 + R_2} = 10 \times \frac{10}{10 + 2} = \frac{100}{12} = 8.333V$$

$$V_2 = V \times \frac{R_2}{R_1 + R_2} = 10 \times \frac{2}{10 + 2} = 1.667V$$

Illustration 2

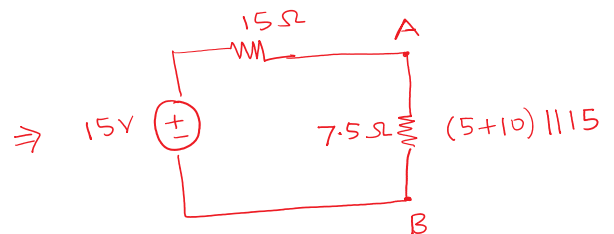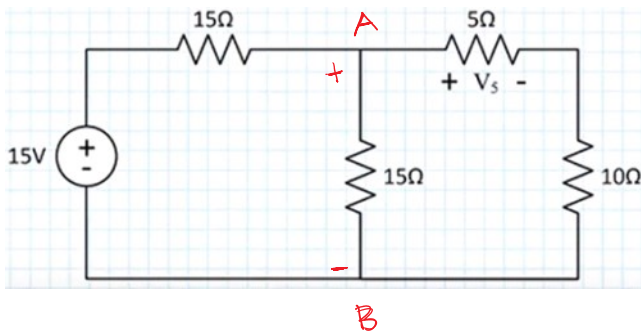Find voltage V_5 as marked in the given circuit using voltage division rule.




$$V_{AB} = \frac{15 \times 7.5}{15 + 7.5} = 5V$$



$$\Rightarrow V_5 = \frac{5 \times 5}{10 + 5} = 1.667V$$

Illustration 3

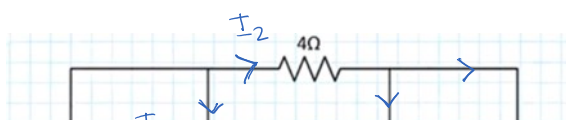Find current I_x as marked in the given circuit using current division rule.


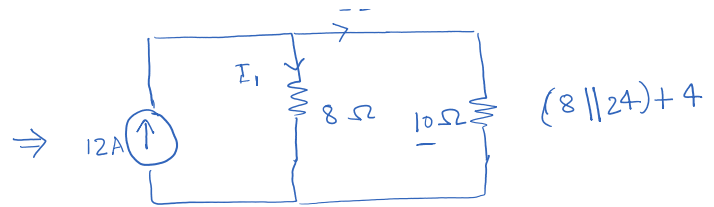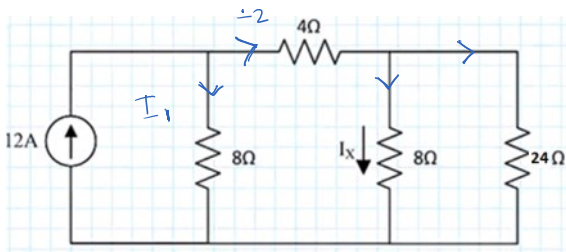
$$R \parallel \frac{R}{n} \Rightarrow \frac{R}{n+1}$$



$$I_2 = \frac{12 \times 8}{8 + 10} = 5.333 \text{ A}$$

$$I_x = \frac{5.333 \times 24}{(24 + 8)} = \boxed{4 \text{ A}}$$


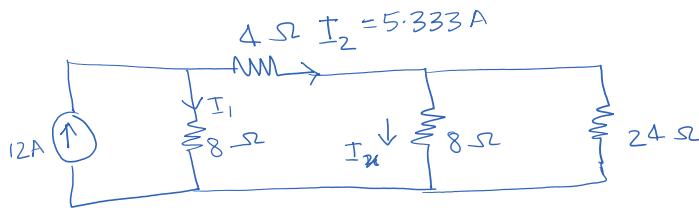


Illustration 4

Find current in 6 kΩ resistor by converting current source to a voltage source.

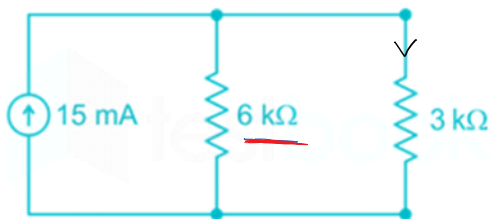The voltage across and current through a resistance (in the converted circuit) cannot be computed if that resistance is involved in the source conversion.



$$I_{3k\Omega} = \frac{15\text{mA} \times 6k\Omega}{9k\Omega} = 10\text{mA} \checkmark$$

$$I_{6k\Omega} = \frac{15\text{mA} \times 3k\Omega}{9k\Omega} = 5\text{mA} \text{ Correct}$$

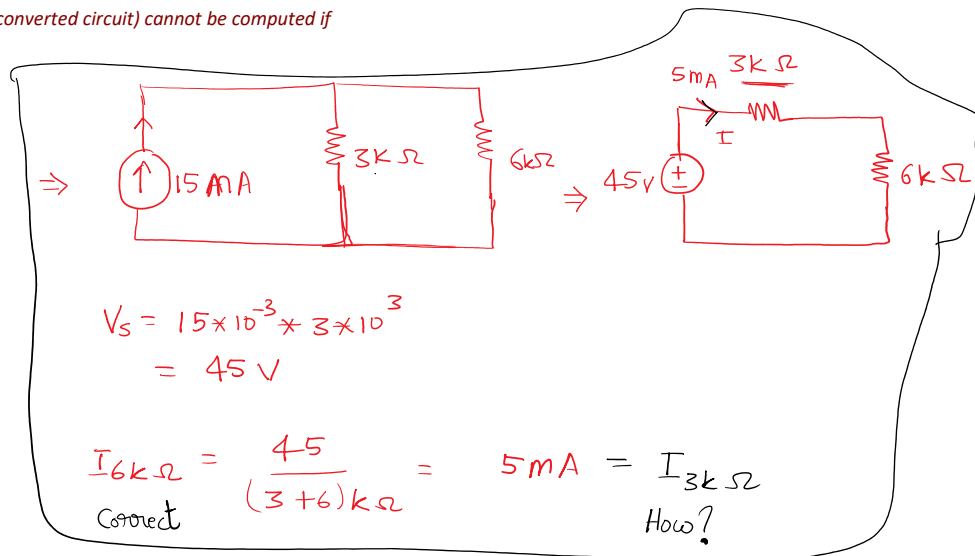


Illustration 5

Reduce the following circuit to a current source in parallel with a resistor across the terminals A & B.

$$1\Omega \quad 2V \quad 2/3 = 1A$$

Reduce the following circuit to a current source in parallel with a resistor across the terminals A & B.


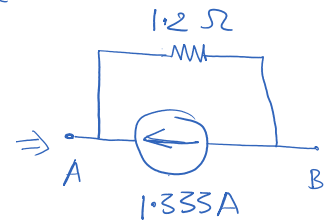
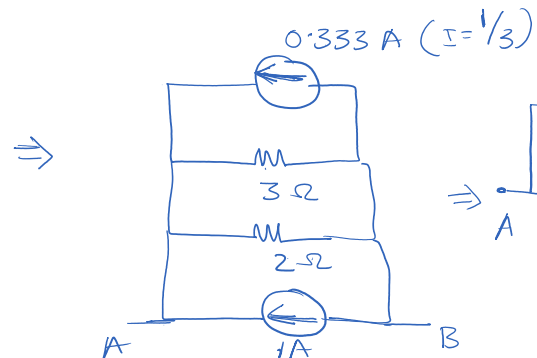
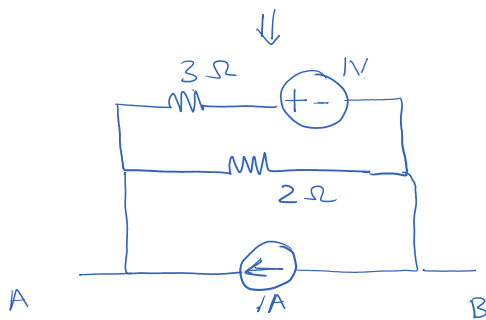
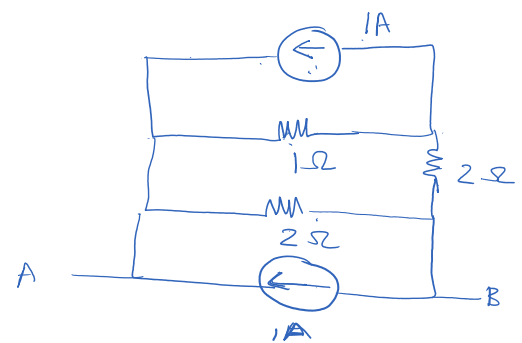
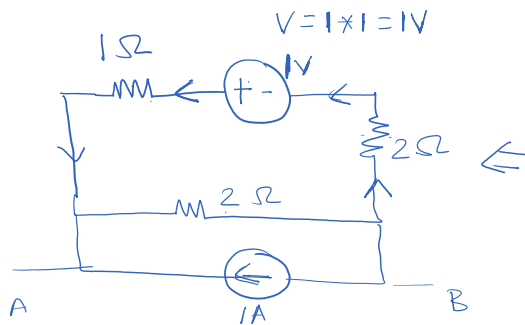
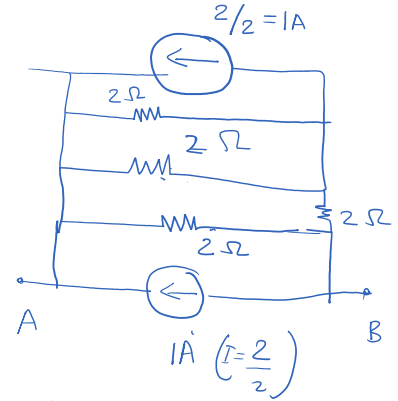
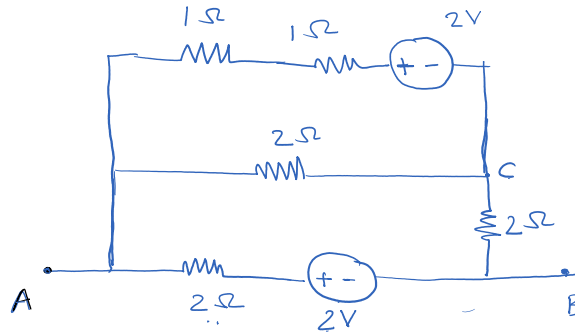
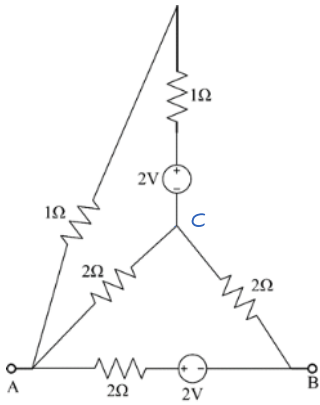
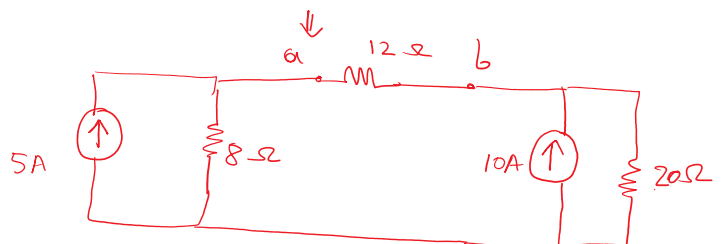
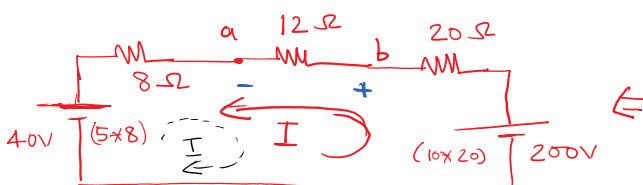
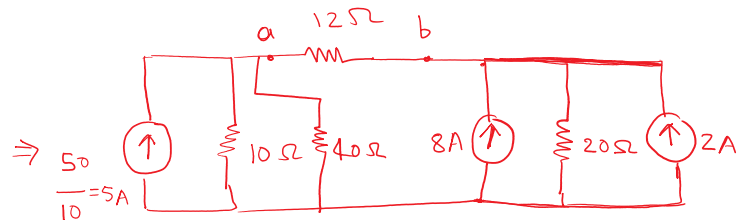


Illustration 6

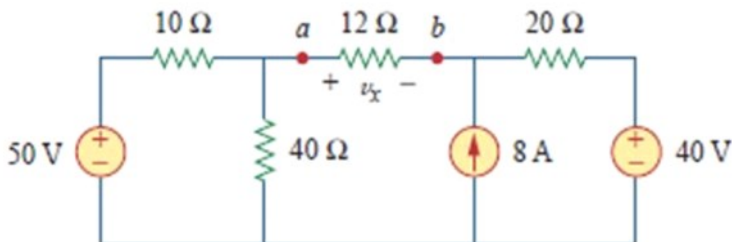Find the voltage across 12 Ω resistor (i.e., V_x) by source transformation method.



$$200 - 20I - 12I - 8I - 40 = 0$$

$$I = 4A$$

$$V_{ba} = 4 \times 12 = 48 \text{ volts}$$

$$V_x = V_{ab} = -V_{ba} = -48 \text{ volts}$$

$$\Rightarrow 40 + 8I + 12I + 20I - 200 = 0$$

$$I = 4A$$



$$40 - 8I - 12I - 20I - 200 = 0$$

$$I = -4A$$


~~TH~~
y

Quiz Question

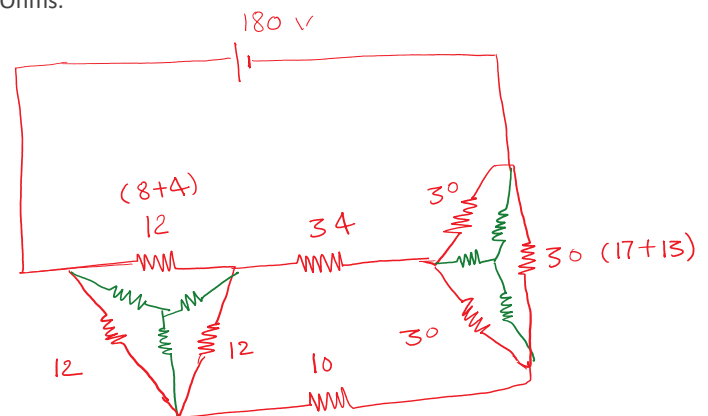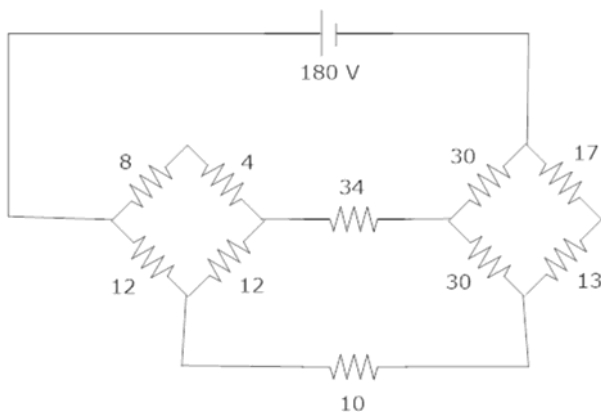
Determine current flowing through 10 Ohm resistor. All resistances are in Ohms.


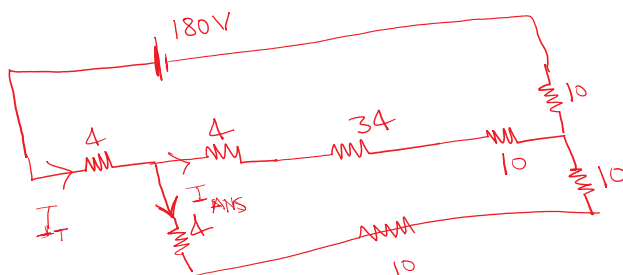
$$\text{Balanced Y-}\Delta: R_{\Delta} = 3R_Y \text{ or } R_Y = \frac{R_{\Delta}}{3}$$



\Rightarrow

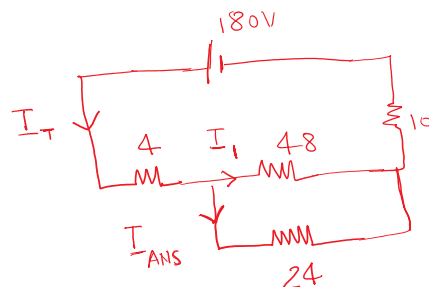

$$I_T = \frac{180}{4 + (48 \parallel 24) + 10}$$

$$= 6A$$

$$I_{ANS} = \frac{I_T \times 48}{48 + 24} = \frac{6 \times 48}{72}$$

$$\text{or } I_{ANS} = 4A$$