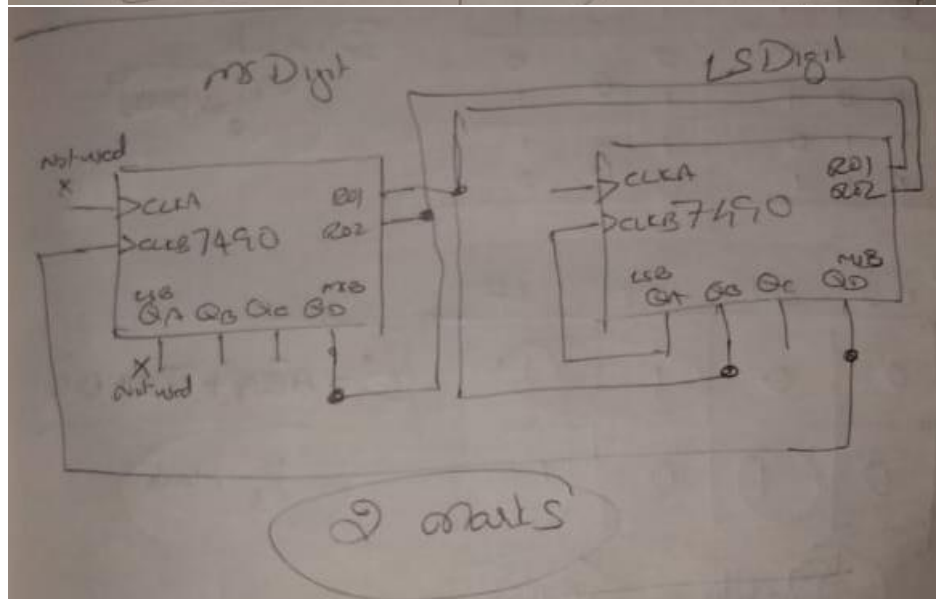
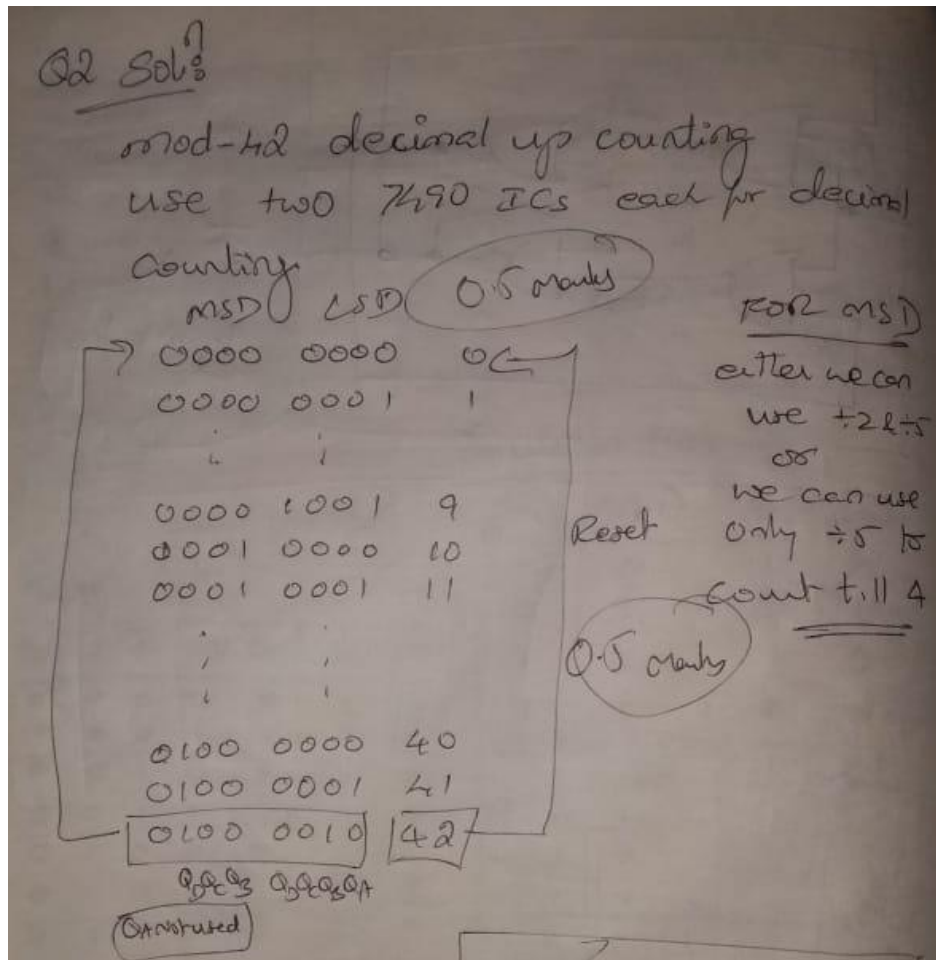


**Q2.** Construct a mod-42 decimal up counting circuit using only asynchronous ICs. Draw the logic diagram. 3 Marks



**Q4.** Function table defines the working of a fictitious AB flip flop. Design the AB flip flop using D flip flop and external gates. **3 Marks**

A	B	Q(t+1)
0	0	0
0	1	1
1	0	Q
1	1	Q'

A

B

Clk

Q

Q4.

A	B	Q(t)	Q(t+1)	input D
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	Q	Q
1	0	1	Q	Q
1	1	0	Q'	Q'
1	1	1	Q'	Q'

Table 1/2 marks

Diagram

1/2 marks

A \ B	00	01	11	10
0	0	0	1	1
1	0	1	0	1

$D = A\bar{B}Q + \bar{A}B + B\bar{Q}$

1/2 marks

1/2 marks Entry

1/2 marks

Circuit 1/2 marks

**Q5.** Design a T flip flop using a basic NOR latch and gates

Q5 Design a T flip flop using a basic NOR latch

Functional Table of T Flip/flop

clk	T	Q(t+1)
0	X	Nochange
1	0	Nochange
1	1	Toggle

NOR-Latch Active High latch

Set	Reset	Q(t+1)
0	0	Q(t) Nochange
0	1	0 Reset
1	0	1 Set
1	1	Invalid

Excitation table

Q(t)	Q(t+1)	Set	Reset
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Truth Table for Set and Reset

Q(t)	Q(t+1)	Set	Reset
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Logic Equations

Set =  $CLK \cdot T \cdot \bar{Q}$

Reset =  $CLK \cdot T \cdot Q$

Circuit Diagram

1/2 Marks