






# ASYNCHRONOUS COUNTER(RIPPLE COUNTER)

   
# Counters:

- Register that goes through prescribed sequence of states upon the application of input pulses is called a counter.
- There are 2 types of counters:
  - *Asynchronous counters (Ripple counters)* : Clock inputs are triggered by transitions of other flipflop.
  - *Synchronous counters* : The clock inputs of all flip flops receive common clock.

- Design a 3 – bit Asynchronous UP counter using positive edge triggered D flip flops.



 - Design a 4 – bit ( MOD 16/ Divide by 16) Asynchronous UP counter using negative edge triggered SR flip flops.
- Design a 4 – bit Asynchronous UP counter using positive edge triggered SR flip flops.








# **DOWN COUNTERS**


MOD4 down  $\Rightarrow$  2-bit

-ve edge triggered (JK, T, SR, D)


$Q_1, Q_0$

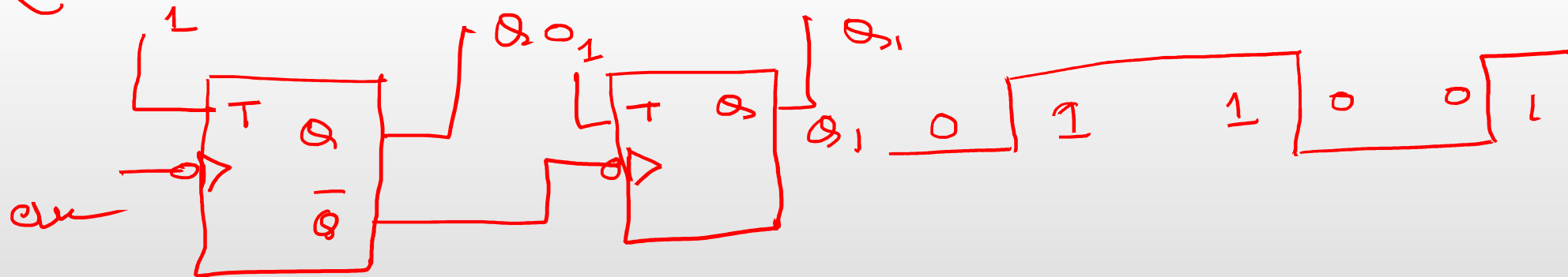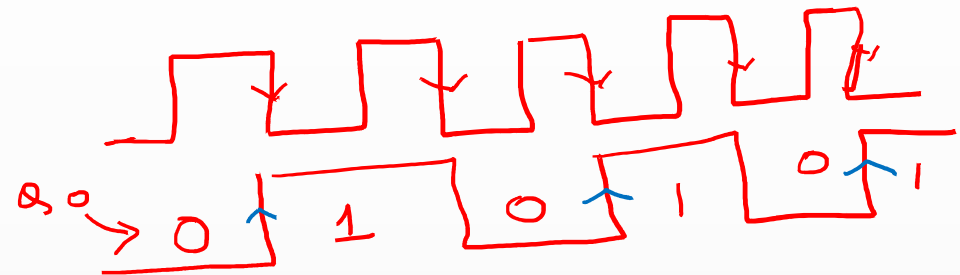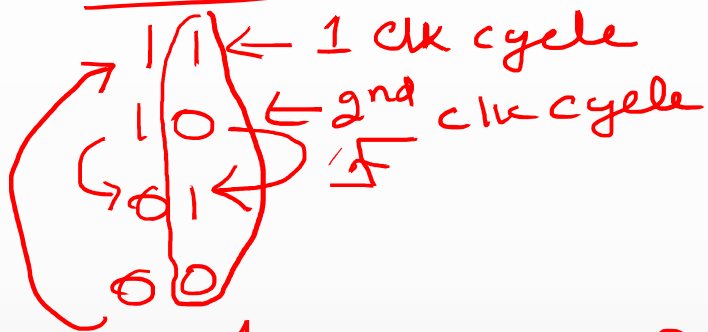

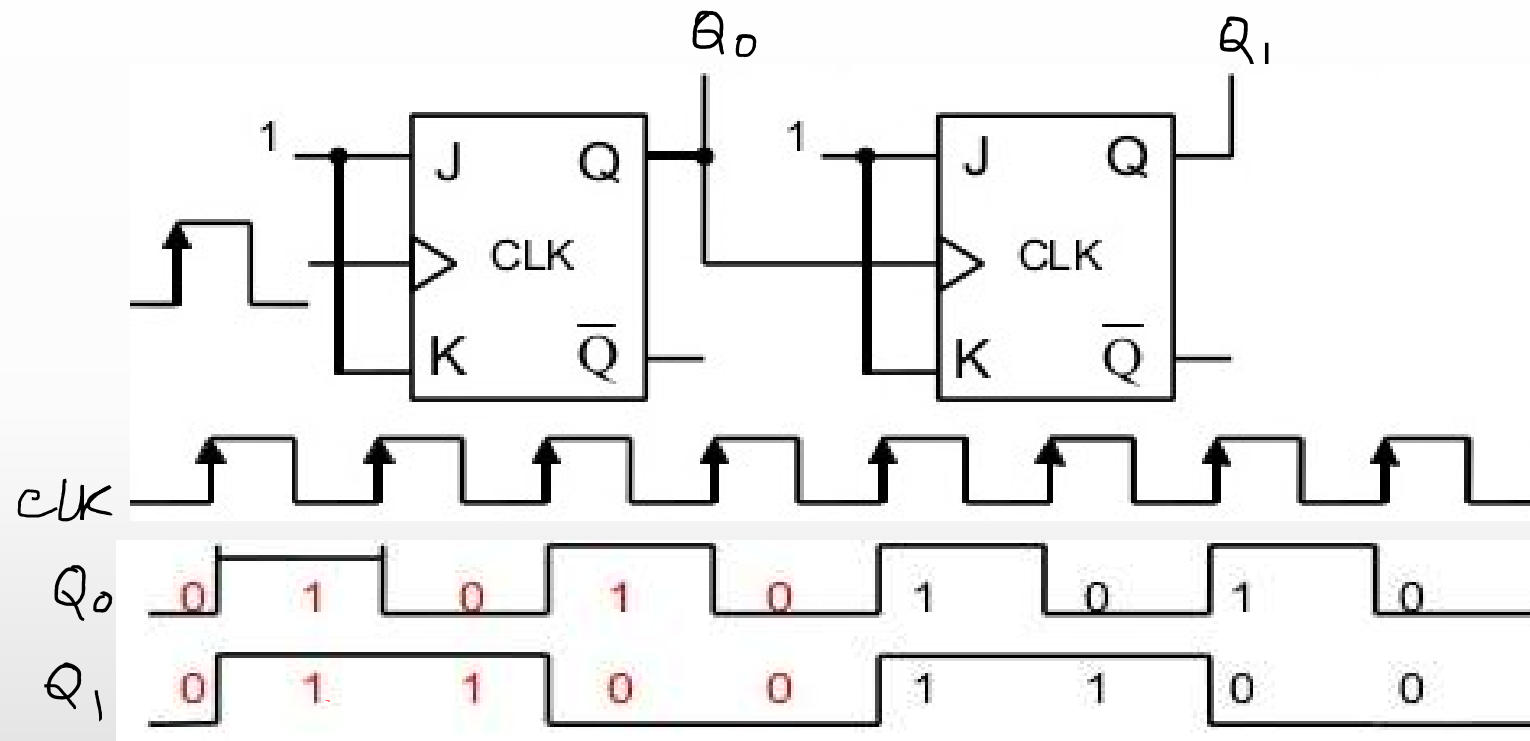- Design a 2 – bit Asynchronous DOWN counter using positive edge triggered JK flip flops.



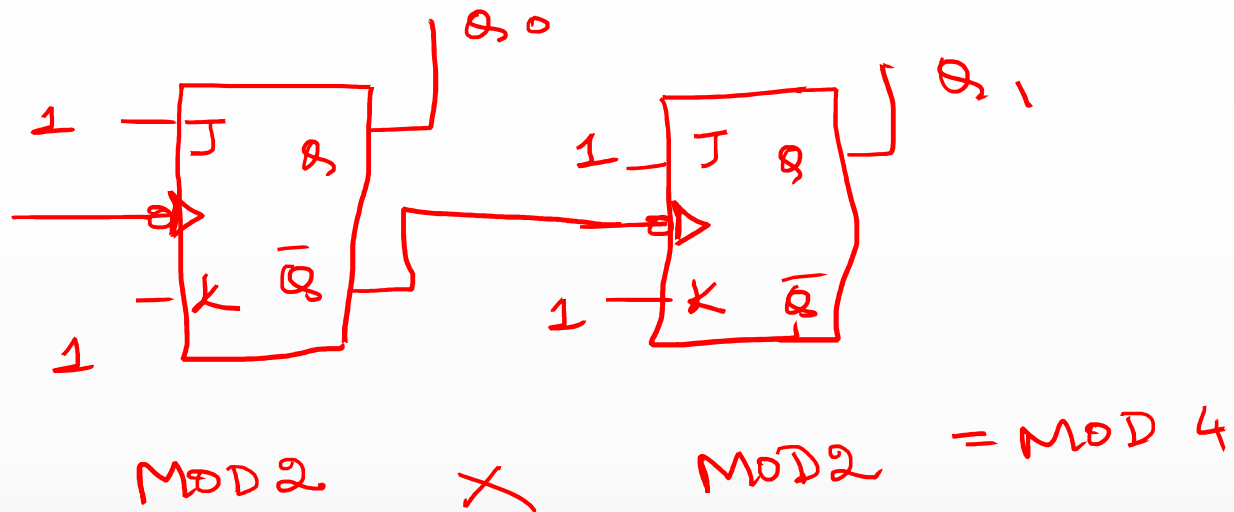- Design a 2 – bit Asynchronous DOWN counter using negative edge triggered JK flip flops.





- Design a 2 – bit Asynchronous DOWN counter using negative edge triggered T flip flops.


- Design a 2 – bit Asynchronous DOWN counter using positive edge triggered T flip flops.

*Draw the circuit*

- Design a 3 – bit Asynchronous DOWN counter using negative edge triggered D flip flops.

$$\text{MOD } 8 \Rightarrow \text{MOD } 4 \times \text{MOD } 2 = \underline{\text{MOD } 2 \times \text{MOD } 4} \quad \checkmark$$
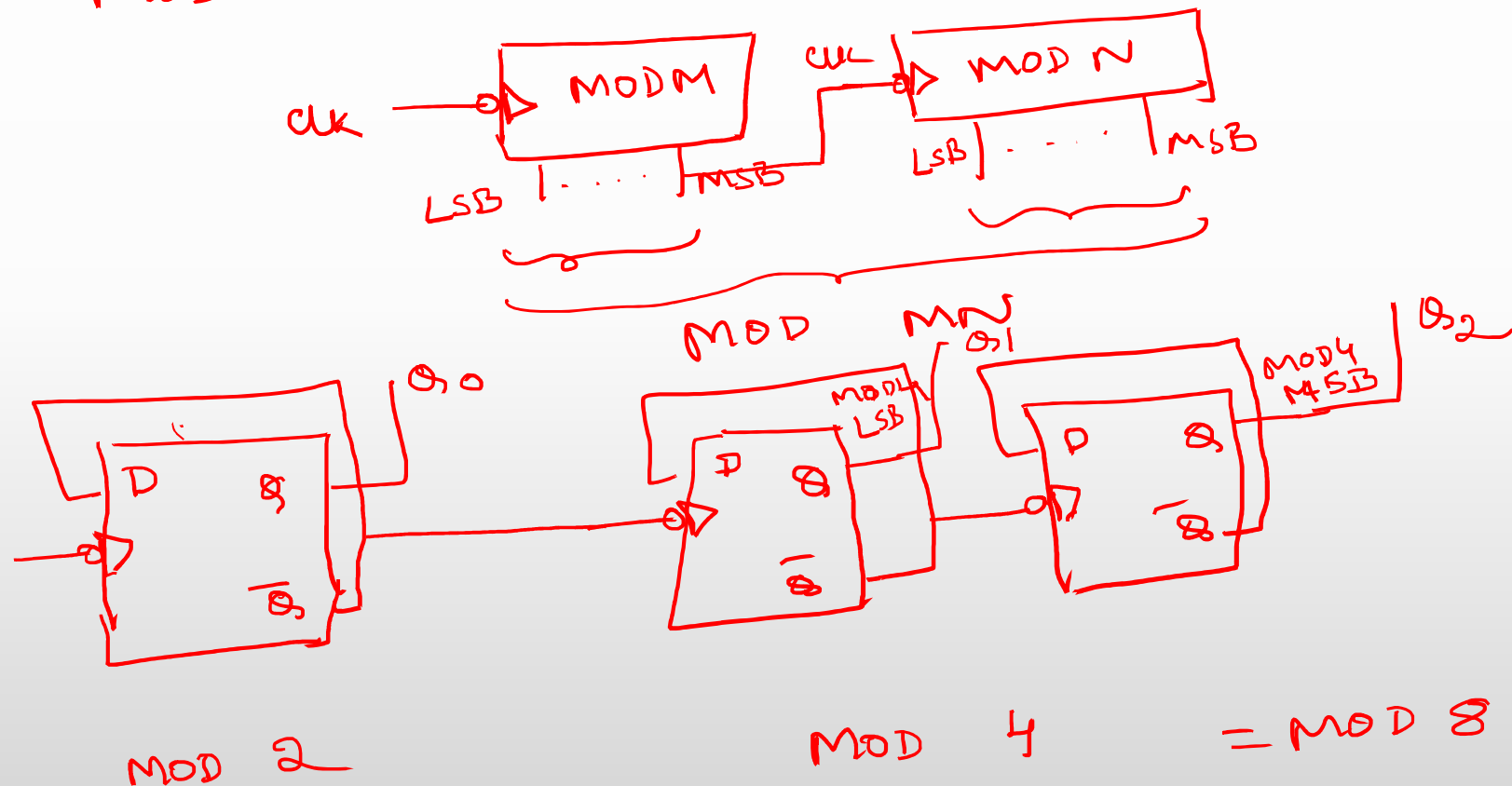
$$\text{MOD } MN \Rightarrow \text{MOD } M \times \text{MOD } N$$




- Design a 3 – bit Asynchronous DOWN counter using positive edge triggered D flip flops.

- Design a MOD 5 Asynchronous UP counter using negative edge triggered JK Flip Flops.

$0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 4 \rightarrow 0$   
 $1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6^{th}$


$000 \rightarrow 001 \rightarrow 010 \rightarrow 011 \rightarrow 100 \rightarrow 101$

decoding State

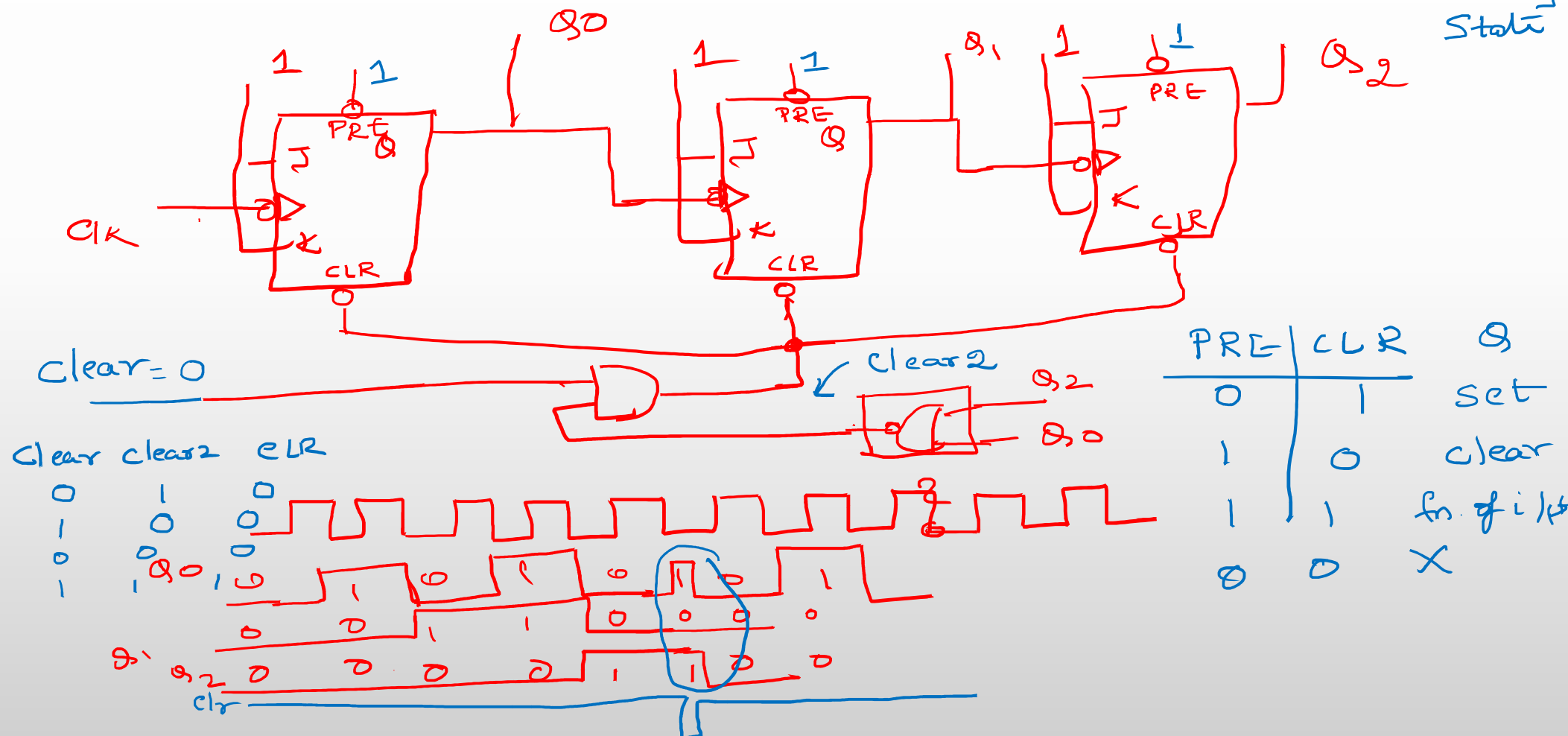

- Design a MOD 10 Asynchronous UP counter using positive edge triggered D Flip Flops.

0-1-2-3-4-5-6-7-8-9-0 *Decade/Decimal*

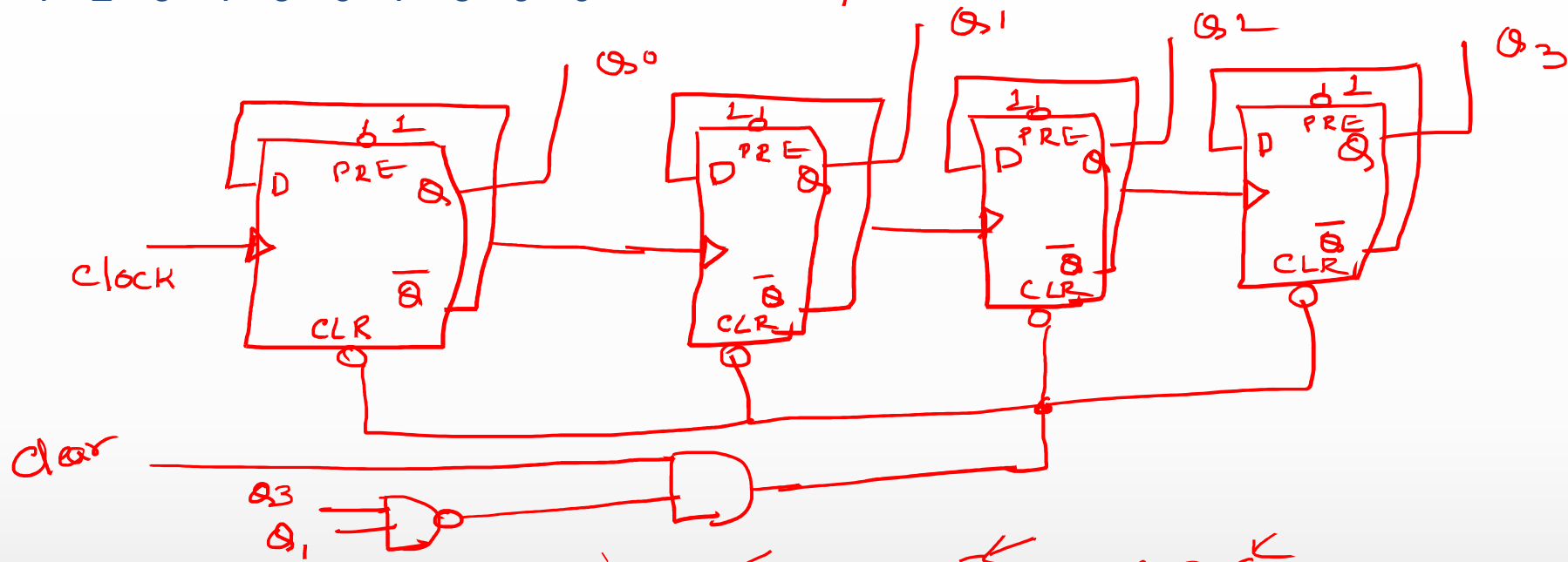

decoding state }  $Q_3 \quad Q_1$   
1010


MOD 4  
{ 00  
01  
10  
11  
=

MOD 5  
{ 000  
001  
010  
011  
100  
4  
1

MOD 6  
{ 000  
001  
010  
011  
100  
101

Design a MOD 5 Asynchronous DOWN counter using positive edge triggered T Flip Flops.

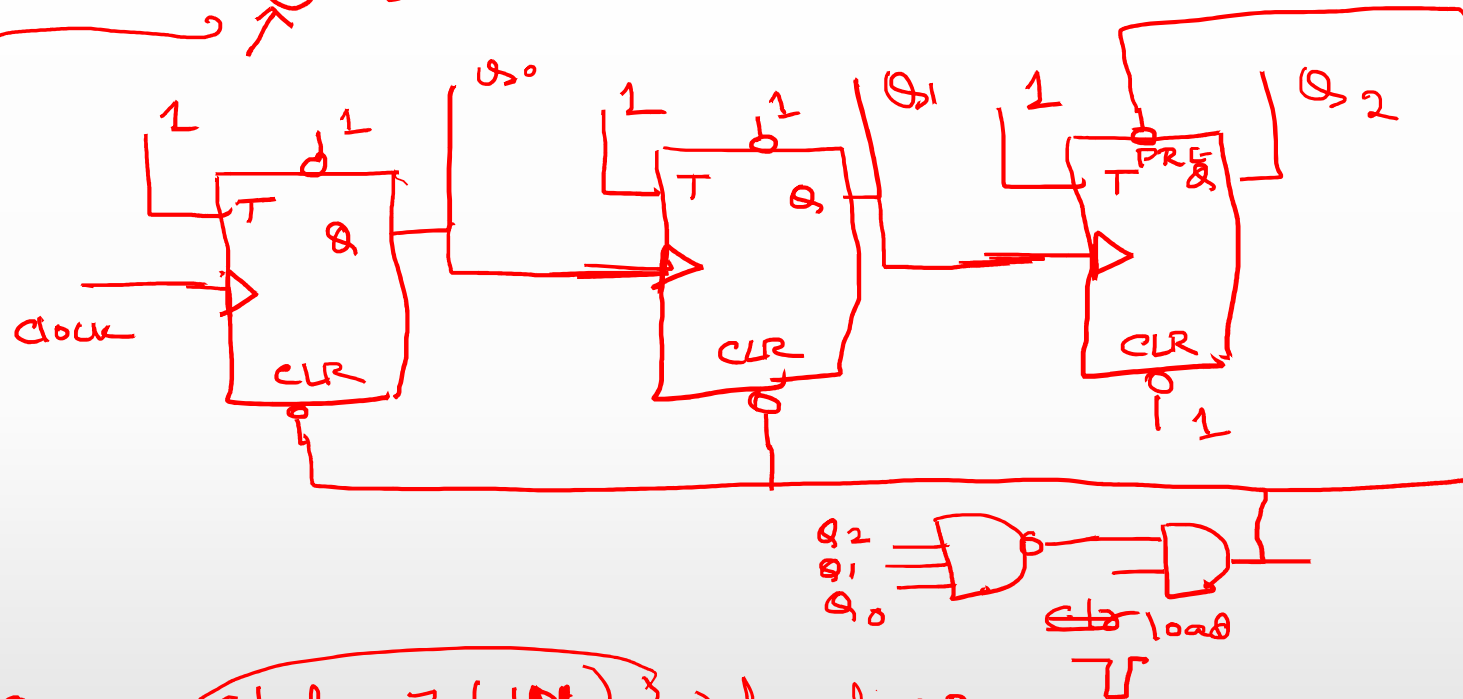4 → 3 → 2 → 1 → 0 → 4 → 3 → 2 → 1 → 0 → ...




State 0 → State 7 (111) → decoding state  
 ↓  
 State 4 (100)  
 $Q_2, Q_1, Q_0$

- Design a MOD 12 Asynchronous DOWN counter using positive edge triggered T Flip Flops.

11->10->9->8->7->6->5->4->3->2->1->0->11

(1011)  
15 (1111)

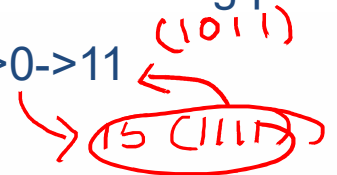



- Design a MOD 18 Asynchronous DOWN counter using positive edge triggered JK Flip Flops.

- Design a 3 bit Asynchronous UP/DOWN counter using negative edge triggered JK Flip Flops.

Design a counter to obtain a 1KHz clock signal from a 10KHz clock signal with 50% duty cycle using negative edge triggered JK Flip Flops. UP counter

Square

$$\text{MOD } 10 = \text{MOD } 5 \times \text{MOD } 2, \quad 4 \text{ ffs.}$$

Dec. count	$Q_3$	$Q_2$	$Q_1$	$Q_0$	clk cycle
0	0	0	0	0	1
1	0	0	0	1	2
2	0	0	1	0	3
3	0	0	1	1	4
4	0	1	0	0	5
8	1	0	0	0	6
9	1	0	0	1	7
10	1	0	1	0	8
11	1	0	1	1	9
12	1	1	0	0	10
	0	0	0	0	
		0	0	1	

Design a MOD 6 Asynchronous counter with 50% duty cycle using negative edge triggered D Flip Flops.

$$f_{\text{output}} = \frac{f_{\text{clk}}}{6}$$

$$\text{MOD } MN = \text{MOD } M \times \text{MOD } N \rightarrow = 2^{\text{power}}$$

$$MN \neq 2^{\text{power}}$$

$$\text{MOD } 6 = \text{MOD } 3 \times \text{MOD } 2 \rightarrow 50\%$$

$$\text{MOD } 2 \times \text{MOD } 3$$

$$Q_2, Q_1, Q_0$$

0	0	0	0
1	0	0	1
2	0	1	0
3	1	0	0
4	1	0	1
5	1	1	0
6	0	0	0

MOD 6

MOD 3			MOD 2		MOD 3	
$Q_2, Q_1$	$Q_0$		$Q_1$	$Q_0$		
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	1	0	1	0
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	1	0	1	0	1
1	1	0	1	0	1	0
1	1	1	1	1	1	1

