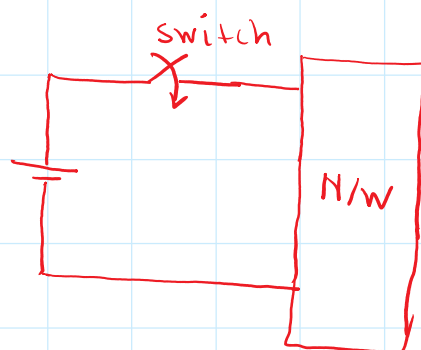


Transient Analysis

Saturday, November 27, 2021

12:44 PM



opened.

$0^- / 0^+$ $\rightarrow t$

$t = 0^-$ Just before the switch is opened or closed.
 $t = 0^+$ Just after the switch is opened or closed.

The current in the inductor cannot change instantaneously

$$i_L(0^-) = i_L(0^+)$$

The voltage in the capacitor cannot change instantaneously


$$v_C(0^-) = v_C(0^+)$$

Growth of Current in an Inductive Circuit

Saturday, November 27, 2021 12:36 PM

$t=0^-$ switch was open.

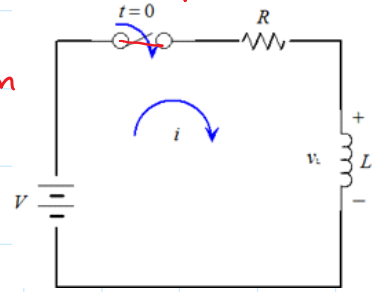* $i_L(0^-) = i_L(0^+) = 0$ initial condition



$$V - V_R - V_L = 0$$

$$V - iR - L \frac{di}{dt} = 0$$

$$0 = iR + L \frac{di}{dt}$$

$$V = iR + L \frac{di}{dt} \rightarrow \text{First order linear differential equation}$$

$$i(t) = i_h(t) + i_p(t)$$

homogeneous solution

Particular solution

$$V = iR + L \frac{di}{dt} + C \frac{d^2 i}{dt^2}$$

$$C D^2 + L D + R = 0$$

Homogeneous solution

characteristic equation

$$L D + R = 0$$

$$D = -\frac{R}{L} = \alpha \text{ Roots of the characteristic equation}$$

$$i_h(t) = A e^{-\frac{R}{L} t} = A e^{\alpha t} \rightarrow \text{homogeneous solution}$$

* Particular solution \rightarrow same form as the input $V \rightarrow dc$

$$i_p(t) = C$$

$$V = \sin(t) \rightarrow \phi$$

$$V = iR + L \frac{di}{dt}$$

$$i_p(t) = C_1 \sin(t) + C_2 \cos(t)$$

$$V = CR + L \cdot 0$$

$$C = \frac{V}{R} \quad i_p(t) = \frac{V}{R}$$


$$i(t) = i_h(t) + i_p(t) \\ = \textcircled{A} e^{-\frac{R}{L}t} + \frac{V}{R}$$

$$i(0^+) = 0$$

$$i(0^+) = A + \frac{V}{R} = 0$$

$$A = -\frac{V}{R}$$
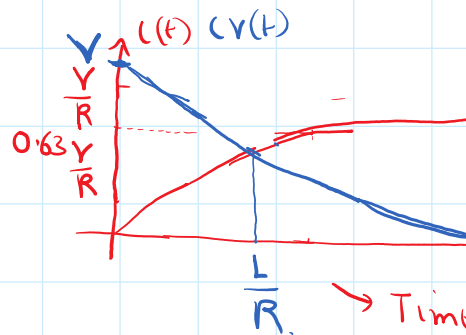
$$i(t) = -\frac{V}{R} e^{-\frac{R}{L}t} + \frac{V}{R} = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$



$$t=0 \quad i=0 \\ t=\infty \quad i=\frac{V}{R}$$

$$t = \frac{L}{R} \quad \frac{V}{R} (1 - e^{-1})$$

$$i\left(\frac{L}{R}\right) = 0.63 \frac{V}{R}$$

$$v_L(t) = L \frac{di_L}{dt}$$

$$= \frac{V}{R} \times \cancel{R} \times \cancel{L} e^{-\frac{R}{L}t}$$


$$v_L(t) = V e^{-\frac{R}{L}t}$$

$$v_R = i_L(t) R$$



Decay of current in an Inductive Circuit

Saturday, November 27, 2021 12:36 PM

$$i(t) = \frac{V}{R} (1 - e^{-t/\tau})$$

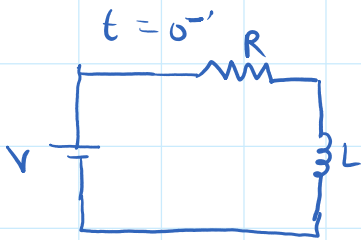

$$i(0^-) = \frac{V}{R} = i(0^+)$$

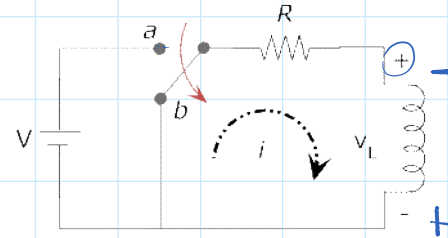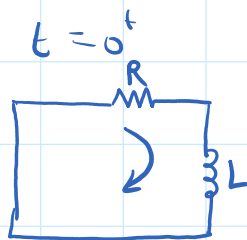

$$-iR - L \frac{di}{dt} = 0$$

$$iR + L \frac{di}{dt} = 0$$

$$i_h(t) + i_p(t)$$

$$i_p(t) = 0$$

$$DL + R = 0$$

$$D = -\frac{R}{L}$$

$$i_h(t) = A e^{-\frac{R}{L}t}$$

$$i(t) = i_h(t) = A e^{-\frac{R}{L}t}$$

$$t=0 \quad i(0^+) = \frac{V}{R}$$

$$\frac{V}{R} = A$$


$$i_L(t) = \frac{V}{R} e^{-\frac{R}{L}t}$$

$$v_L(t) = L \frac{di_L}{dt} = L \frac{V}{R} \times -\frac{R}{L} e^{-\frac{R}{L}t}$$

$$v_L(t) = -V e^{-\frac{R}{L}t}$$

$$V_L(t) = -V e^{-\frac{R}{L}t}$$

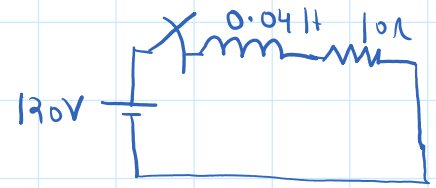- A coil of inductance 0.04 H and resistance 10 is connected to a 120 V, d.c. supply. Determine
- (a) the final value of current.
- (b) the time constant of the circuit.
- (c) the value of current after a time equal to the time constant from the instant the supply voltage is connected.
- (d) the expected time for the current to rise to within 1% of its final value.



$$I(\infty) = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$I(\infty) = \frac{V}{R} = \frac{120}{10} = 12A$$

$$\tau = \frac{L}{R} = \frac{0.04}{10} = 0.004 \text{ sec}$$

$$\begin{aligned} I(\tau) &= 0.63 \frac{V}{R} \\ &= 0.63 \times 12 \\ &= 7.56A. \end{aligned}$$

$$\frac{1\% \text{ of } \frac{V}{R}}{\text{final value}}$$

$$I_L(t) = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$\frac{\cancel{V}}{\cancel{R} \times 100} = \frac{\cancel{V}}{\cancel{R}} (1 - e^{-\frac{t}{0.004}})$$

$$t = 18.421 \text{ ms.}$$

- An R-L series circuit is designed for a steady current of 250mA. A current of 120 mA flows in the circuit at an instant 0.1 sec after connecting the supply voltage. Calculate i) time constant of the circuit ii) the time from closing the circuit at which the circuit current has reached 200 mA.

$$\frac{V}{R} = 250 \text{ mA}$$

$$I_L(t) = \frac{V}{R} \left(1 - e^{-\frac{t}{\tau}}\right)$$

$$120 \text{ mA} = 250 \text{ mA} \left(1 - e^{-\frac{0.1}{\tau}}\right)$$


$$\frac{120}{250} = 1 - e^{-\frac{0.1}{\tau}}$$

$$\tau = 0.1529 \text{ sec.}$$

$$200 \text{ mA} = 250 \text{ mA} \left(1 - e^{-\frac{t}{0.1529}}\right)$$


$$t = 0.2461 \text{ sec.}$$

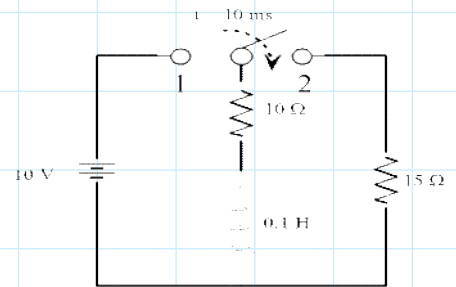- In the network shown in figure, the switch is closed to position 1 at $t = 0$ and is moved to position 2 at 10 ms. Determine $i_L(t)$ & sketch it.



$$0 < t < 10 \text{ ms}$$

$$i_L(0^-) = 0 \quad i_L(0^+)$$

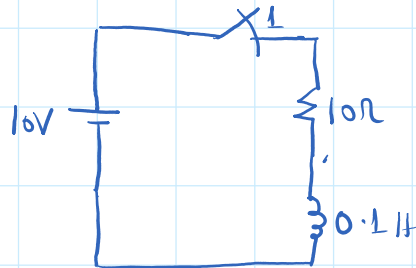


$$\begin{aligned} i_L(t) &= \frac{V}{R} (1 - e^{-\frac{R}{L}t}) \\ &= \frac{10}{10} (1 - e^{-0.1t}) \\ i_L(t) &= (1 - e^{-100t}) \end{aligned}$$

2)

$$t > 10 \text{ ms.}$$

$$i_L(0^-) = i_L(0^+)$$

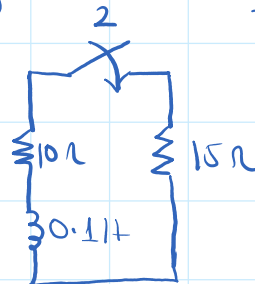

$$= 1 - e^{-100 \times 10 \times 10^{-3}} = 0.63 \text{ A}$$

$$i_L(t) = 0.63 e^{-\frac{25}{0.1}(t-10\text{ms})}$$

$$i(t) = \begin{cases} 1 - e^{-100t} & 0 \leq t < 10 \text{ ms} \\ 0.63 e^{-\frac{25}{0.1}(t-10\text{ms})} & t \geq 10 \text{ ms.} \end{cases}$$

Ans: (a) 12A ; (b) 4ms (c) 7.58A (d) 18.421ms

Ans: i) Time constant = 0.1529 s ii) $t = 0.2461$ s

