



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)




Basic Electrical Technology


LECTURE 4 – 30 OCTOBER 2021

- NETWORK REDUCTION

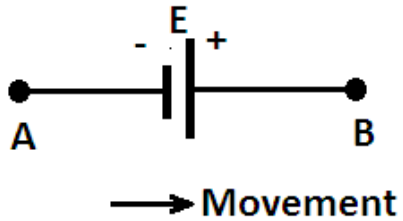
Sign Convention for Kirchhoff's Voltage Law (KVL)



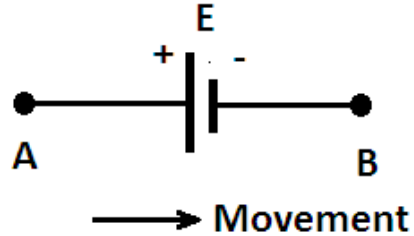
Rise in potential, because we are going negative terminal of the battery to positive terminal.
Therefore, $\text{EMF} = +E$



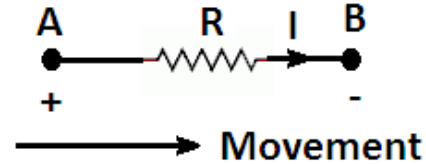Fall in potential, because we are going positive terminal of the battery to negative terminal.
Therefore, $\text{EMF} = -E$



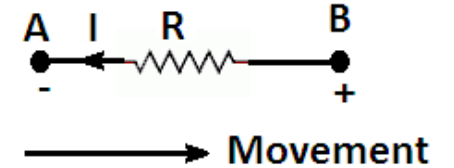
Fall in potential, because we are going in the direction of current.
Therefore, voltage drop $= -IR$




Rise in potential, because we are going in opposite direction of current.
Therefore, voltage drop $= +IR$

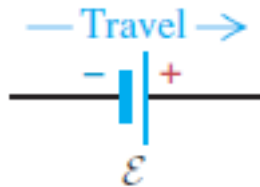(a) Sign conventions for emfs

$+\mathcal{E}$: Travel direction from $-$ to $+$:




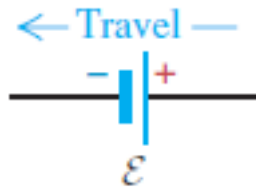$-\mathcal{E}$: Travel direction from $+$ to $-$:



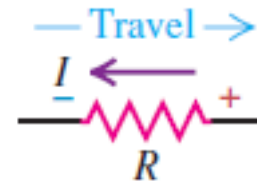(b) Sign conventions for resistors

$+IR$: Travel *opposite* to current direction:



$-IR$: Travel *in* current direction:




Voltage Division (in Series Circuit)

$$V = V_1 + V_2$$

$$V = V_1 + V_1 \frac{R_2}{R_1}$$

$$V_1 = V \frac{R_1}{R_1 + R_2}$$

$$V_2 = V \frac{R_2}{R_1 + R_2}$$

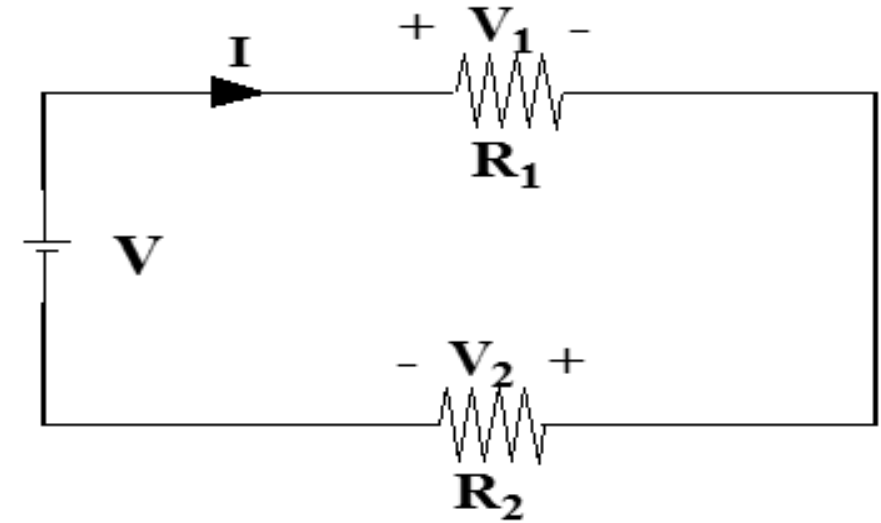

Current Division (in Parallel Circuit)

$$I = I_1 + I_2$$

$$I = I_1 + I_1 \frac{R_1}{R_2}$$

$$I_1 = I \frac{R_2}{R_1 + R_2}$$

$$I_2 = I \frac{R_1}{R_1 + R_2}$$


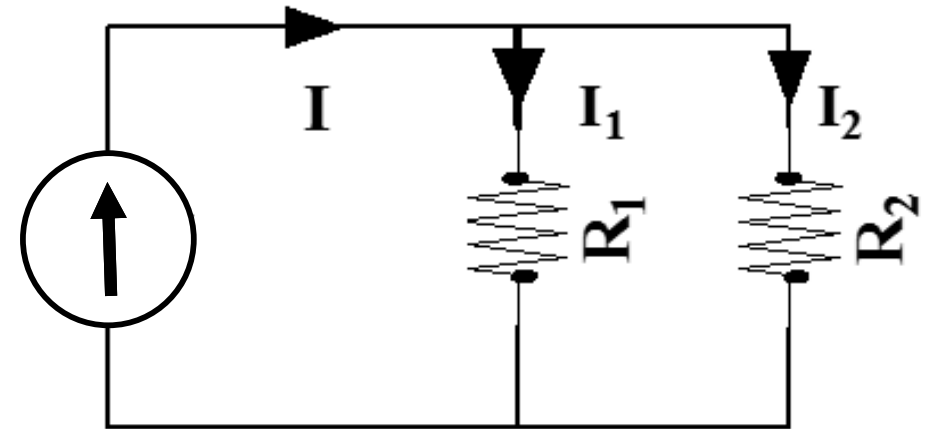


Illustration 1

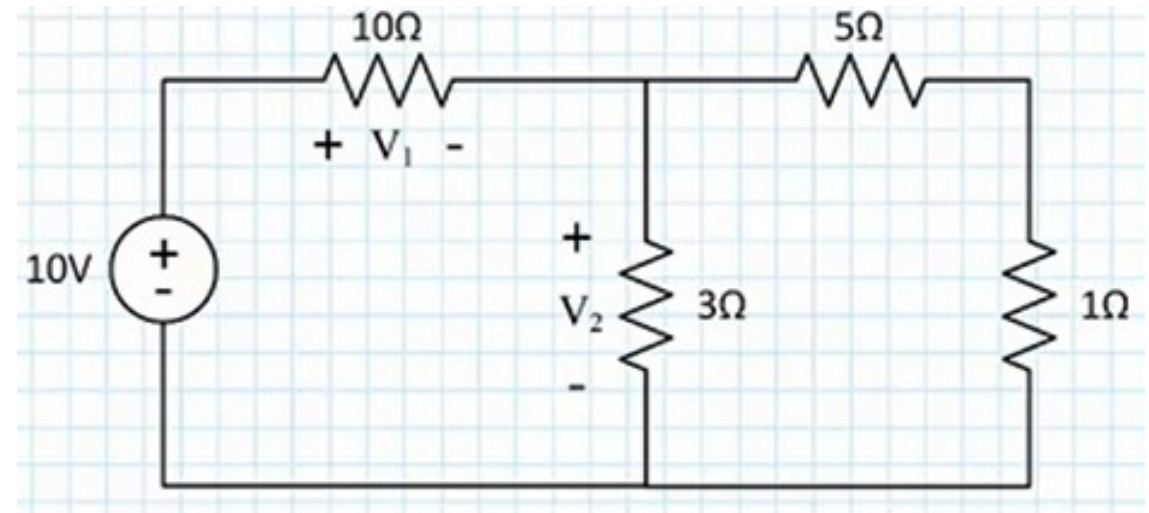

Find voltage V_1 and V_2 as marked in the given circuit using voltage division rule.




Ans: 8.333 V and 1.667 V

Illustration 2



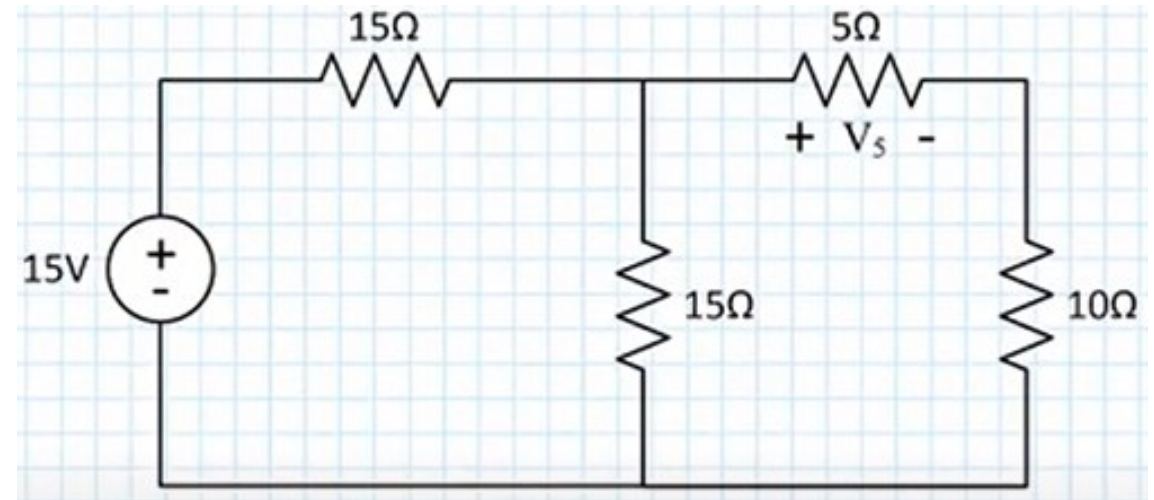Find voltage V_5 as marked in the given circuit using voltage division rule.




Ans: 1.667 V

Illustration 3



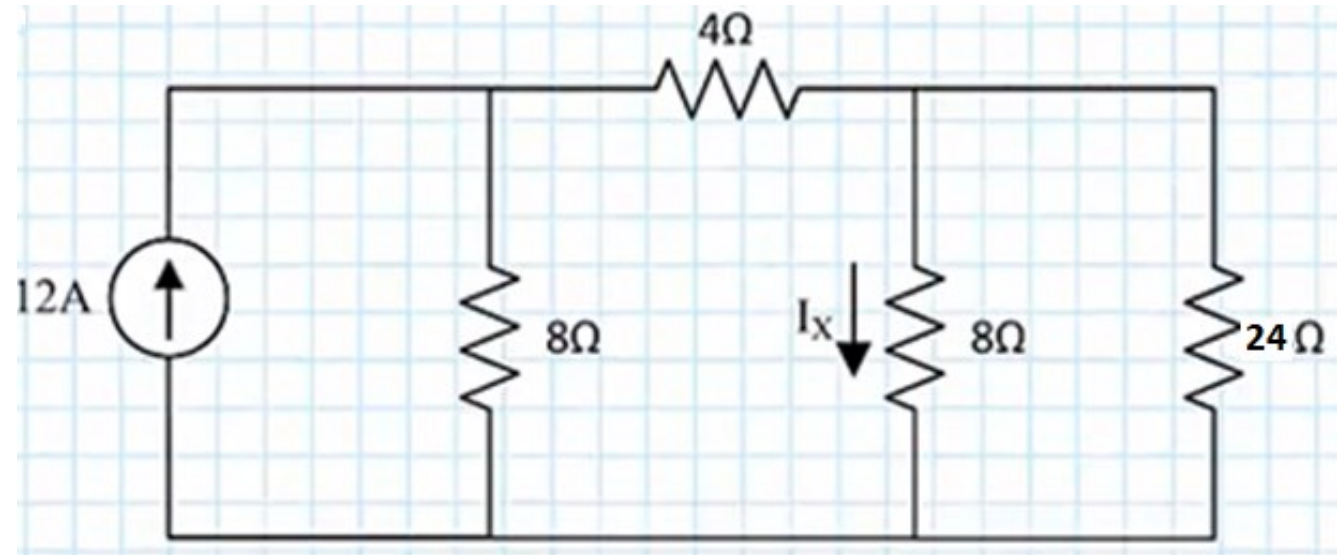Find current I_x as marked in the given circuit using current division rule.



Ans: 4 A



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)



Source Transformation


NETWORK REDUCTION TECHNIQUE

Source Transformation




Source Transformation

Practical Voltage source

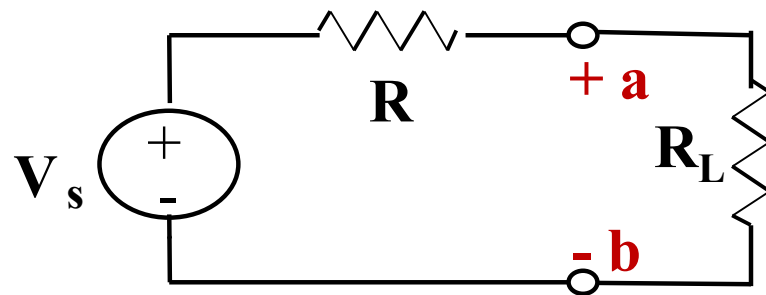


Practical Current source

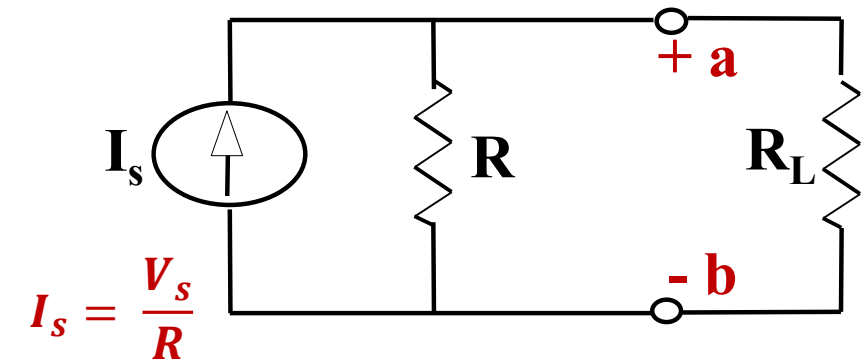

Source Transformation

Practical Voltage source

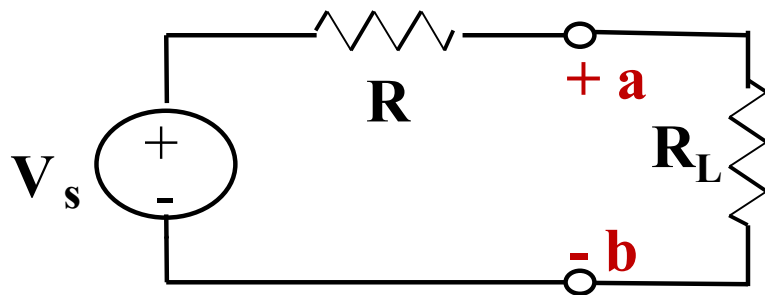

$$V_s = R \times I_s$$



Practical Current source


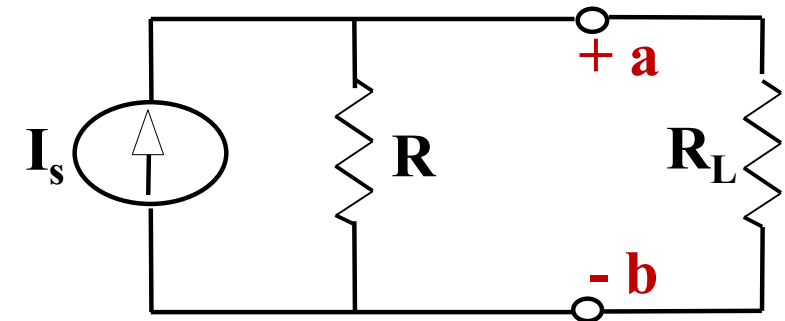


Illustration 4

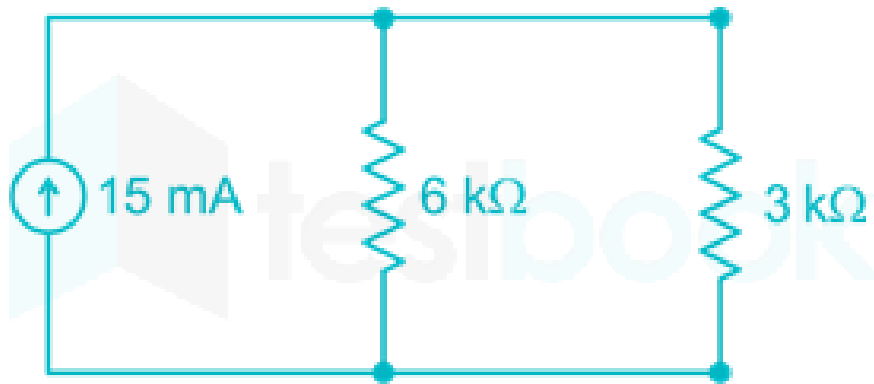
Find current in $6\text{ k}\Omega$ resistor by converting current source to a voltage source.



Ans: 5 mA

Illustration 5


Reduce the following circuit to a current source in parallel with a resistor across the terminals A & B.

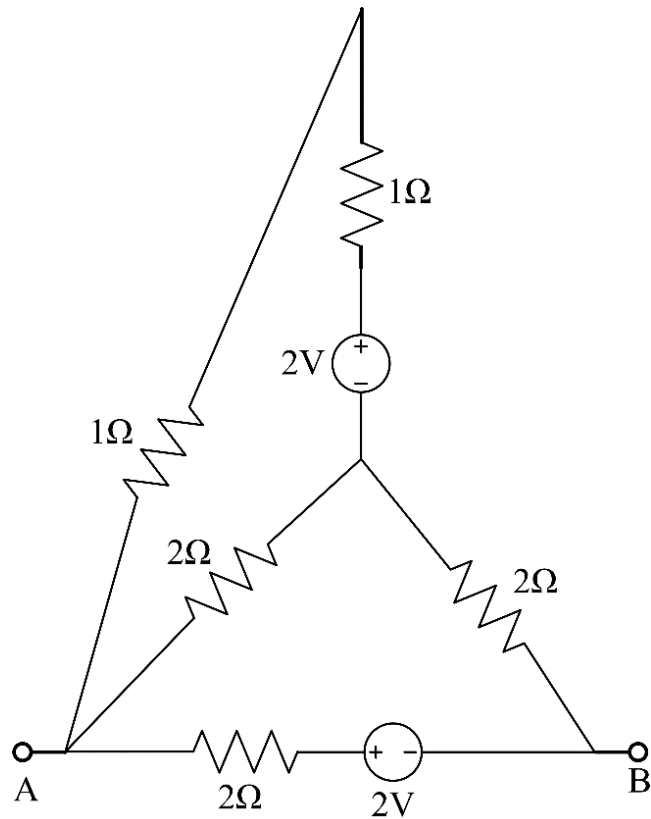

Ans. 1.33 A (from B to A) in parallel with 1.2 Ohms

Illustration 6

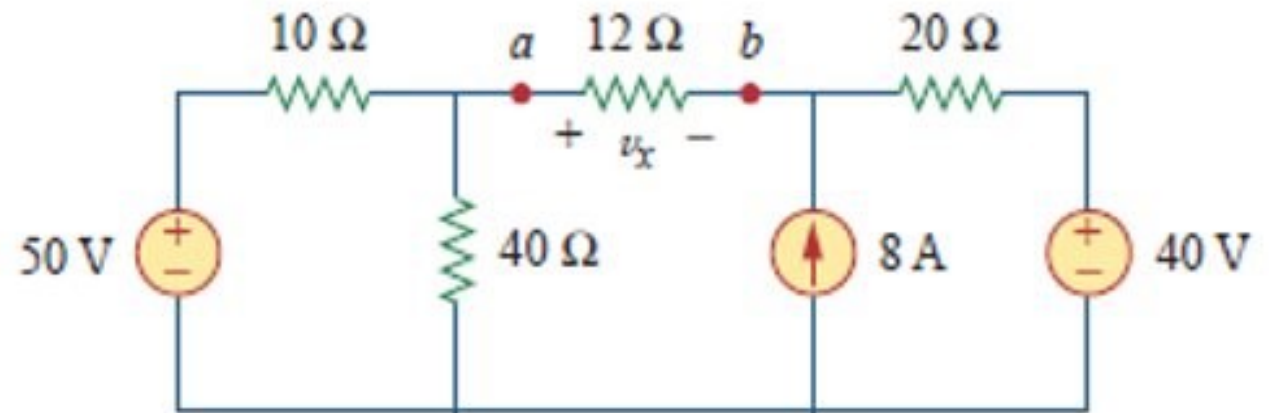Find the voltage across $12\ \Omega$ resistor (i.e., V_x) by source transformation method.




Ans. - 48 V

Homework 1



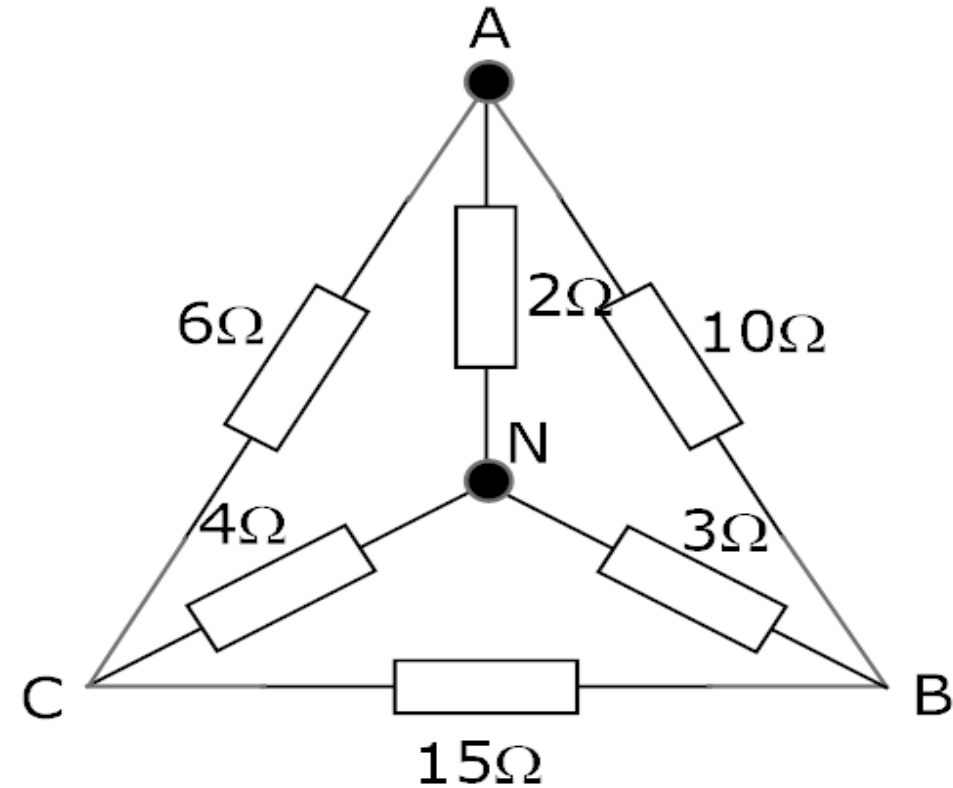Calculate the equivalent resistance across the terminals A and N.




$$R_{AN} = 1.4741 \, \Omega$$

Homework 2



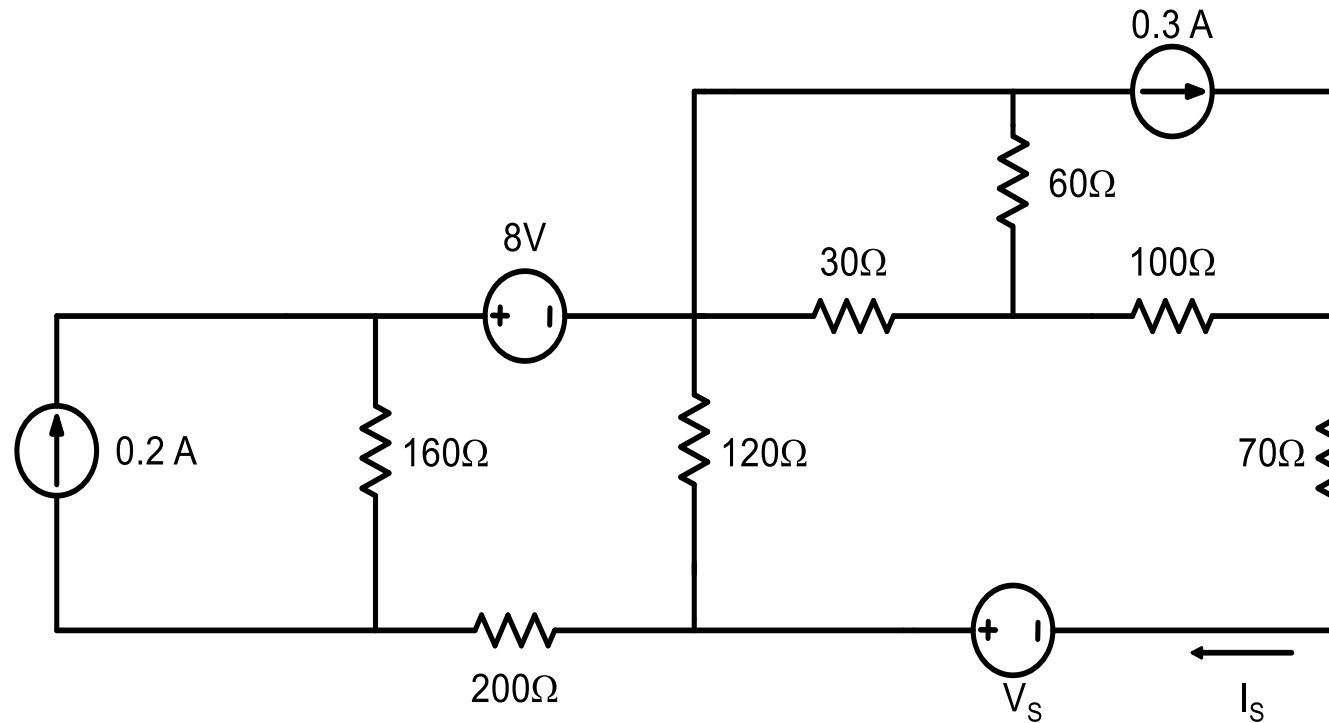In the circuit shown, compute the value of V_s needed to deliver a current of $I_s = 0.25\text{ A}$ using source transformation.



Ans: $V_s = 28\text{ V}$



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)




Quiz Time (Ungraded)

Quiz Question



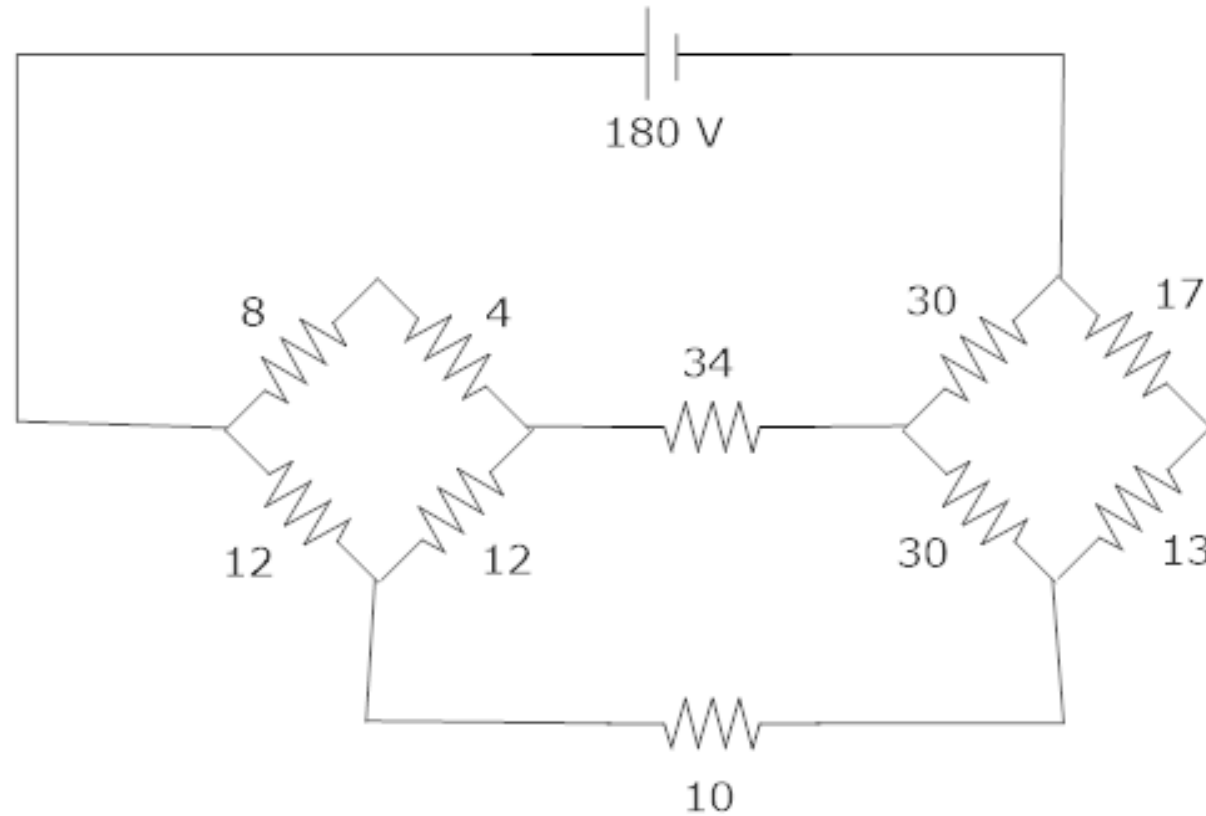Determine current flowing through 10 Ohm resistor. All resistances are in Ohms.



Ans. 4 A