

III sem B.Tech (IT/CCE)

**ICT 2154 Digital Systems
&
ICT 2171 Digital systems and computer organisation**

- **Topics covered**
- MINTERM, MAXTERM
- Writing Boolean expressions for the given truth table
- Design of a combinational circuit for the given problem
- Realization of a logic circuit using Universal gates

MINTERMS & MAXTERMS

- MIN and MAX are means to represent the inputs through logical AND /OR operations
- Consider a 3-variable Boolean function, $F(a,b,c)$
- Prepare a table with 6 columns
- In first column, write all possible binary combinations, possible with three input variables, one below the other. Ex:000,001....., .. . 111
- In 2nd column, write decimal equivalent of all the corresponding input combinations.

Rough

	INPUTS A B C ✓	MINTERMS product	Decimal notation of minterms	Maxterms SUM	Decimal notation of minterms max
0	0 0 0	$\bar{A}\bar{B}\bar{C} = 1.1.1$	m_0	$A+B+C$	M_0
1	0 0 1	$\bar{A}\bar{B}C$	m_1	$A+B+\bar{C}$ <small>0+0+0=0</small>	M_1
2	0 1 0	$\bar{A}B\bar{C}$	m_2	$A+\bar{B}+C$	M_2
3	0 1 1	$\bar{A}BC$	m_3	$A+\bar{B}+\bar{C}$	M_3
4	1 0 0	$A\bar{B}\bar{C}$	m_4	$\bar{A}+B+C$	M_4
5	1 0 1	$A\bar{B}C$	m_5	$\bar{A}+B+\bar{C}$	M_5
6	1 1 0	$AB\bar{C}$	m_6	$\bar{A}+\bar{B}+C$	M_6
7	1 1 1	ABC	m_7	$\bar{A}+\bar{B}+\bar{C}$	M_7

Minterms (Standard products) and Maxterms (standard sums)

Row No.	A B C	Minterms	Maxterms
0	0 0 0	$A'B'C' = m_0$	$A + B + C = M_0$
1	0 0 1	$A'B'C = m_1$	$A + B + C' = M_1$
2	0 1 0	$A'BC' = m_2$	$A + B' + C = M_2$
3	0 1 1	$A'BC = m_3$	$A + B' + C' = M_3$
4	1 0 0	$AB'C' = m_4$	$A' + B + C = M_4$
5	1 0 1	$AB'C = m_5$	$A' + B + C' = M_5$
6	1 1 0	$ABC' = m_6$	$A' + B' + C = M_6$
7	1 1 1	$ABC = m_7$	$A' + B' + C' = M_7$

Write the Boolean function for $f(x, y, z)$ given below

	x	y	z	f
	0	0	0 ✓	1
	0	0	1 ✓	1
2	0	1	0	0 ✓
3	0	1	1	0 ✓
	1	0	0 ✓	1
	1	0	1 ✓	1
	1	1	0 ✓	1
7	1	1	1	0 ✓

$$\begin{aligned}
 f(x, y, z) &= \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}\bar{z} + x\bar{y}z + x y \bar{z} \\
 &= m_0 + m_1 + m_4 + m_5 + m_6 \\
 &= \sum_m(0, 1, 4, 5, 6)
 \end{aligned}$$

$$\begin{aligned}
 f(x, y, z) &= (x + \bar{y} + z) \cdot (x + \bar{y} + \bar{z}) \cdot (\bar{x} + \bar{y} + \bar{z}) \\
 &\quad \begin{array}{l} x=0 \ y=0 \ z=0 \quad 1 \cdot 1 \cdot 1 = 1 \\ x=1 \ y=1 \ z=1 \Rightarrow f = 1 \cdot 1 \cdot 0 = 0 \end{array} \\
 &= M_2 \cdot M_3 \cdot M_7 = \prod M(2, 3, 7)
 \end{aligned}$$

Boolean function can be represented as (i) sum of minterms and (ii) product of maxterms.

Sum of Minterms and product of maxterms expressions

x	y	z	f	
0	0	0	1	0
0	0	1	1	0
0	1	0	0	1 ✓
0	1	1	0	1 ✓
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1 ✓

$$\boxed{A} + \boxed{\bar{A}}B = A + B$$

Sum of minterms : Canonical form ✓

$$\begin{aligned}
 F(x, y, z) &= \underline{x'y'z'} + \underline{x'y'z} + \underline{xy'z'} + \underline{xy'z} + \underline{xyz'} \\
 &= m_0 + m_1 + m_4 + m_5 + m_6 \\
 &= \Sigma (0, 1, 4, 5, 6) \checkmark
 \end{aligned}$$

Sum of product(simplified) : Standard forms

$$F(x, y, z) = \boxed{\bar{y} + x\bar{y}\bar{z}} = \underline{\bar{y}} + \underline{x\bar{z}}$$

Product of maxterms : Canonical form

$$\begin{aligned}
 F(x, y, z) &= (x+y'+z).(x+y'+z') .(x'+y'+z') \\
 &= M_2. M_3. M_7 \\
 &= \Pi (2, 3, 7) \checkmark
 \end{aligned}$$

Product of sum : Standard forms

$$F(x, y, z) = (x+y')(y'+z') \checkmark$$

Rough

Relationship between sum of minterms and product of maxterms

- Sum of minterms : Canonical form

$$\begin{aligned}
 F(x, y, z) &= x'y'z' + x'y'z + xy'z' + xy'z + xyz' \\
 &= m_0 + m_1 + m_4 + m_5 + m_6 \\
 &= \sum_{m_i} (0, 1, 4, 5, 6) \quad \checkmark \checkmark
 \end{aligned}$$

$$\left. \begin{aligned}
 f(x, y, z) &= \\
 \sum m(0, 1, 4, 5, 6) &= \\
 \prod M(2, 3, 7) &=
 \end{aligned} \right\}$$

$$\underline{F'}(x, y, z) = \sum_{m_i} (\underline{2, 3, 7}) = m_2 + m_3 + m_7$$

Taking complement on both sides and applying DeMorgan's theorem

$$\begin{aligned}
 \underline{F} &= F(x, y, z) = (m_2 + m_3 + m_7)' = m_2' . m_3' . m_7' \\
 &= (\underline{x'yz'})' . (\underline{x'yz})' . (\underline{xyz})' = (\underline{x+y'+z}) . (\underline{x+y'+z'}) . (\underline{x'+y'+z'}) \\
 &= M_2 . M_3 . M_7 = \underline{\prod (2, 3, 7)} \Rightarrow \text{Product of Maxterm for } f \\
 &\quad \underline{m_j' = M_j}
 \end{aligned}$$

Express the Boolean function $F(a,b,c) = ab' + c'$ using Sum of minterms and Product of maxterms

$$\overline{c + \bar{c}} = 1$$

- Two methods

1. Identify the missing term and include them in the expression using the postulates : $x+0 = x$, $x.1 = x$, $x+x'=1$, $x.x'=0$
2. Write the truth table from the given expression and then write sum of minterms and product of maxterms

$F(a,b,c) = \underline{ab'} + c'$ using method 1

$$= a\bar{b} \cdot 1 + c' \cdot 1$$

$$\bullet = a\bar{b} \cdot (c + \bar{c}) + \bar{c} \cdot (a + \bar{a})$$

$$= \underbrace{a\bar{b}c + a\bar{b}\bar{c}} + a\bar{c} + \bar{a}\bar{c}$$

$$,, + a\bar{c}(b + \bar{b}) + \bar{a}\bar{c}(b + \bar{b})$$

$$= m_4 + m_5 + m_1 + m_0$$

$$= \sum_m (0, 2, 4, 5, 6)$$

$$\Rightarrow \bar{f}(a,b,c) = \sum_m (1, 3, 7)$$

$$F(a,b,c) = \prod M(1, 3, 7) \Rightarrow \bar{f}(a,b,c) = \prod M(0, 2, 4, 5, 6)$$

$$F(a,b,c) = \underline{ab'} + \underline{c'}$$

$\rightarrow c=0$
 $\rightarrow a=1 \quad b=0$

a	b	c	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$f(a,b,c) = \sum m(0, 2, 4, 5, 6)$$

$$= \prod M(1, 3, 7)$$

Design a combinational circuit that takes 3-bit input and generates an output high whenever the input is a prime number.

Draw the circuit using basic logic gates

$F(A, B, C)$

- ① Truth table
- ② $F = \sum m(\)$ or $\prod M(\)$
- ③ Simplified expression for F
- ④ Draw the ext

①

	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1


$$\frac{\bar{A} \bar{B} \bar{C} + \bar{A} B C}{(\bar{A} B C)}$$

$$F(A, B, C) = \sum m(2, 3, 5, 7)$$

$$= \bar{A} B + A C \checkmark$$

Rough

$$F(A, B, C) = \bar{A}B + AC$$

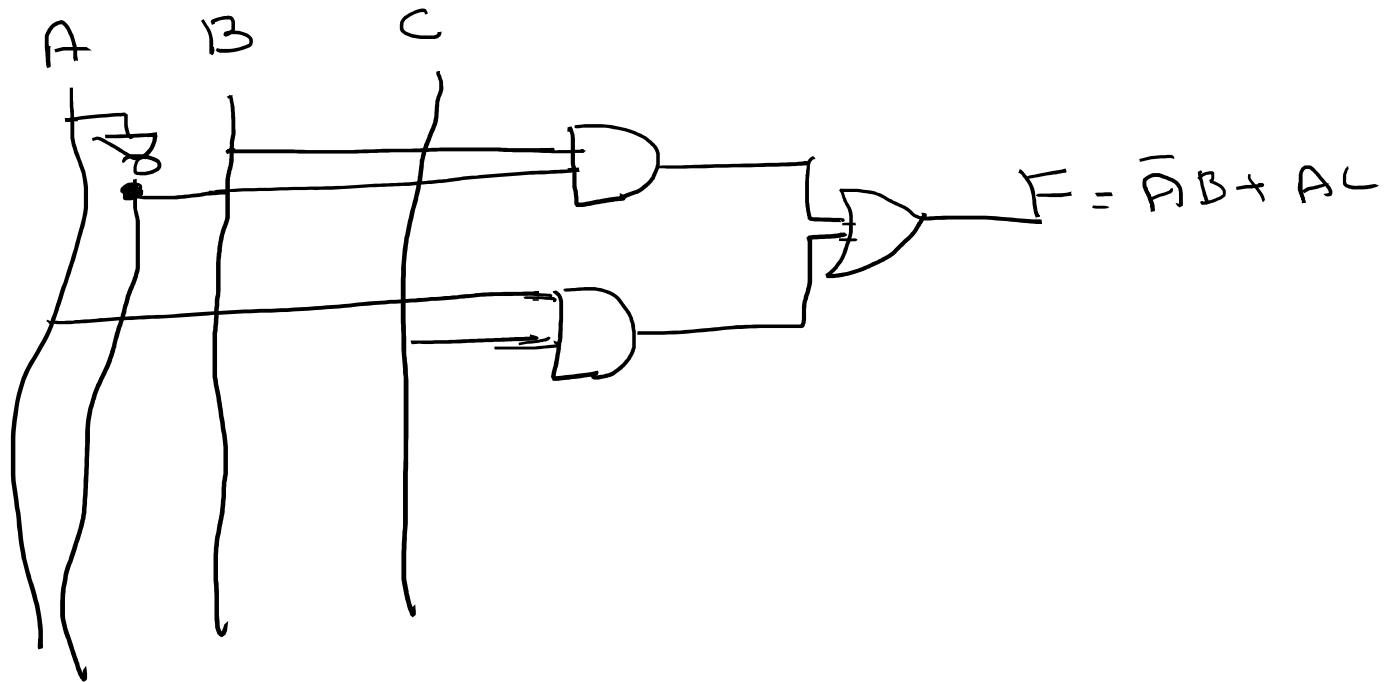

Design a combinational circuit that takes 2-bit input and outputs the square of the input

①

	A_1	A_0	Y_3	Y_2	Y_1	Y_0	
0	0	0	0	0	0	0	0
1	0	1	0	0	0	1	1
2	1	0	0	1	0	0	4
3	1	1	1	0	0	1	9

msB ← LSB


②

$$Y_3 = A_1 \cdot A_0 = \Sigma m(3)$$

$$Y_2 = A_1 \bar{A}_0 = \Sigma m(2)$$

$$Y_1 = 0$$

$$Y_0 = \bar{A}_1 A_0 + A_1 A_0 = \Sigma m(1, 3)$$
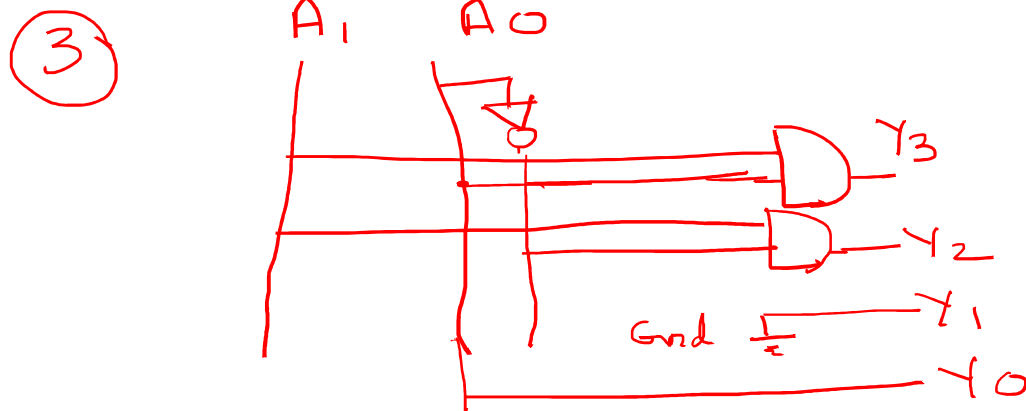
$$= A_0$$


if $01P F = 1$
 V_{CC} Γ F

Rough



Drawing the circuit using only universal gates

- 1. $F(A,B,C,D) = AB + CD$ using only NAND Gates

$$\overline{F} = \overline{AB + CD} = \overline{AB} \cdot \overline{CD}$$

$$\overline{\overline{F}} = \overline{(\overline{AB})(\overline{CD})} = F$$

X Y

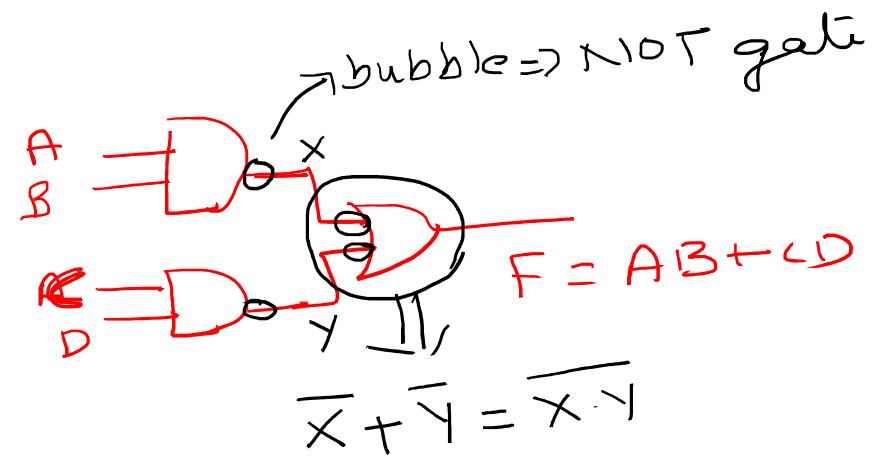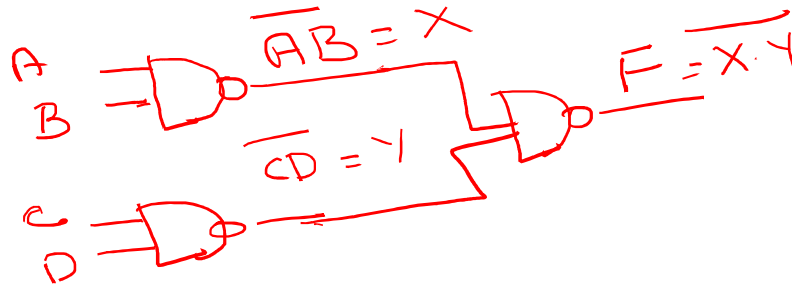


$$A + \bar{A}B = A + B$$

2. $F(x,y,z) = xz + y'z + x'yz$ using only NAND gates

$$= xz + z(\bar{y} + \bar{x}y) = xz + z(\bar{y} + \bar{x})$$

$$F = z$$

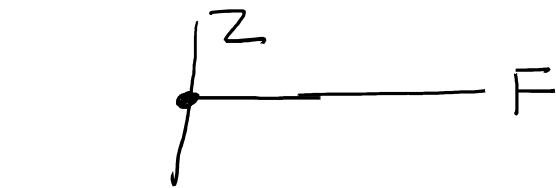


$$= \cancel{xz} +$$

$$= z(x + \bar{y} + \bar{x}) = z(1 + \bar{y}) = z$$

⑤ $F(x,y,z) = \bar{x}z + xy$

$$\bar{F} = \overline{\bar{x}z \cdot xy}$$

$$F = \overline{\bar{x}z \cdot xy}$$

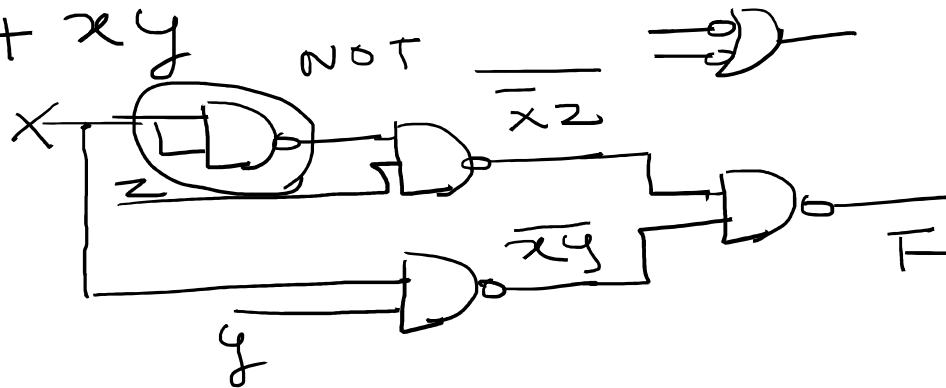



3. Realize the simplified $F(x,y,z) = \Sigma (1,2,3,4,5,7)$ using only NAND gates

-

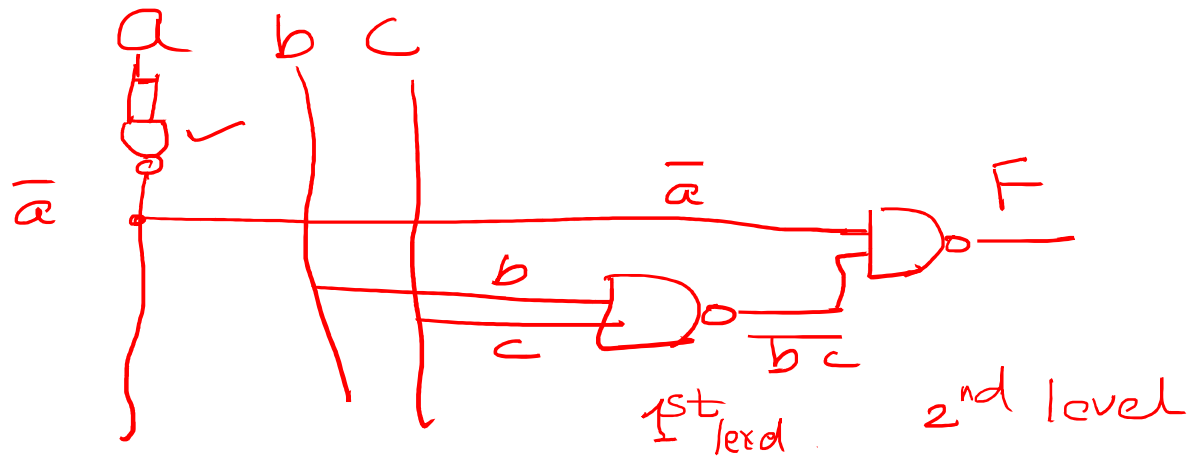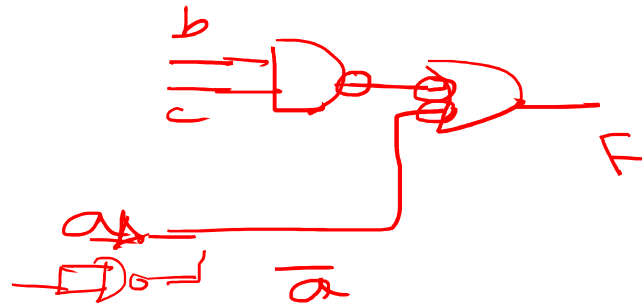4. $F(a,b,c) = \overline{a} + bc$ using only NAND gates

•
$$\overline{F} = \overline{\overline{a} + bc}$$


$$\overline{\overline{F}} = \overline{\overline{a} + bc}$$



Drawing the circuits using only NOR gates

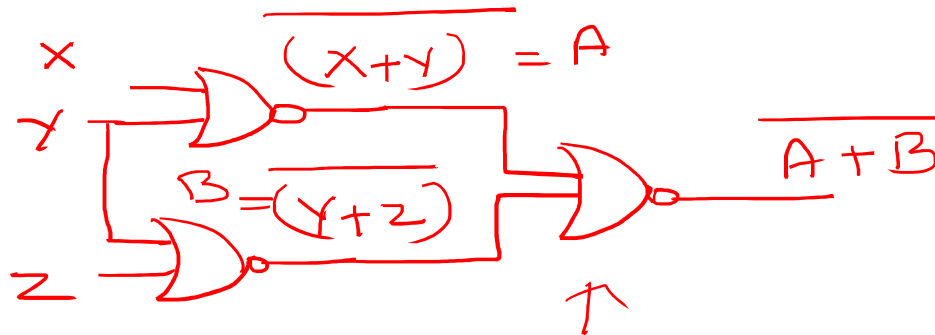
- 1. $F(x,y,z) = \underline{(x+y)} \underline{(y+z)}$

$$\begin{aligned} \overline{F} &= \overline{(x+y) + (y+z)} \\ \overline{F} &= \overline{(x+y)} + \overline{(y+z)} \end{aligned}$$



NOT using NOR

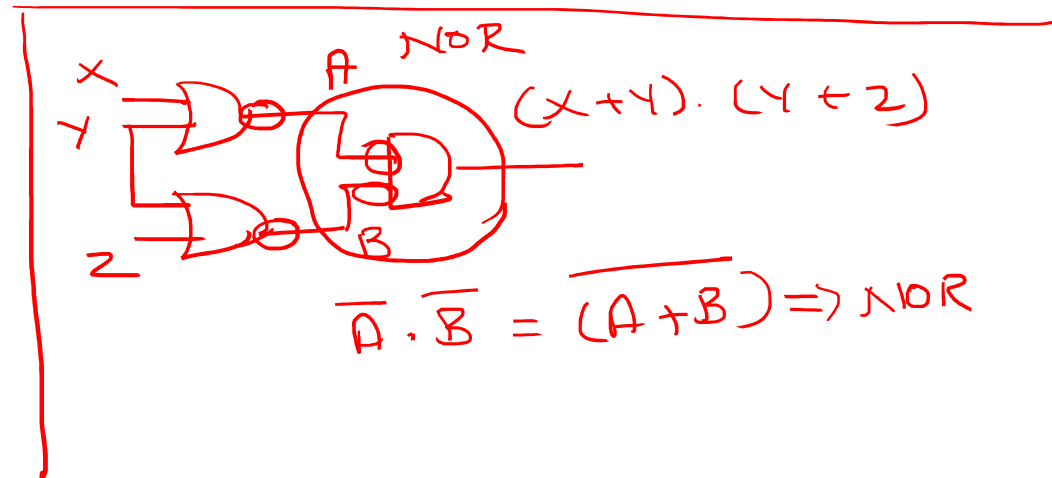
$$\begin{aligned} F &= \overline{A+B} \\ &= \overline{A+A} = \overline{A} \end{aligned}$$




$$\overline{A} \cdot \overline{B} = \overline{(A+B)} \Rightarrow \text{NOR}$$

$$2. F(a, b, c, d) = \overbrace{(a+b')}^3 \overbrace{(c'+d)}^4$$

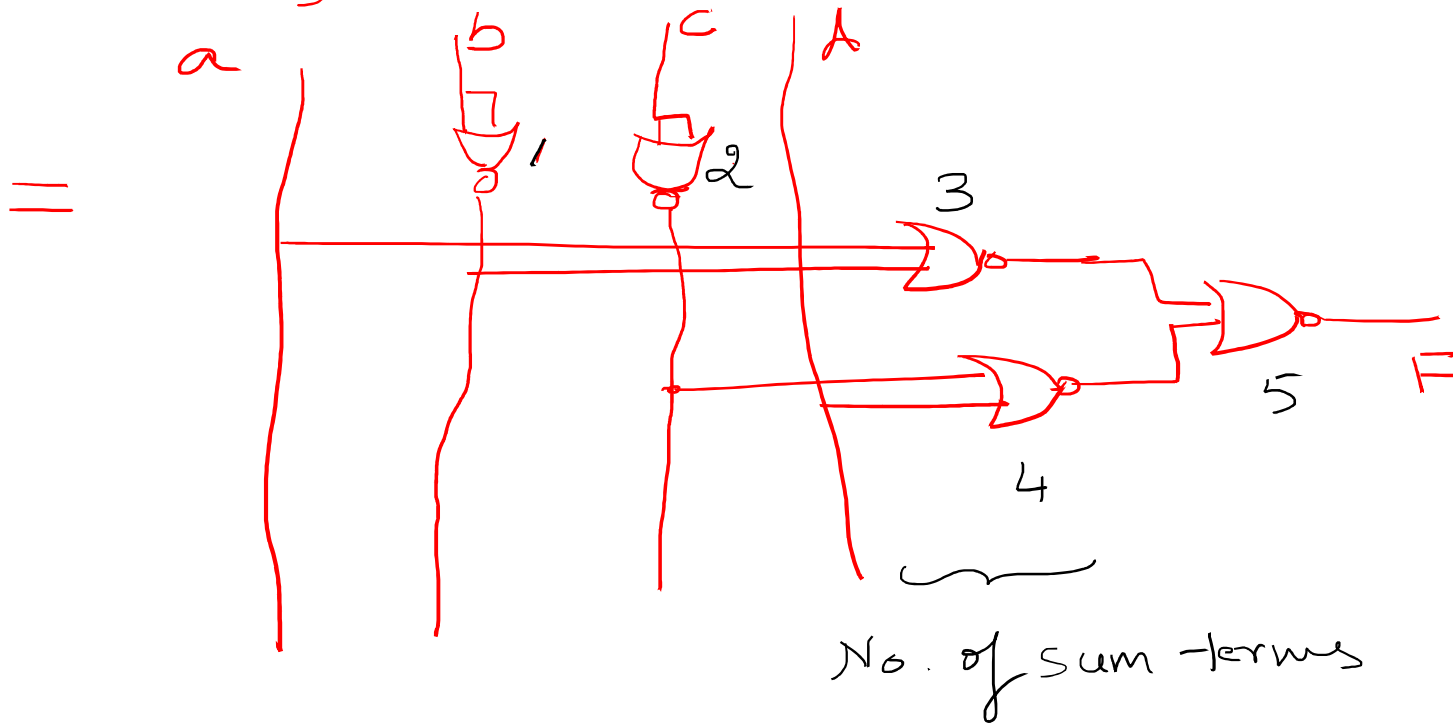$\xrightarrow{1} \quad \xrightarrow{2}$
 $\xrightarrow{5}$


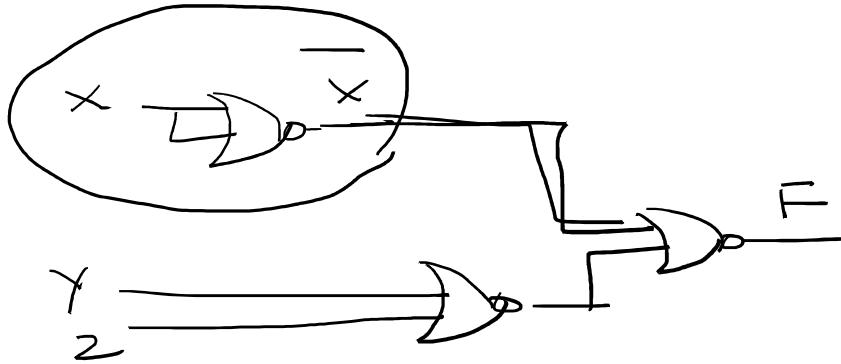
$$3. \underline{f(x,y,z) = x \cdot (y+z)} \Rightarrow f = \overline{\overline{x} + \overline{(y+z)}}$$



$$4. f(a, b, c, d) = a.b.(c+d)$$

$$= \underbrace{\bar{a}}_1 + \underbrace{\bar{b}}_2 + \underbrace{(c+d)}_3$$

Any questions