




# Basic Electrical Technology

## Circuit Elements

---

# Classification of Circuit Elements

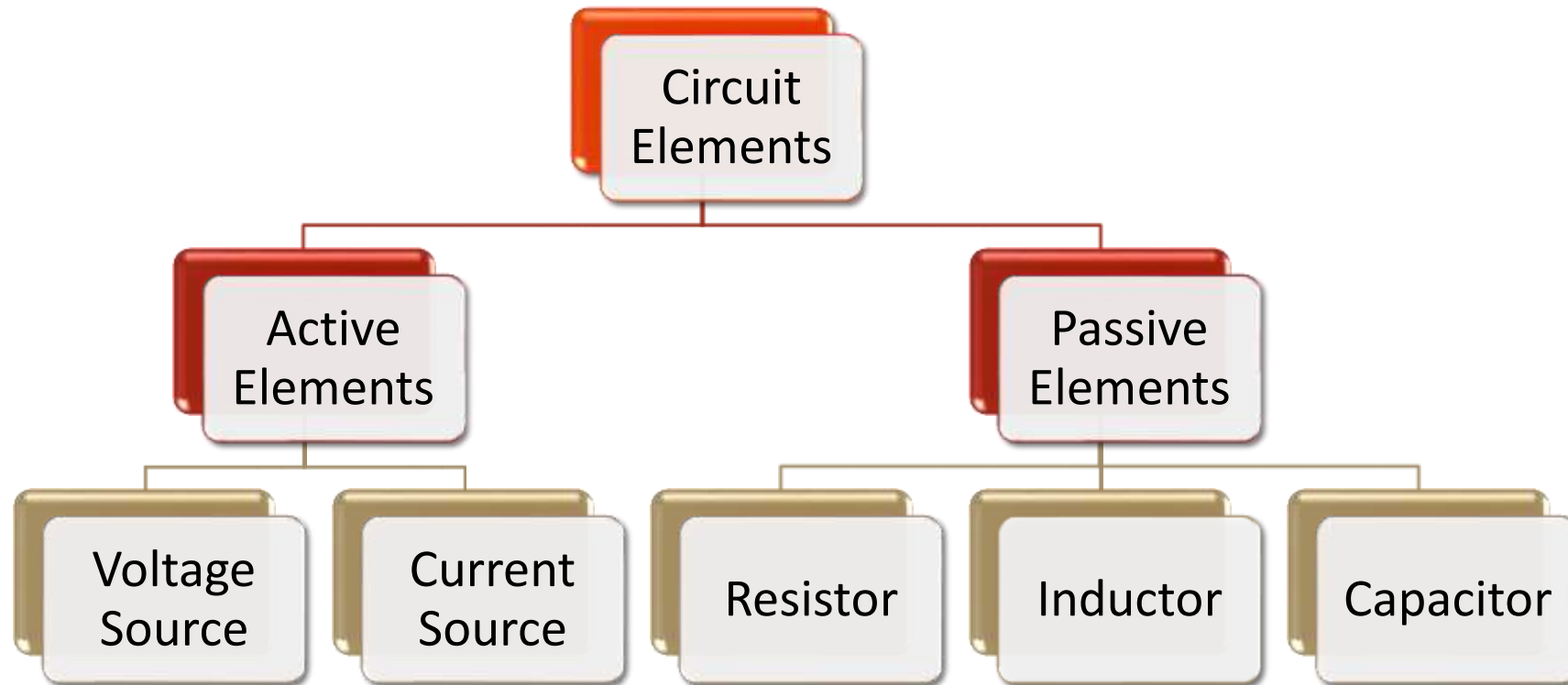


# Active Elements - Sources

## Voltage Source:

### ➤ Ideal:

- Maintains constant voltage irrespective of connected load
- Internal resistance  $R_s = 0$


### Ideal Voltage Source (DC)

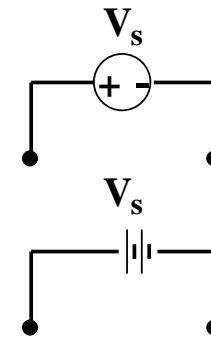

### ➤ Practical:

- Terminal voltage changes based on the connected load
- Internal resistance  $R_s \neq 0$

### Practical Voltage Source

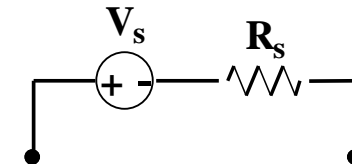


# Active Elements - Sources

## Current Source:

### ➤ Ideal:

- Maintains constant current irrespective of the load connected
- Internal resistance  $R_s = \infty$


### Ideal Current Source (DC)

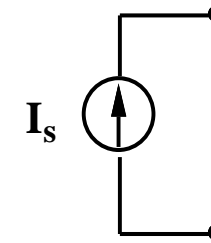

### ➤ Practical:

- Output current changes based on the connected load
- Internal resistance  $R_s < \infty$

### Practical Current Source

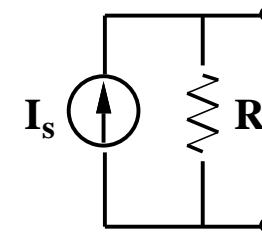



# Resistor

---

Energy Consuming Element

# Resistor

➤ **Passive electric device** that **dissipates energy**

➤ **Resistance:** property which opposes flow of current

- Symbol:  $R$
- Unit: Ohms ( $\Omega$ )
- Power Consumed =  $I^2 R$

➤ **Conductance**

- Reciprocal of resistance
- Symbol:  $G$
- Unit – Siemens (S)






# Resistors in Series

Current ( $I$ ) is same

$$V = V_1 + V_2 + V_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

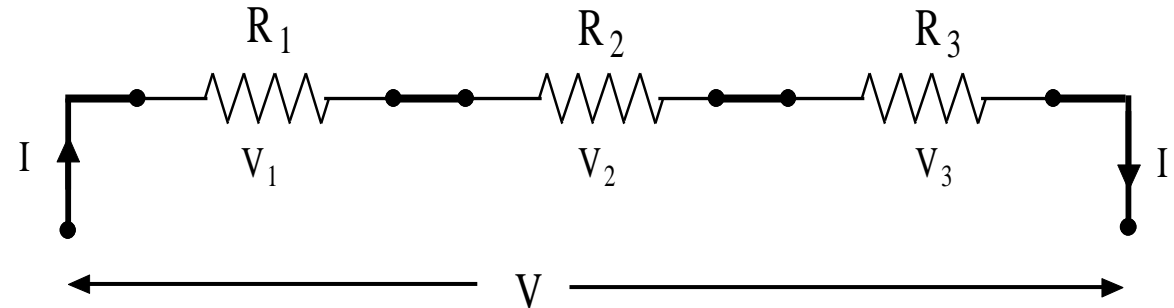




# Resistors in Parallel

Voltage (V) is same

$$I = I_1 + I_2 + I_3$$
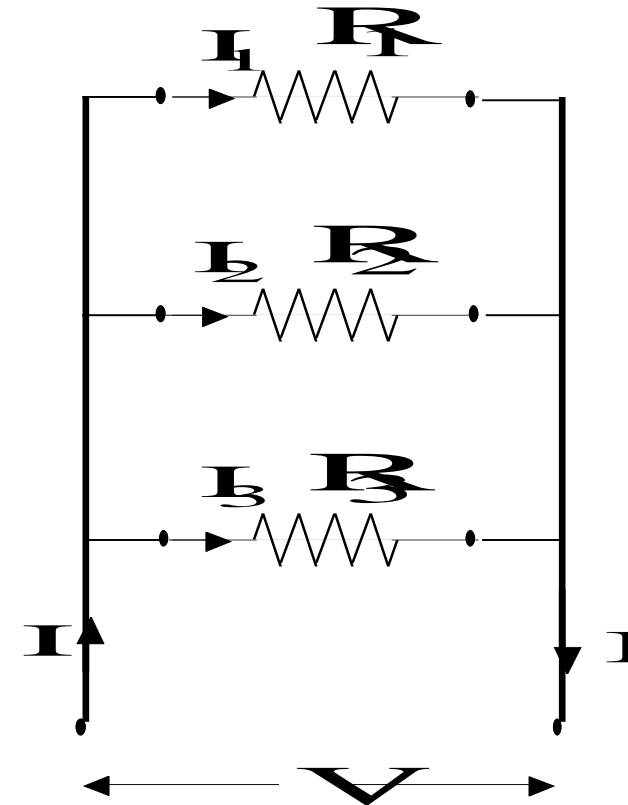
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$







# Inductor

---

## Energy Storing Element

# Inductor

- **Passive** electric device that **stores energy in its magnetic field** when current flows through it
- A coil of wire wound on a core
  - Eg.: Air core Inductor, iron core inductor
- **Inductance**: property which opposes rate of change of current
  - Symbol: **L**
  - Unit: Henry (H)
- The voltage across inductor is proportional to the rate of change of current through it

$$v_L = L \frac{di}{dt}$$





# Inductive Circuit

---

For a coil uniformly wound on a **non-magnetic core** of uniform cross section, self inductance is given by

$$L = \frac{\mu_0 AN^2}{l}$$

Where,

$l$  = length of the magnetic circuit in meters

$A$  = cross sectional area in square meters


$\mu_o$  = Permeability of air =  $4 \times 10^{-7}$

$N$  = *No. of turns in the coil*

# Equivalent Inductance


## Inductors in series

$$L_{eq} = L_1 + L_2 + \dots + L_n$$

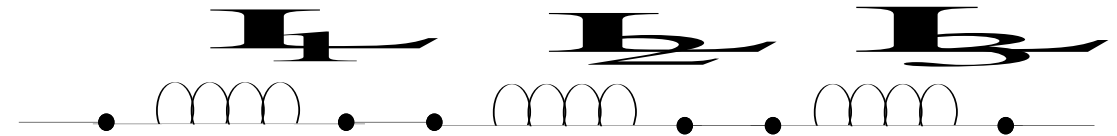
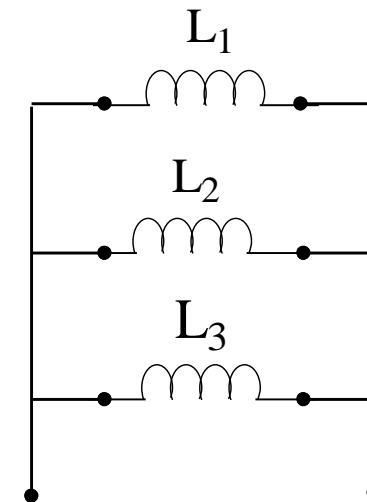
## Inductors in Parallel

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$





# Energy Stored in an Inductor

➤ Instantaneous power,

$$p = v_L \cdot i = L i \frac{di}{dt}$$

➤ Energy absorbed in ' $dt$ ' time is

$$dw = L i di$$

➤ Energy absorbed by the magnetic field when current increases from **0** to  **$I$**  amperes, is

$$W = \int_0^I L i di = \frac{1}{2} L I^2$$



# Capacitor

---

## Energy Storing Element

# Capacitors

➤ **Passive electric device** that **stores energy in the electric field** between a pair of closely spaced conductors

➤ **Capacitance:** Property which opposes the rate of change of voltage

○ Symbol: **C**


○ Unit: Farad (F)

➤ The capacitive current is proportional to the rate of change of voltage across it

$$i_c = C \frac{dv_c}{dt}$$

➤ Charge stored in a capacitor whose plates are maintained at constant voltage:

$$Q = CV$$

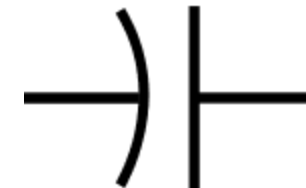

# Terminologies

- Electric field strength,

$$E = \frac{V}{d} \text{ volts/m}$$

- Electric flux density,

$$D = \frac{Q}{A} \text{ C/m}^2$$


- Permittivity of free space,

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

- Relative permittivity,  $\epsilon_r$

- Capacitance of parallel plate capacitor
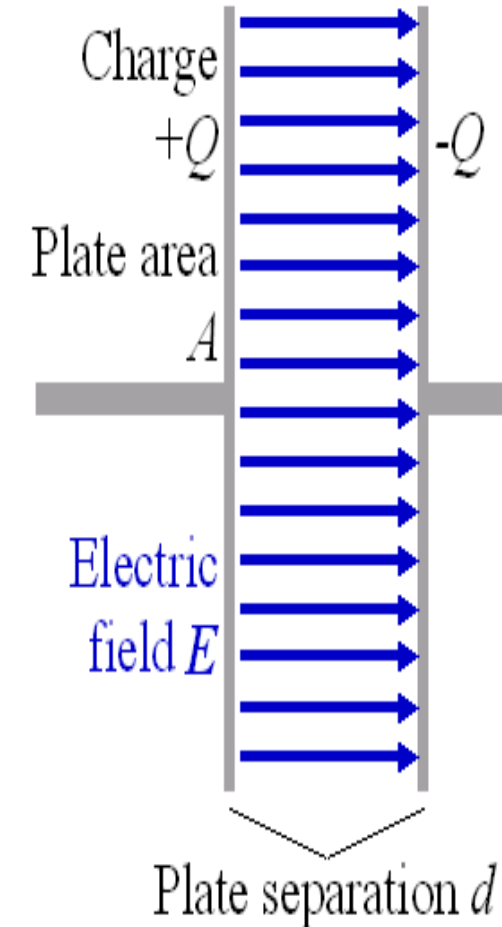
$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$






# Equivalent Capacitance

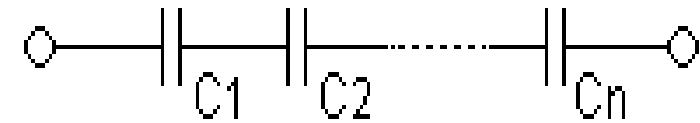
## Capacitors in Series

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$



## Capacitors in Parallel

$$C_{eq} = C_1 + C_2 + \dots + C_n$$

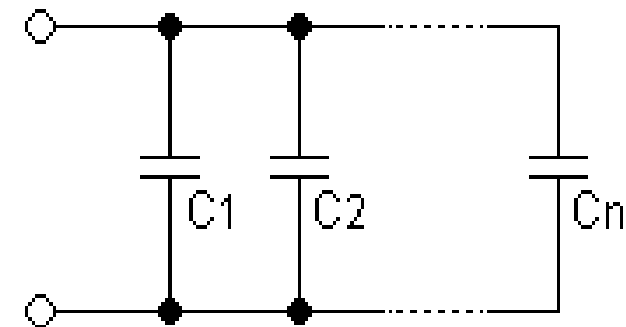



# Energy stored in a Capacitor

➤ Instantaneous power

$$p = v_c \times i = C v_c \frac{dv_c}{dt}$$

➤ Energy supplied during ' $dt$ ' time is:


$$dw = C v_c dv_c$$

➤ Energy stored in the electric field when potential rises from **0** to  **$V$**  volts is,

$$W = \int_0^V C v_c dv_c = \frac{1}{2} CV^2 \text{ Joules}$$

# Illustration 1

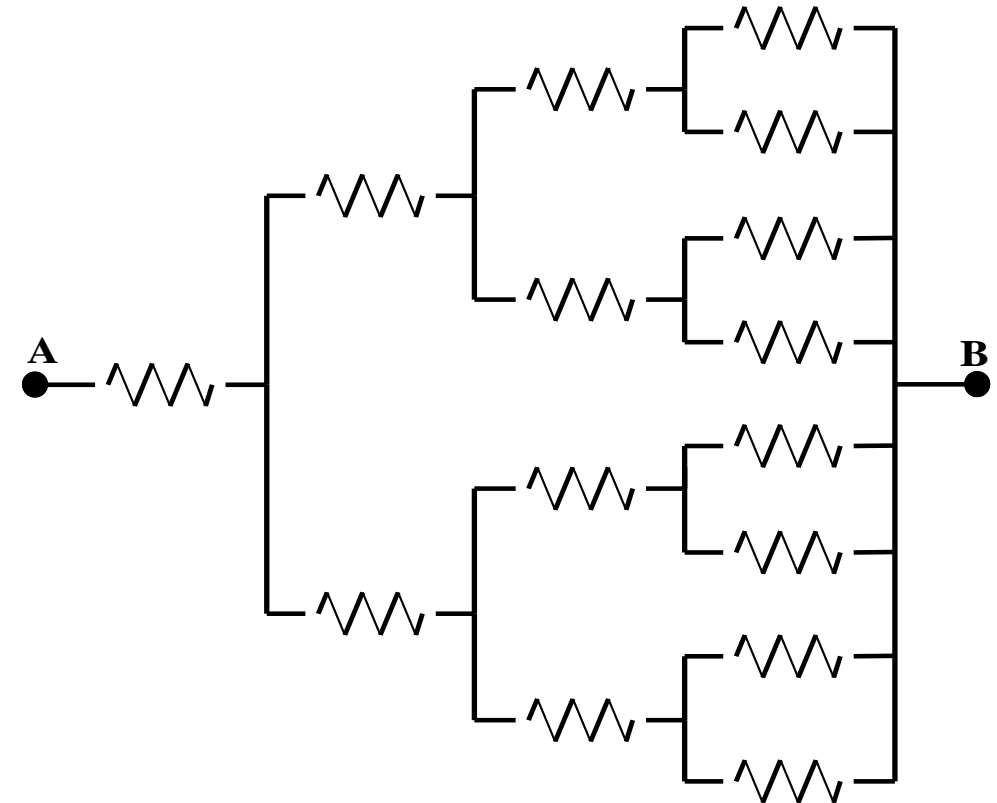- a) 15 resistors are connected as shown in the diagram. Each of the resistors has resistance  $1\ \Omega$ . Find the equivalent resistance of the network between A & B.
- b) What will be the equivalent resistance of this network if the resistors arranged in the sequence extends to infinity?



**Ans:**

**a)  $1.875\ \Omega$**

**b)  $2\ \Omega$**



# Illustration 2

Two incandescent bulbs have the following ratings:

**Bulb-1:** 120 V, 60 W;

**Bulb-2:** 240 V, 480 W

- a) Both of them are connected in series with a voltage source.
  - i. Which bulb will glow brighter and why?
  - ii. What is the maximum voltage that can be applied so that non of the bulbs fuse?
- b) Now both of them are connected in parallel with a voltage source.
  - i. Which bulb will glow brighter and why?
  - ii. What is the maximum voltage that can be applied so that non of the bulbs fuse?

Assume that the incandescent bulbs are purely resistive.

**Ans:**

**a) i) Bulb-1 since it consumes more power, ii) 180 V**

**b) i) Bulb-2 since it consumes more power, ii) 120 V**



# Illustration 3

---

Two incandescent bulbs of 40 W and 60 W ratings are connected in series across the mains. Then which of the following statement(s) is(are) correct?


- a) The bulbs together will consume 100 W
- b) The bulbs together will consume 50 W
- c) The 60 W bulb glows brighter
- d) The 40 W bulb glows brighter

Assume the voltage rating of both the bulbs to be same.

**Ans: d) The 40 W bulb glows brighter**
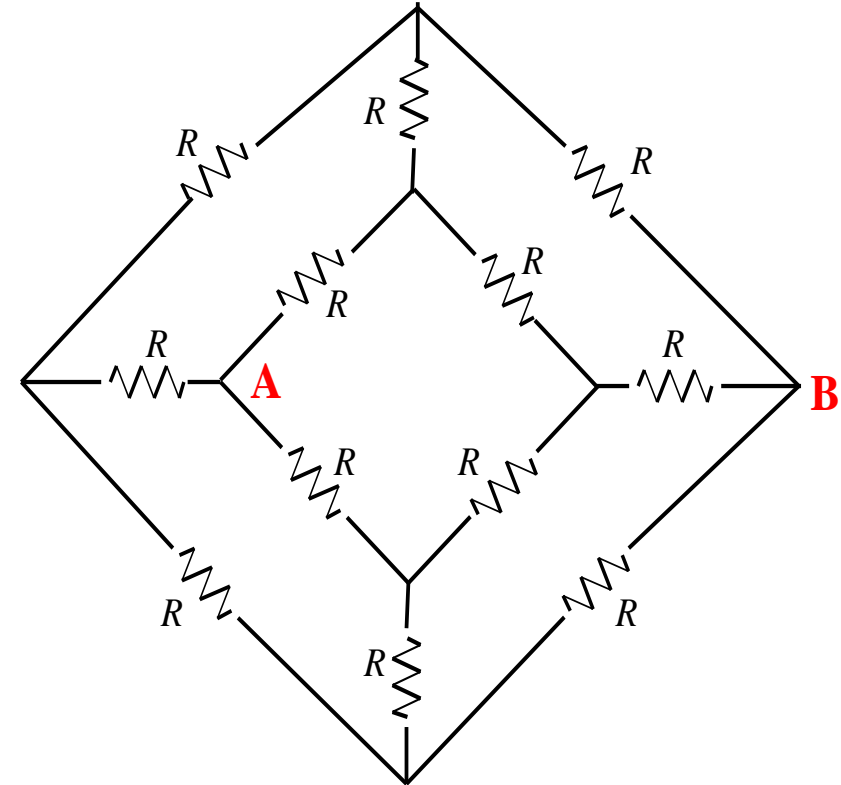
# Homework 1

Reduce the network to its equivalent resistance between terminals A and B



**Ans:  $\frac{5}{6}R$**