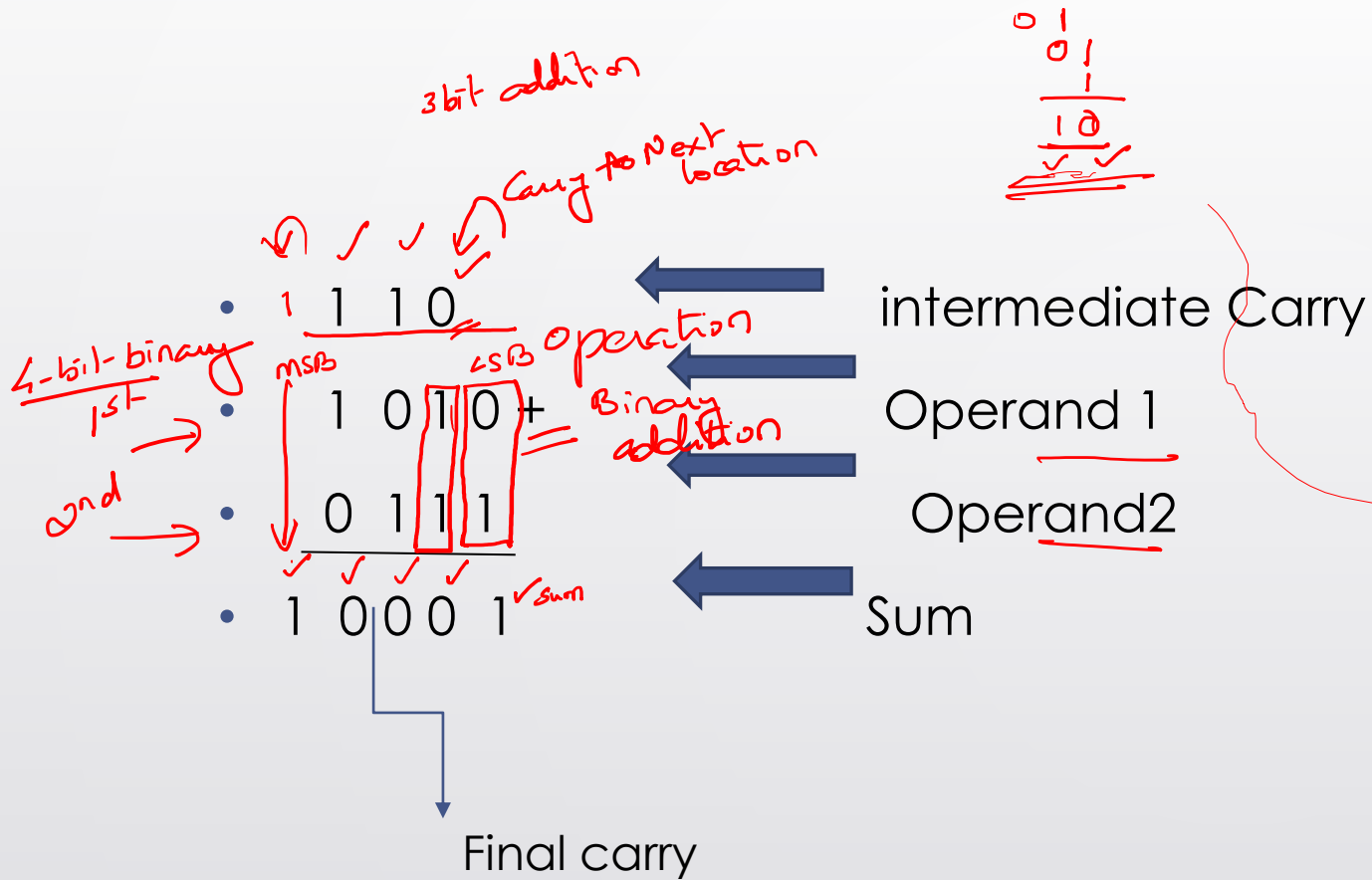




# Binary adders and subtractors



- Half adder, full adder, parallel adder
- Half subtractor , full subtractor, parallel subtractor
- Subtraction using complements, parallel adder/subtractor
- Carry Look ahead adder, Decimal adder

# Binary Addition



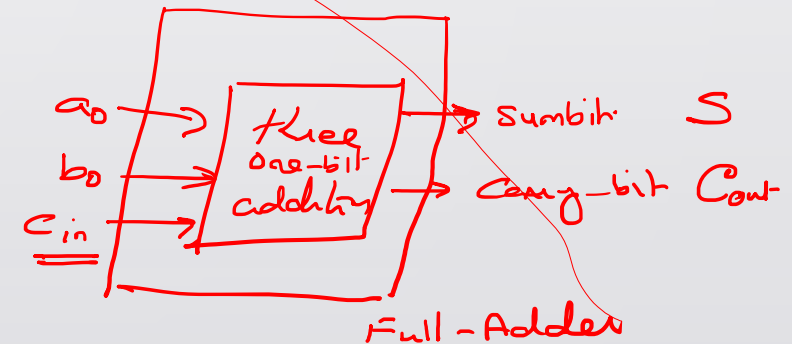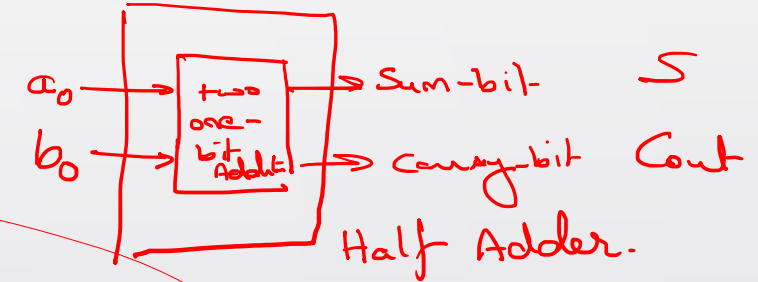
## Bit-Wise addition

- two, one bit addition
- addition of three one-bits


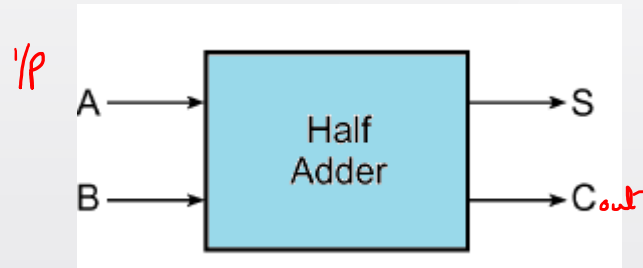
# Half adder(HA)

- Adds 2, 1-bit numbers A and B , generated two outputs sum(S) and carry (C).



4 combinations

A	B	S	C <sub>out</sub>
0	0	<u>0</u>	<u>0</u>
0	1	<u>1</u>	<u>0</u>
1	0	<u>1</u>	<u>0</u>
1	1	<u>0</u> ✓	<u>1</u> ✓

Expression for sum and carry :

$$S(A, B) = S = \sum_m 1, 2 \quad \text{or} \quad \prod_m 0, 3$$

$$C_{out}(A, B) = C_{out} = \sum_m 3 \quad \text{or} \quad \prod_m 0, 1, 2$$

$$\begin{array}{r} 1 \quad 0 \\ 0 \quad 1 \\ \hline 0 \quad 1 \\ \hline \text{Cout} \quad S \end{array}$$

$$\begin{array}{r} 0 \quad 1 \\ 1 \quad 0 \\ \hline 1 \quad 0 \\ \hline \text{Cout} \quad S \end{array}$$

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C_{out} = A \cdot B$$

A \ B	0	1
0	0 <sup>0</sup>	1 <sup>1</sup>
1	1 <sup>2</sup>	0 <sup>3</sup>



$$S = \bar{A}B + A\bar{B}$$

A \ B	0	1
0	0 <sup>0</sup>	0 <sup>1</sup>
1	0 <sup>2</sup>	1 <sup>3</sup>


$$C_{out} = A \cdot B$$

# HA circuit

Using basic logic gates

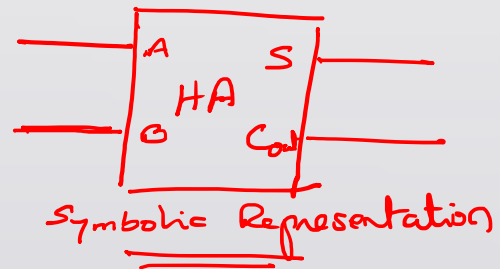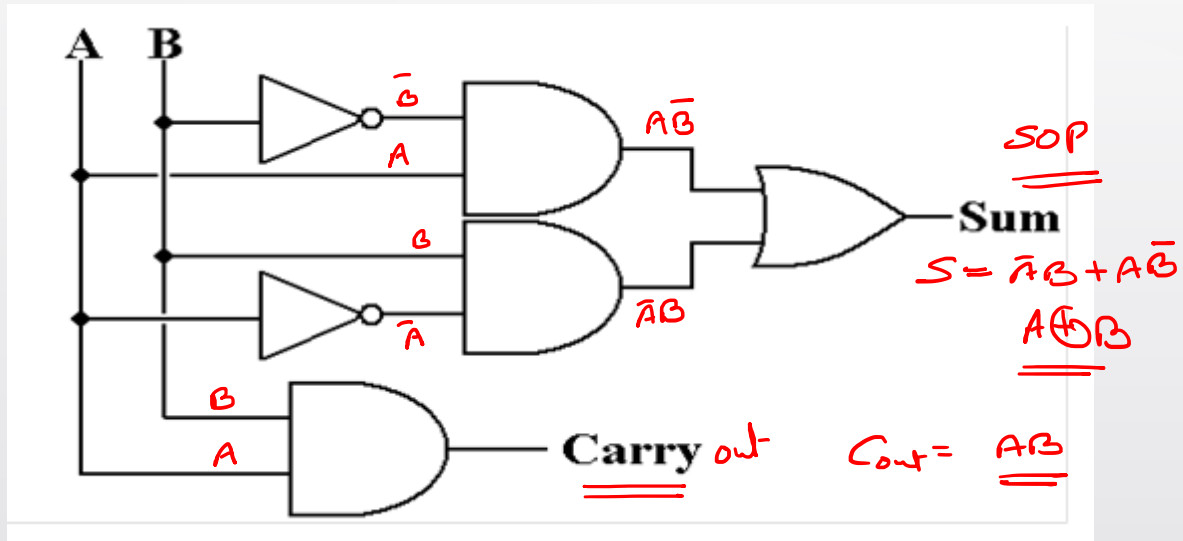

Using XOR and AND gate

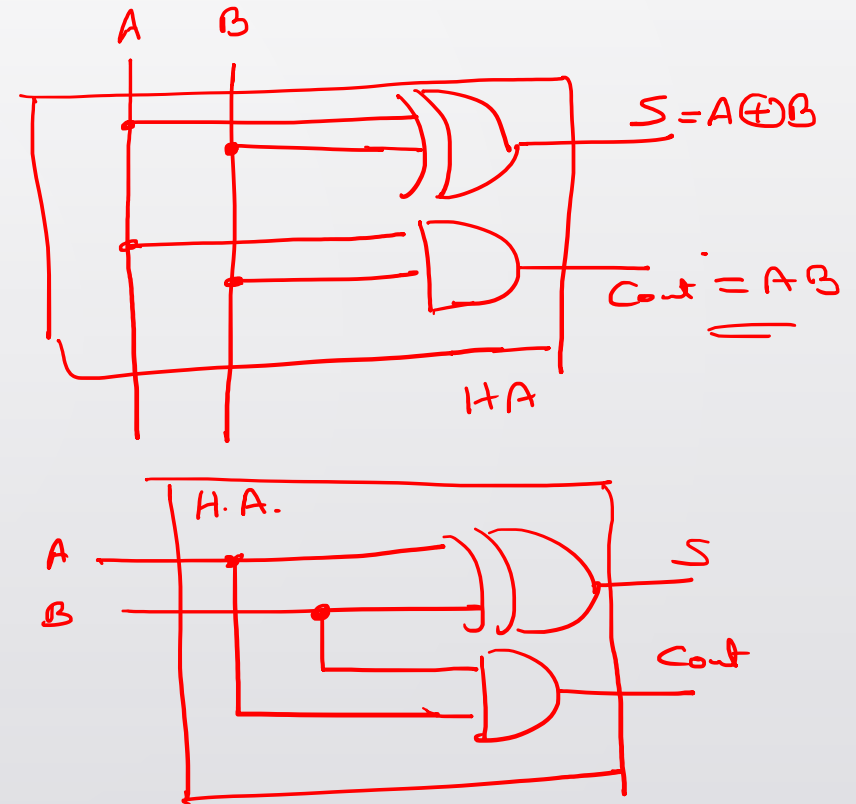


# Full adder

Truth Table


A B C <small>LSB</small>	Carry	Sum
0 0 0	0	0
0 0 1	0	1
0 1 0	0	1
0 1 1	<u>1</u>	0
1 0 0	0	1
1 0 1	<u>1</u>	0
1 1 0	<u>1</u>	0
1 1 1	<u>1</u>	1

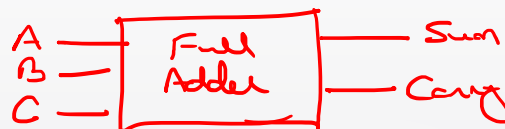A, B, C → 3, one-bit inputs. each → 0 or 1



$$\text{Carry} = \sum_{m=3,5,6,7}$$

$$\text{Sum} = \sum_{m=1,2,4,7}$$

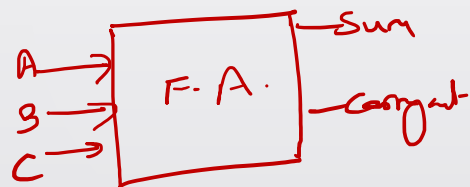

	BC	00	01	11	10
A 0		0 <sup>0</sup>	0 <sup>1</sup>	1 <sup>3</sup>	0 <sup>2</sup>
A 1		0 <sup>4</sup>	1 <sup>5</sup>	1 <sup>7</sup>	1 <sup>6</sup>

	BC	00	01	11	10
A 0		0 <sup>0</sup>	1 <sup>1</sup>	0 <sup>3</sup>	1 <sup>2</sup>
A 1		1 <sup>4</sup>	0 <sup>5</sup>	1 <sup>7</sup>	0 <sup>6</sup>

$$\text{Carry} = BC + AC + AB$$

(m<sub>3</sub>, m<sub>5</sub>) (m<sub>5</sub>, m<sub>7</sub>) (m<sub>6</sub>, m<sub>7</sub>)

$$\text{Sum} = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$= \bar{A}(\bar{B}C + B\bar{C})$$

$$+ A(\bar{B}\bar{C} + BC)$$

$$= \bar{A}(\underbrace{\bar{B}C + B\bar{C}}_X) + A(\underbrace{\bar{B}\bar{C} + BC}_{\bar{X}})$$

$$= \bar{A}X + A\bar{X}$$

$$= A \oplus X$$


$$\text{Sum} = A \oplus B \oplus C$$

C<sub>0</sub> 3  
0 1


C<sub>1</sub> S  
1 1



# FA circuit using basic logic gates

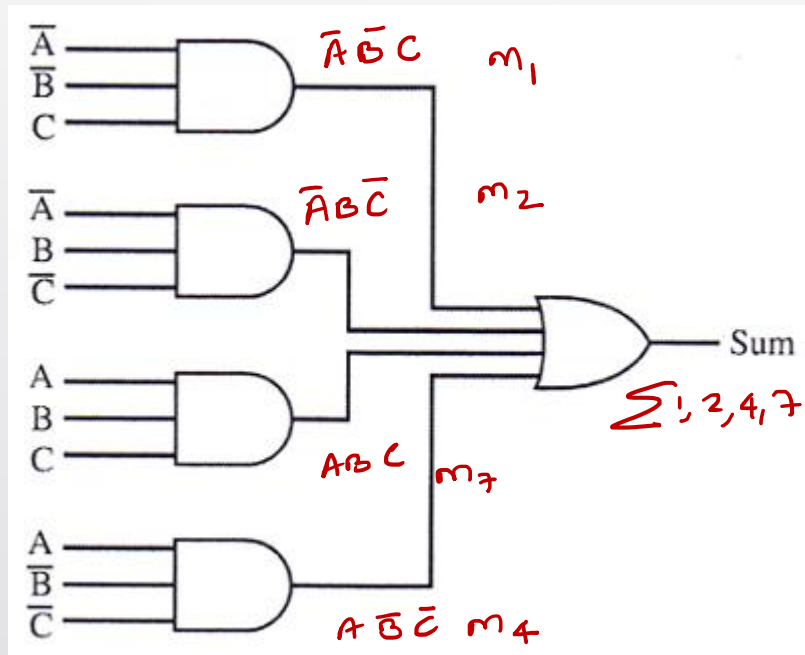


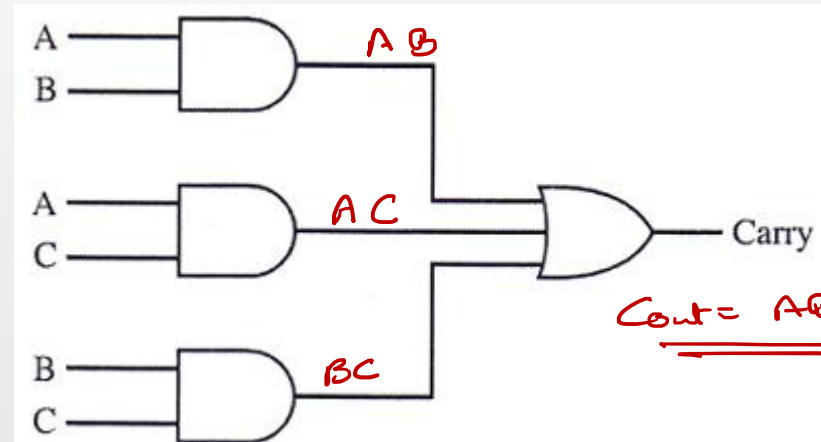
$$\text{Sum} = \sum 1, 2, 4, 7 = \underline{\underline{A \oplus B \oplus C}}$$



$$\underline{\underline{\text{Carry} = AB + AC + BC}}$$

$$\underline{\underline{\text{Carry} = AB + AC + BC}}$$
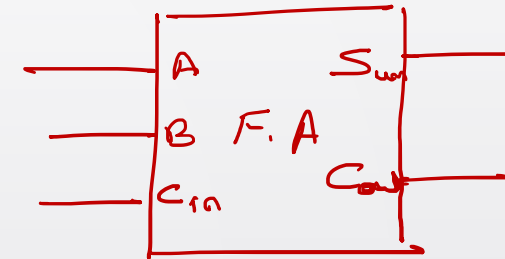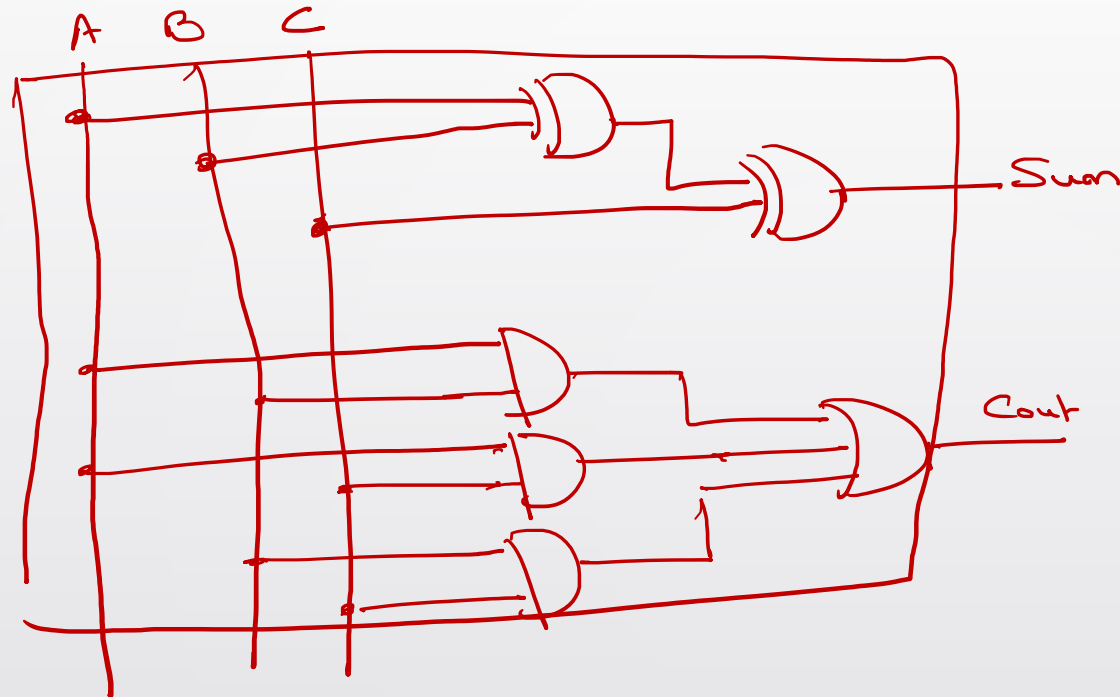
# Full adder circuit using XOR operations



# FA using 2 HA s and one external gate

Expressions for F.A

$$\underline{\text{Sum}} = A \oplus B \oplus C$$

$$\underline{\text{Carry out}} = AB + BC + AC$$

from H.A.


$$\underline{\text{S}} = A \oplus B$$

$$\underline{\text{Cout}} = A \cdot B$$

OR Gate

$$S \oplus C$$

$$\text{Sum} = (A \oplus B) \oplus C$$

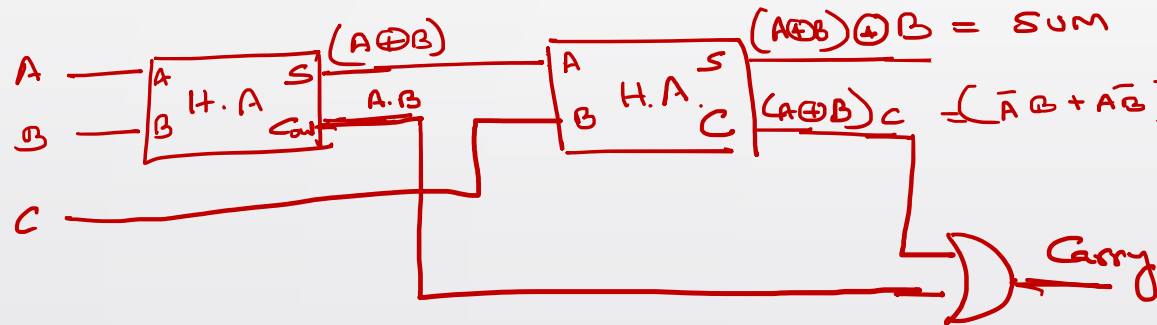

$$(A \oplus B) \cdot C = (\bar{A}B + A\bar{B})C = \bar{A}BC + A\bar{B}C$$

$m_3 \quad m_5$   
✓      ✓


$$(m_3 + m_5) + (m_6 + m_7) = \underline{\underline{\text{Cout} = \text{Carry}}}$$

↓  
OR

$$AB = AB(\bar{C} + C)$$

$$= AB\bar{C} + ABC$$

$m_6 \quad m_7$   
✓      ✓

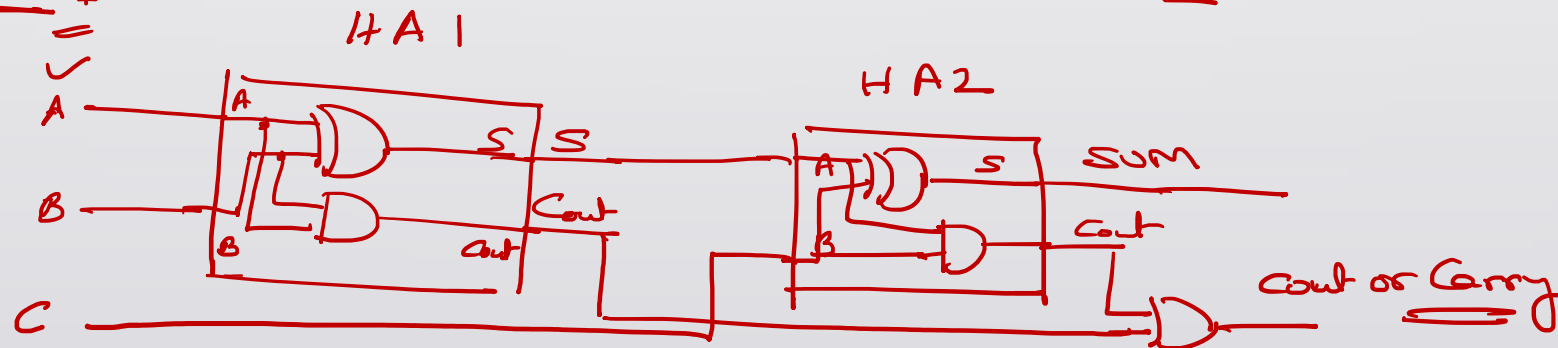




# 4-bit Parallel adder using FA blocks

- Consider addition of 2, 4-bit numbers:  $(A_3 A_2 A_1 A_0)$  and  $(B_3 B_2 B_1 B_0)$  → Results a 5-bit Number  
1-bit + 4-bit Sum carry

A → 4-bit Number

B → 4-bit Number

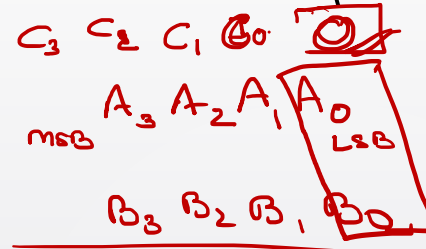

C<sub>3</sub> S<sub>3</sub> S<sub>2</sub> S<sub>1</sub> S<sub>0</sub>


Carry  
1-bit

4-bit Sum

FA<sub>3</sub> FA<sub>2</sub> FA<sub>1</sub> HA  
+ 0

FA<sub>3</sub> FA<sub>2</sub> FA<sub>1</sub> FA<sub>0</sub>

C<sub>in</sub> = 0

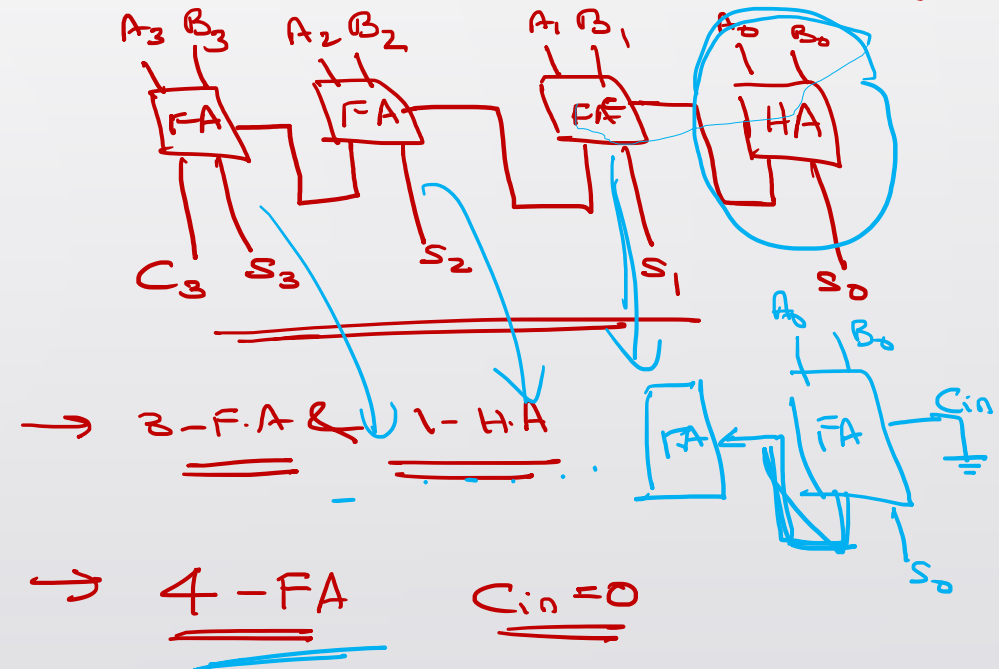


→ 3-FA & 1-HA

4-FA

C<sub>in</sub> = 0



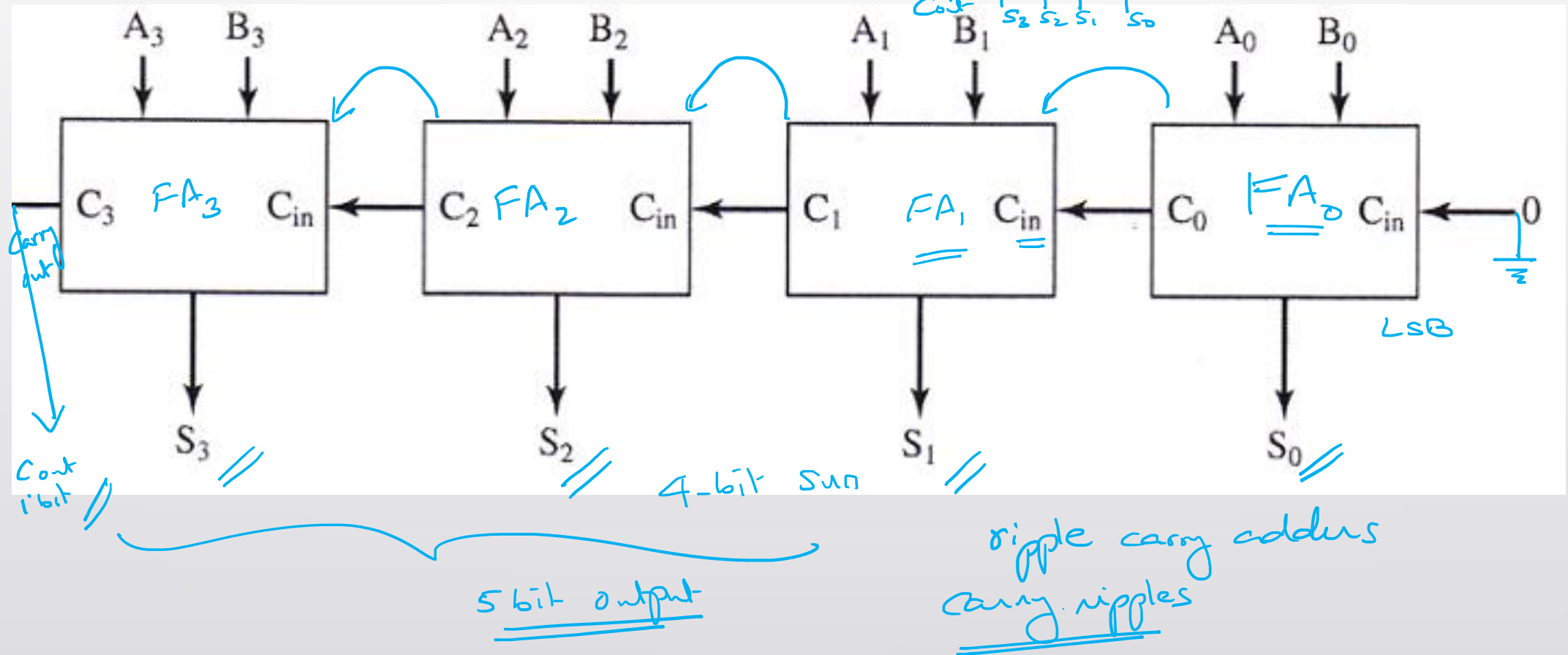
# 4-bit parallel adder

Also called as Carry Propagation Adder (CPA)


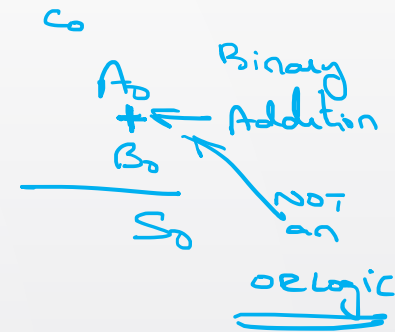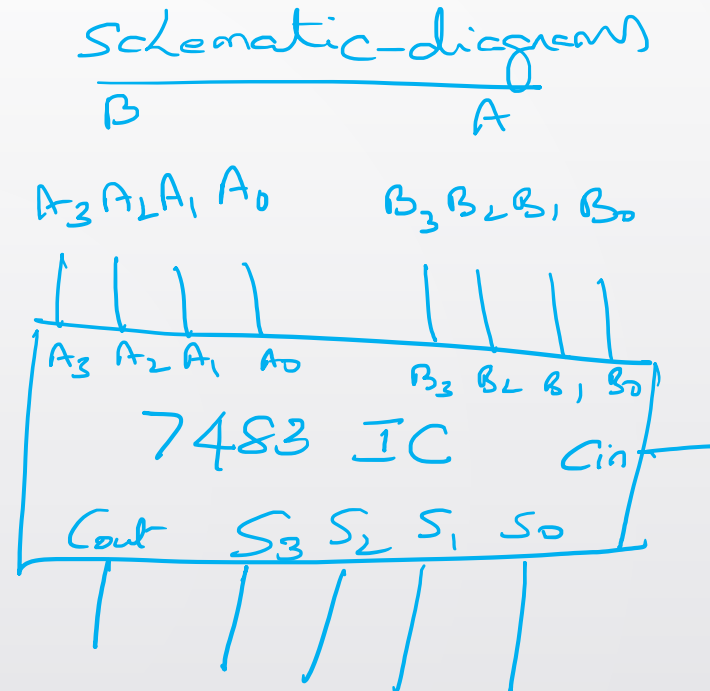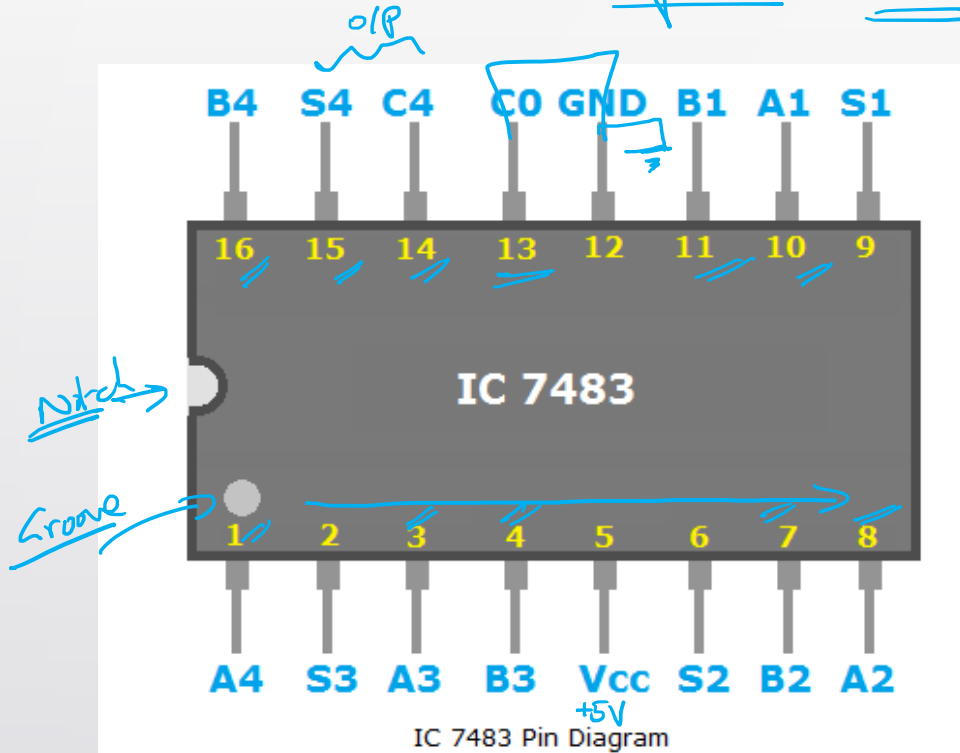
# 7483 IC : 4-BIT PARALLEL ADDER

pin diagram of 7483 4-bit Binary adders  
16 pin IC DIP



# Half subtractor

- Write the truth table and circuit for half subtractor

$A - B \rightarrow A \text{ \& B are 1-bit Numbers}$   
 Arithmetic minus  $A \rightarrow 0$   
 $B \rightarrow 0$   
 $\begin{array}{r} 00 \\ \uparrow \\ B \end{array}$

Truth-Table

A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

otherwise  $\begin{array}{r} 10 \\ \underline{0} \\ 10 \end{array}$   
 $\begin{array}{r} 1 \\ \underline{0} \\ 10 \end{array}$   
 $\begin{array}{r} 1 \\ \underline{0} \\ 10 \end{array}$


$$\begin{aligned}
 \text{Diff} &= \sum_m 1, 2 \quad \text{sop} \\
 &= \prod_m 0, 3 \quad \text{pos}
 \end{aligned}$$

$$\text{Diff} = \bar{A}B + A\bar{B}$$

$$\boxed{\text{Diff} = A \oplus B}$$



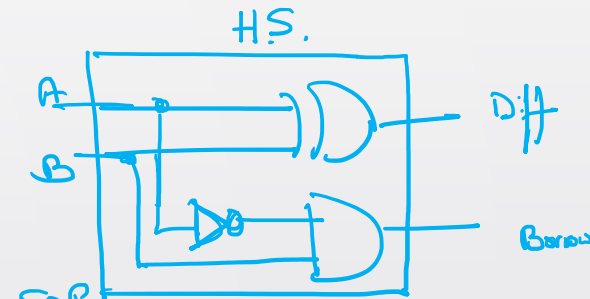$\begin{array}{r} 1 \\ \underline{0} \\ 00 \end{array}$   
 $\begin{array}{r} 1 \\ \underline{0} \\ 00 \end{array}$



$$\begin{aligned}
 \text{Borrow} &= \sum_m 1 \quad \text{sop} \\
 &= \prod_m 0, 2, 3 \quad \text{pos}
 \end{aligned}$$

$$\boxed{\text{Borrow} = \bar{A}B}$$

# Full subtractor

DIFFERENCE (D) = X-Y-Z, Borrow (B)



X	Y	Z	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Expressions for D and B:



$$D = \sum_3 1, 2, 4, 7 \quad \prod_m (0, 3, 5, 6)$$

$$B = \sum_3 1, 2, 3, 7 = \prod_m (0, 4, 5, 6)$$

$$\begin{aligned} D &= \bar{x}\bar{y}z + \bar{x}y\bar{z} \\ &\quad + x\bar{y}\bar{z} + xy z \\ &= \bar{x}(\bar{y}z + y\bar{z}) + x(\bar{y}\bar{z} + yz) \\ &= \bar{x}(y \oplus z) + x(\overline{y \oplus z}) \end{aligned}$$

$$D = x \oplus y \oplus z$$

$$B = \bar{x}z + \bar{x}y + yz$$

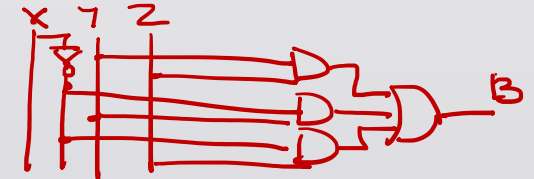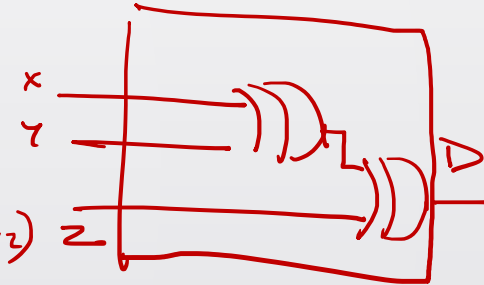

Handwritten notes on the left margin showing binary subtraction:  $10 - 00 = 10$  and  $10 - 01 = 01$ .



# FS circuit

- Draw the circuit for FS using
- (i) basic logic gates only
- (ii) XOR and basic logic gates

$$\begin{array}{c} 1/p \\ x \quad y \quad z \end{array}$$


$$\begin{array}{c} 0/p \\ \underline{\underline{D \quad B}} \end{array}$$

$$B = \bar{x}y + \bar{x}z + yz = \sum 1, 2, 3, 7$$

$$D = x \oplus y \oplus z$$

$$= \sum 1, 2, 4, 7$$

i)

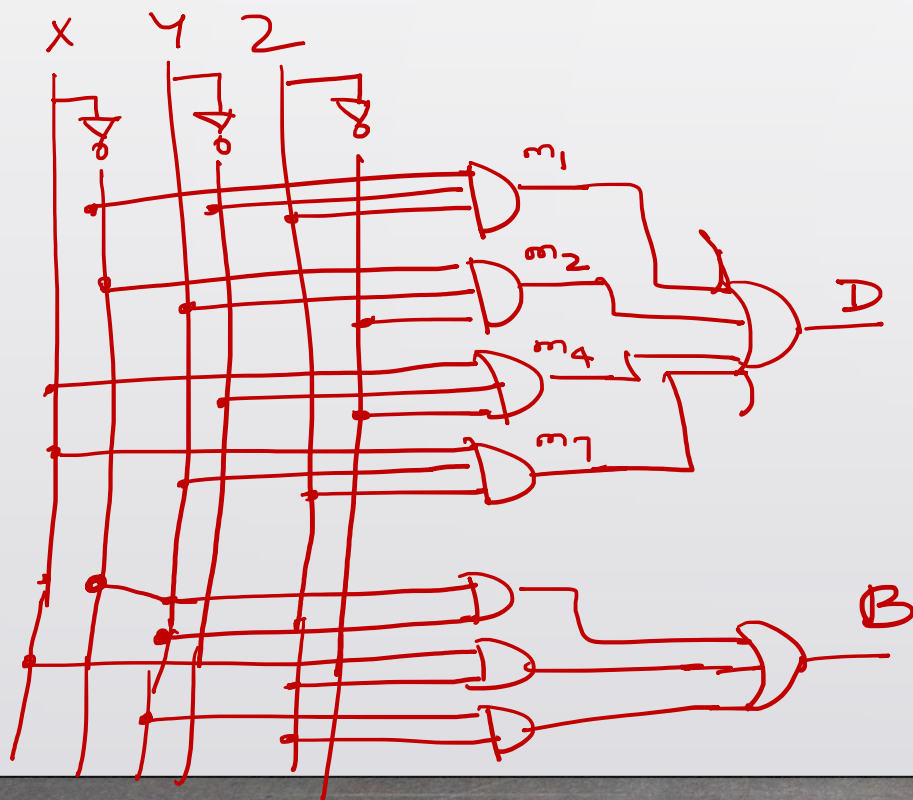

gate

H.S Diff =  $x \oplus y$



$$\text{Borrow} = \bar{x}_4$$

F.S  $D = x \oplus y \oplus z$  ✓

$$B = \bar{x}_1 + \bar{x}_2 + 72$$

$$D = \sum_3 1, 2, 4, 7$$


$$B = \sum_{\mathbb{N}} 1, 2, 3, 7$$

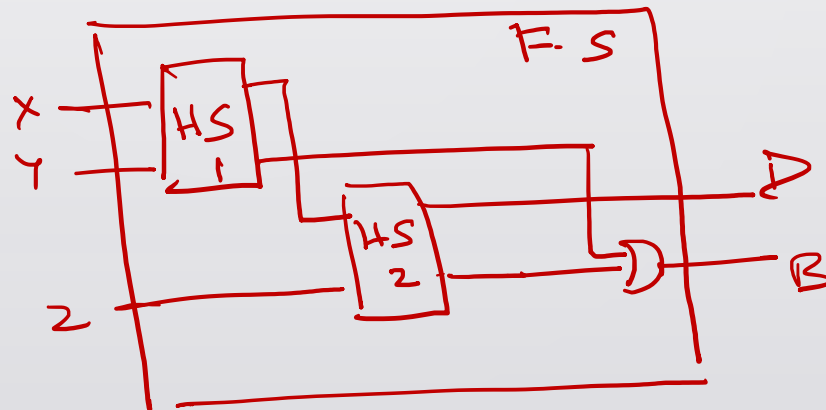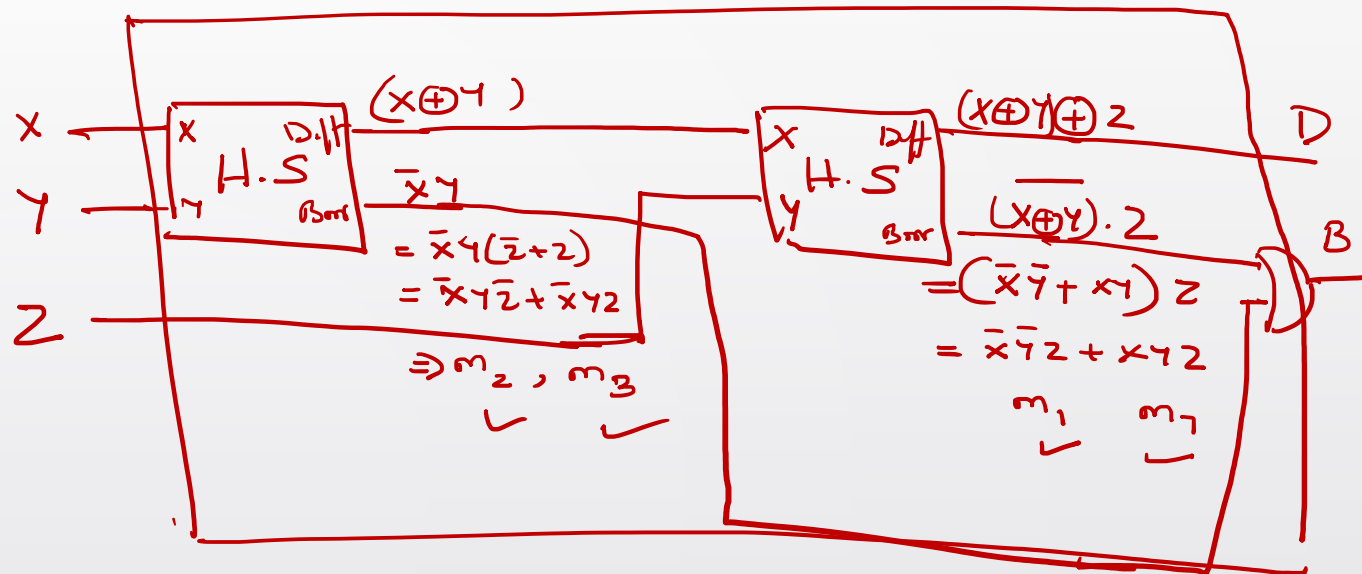
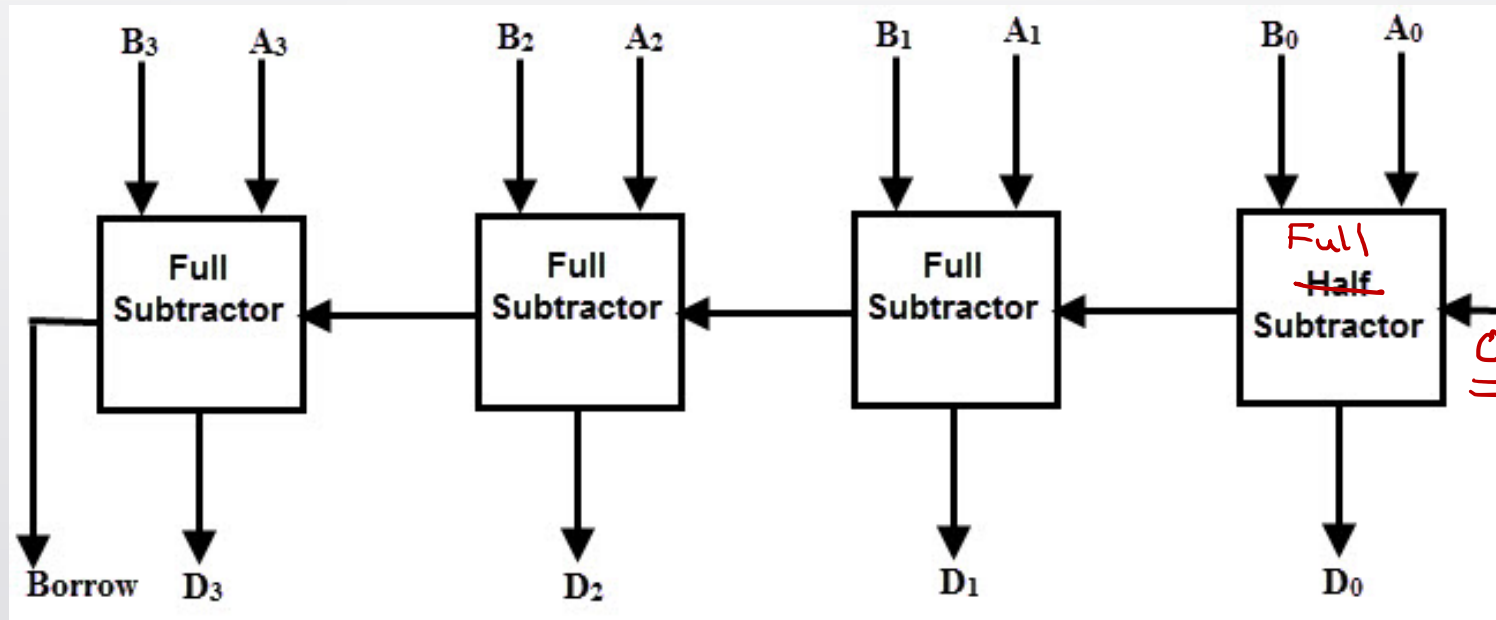
# 4-bit parallel subtractor using FS blocks



Consider subtraction of 2, 4-bit numbers:  $(A_3 A_2 A_1 A_0)$  and  $(B_3 B_2 B_1 B_0)$



$$\begin{array}{r} A \\ - B \\ \hline \end{array}$$

$A_3 A_2 A_1 A_0$   
 $B_3 B_2 B_1 B_0$  Lsb

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 28 29 30 31 32 33 34 35 36 37 38 39 40 41 42 43 44 45 46 47 48 49 50 51 52 53 54 55 56 57 58 59 60 61 62 63 64 65 66 67 68 69 70 71 72 73 74 75 76 77 78 79 80 81 82 83 84 85 86 87 88 89 90 91 92 93 94 95 96 97 98 99 100

# Subtraction using complements

□ Using 2's complement method

□ Using 1's complement method

$$\begin{array}{r} 2 = 0010 \\ - 8 = 1000 \\ \hline \end{array}$$

2's Complement method for realizing subtraction

$$\begin{array}{r} 8 \rightarrow 1000 \\ - 2 \\ \hline 6 \end{array}$$

as it is  $1000$

$$\begin{array}{r} 1000 \\ - 0010 \\ \hline \end{array}$$

2's  
↳ 1's comp + 1

$$\begin{array}{r} 1101 \\ + 1 \\ \hline 110110 \end{array}$$

the & drop carry

Ans  $110$

+ 6

$$\begin{array}{r} 1111 \\ 0010 \\ \hline 1101 \end{array}$$

is  $0111$

$$\begin{array}{r} 0010 \\ \hline \end{array}$$

is  $0111$  } 2's comp

+ 1

$$\begin{array}{r} 1010 \\ \hline \end{array}$$


Ans is in 2's complement

ve

$$\begin{array}{r} 0101 \\ \hline 0110 \end{array}$$

6

# Subtraction using complements

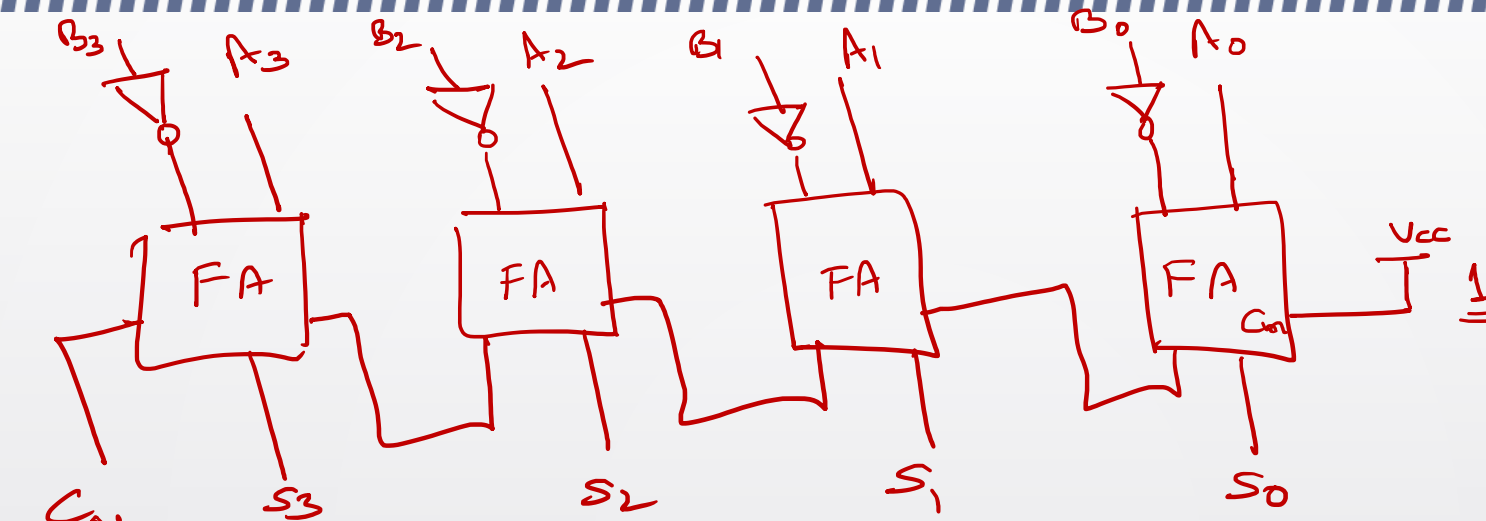

1 → +ve  
0 → -ve

any carry

Ans is in its form

Ans is in its 2's complement form

$A_3 A_2 A_1 A_0$   
 $\overline{B_3} \overline{B_2} \overline{B_1} \overline{B_0}$

2's complement

$C_{in} = 1$

