

LECTURE 5 & 6

KARNAUGH MAP (K – MAP)



EXAMPLE 4:

$$F(x, y, z) = \prod_m (0, 2, 5, 7) = \sum_m (1, 3, 4, 6)$$

	00	01	11	10
x \ z	0	1	1	0
0	0	1	1	0
1	1	0	0	1

POS

$$F = (x + z) (\bar{x} + \bar{z})$$

SOP

$$F = \bar{x}z + x\bar{z}$$

NAND

$$\bar{F} = \bar{x}z + x\bar{z} = \bar{F}$$

$$= \overline{\bar{x}z} \cdot \overline{x\bar{z}}$$

Draw ckt here
NAND ONLY

NOR

$$F = \overline{\overline{F}} = \overline{(x+z)(\bar{x}+\bar{z})}$$

$$= \overline{(x+z) + (\bar{x}+\bar{z})}$$

NOR ONLY

FOUR VARIABLE K – MAP

4 variables $2^4 = 16$ combinations

SOP using minterms

A. SOP: -

AB \ CD	$\overline{C}\overline{D}$ 00	$\overline{C}D$ 01	CD 11	$C\overline{D}$ 10
$\overline{A}\overline{B}$ 00	$\overline{A}\overline{B}\overline{C}\overline{D}$ m_0 0	$\overline{A}\overline{B}\overline{C}D$ m_1 1	$\overline{A}\overline{B}C\overline{D}$ m_3 3	$\overline{A}\overline{B}CD$ m_2 2
$\overline{A}B$ 01	$\overline{A}B\overline{C}\overline{D}$ m_4 4	$\overline{A}B\overline{C}D$ m_5 5	$\overline{A}BC\overline{D}$ m_7 7	$\overline{A}BCD$ m_6 6
AB 11	$AB\overline{C}\overline{D}$ m_{12} 12	$AB\overline{C}D$ m_{13} 13	$ABC\overline{D}$ m_{15} 15	$ABCD$ m_{14} 14
$A\overline{B}$ 10	$A\overline{B}\overline{C}\overline{D}$ m_8 8	$A\overline{B}\overline{C}D$ m_9 9	$A\overline{B}C\overline{D}$ m_{11} 11	$A\overline{B}CD$ m_{10} 10

$\overline{A}\overline{B}$	$\overline{C}\overline{D}$ 00	$\overline{C}D$ 01	CD 11	$C\overline{D}$ 10
$\overline{A}B$	0	1	3	2
AB	4	5	7	6
$A\overline{B}$	12	13	15	14
AB	8	9	11	10

$ABCD$	
0000	
0001	
0010	
0011	
0100	
0101	
0110	
0111	
<hr/>	
1000 m_8	
1001	
1010	
1011	
1100	
1101	
1110	
1111	

FOUR VARIABLE K – MAP

POS: -

POS:-

A+B	C+D	C+D̄	C̄+D	C̄+D̄
	0 0	0 1	1 1	1 0
A+B 0 0	A+B+C+D 0	A+B+C+D̄ 1	A+B+C̄+D̄ 3	A+B+C̄+D 2
A+B̄ 0 1	A+B̄+C+D 4	A+B̄+C+D̄ 5	A+B̄+C̄+D̄ 7	A+B̄+C̄+D 6
Ā+B 1 1	Ā+B+C+D 12	Ā+B+C+D̄ 13	Ā+B+C̄+D̄ 15	Ā+B+C̄+D 14
Ā+B̄ 1 0	Ā+B̄+C+D 8	Ā+B̄+C+D̄ 9	Ā+B̄+C̄+D̄ 11	Ā+B̄+C̄+D 10

		CD	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$C\bar{D}$
AB		00	01	11	10	
✓ $\bar{A}\bar{B}$	0	$\bar{A}\bar{B}\bar{C}\bar{D}$				
	1					
	2					
	3					
$\bar{A}B$	01	4	5	7	6	
AB	11	12	13	15	14	
$A\bar{B}$	10	8	9	11	10	

for SOP


		CD	$C+D$	$C+\bar{D}$	$\bar{C}+D$	$\bar{C}+\bar{D}$
AB		00	01	11	10	
✓ $A+B$	00	M_0 $A+B+C+D$	M_1 $A+B+C+\bar{D}$			
$A+\bar{B}$	01					
$\bar{A}+B$	11					
$\bar{A}+\bar{B}$	10					

for POS

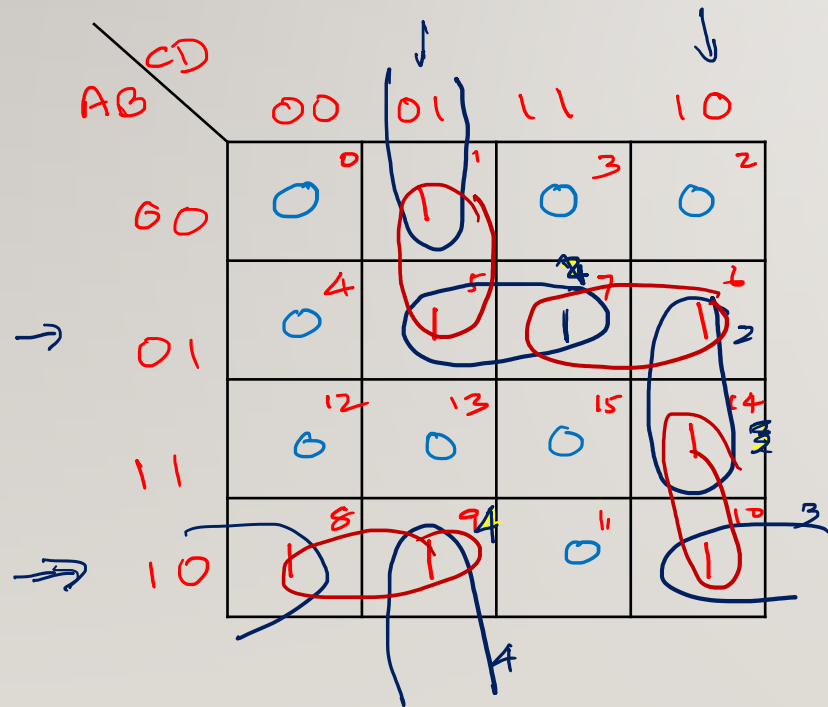EXAMPLE 1:

- Simplify the following expression into
 - SOP & give NAND realization
 - POS & give NOR realization

$$F(A,B,C,D) = \sum_m (1,5,6,7,8,9,10,14) = \prod_n (0,2,3,4,11,12,13,15)$$



SOP Group 1's

$$F = \bar{A}\bar{C}D + \bar{A}BC + A\bar{C}\bar{D} + A\bar{B}\bar{C} \checkmark$$

$$\bar{F} = \bar{A}BD + B\bar{C}\bar{D} + A\bar{B}\bar{D} + \bar{B}\bar{C}D \checkmark$$

$$m_5 + m_7 \Rightarrow \bar{A}\bar{B}\bar{C}D + \bar{A}BCD \Rightarrow \bar{A}\bar{B}(\bar{C}+C)D = \underline{\underline{\bar{A}\bar{B}D}}$$

CONTINUED...

$$F(A,B,C,D) = \sum (1,5,6,7,8,9,10,14) = \prod_m (0, 2, 3, 4, 11, 12, 13, 15)$$

- POS

AB \ CD	\downarrow C+D C+ \bar{D} \bar{C} + \bar{D} \bar{C} +D			
	00	01	11	10
A+B 00	0	1	0	0
A+ \bar{B} 01	0	1	1	1
\bar{A} + \bar{B} 11	0	0	0	1
\bar{A} +B 10	1	1	0	1

POS


$$F = (A + C + D) \cdot (A + B + \bar{C}) \cdot (\bar{A} + \bar{B} + C) \cdot (\bar{A} + \bar{C} + \bar{D})$$

OR

$$F = (\bar{B} + C + D) (\bar{A} + \bar{B} + \bar{D}) (B + \bar{C} + \bar{D}) (A + B + \bar{D})$$

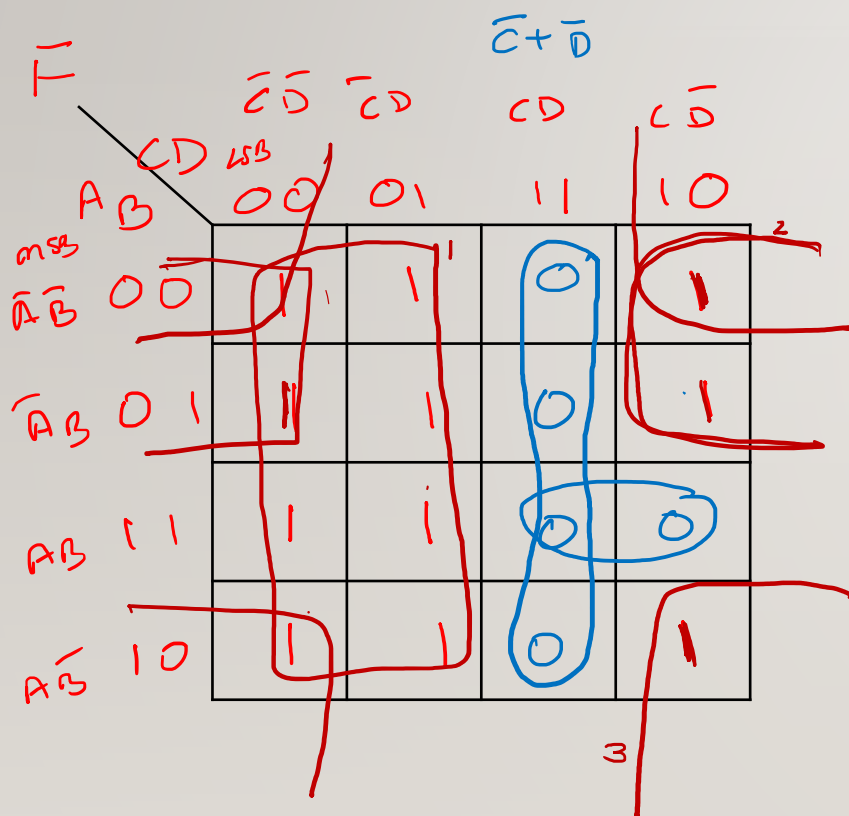EXAMPLE 2:

$$F(A, B, C, D) = \sum_{m \substack{\text{MSB} \\ \text{LSB}}} (0, 1, 2, 4, 5, 6, 8, 9, 10, 12, 13)$$



SOP: club 1's

$$F = \bar{C} + \bar{A}\bar{D} + \bar{B}\bar{D}$$

POS

$$F = (\bar{C} + \bar{D})(\bar{A} + \bar{B} + \bar{C})$$

$$F = m_0 + m_1 + m_2 + m_4 + m_5 + m_6 + m_8 + m_9 + m_{10} + m_{12} + m_{13}$$

Note: A pair of minterms combined \rightarrow 1 variable
Variables

For Ex:

$$m_{10} + m_2$$

$$\bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} \rightarrow \bar{A}\bar{B}C\bar{D}$$

$$\rightarrow (A + \bar{A})\bar{B}C\bar{D} = \bar{B}C\bar{D}$$

ONE 3/1P AND

possible


$$\underline{\underline{m_0 + m_2 + m_8 + m_{10}}}$$

$$x + x + x + x + \dots \Rightarrow x$$

EXAMPLE 3:

$$F(A, B, C, D) = \prod_m (0, 2, 3, 4, 8, 9, 10, 14)$$

$$= \sum (1, 5, 6, 7, 11, 12, 13, 15)$$

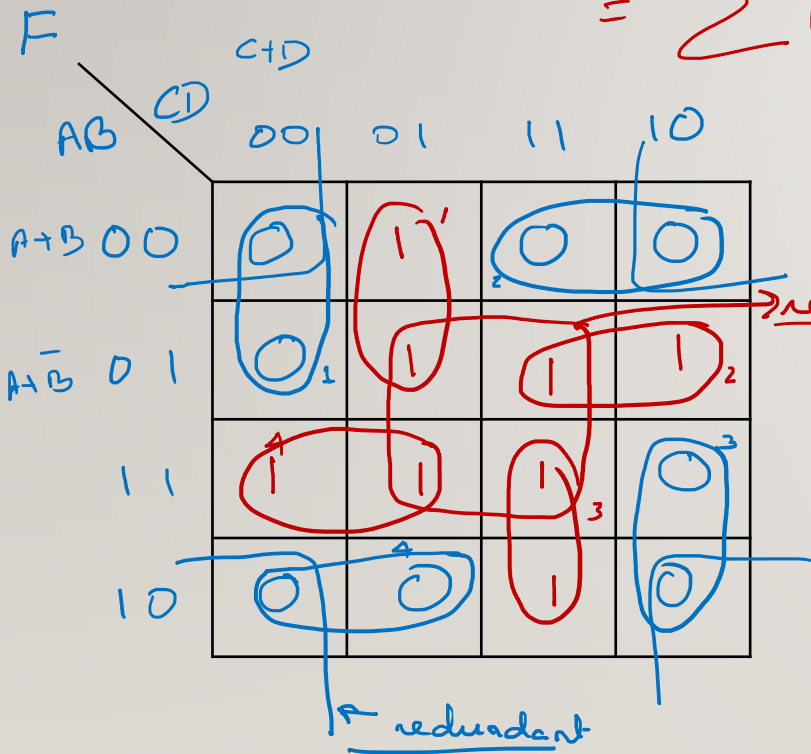

POS

$$F = (A+C+D) (A+B+\bar{C}) (\bar{A}+\bar{C}+D) (\bar{A}+B+C)$$

SOP

$$F = \bar{A}\bar{B}D + \bar{A}BC + ACD + AB\bar{C} + (\text{redundant})$$

$(1, 5)$ $(6, 7)$ $(15, 11)$ $(12, 13)$ $(5, 7, 13, 15)$
 Quad



EXAMPLE 4:

$$F(A,B,C,D) = \bar{C}(\bar{A}\bar{B}\bar{D} + D) + A\bar{B}C + \bar{D}$$

AB

LSB
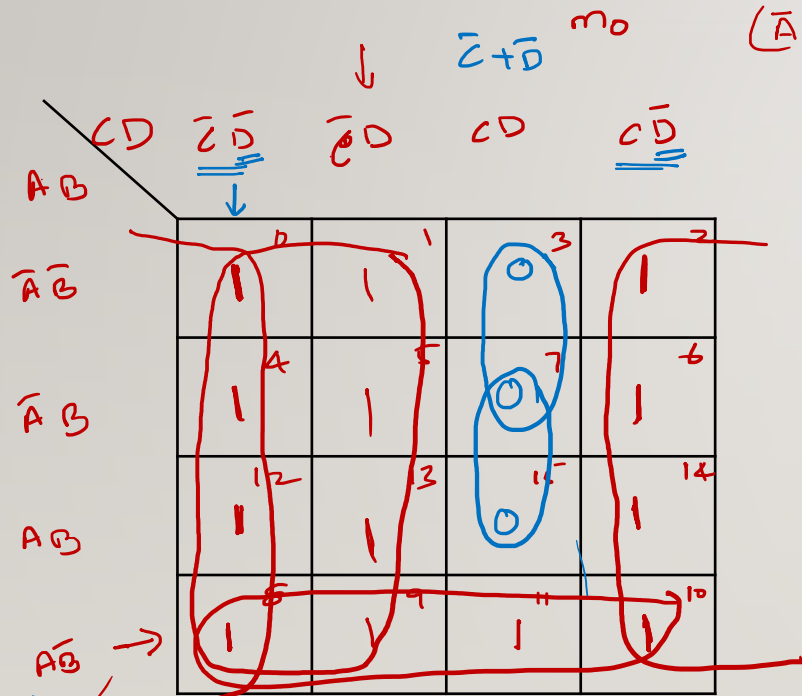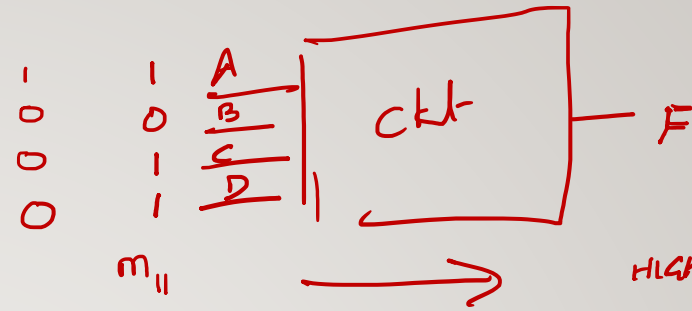
$$= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{C}D + A\bar{B}C + \bar{D}$$



$$(\bar{A}+A)(\bar{B}+B)\bar{C}D$$

$$\bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D + A\bar{B}\bar{C}D + AB\bar{C}D$$

$\bar{C}D \rightarrow$ A & B are missing
quad group

$A\bar{B}C \rightarrow$ 1 variable missing D
pair group $m_{10} \& m_{11}$

$$\bar{A}\bar{B}C(\bar{D}+D) = \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD$$

$\bar{D} \rightarrow$ 3 variable missing
group 8 minterms

Simplified Expression

$$F = \bar{C} + \bar{D} + A\bar{B}$$

POS

$$F = (A + \bar{C} + \bar{D})(\bar{B} + \bar{C} + \bar{D})$$

Distributive law

$$x + y \cdot z = (x+y)(x+z)$$

$$x(y+z) = xy + xz$$

$$F = (\bar{C} + \bar{D} + A)(\bar{C} + \bar{D} + \bar{A})$$

$$F = \sum_{m=0}^n (0, 1, 2, 4, 5, 6, 8, 9, 10, 11, 12, 13, 14)$$

EXAMPLE 5:

$$F(A,B,C,D) = D(\bar{A} + B) + \bar{B}(C + AD)$$

$$= \bar{A}D + BD + \bar{B}C + A\bar{B}D$$

$$= \sum_m (1, 2, 3, 5, 7, 9, 10, 11, 13, 15)$$

$$= \prod_m (0, 4, 6, 8, 12, 14)$$

F		CD			
		00	01	11	10
AB	$\bar{A}\bar{B}$ 00	0	1	1	1
	$\bar{A}B$ 01	0	1	1	0
	$A\bar{B}$ 11	0	1	1	0
	AB 10	0	1	1	1

$$A+B \quad \underline{\underline{POS = (C+D)(\bar{B}+D)}}$$

distributive law



$$SOP = \underline{\underline{D + (\bar{B}C)}}$$

$$\rightarrow (\bar{B}+D)(C+D)$$

distributive law

DON'T CARE CONDITION

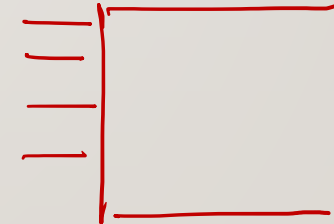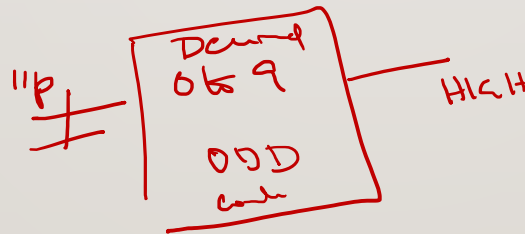- The “Don’t Care” conditions indicate the input combinations which are invalid for a particular circuit.
 ϕ d
- While forming groups of cells, we can consider a “Don’t Care” cell as either 1 or 0 or we can simply ignore that cell.
- Therefore, “Don’t Care” condition are used to form a larger group of cells.



0	0000	0
1	0111	1
2	0111	1
3	1000	0
4	1001	1
5	1010	0
6	1011	0
7	1100	0
8	1101	0
9	1110	0
10	1111	0

EXAMPLE I:

$$F(A,B,C) = \sum_m (1,3,5,7) + \sum_d (0,2)$$



$$= \prod_m (4,6) \cdot \prod_d (0,2)$$

F A	BC			
	00	01	11	10
0	0	1	1	0
1	0	1	1	0


$F = C$ SOP
only 0's
 $POS = (\bar{A} + C)$
with don't-care

$F = C$ POS

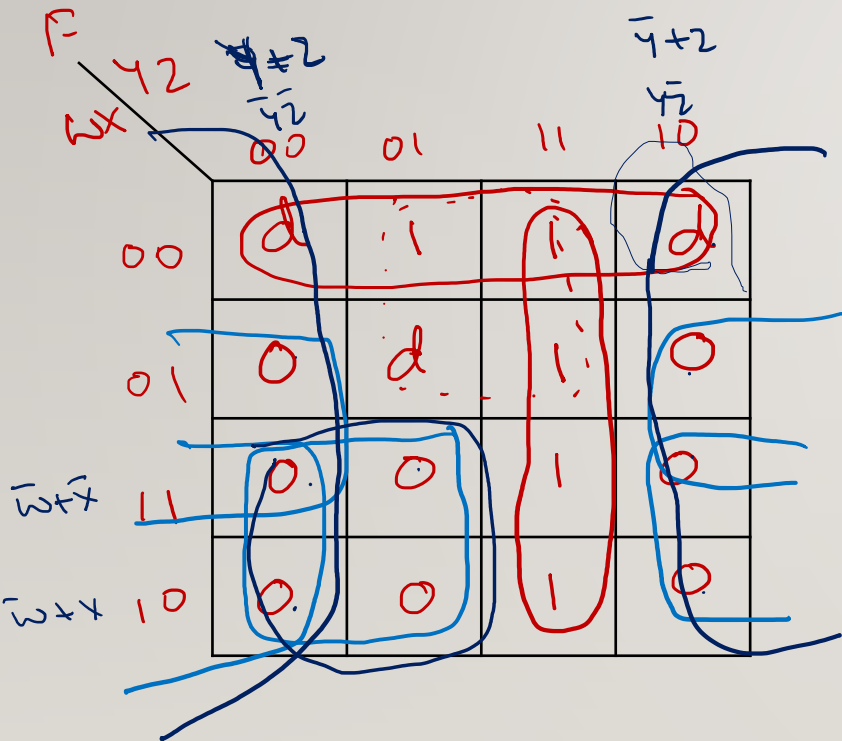EXAMPLE 2:

$$F(W,X,Y,Z) = \sum_m (1,3,7,11,15) + \sum_d (0,2,5)$$

$$= \prod_m (4,6,8,9,10,12,13,14) \cdot \prod_d (0,2,5)$$



SOP

$$F = YZ + \bar{W}X$$

OR

$$F = YZ + \bar{W}Z$$

POS $F = (\bar{W} + Y)(\bar{W} + Z)(\bar{X} + Z)$

Consider clubing with don't cares

$$F = \underline{\underline{Z + (\bar{W} + Y)}}$$

$$\underline{\underline{YZ + \bar{W}Z}}$$

EXAMPLE 3:

$$F(W, X, Y, Z) = \prod_M (0, 1, 3, 5, 8, 9, 14) \cdot \prod_D (2, 6, 10) = \sum_m 4, 7, 11, 12, 13, 15 + \sum_d 2, 6, 10$$

F \ WX \ YZ		00 01 11 10			
		0	1	3	2
00	0	0	0	0	0
01	1	1	0	1	0
11	1	1	1	1	0
10	0	0	1	0	0

$$SOP = x\bar{y}\bar{z} + wx\bar{y} + x\bar{y}z + wx\bar{y}z$$

$$POS = (w+x)(\bar{y}+z)(x+\bar{y})(w+\bar{y}+z)$$

P. Note:

clubbing rule


1. Club max number of 1's / 0's along with '0' to get max combinations
2. Check for uncovered 1's / 0's
3. if Any uncovered 1's / 0's → along with 0's go for max clubbing

EXAMPLE 4:

$$F(W, X, Y, Z) = \sum_m (1, 4, 5, 7, 9, 10, 11) + D(14, 15)$$

$$= \prod_m (0, 2, 3, 6, 8, 12, 13) \cdot D(14, 15)$$

$\phi (\quad)$
 $d (\quad)$
 $D (\quad)$

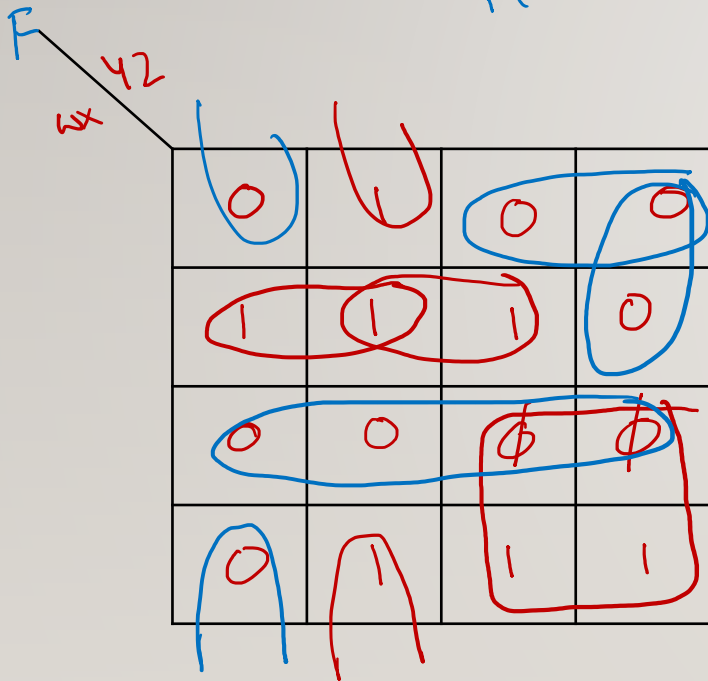

SOP $\Rightarrow F =$


pls. write

POS $\Rightarrow F =$

pls. write

EXAMPLE 5:

Design a combinational circuit with 4- input lines that represents a decimal digit in BCD and 4- output lines that generates 2's complement of input digit.

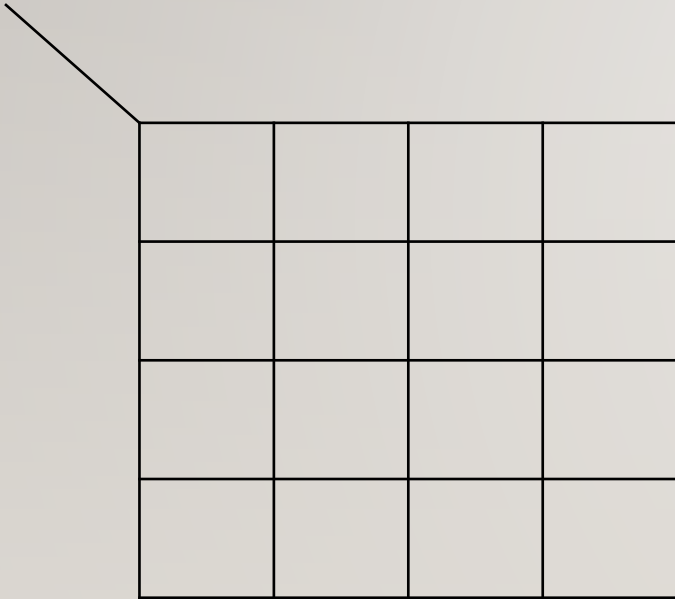

EXAMPLE 6:

Design a combinational circuit to check for even parity of 4 bits. A logic '1' output is required when the 4 bits constitute an even parity.

Karnaugh Map:

f \ wx	00	01	11	10
00	1	0	1	0
01	0	1	0	1
11	1	0	1	0
10	0	1	0	1

EX-OR gates

$A \oplus B = \overline{A}B + A\overline{B}$

Logic Diagram:

Handwritten Notes:

1's in w, x, y, z → if Yes → 1
 No → 0

4-bit

Truth Table:

w	x	y	z	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

Boolean Expression Derivation:

$$\begin{aligned}
 &= \overline{w}\overline{x}\overline{y}\overline{z} + \overline{w}\overline{x}y\overline{z} + \overline{w}x\overline{y}\overline{z} + \overline{w}xy\overline{z} \\
 &\quad + \overline{w}x\overline{y}z + \overline{w}xyz + w\overline{x}\overline{y}\overline{z} + w\overline{x}y\overline{z} \\
 &= \overline{w}\overline{x}(\overline{y}\overline{z} + y\overline{z}) + \overline{w}x(\overline{y}\overline{z} + y\overline{z}) + \overline{w}x(\overline{y}z + yz) + w\overline{x}(\overline{y}\overline{z} + y\overline{z}) \\
 &= \overline{w}\overline{x}(\overline{y} \oplus z) + \overline{w}x(\overline{y} \oplus z) + \overline{w}x(y \oplus z) + w\overline{x}(y \oplus z) \\
 &= (\overline{w}\overline{x} + \overline{w}x)(\overline{y} \oplus z) + (\overline{w}x + w\overline{x})(y \oplus z) \\
 &= (\overline{w} \oplus x)(\overline{y} \oplus z) + (w \oplus \overline{x})(y \oplus z) = \underline{\underline{w \oplus x \oplus y \oplus z}}
 \end{aligned}$$

EXAMPLE 7:

Design a combinational circuit that multiplies by '5' an input decimal digit represented in BCD. The output is also in BCD.

