

2011  
WEEK-31

BET

WEDNESDAY  
DAY (208-157)

27

WORK TO DO

BET Dr. Prateek Jain prateek.Jain@manipal.edu

- ① DC circuit analysis
- ② magnetic circuit analysis
- ③ Single phase AC circuits analysis
- ④ 3 phase AC circuit analysis
- ⑤ Power System components

$$R = \frac{fl}{A}$$

$$P = V^2/R$$
$$P = I^2 R$$

$P = \frac{l}{R}$   
less length  
more power  
less resistance

### Assessment

• 10% Quiz	<u>continuous assessment</u>
• 5 <sup>th</sup> calendar week	• 20% • 2 marks each quiz immediately after every class 5 <sup>th</sup> calendar week
• 30 minutes	• 10-15 min

### In sem

• 20%	APPOINTMENTS
• 90 min	• 50%
• 4 ques - 10 marks each	• 180 min
	• 5 ques
	- 50 marks by
	13
	14
	15
	16
	17
	18
	PHONES

### References for Numericals

- (1) Hughes C. Electrical and Electronic Technology (12e) Pearson Education
- (2) BET
- (3)
- (4)

### Scientific Calculator

casio fx-991ES plus (2<sup>nd</sup> edition) [non graphical]  
[non programmable]

### What is an electric Circuit?

An interconnection of simple electrical devices with at least one closed path in which current may flow.

- consists of a source of electrical energy, elements that either transform, dissipate or store energy, connecting wires


To prevent power overload, circuits often include fuse or circuit breaker.

JULY	2011				AUGUST				2011				
Wk	S	M	T	W	T	F	S	Wk	S	M	T	F	S
27	31	1	2	32	1	2	3	4	5	6	7	8	9
28	3	4	5	6	7	8	9	10	11	12	13	14	15
29	10	11	12	13	14	15	16	17	18	19	20	21	22
30	17	18	19	20	21	22	23	35	21	22	23	24	25
31	24	25	26	27	28	29	30	36	28	29	30	31	

**28** THURSDAY  
DAY (209-156)

July  
WEEK-31

### WORK TO DO

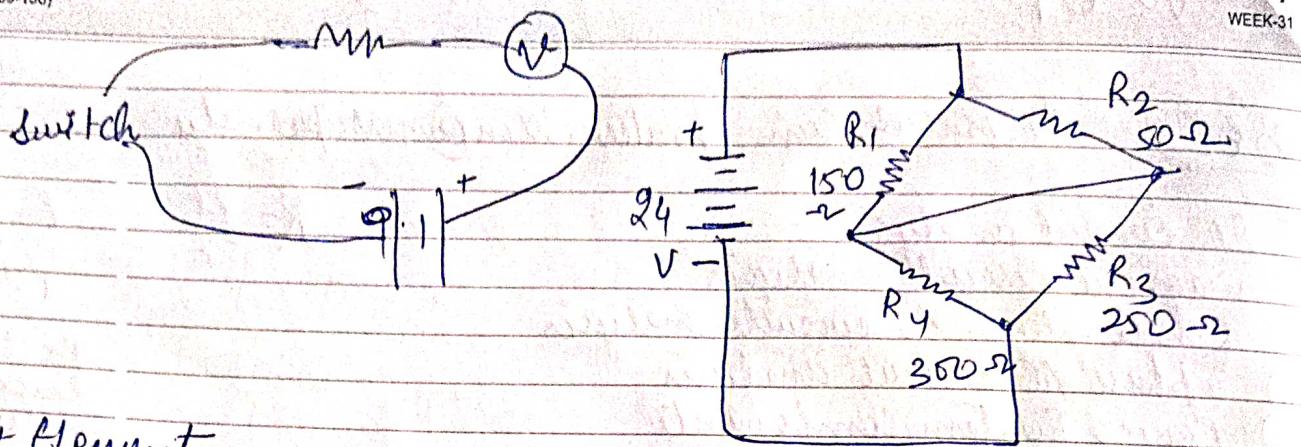

## Circuit Elements

\* Active and Passive : • Active Elements: Voltage & current sources.  
• Passive elements: Resistor, Inductor, Capacitor.

\* Linear & Non-linear Elements: • Linear: Resistor, Inductor, Capacitor

- Non-linear: Diode, ADR  
(Light dependent resistor)  
Thermistor

<sup>18</sup> ~~A~~ Unilateral & Bilateral: Unilateral (current flow in one direction) : Diode, transistor  
PHONES

Bilateral: Resistor, Inductor, capacitor

\* Lumped & distributed: lumped elements are simplified version of distributed elements.

Our study is limited to lumped linear bilateral circuit elements. 7

2011


WEEK-33

## Active elements - sources

### Voltage source

- Ideal: Maintains constant voltage irrespective of connected load.  $I_L \rightarrow$
- Internal Resistance  $R_s = 0$

Ideal Voltage Source  
(DC)

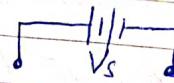

$$V_L = V_s$$

FRIDAY  
DAY (224-141)


12

WORK TO DO

### Practical : (Real voltage source)

- Terminal voltage changes based on the connected load.
- Internal resistance  $R_s \neq 0$

$\downarrow$   
should be small.

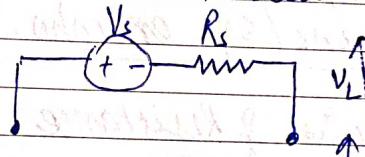



$$V_L = V_s - I_L R_s$$

### Current source

- Ideal : Maintains constant current irrespective of the load connected.

- Internal resistance  $R_s = \infty$

Ideal Current Source (DC)

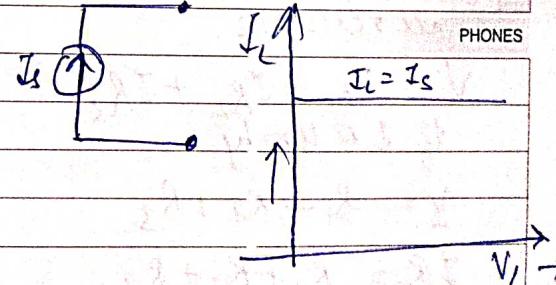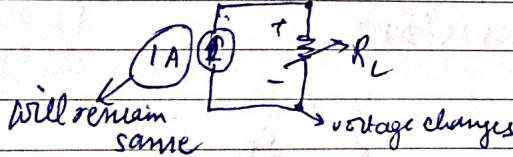

### Practical (Real current source)


- Output current changes based on the connected load.

- Internal Resistance  $R_s < \infty$

v. high

if  $R_s = \infty$

Practical current source = Ideal.

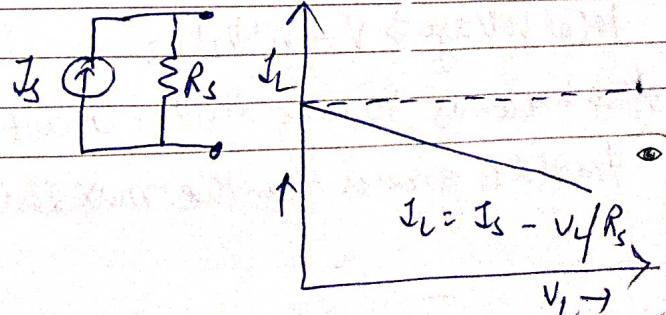

$$I_L = I_s - V_L / R_s$$

AUGUST 2011							SEPTEMBER 2011								
Wk	S	M	T	W	T	F	S	Wk	S	M	T	W	T	F	S
32	1	2	3	4	5	6		36		1	2	3			
33	7	8	9	10	11	12	13	37	4	5	6	7	8	9	10
34	14	15	16	17	18	19	20	38	11	12	13	14	15	16	17
35	21	22	23	24	25	26	27	39	18	19	20	21	22	23	24
36	28	29	30	31				40	25	26	27	28	29	30	



2011

WEEK-39

MONDAY


DAY (262-103)

19

WORK TO DO

## RESISTORS


Series Resistors

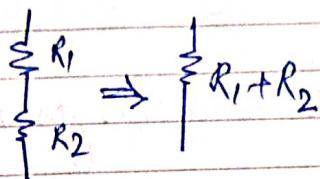

eq. Resistance

$$R_1 + R_2$$


Voltage Divider

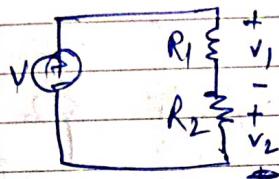

$$V_1 = \frac{R_1}{R_1 + R_2} V_s$$

$$V_2 = \frac{R_2}{R_1 + R_2} V_s$$

Parallel Resistors

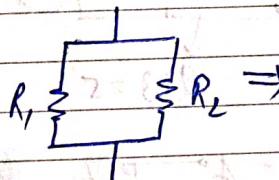


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

APPOINTMENTS

Current Divider

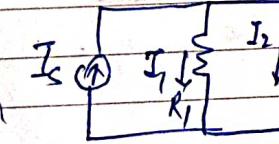

$$I_1 = \frac{R_2}{R_1 + R_2} I_s$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$

# Delivering and absorbing power by a source

A battery is discharging (delivering power/energy) if,

- Current coming out from positive (+) terminal

A battery is charging (absorbing power/energy) if,  
current flowing into positive (+) terminal# When current flows through a resistor,  
o Power is dissipated.

SEPTEMBER 2011						
Wk	S	M	T	W	F	S
36				1	2	3
37	4	5	6	7	8	9
38	11	12	13	14	15	16
39	18	19	20	21	22	23
40	25	26	27	28	29	30

OCTOBER 2011						
Wk	S	M	T	W	F	S
40	30	31				1
41	2	3	4	5	6	7
42	9	10	11	12	13	14
43	16	17	18	19	20	21
44	23	24	25	26	27	28

20

# TUESDAY


## DAY (263-102)

# September

## WORK TO DO


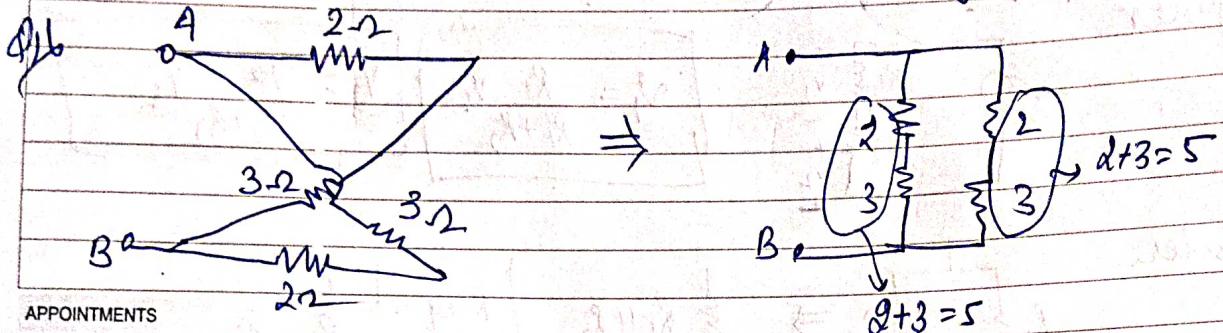
## ILLUSTRATIONS - 1

Find the equivalent resistance of the networks given below.




$$= \frac{1}{5} + \frac{1}{5} = \frac{2}{5}$$

$$\text{Req} = \frac{5/2 - 2}{2}$$

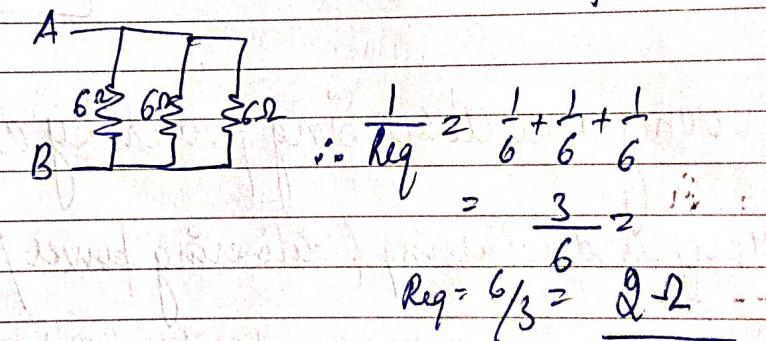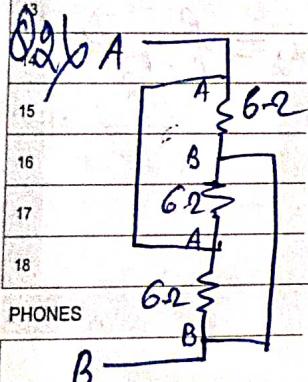

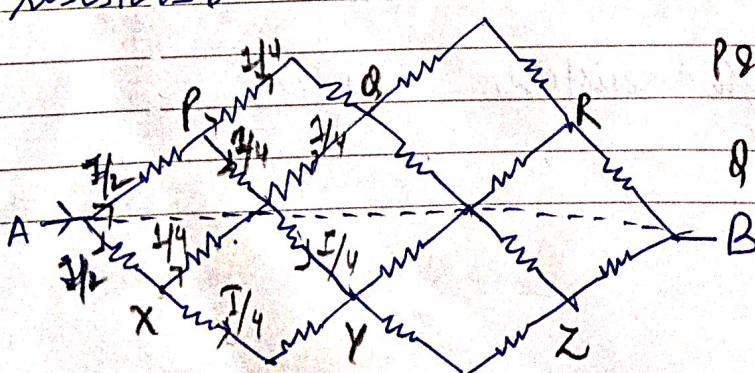Determine the Reg between A and B for given resistive network with 1-2 resistors.



$P_2 X = \text{same potential}$  HORIZONTAL WAY OF SYMMETRY

JULY	2011					AUGUST					2011				
WK.	S	M	T	W	T	F	S	S	M	T	W	T	F	S	S
27	31								3	4	5	6	7	8	9
28									33	7	8	9	10	11	12
29	10	11	12	13	14	15	16		34	14	15	16	17	18	19
30	17	18	19	20	21	22	23		35	21	22	23	24	25	26
31	24	25	26	27	28	29	30		36	28	29	30	31		


2011

WEEK-39

WEDNESDAY  
DAY (264-101) 21


current cannot flow through same potential points hence is can be treated as open circuit

WORK TO DO

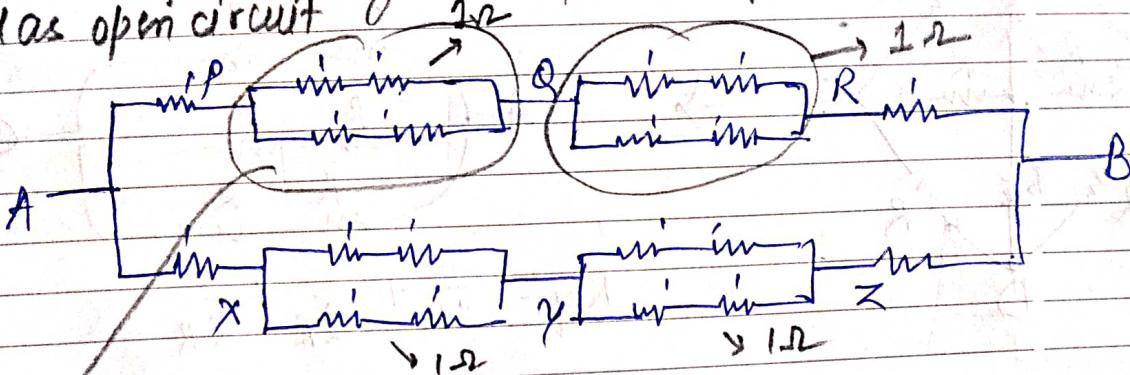

$$R_{eq} = \frac{1}{\frac{1}{2} + \frac{1}{2}}$$

$$\frac{2}{2} = 1$$

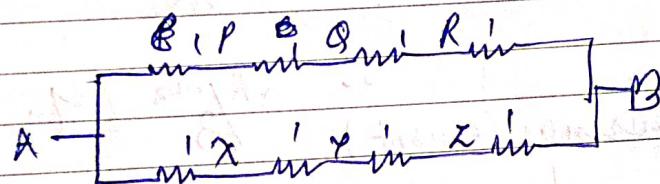


$$R_{eq} = \frac{1}{4} + \frac{1}{4} = \frac{2}{4} = R_{eq} = \frac{1}{2}$$

$\boxed{2-2}$

Q4) Determine the equivalent resistance between points A and C for given resistive network.

VERTICAL PLANE OF SYMMETRY

PHONES

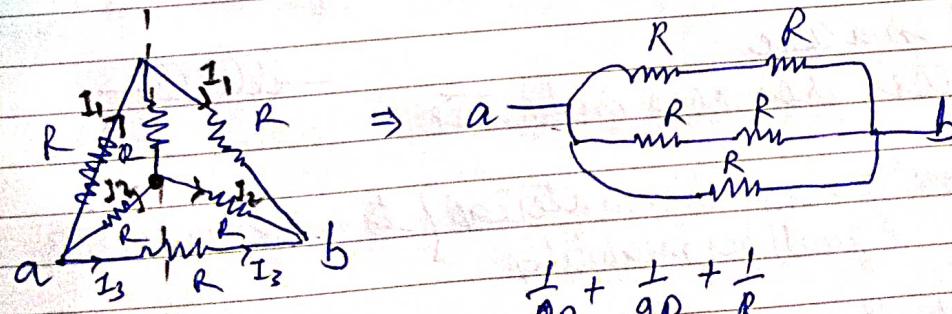

$$\frac{1}{R} + \frac{1}{2R} + \frac{1}{R}$$

$$\Rightarrow \frac{1+1+2}{2R}$$

$$= \frac{4}{2R}$$

$$\frac{2R}{4} = \boxed{\frac{R}{2} = R_{eq}}$$

Points of vertical plane of symmetry have same potential

→ Branches have same

current

Points having same potential means no current can pass through them so,



SEPTEMBER 2011							OCTOBER 2011							
Wk	S	M	T	W	T	F	S	Wk	S	M	T	W	F	S
36	4	5	6	7	8	9	10	40	30	31	1			
37	11	12	13	14	15	16	17	41	2	3	4	5	6	7
38	18	19	20	21	22	23	24	42	9	10	11	12	13	14
39	25	26	27	28	29	30		43	16	17	18	19	20	21
40								44	23	24	25	26	27	28

08

22

THURSDAY  
DAY (205-100)September  
WEEK-39

WORK TO DO

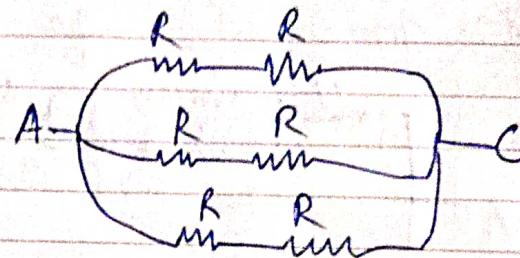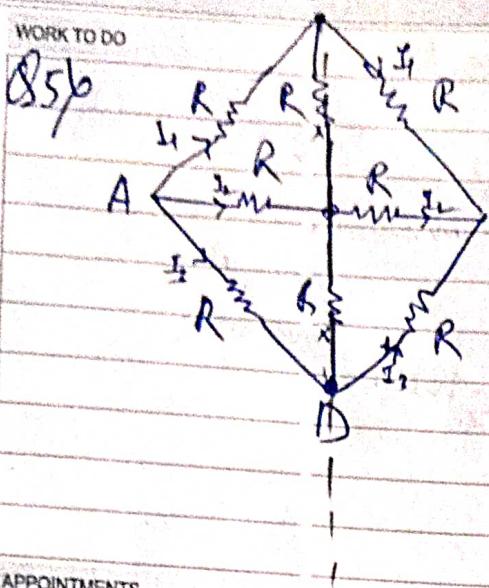

$$\frac{1}{R_{eq}} = \frac{1}{2R} + \frac{1}{2R} + \frac{1}{\frac{R}{2}}$$

$$\frac{1+1+1}{2R} = \frac{3}{2R}$$

$$\therefore \frac{2R}{3} = R_{eq}$$

APPOINTMENTS

09

10

11

12

335

2011  
WEEK 41FRIDAY  
DAY (280-085) 07

## Inductive Circuit

WORK TO DO


For a coil uniformly wound on a non-magnetic core of uniform cross section, self inductance is given by

$$L = \frac{4\pi A N^2}{l}$$

Where,  $l$  = length of the magnetic circuit in metres  
 $A$  = cross sectional area in sq. meters  
 $\mu_0$  = Permeability of air =  $4\pi \times 10^{-7}$   
 $N$  = No of turns in the coil.


APPOINTMENTS

## Equivalent Inductance

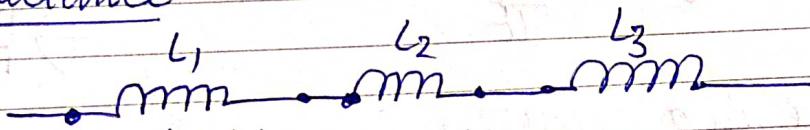

$$\text{In series} = L_{eq} = L_1 + L_2 + L_3 + \dots + L_n$$

In parallel

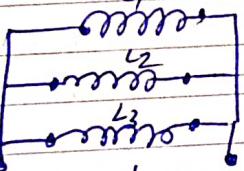

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_n}$$

## Energy stored in an Inductor

$$\text{Instantaneous Power, } P = V_i i = L i \frac{di}{dt}$$

- energy absorbed in  $dt$  time is  $dW = L i di$

- energy absorbed by the magnetic field when current increases from 0 to  $I$  amperes is,


$$W = \int_0^I L i dt = \frac{1}{2} L I^2$$

OCTOBER 2011						NOVEMBER 2011							
W	S	M	T	W	F	S	W	S	M	T	W	F	S
40	30	31	1	2	3	4	45	1	2	3	4	5	
41	2	3	4	5	6	7	46	6	7	8	9	10	11
42	9	10	11	12	13	14	15	13	14	15	16	17	18
43	16	17	18	19	20	21	22	20	21	22	23	24	25
44	23	24	25	26	27	28	29	27	28	29	30		

WORK TO DO

Capacitors

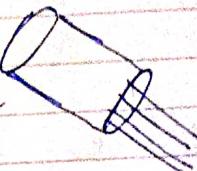- Passive electric device that stores energy in the electric field between a pair of closely spaced conductors.
- Capacitance - property which opposes the rate of change of voltage  
Symbol:  $C$   
Unit: ~~F~~ Farad ( $F$ )
- The capacitive current is proportional to the rate of change of voltage across it.



$$i_c = C \frac{dv_c}{dt}$$

$$\rightarrow +$$

APPOINTMENTS

09

10

11

12

13

14

15

16

17

18

PHONES

Electric field strength,  $E = \frac{V}{d}$  [Volts/m]

Electric Flux density =  $D = \frac{Q}{A}$  [ $C/m^2$ ]

Permitivity of free space =  $8.854 \times 10^{-12} F/m$

$$E_0 = \frac{Q}{A} = \frac{Q}{dA}$$

Relative permittivity =  $\epsilon_r$

- Capacitance of parallel plate capacitor

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

Farad = coulomb  
volt.



AUGUST 2011							SEPTEMBER 2011								
Wk	S	M	T	W	T	F	S	Wk	S	M	T	W	T	F	S
32		1	2	3	4	5	6	36		1	2	3			
33	7	8	9	10	11	12	13	37	4	5	6	7	8	9	10
34	14	15	16	17	18	19	20	38	11	12	13	14	15	16	17
35	21	22	23	24	25	26	27	39	18	19	20	21	22	23	24
36	28	29	30	31				40	25	26	27	28	29	30	


2011  
WEEK-42

$$P = VI$$

$$P = I^2 R$$

$$V = IR$$

## Equivalent Capacitance

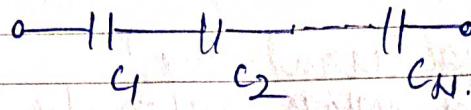

Capacitance in series

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n}$$

Capacitance in Parallel

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_n$$

## Energy Stored in a Capacitor

Instantaneous power  $P = V_c \times i = C V_c \frac{dv_c}{dt}$

Energy supplied during  $dt'$  time is:  $dW = C V_c dv_c$

Energy stored in the electric field when potential rises from 0 to  $V$  volts is

$$W = \int_0^V C V_c dv_c = \frac{1}{2} CV^2 \text{ Joules}$$

## Illustrations & Star Delta

Two incandescent bulbs have following ratings:

Bulb 1 = 120V, 60W


Bulb 2 = 240V, 480W,

(a) Both of them are connected in series across a voltage source.

OCTOBER 2011				NOVEMBER 2011			
W.	S	M	T	W	F	S	T
40	30	31	1	45	1	2	3
41	2	3	4	5	8	6	7
42	9	10	11	12	15	13	14
43	16	17	18	19	21	19	20
44	23	24	25	26	27	28	29

(b) Which will glow brighter and why?

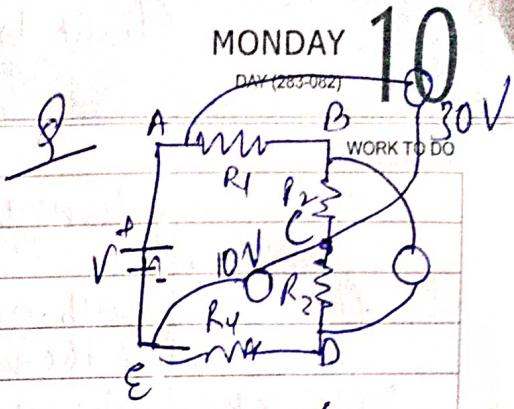(c) What is the maximum voltage that can be applied so that none of the bulbs fuse.



$$\begin{aligned} \text{Source Voltage} &= [V_{AB} + V_{BC}] \\ &\quad + V_{CD} + V_{DE} \\ &= 80 + 10V \\ &= 90V \end{aligned}$$

APPOINTMENTS

09

10

11

12

13

14

15

16

17

18

PHONES


11

TUESDAY (Limit to lower limit),  
DAY (284-081)

WORK TO DO

(b) Now both of them are connected in parallel across a voltage source.

- (i) which bulb will glow brighter and why?  
(ii) what is the maximum voltage that can be applied so that none of the bulbs fuse?

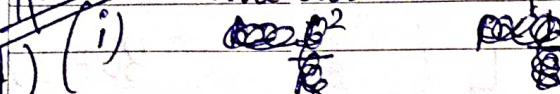~~Ans~~ Same current will flow.

$$P_1 = \frac{V^2}{R}$$

$$P_1 = \frac{120 \times 120}{R}$$

$$R = \frac{120 \times 120}{240} = 60\Omega$$

$$R_1 = \frac{60}{120} = 0.5\Omega$$

$$R_1 = \frac{120 \times 120}{R}$$


$$= \frac{120 \times 120}{240} = 60\Omega$$

$$P_2 = \frac{V^2}{R}$$

$$P_2 = \frac{240 \times 240}{R}$$


$$\Rightarrow R = \frac{240 \times 240}{120} = 120\Omega$$

$$I_{R_2} = \frac{980}{240} = 2A$$

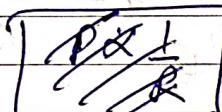


~~Since resistance is inversely proportional to power, Hence bulb B<sub>2</sub> has less resistance and more power. Hence it will glow brighter.~~

PHONES

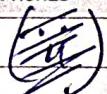

series connection

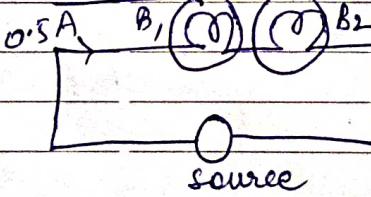

max current permitted will be 0.5A, otherwise the bulb L<sub>1</sub> will fuse in case of 2A.

$$P_1 = (0.5)^2 \times R_1 \Rightarrow (0.5)^2 \times 240\Omega = 60W$$

$$P_2 = (0.5)^2 \times 120\Omega = 30W$$

$P_1 > P_2$ , B<sub>1</sub> will glow brighter.

$$(ii) V_{total} = 0.5 \times R_1 + 0.5 \times R_2$$

$$= 0.5(R_1 + R_2)$$


$$= 0.5(360)$$

$$= 180V \rightarrow \text{max voltage.}$$

AUGUST 2011							SEPTEMBER 2011							
Wk.	S	M	T	W	T	F	S	Wk.	S	M	T	W	T	F
32		1	2	3	4	5	6	36		1	2	3		
33	7	8	9	10	11	12	13	37	4	5	6	7	8	9
34	14	15	16	17	18	19	20	38	11	12	13	14	15	17
35	21	22	23	24	25	26	27	39	18	19	20	21	22	23
36	28	29	30	31				40	25	26	27	28	29	30

2011

WEEK-42

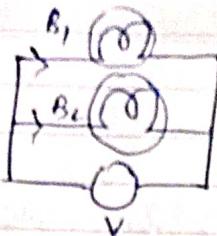WEDNESDAY  
DAY (085-086) 12B (i)

$$\text{max voltage permitted} = \underline{120 \text{ V}}$$

(Remains same)

In case of 240, bulb will  
fuse.

$$P_1 = \frac{V^2}{R} \Rightarrow \frac{120^2}{240} = 60 \text{ W}$$

$$P_2 = \frac{V^2}{R} = \frac{120^2}{120} = 120 \text{ W.}$$


∴ since  $P_2 > P_1$ 

Bulb 2 will glow brighter.


(ii) 120 V is max voltage that can be applied, as same voltage flows.

Illustration - 2

- What is the equivalent resistance across the terminals A & B in the network shown.

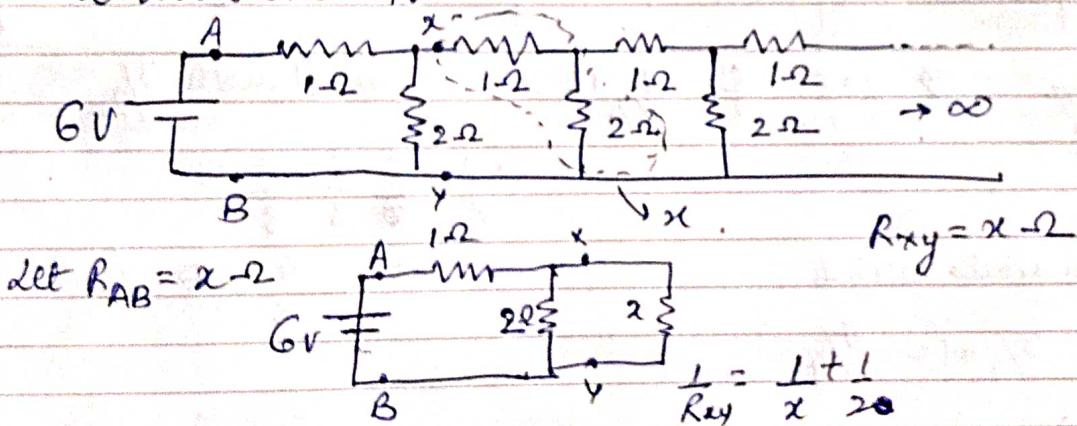Infinite ladder  
Circuit

$$\text{Let } R_{AB} = x \Omega$$

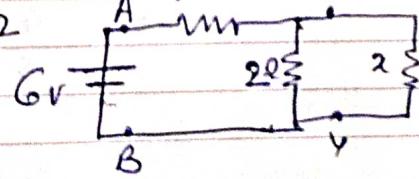

$$R_{xy} = x \Omega$$

$$\frac{1}{R_{xy}} = \frac{1}{x} + \frac{1}{2}$$

$$\frac{1}{R_{xy}} = \frac{2+x}{2x}$$

$$R_{AB} = 1 + \frac{2x}{2+x}$$

$$R_{xy} = \frac{2x}{2+x}$$

$$x = 1 + \frac{2x}{2+x}$$

$$x = \frac{2x+x+2x}{2x+x} \Rightarrow 2x+x^2 = 2+x+2x$$

$$2x+x^2 = 2x+2x+2x$$

$$x^2 - x - 2 = 0$$

$$x^2 - x - 2 = 0$$

$$x^2 - 2x + x - 2 = 0$$

$$x(x-2) + 1(x-2) = 0$$

$$(x+1)(x-2) = 0$$

$$x = -1 \quad x = 2 \Omega$$

$$R_{AB} = x \Omega \\ = 2 \Omega$$

OCTOBER	2011	NOVEMBER	2011			
S	M	T	W	T	F	S
30	31		1	2	3	4
31	1	2	3	4	5	6
2	3	4	5	6	7	8
3	4	5	6	7	8	9
4	5	6	7	8	9	10
5	6	7	8	9	10	11
6	7	8	9	10	11	12
7	8	9	10	11	12	13
8	9	10	11	12	13	14
9	10	11	12	13	14	15
10	11	12	13	14	15	16
11	12	13	14	15	16	17
12	13	14	15	16	17	18
13	14	15	16	17	18	19
14	15	16	17	18	19	20
15	16	17	18	19	20	21
16	17	18	19	20	21	22
17	18	19	20	21	22	23
18	19	20	21	22	23	24
19	20	21	22	23	24	25
20	21	22	23	24	25	26
21	22	23	24	25	26	27
22	23	24	25	26	27	28
23	24	25	26	27	28	29
24	25	26	27	28	29	30

www


13 THURSDAY  
DAY (286-079)

WORK TO DO

Illustration - 3

15 resistors are reconnected as shown in diagram. Each of the resistors has resistance  $1\ \Omega$ .

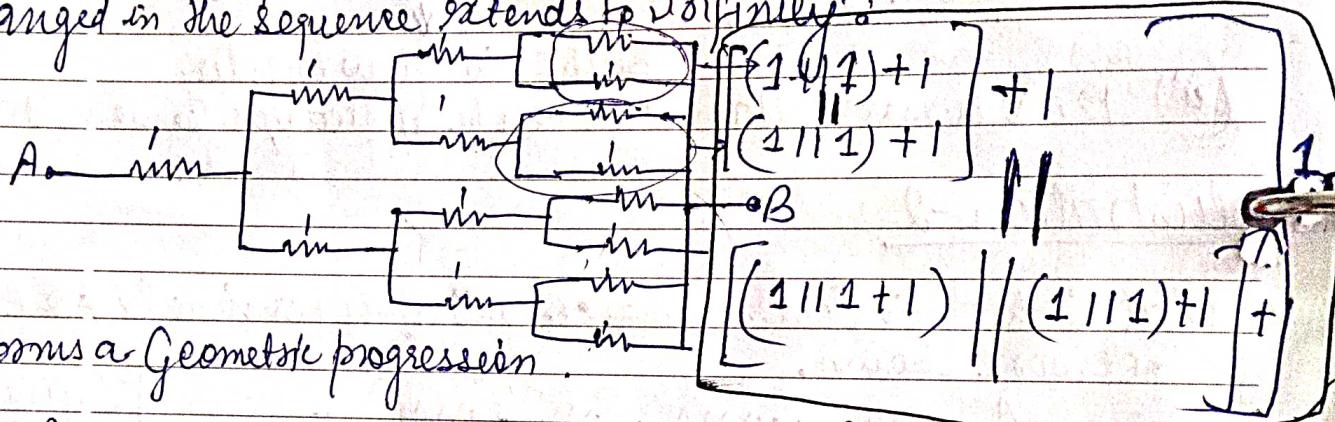- Find the equivalent resistance of the network between A & B.
- What will be the equivalent resistance of this network if the resistors arranged in the sequence extends to infinity?



This forms a Geometric progression.

$$\frac{1}{R} = \frac{1}{1+1} = \frac{1}{2} = \frac{1}{1+1} + 1 = \frac{3}{2} \text{ or } 1 \text{ with } \frac{3}{2}$$

$$\therefore \frac{1}{R} = \frac{1}{3} + \frac{2}{3}$$

$$= \frac{4}{3} \Rightarrow \frac{3}{4}$$

$$\frac{3}{4} + 1 = \frac{7}{4}$$

Similarly  $\frac{7}{4}$  is in parallel  $\frac{7}{4}$ .

$$\therefore \frac{1}{R} = \frac{4}{7} + \frac{4}{7}$$

$$= \frac{8}{7} \Rightarrow \frac{7}{8} \Omega$$

$\frac{7}{8} \Omega$  is in series with  $1 \Omega$

$$= \frac{7}{8} + 1 = \boxed{\frac{15}{8} \Omega} = \boxed{1.875 \Omega}$$

Ans //,

AUGUST

2011

Wk.	S	M	T	W	T	F	S
32	1	2	3	4	5	6	
33	7	8	9	10	11	12	13
34	14	15	16	17	18	19	20
35	21	22	23	24	25	26	27
36	28	29	30	31			

SEPTEMBER

2011

Wk.	S	M	T	W	T	F	S
36	4	5	6	7	8	9	10
37	11	12	13	14	15	16	17
38	18	19	20	21	22	23	24
39	25	26	27	28	29	30	

2011

WEEK 44

(b) This extends to a Geometric Progression.

$$a, ar^2, ar^3, ar^4, \dots, ar^{n-1}$$

$$\text{1st term} = a$$

$$\text{n}^{\text{th}} \text{ term} = a(r^{n-1})$$

$$\text{Sum of } n \text{ terms} = \frac{a(1-r^n)}{1-r}$$

Sum of upto  $\infty$

$$S_{\infty} = \frac{a}{1-r}$$

$$\text{Here } a=1$$

$$r = 1/2 \text{ because I and II in parallel}$$

MONDAY  
DAY (297-068)

24

WORK TO DO

~~$$R = \frac{ar^0}{r}$$~~



$$R = \frac{a}{r}$$

$$\frac{32}{2} = \frac{2, 4, 8, 16, 32}{2, 2} \text{ in each } 2, 2 \text{ resistances are in II therefore } r = 1/2$$

$$S_{\infty} = \frac{1}{1-1/2} = \frac{1}{1/2} = \underline{\underline{2\Omega}}$$

## Star Delta Transformation.

[Network reduction technique]

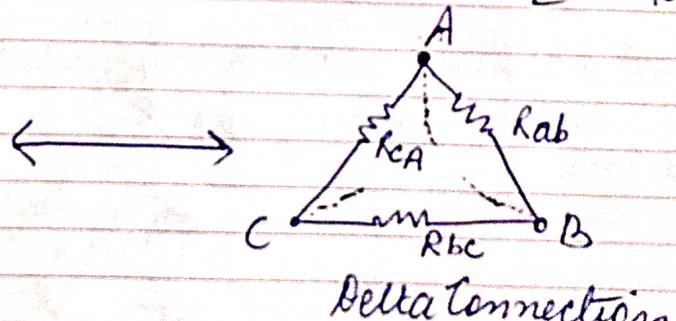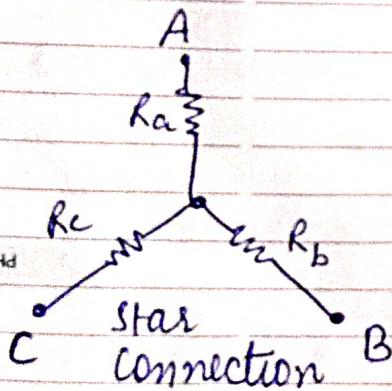

(1) From Delta to Star

$$R_A = \frac{R_{CA} * R_{AB}}{R_{CA} + R_{AD} + R_{BC}}$$

$$R_B = \frac{R_{AB} * R_{BC}}{R_{CA} + R_{AD} + R_{BC}}$$

$$R_C = \frac{R_{CA} * R_{BC}}{R_{CA} + R_{AD} + R_{BC}}$$

25 TUESDAY  
DAY (298-067)

October  
WEEK 44

WORK TO DO

(2) Star to Delta

$$R_{ab} = \frac{R_a + R_b + R_c}{R_c}$$

$$R_{bc} = \frac{R_b + R_c + R_a}{R_a}$$

$$R_{ca} = \frac{R_c + R_a + R_b}{R_b}$$

$$R_\star = R_A = R_B = R_C$$

$$R_\Delta = R_{AB} = R_{BC} = R_{CA}$$


$$R_\Delta = 3R_\star$$

$$R_\star = \frac{1}{3}R_\Delta$$

Illustrations - 4

APPOINTMENTS

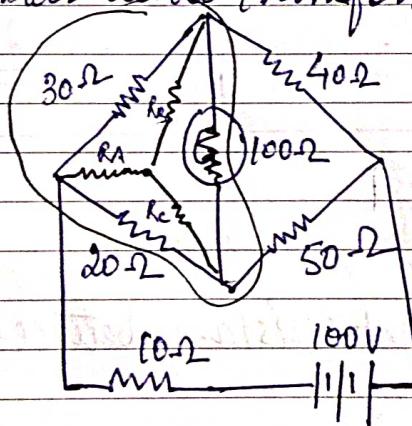For the circuit shown, determine the total power supplied by the source using star-delta transformation.



PHONES

converting to star.  $R_A = \frac{20 \times 30}{5150}$ ,  $R_B = \frac{30 \times 40}{5150}$ ,  $R_C = \frac{20 \times 40}{5150}$


$$\Rightarrow 4 \Omega$$

$$40 \Omega$$

$$60 \Omega$$

$$40/3 \Omega$$

$$= 13.33 \Omega$$

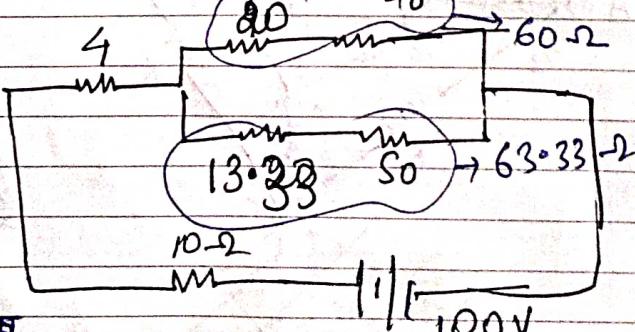

$$\frac{1}{60} + \frac{1}{63.33}$$

$$\frac{60 \times 63.33}{60 + 63.33} = 30.81$$

$$R_{total} = 4 + 10 + 30.81 = 44.81$$

$$\rightarrow P = \frac{V^2}{R}$$

$$\rightarrow \frac{100 \times 100}{44.81} = 223.16 W$$

AUGUST 2011 SEPTEMBER 2011

Wk	S	M	T	W	F	S	Wk	S	M	T	W	F	S
32	2	3	4	5	6	7	33	8	9	10	11	12	13
33	9	10	11	12	13	14	34	14	15	16	17	18	19
34	15	16	17	18	19	20	35	21	22	23	24	25	26
35	21	22	23	24	25	26	36	27	28	29	30	31	1

44.81072


P = 223.16 W

44.81072

Q & 3.16 W
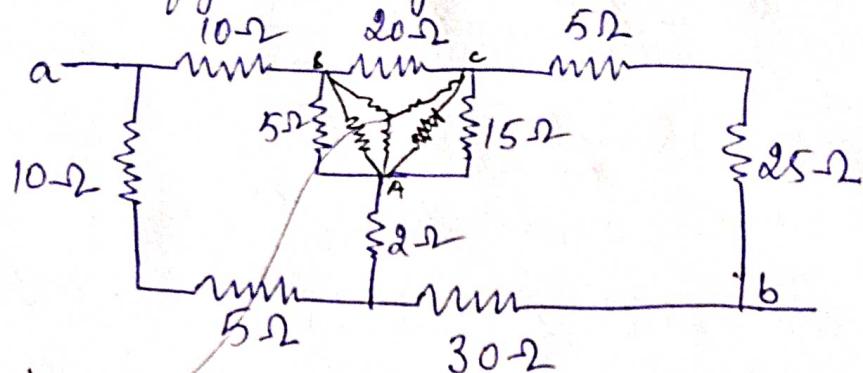
## Illustration - 5


Determine the resistance between the terminals  $a$  and  $b$  of the network shown in figure, using star delta transformation.



→ convert to star transformation

$$R_A = \frac{5 \times 15}{8.75} \quad R_B = \frac{5 \times 20}{24.0} \quad R_C = \frac{20 \times 15}{24.0}$$

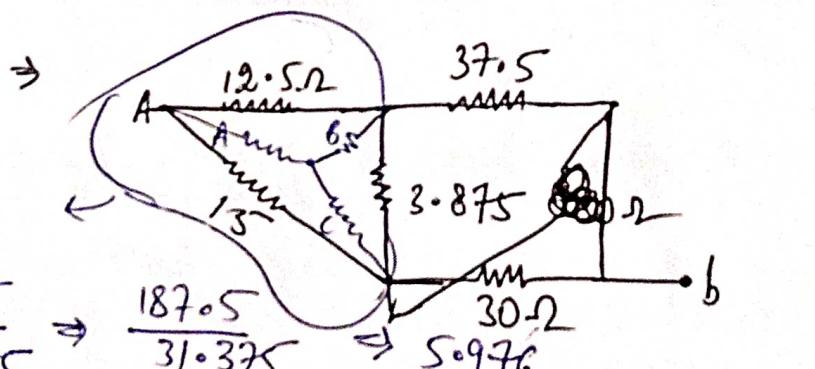
$$\left. \begin{array}{l} R_A = 15/8 \\ 1.875 \end{array} \right] \quad \left. \begin{array}{l} R_B = 5/2 \\ 2.5 \end{array} \right] \quad \left. \begin{array}{l} R_C = 15/2 \\ 7.5 \end{array} \right]$$



$$A = \frac{12.5 \times 15}{31.375} \Rightarrow \frac{187.5}{31.375} \Rightarrow 5.976$$

$$B = \frac{12.5 \times 3.875}{31.375} \Rightarrow \frac{48.4375}{31.375} \Rightarrow 1.544$$
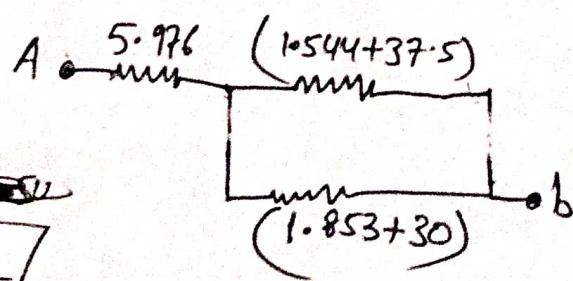
$$C = \frac{15 \times 3.875}{31.375} \Rightarrow \frac{58.125}{31.375} \Rightarrow 1.853$$



$$R_{ab} = \frac{1.544 + 37.5}{1.853 + 30} \Rightarrow 23.518\Omega$$

$$37.549.8 / 12.25 \approx 37$$

Q Two incandescent bulbs of 40 W and 60 W are connected in series across mains. Assuming the voltage to be same.

$$\cancel{P = \frac{V^2}{R}}$$

$$P \propto \frac{1}{R}$$

~~$$P = \frac{V^2}{R}$$~~

$$R_{40} = \frac{x^2}{40}, \quad R_{60} = \frac{x^2}{60}$$

~~$P = \frac{V^2}{R}$~~  when connected in series current flowing through each element is same.

$$\text{then } P_{40W} = I^2 R > P_{60} = I^2 R_{60}$$

40 W will glow brighter

$$P = \frac{40}{40} \left( \frac{40}{x} \right)^2 \times R_{40W}$$

$$= \left( \frac{40}{x} \right) \times \frac{x^2}{40} = 40W$$

$$P_{\text{tot}} = 40 + 26.66$$


$$= \underline{\underline{66.667 \text{ W}}}$$

$$P_{60} = \left( \frac{60}{x} \right) \times \frac{x^2}{60} = \frac{60}{x} = \frac{160}{6}$$


$$\frac{40 \times 40}{x} \times \frac{x^2}{60} = \frac{160}{6}$$



$$= 26.66 \text{ W}$$

## \* Homework - 1 and Homework - 2

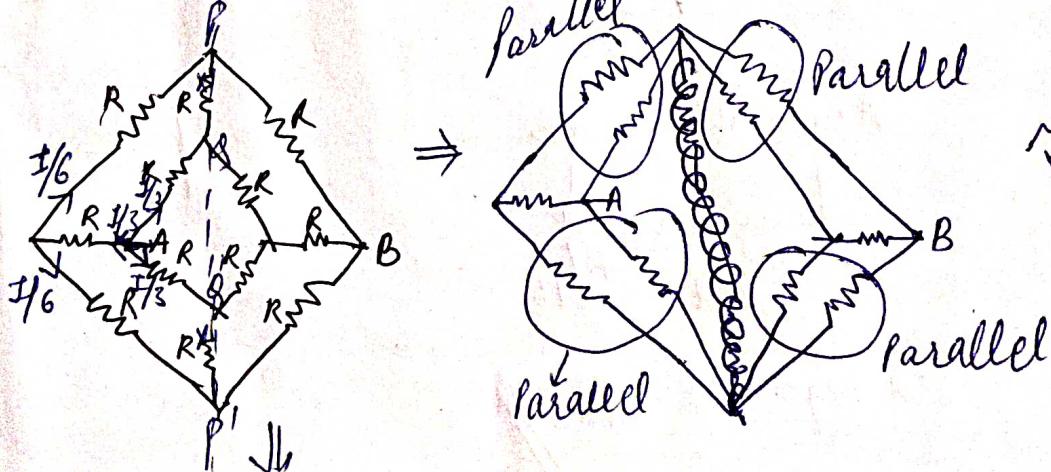

Told into halves horizontally


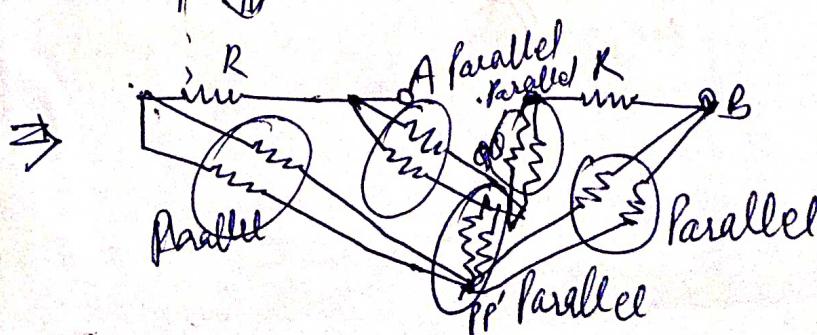


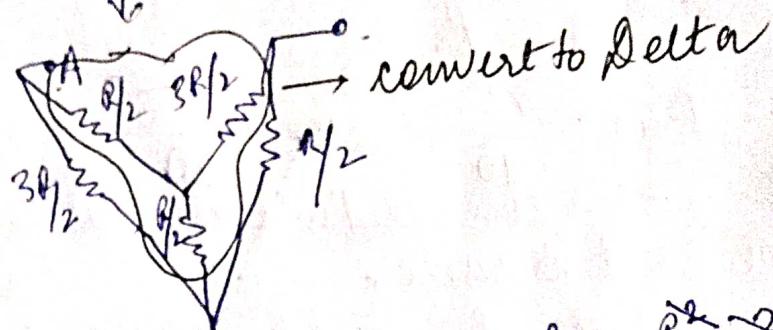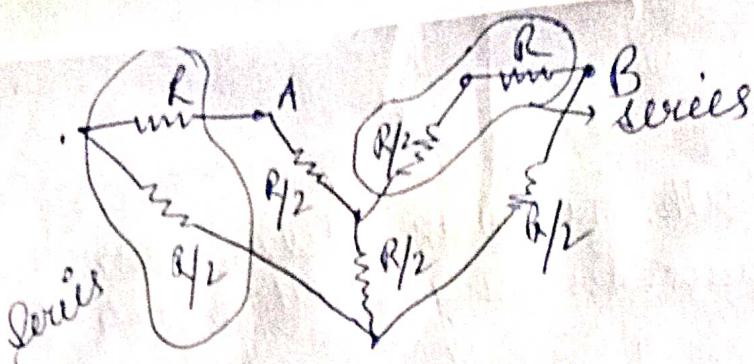

$$R_{AB} = R/2 + R/2 + \frac{R/2 \times R/2}{3R/2} = R + \cancel{\cdot \frac{R/2}{2}} \cancel{\frac{R/2}{2}} \frac{R^2}{3R} = R + \frac{R}{6} = 7R/6$$


$$R_{BC} = \frac{BR}{2} + \frac{R}{2} + \frac{3R/2 \times R/2}{R/2} = 2R + \cancel{\cdot \frac{3R^2}{4}} \cancel{\frac{2}{X}} = 2R + \frac{3R}{2} = 7R/2$$
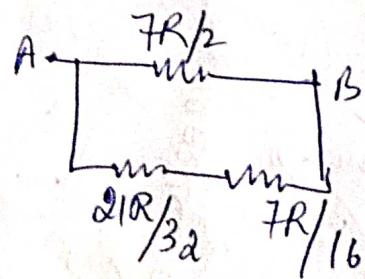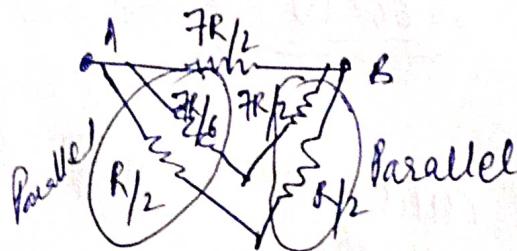
$$R_{AC} = 3R/2 + R/2 + \frac{3R/2 \times R/2}{R/2} = \cancel{3R} \cancel{+} 2R + \cancel{\frac{3R^2}{4}} \cancel{\frac{2}{X}} = 2R + \frac{3R}{2} \geq 7R/2$$




$$\rightarrow \text{leg } \parallel = \frac{SR}{6} \text{ ohms } \parallel$$


## Homework - 2

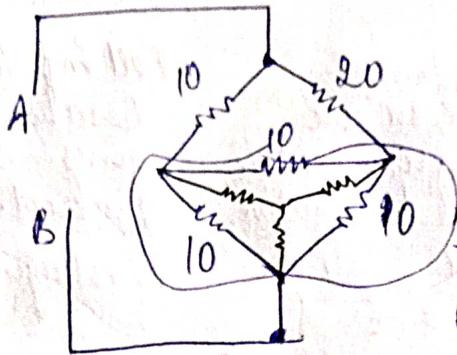
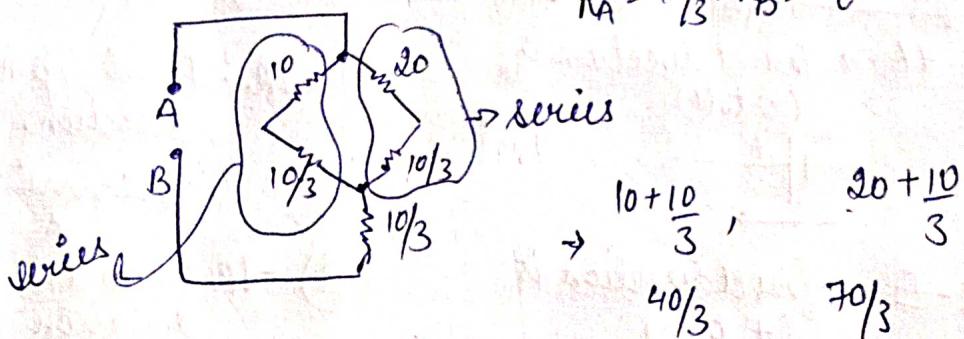
$$\Delta \text{ to } \lambda \rightarrow R_A = \frac{100}{30}, R_B = \frac{100}{30}, R_C = \frac{100}{30}.$$


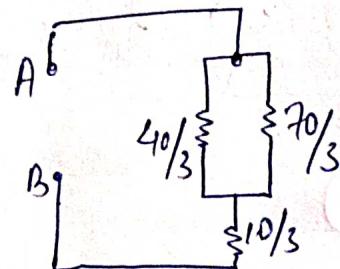
$$R_A = \frac{10}{3} = R_B = R_C \rightarrow 10 + \frac{10}{3}, \frac{20 + 10}{3}, \frac{40}{3}, \frac{70}{3}$$




$$\frac{1}{R} = \frac{3}{40} + \frac{3}{70}$$

$$\frac{1}{R} = \frac{21 + 12}{280}$$

$$\frac{1}{R} = \frac{33}{280}$$

$$R = \frac{280}{33}$$

$$\begin{array}{r|rr} 10 & 40, 70 \\ \hline 4 & 4, 7 \\ \hline 7 & 1, 7 \end{array}$$

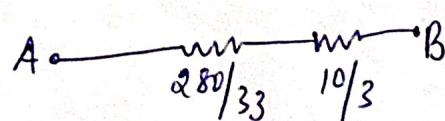

$$\frac{1}{R} = \frac{33}{280}$$

$$R = \frac{280}{33}$$

$$\begin{array}{r|rr} 3 & 33, 3 \\ \hline 11 & 11, 4 \\ \hline \end{array}$$


$$\Rightarrow R_{eq} = \frac{280}{33} + \frac{10}{3}$$

$$= \frac{280 + 110}{33} \Rightarrow \frac{390}{33} \text{ Ans} \Rightarrow$$

$$\boxed{\frac{130}{11}}$$


52  
22
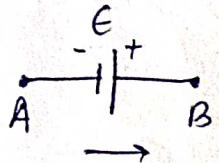
## Sign Convention for Kirchoff's Voltage Law (KVL)




Rise in potential because we are going from negative terminal of the battery to positive terminal.

$$EMF_B = +E$$

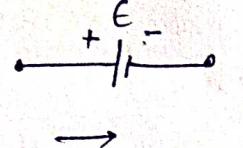


Fall in potential because we are going from positive terminal to negative terminal.

$$\therefore EMF = -E$$

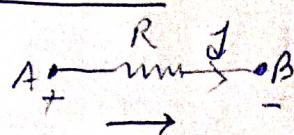

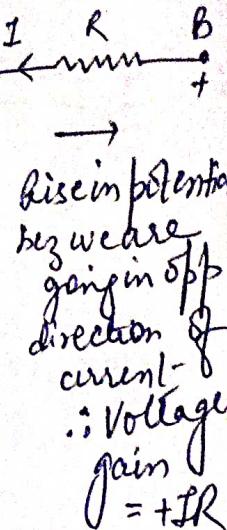
Fall in potential because we are going in the direction of current.  $\therefore$  Voltage drop =  $-IR$




Rise in potential because we are going in opp direction of current.  $\therefore$  Voltage gain =  $+IR$
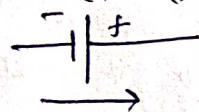
### (a) Sign Convention for EMFs.


①  $+E \rightarrow$  Travel direction is ( $-$ ) to ( $+$ )



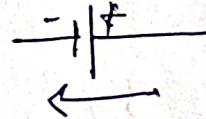②  $-E \rightarrow$  Travel direction is ( $+$ ) to ( $-$ )



### Voltage Division (in series circuit)

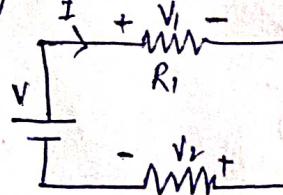

$$V = V_1 + V_2$$

$$V = V_1 + V_1 \left( \frac{R_2}{R_1} \right)$$

$$V_1 = V \left( \frac{R_1}{R_1 + R_2} \right)$$

$$V_2 = V \left( \frac{R_2}{R_1 + R_2} \right)$$

$$V_1 = IR_1$$

$$V = IR_1 + IR_2$$

$$(R = R_1 + R_2)$$


$$\boxed{\frac{V_1}{V} = \frac{R_1}{R_1 + R_2}}$$

$$V_2 = IR_2$$


$$\boxed{\frac{V_2}{V} = \frac{R_2}{R_1 + R_2}}$$
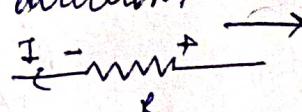
### (b) Sign Convention for resistors

①  $+IR$  : Travel opp to current direction.



②  $-IR$  : Travel in current direction

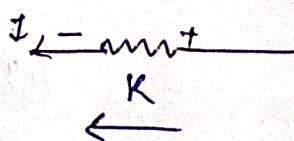

## Current Division (in Parallel circuit)


$$I = I_1 + I_2 \quad R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$I = \frac{V}{R_1} + \frac{V}{R_2}$$

$$I_1 = \frac{V}{R_1} \quad \left| \begin{array}{l} \frac{I_1}{I} \text{ and } \frac{I_2}{I} \\ \end{array} \right.$$


$$I_2 = \frac{V}{R_2} \quad \left| \begin{array}{l} I_1 : I \left( \frac{R_2}{R_1 + R_2} \right) \\ I_2 = I \left( \frac{R_1}{R_1 + R_2} \right) \end{array} \right.$$

$$\begin{aligned} I &= I_1 + I_2 \\ I &= I + I \left( \frac{R_1}{R_2} \right) \quad \left| \begin{array}{l} I_1 = I \left( \frac{R_2}{R_1 + R_2} \right) \\ I_2 = I \left( \frac{R_1}{R_1 + R_2} \right) \end{array} \right. \end{aligned}$$

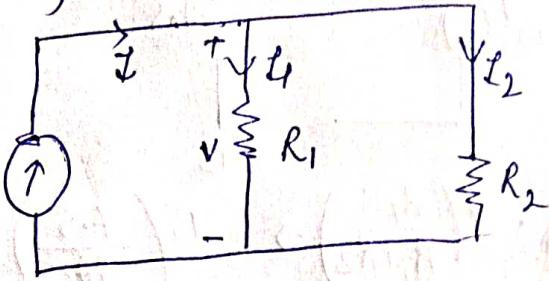

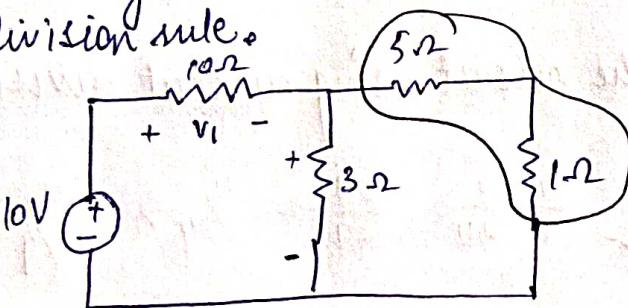
## Illustration-1

Find voltage  $V_1$  and  $V_2$  as marked in the given Circuit using Voltage and division rule.



$$\rightarrow \text{series } (5+1)\Omega \parallel 3\Omega$$
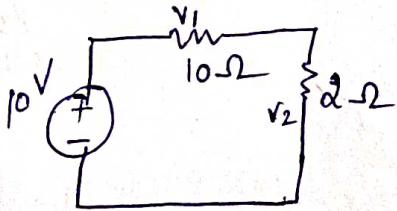
$$\frac{1}{R} = \frac{1}{6} + \frac{1}{3} = \frac{3}{6} = \boxed{\frac{6}{3} = 2\Omega}$$



$$V_1 = V \left( \frac{R_1}{R_1 + R_2} \right) \Rightarrow$$


$$V_1 = 10 \left( \frac{2}{12} \right) = \frac{100}{12} = \frac{50}{6} = \boxed{8.33 \text{ Volts}}$$

$$V_2 = V \left( \frac{R_2}{R_1 + R_2} \right) \Rightarrow$$

$$V_2 = 10 \left( \frac{2}{12} \right) = \frac{20}{12} = \frac{10}{6} = \boxed{1.66 \text{ Volts}}$$
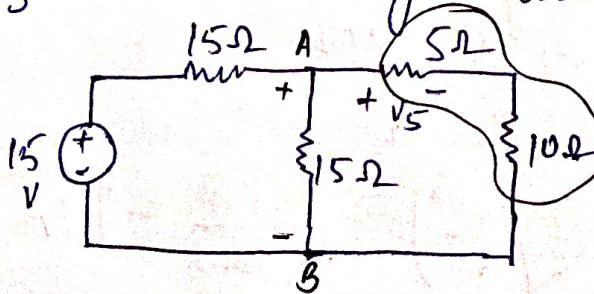
## Illustration-2

Find voltage  $V_5$  as marked in the given Circuit using voltage division rule.




$$\rightarrow (5+10) \parallel 15$$


$$= 15 \parallel 15$$

$$\frac{1}{R} = \frac{1}{15} + \frac{1}{15} = \frac{2}{15}$$

$$\boxed{R = 15/2 \Omega}$$

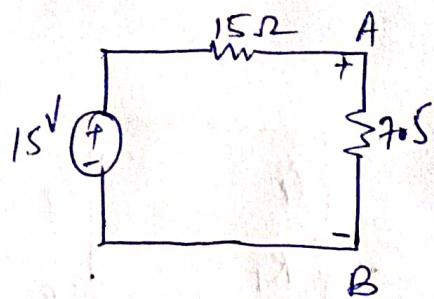
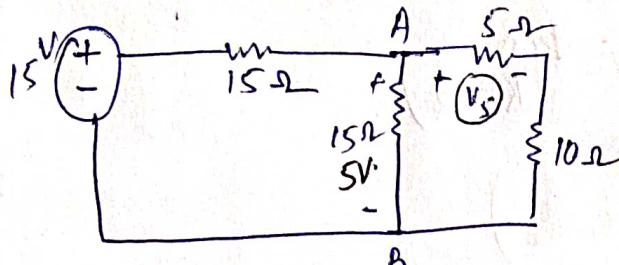
$$V_{AB} = V \left( \frac{R_1}{R_1 + R_2} \right) \Rightarrow 15 \left( \frac{7.5}{22.5} \right) = \frac{112.5}{22.5} = \underline{\underline{5 \text{ volts}}}$$




$$V_S = 5 \left( \frac{5}{15} \right) = \frac{25}{15} = \underline{\underline{5/3 = 1.667 \text{ volts}}}$$


$V \left( \frac{R_1}{R_1 + R_2} \right)$
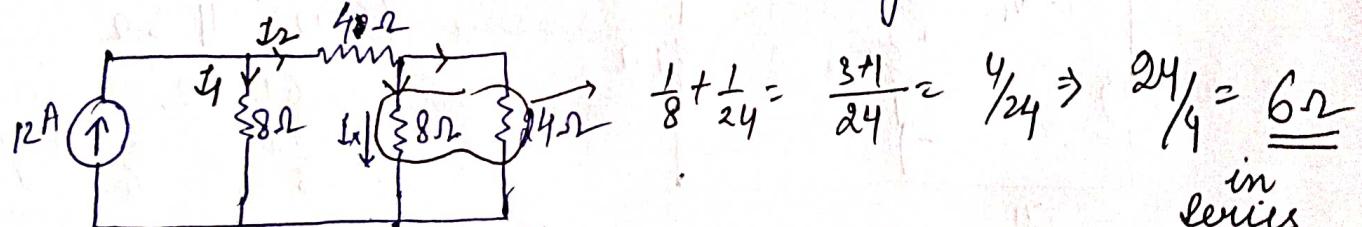
### Illustration-3

Find current  $I_x$ , as marked in the circuit using current division rule.




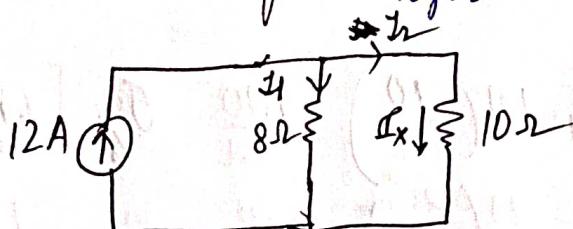higher current will go to higher resistance  
lower current will go with lower resistance



$$I_x = I \left( \frac{R_2}{R_1 + R_2} \right) \Rightarrow I_x = 12 \left( \frac{8}{18} \right) = \frac{12 \times 8}{18 \times 3} = \boxed{\underline{\underline{16/3 \text{ A}}}}$$

Redrawing


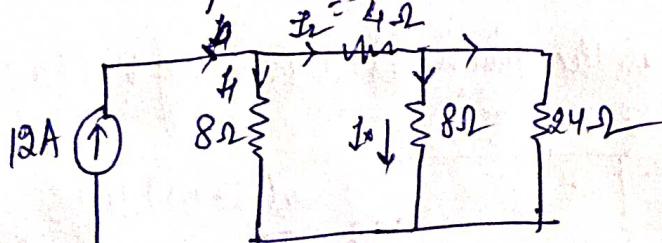


$$I_x = I \left( \frac{R_2}{R_1 + R_2} \right)$$

$$I_x = \frac{16}{3} \left( \frac{24}{32} \right) \Rightarrow \frac{16}{3} \left( \frac{24}{32} \right) = \frac{16 \times 8}{32 \times 2} = \boxed{\underline{\underline{4 \text{ A}}}}$$
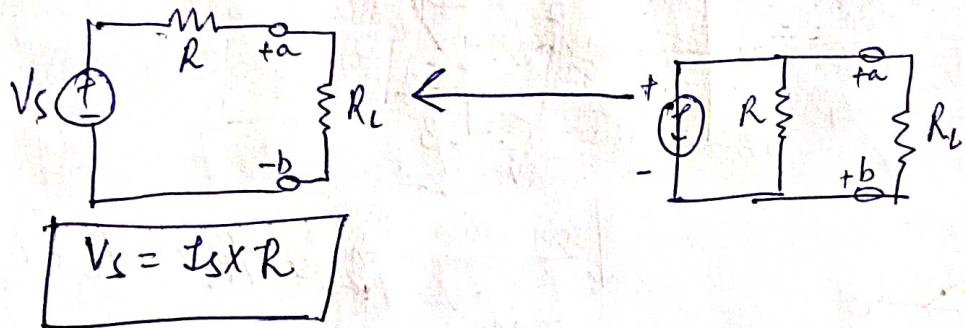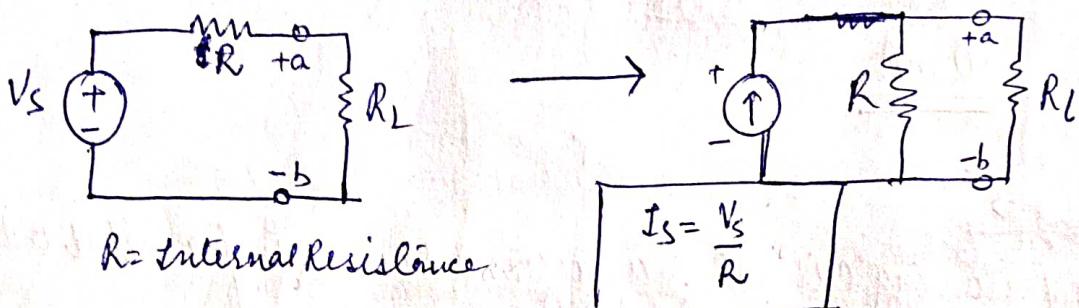
# Source Transformation (V.V.V.V.V Imp)


Practical Voltage Source       $\longleftrightarrow$       Practical current Source  
 (Ideal voltage source in series with  $I_s$ )      (ideal current source in parallel with  $V_s$ )



## Illustration-4

Find current in  $6\text{k}\Omega$  resistor by converting current source to a voltage source.
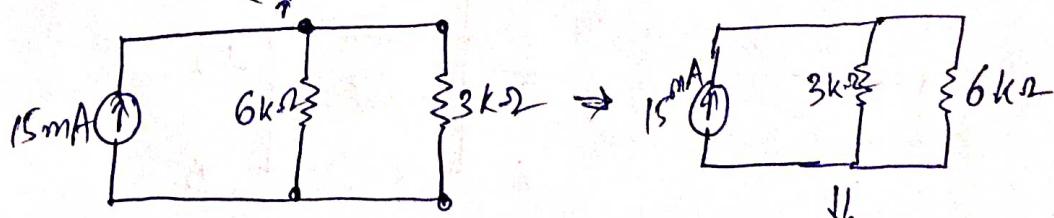
# The voltage across and current through a resistance (in the converted circuit) cannot be computed if that resistance is involved in the source conversion (keep intact)




~~$V_s = I_s \times R$~~ 

$$V_s = 15 \times 10^{-3} \times 3 \times 10^3$$

$$= 45\text{V}$$
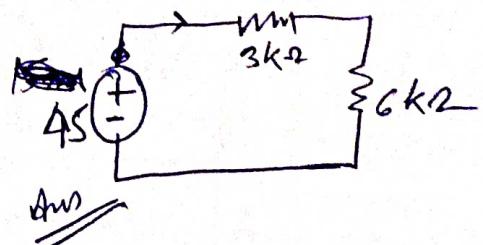
$$I_{6\text{k}\Omega} = \frac{45}{3\text{k}\Omega + 6\text{k}\Omega}$$



$$I = \frac{45}{9 \times 10^3} = \underline{\underline{5 \text{ mA}}}$$

5 mA current flows through  $3\text{k}\Omega$  resistance



$$I_{3\text{k}\Omega} = \frac{15 \text{ mA} \times 6 \text{ k}\Omega}{9 \text{ k}\Omega}$$

$$\Rightarrow \frac{15 \times 10^{-3} \times 6 \times 10^3}{9 \times 10^3}$$






$$\underline{\underline{10 \text{ mA}}}$$
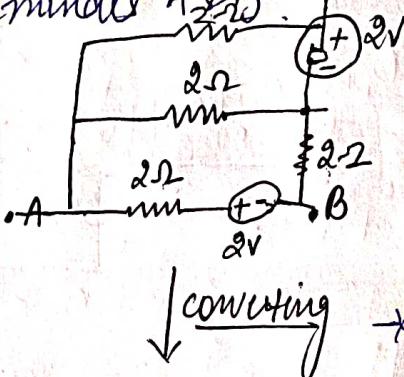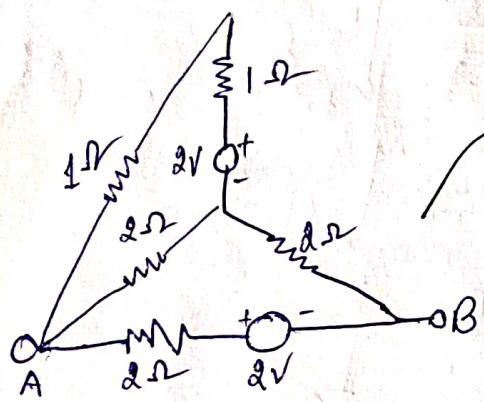
### Illustration-5

Reduce the following circuit to a current source in parallel with a resistor across the terminals A & B.


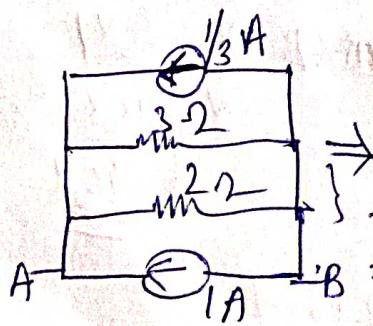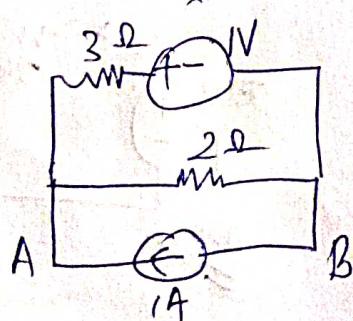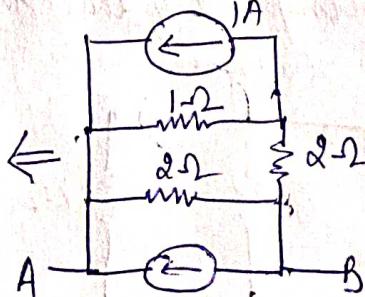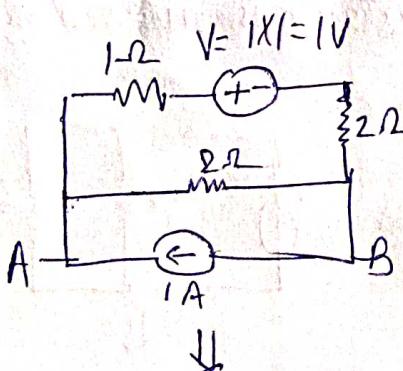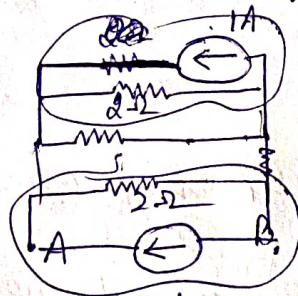
$$\downarrow \text{converting} \rightarrow I_S = \frac{V}{R} \rightarrow 2/2 = 1 \text{ A}$$





$$\frac{6/5}{6} \text{ m} \rightarrow 333 \text{ A}$$



$$\frac{1 + 1/3}{2 + 3} = \frac{4/3}{6} = \frac{6/5}{6}$$
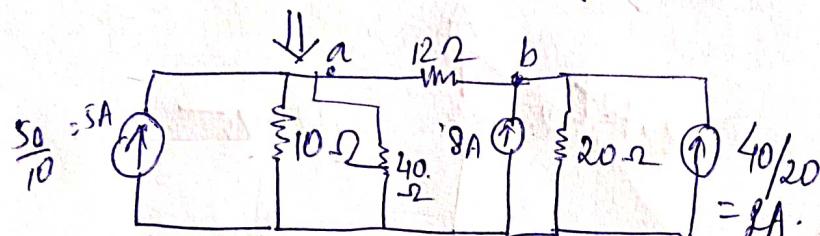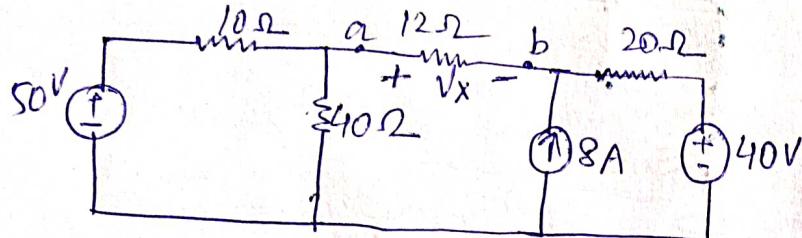
## Illustration - 6

Find the voltage across  $12\Omega$  resistor ( $v_x$ ) by source transformation method.



( $40\Omega$  and  $10\Omega$  in II)

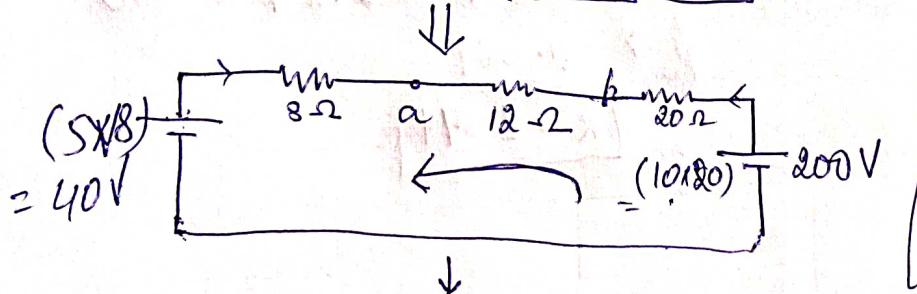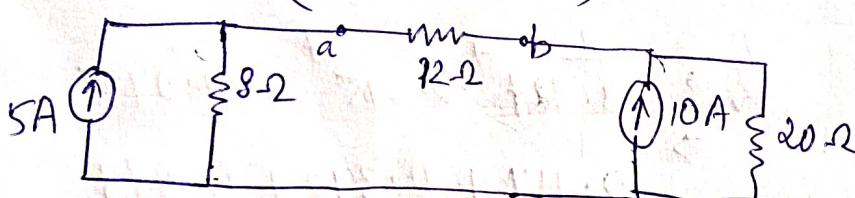

OR

$$40V + 8I + 12I + 20I - 200 = 0$$

Using KVL

$$+200 + (-20 \times I) - 12I - 8I - 40 = 0$$

$$160 - 40I = 0$$

$$160 = 40I$$



$$I = \frac{160}{40} = 4A$$

$$V_{ba} = 4 \times 12 = 48 \text{ Volts}$$

$$V_x = V_{ab} = -V_{ba} = -48 \text{ Volts}$$
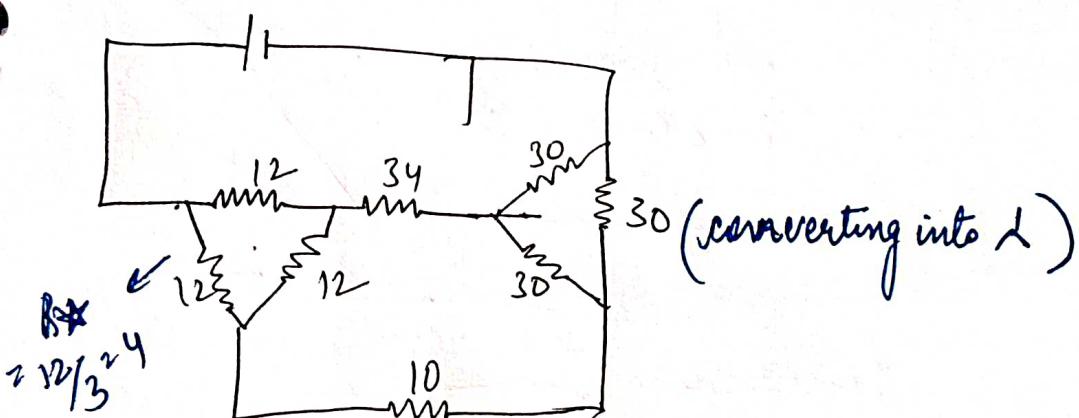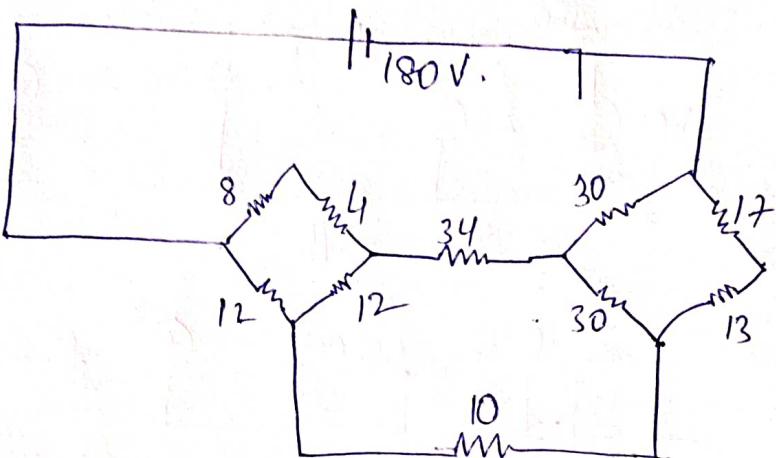
# Quiz Question



Determine current flowing through  $10\Omega$  resistor. All resistances are in ohms.



Since  $R_\Delta$  is balanced.

$$R_\Delta = 3 R^*$$


$$R^* = \frac{R_\Delta}{3}$$

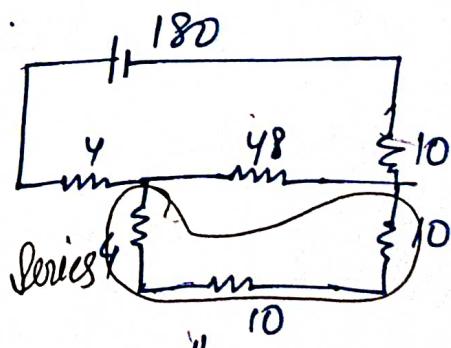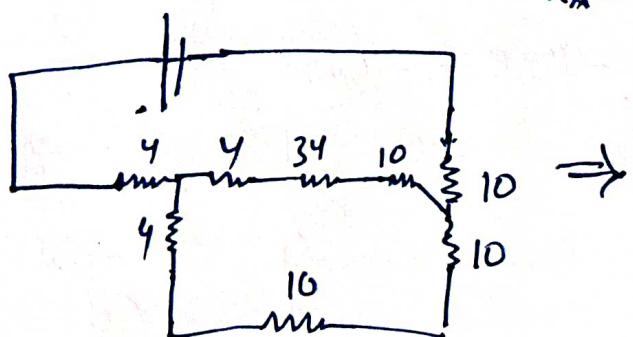

$$I_T = \frac{180}{4 + (48/12) + 10}$$

$$I_T = \frac{180}{4 + 16 + 10} = \frac{180}{30} = 6A$$
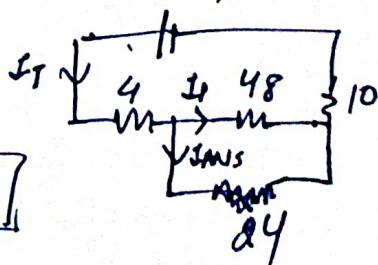
$$I_{ANS} = I_T \times \frac{48}{48+24} = 6 \times \frac{48}{72} = 4A \text{ (ans)}$$



$$\begin{aligned} &= \frac{48+12}{48} \\ &= \frac{1+2}{48} \\ &= \frac{48}{48} \\ &= 18 \end{aligned}$$


# Mesh Current Analysis (network reduction technique)

(valid for planar circuit)

Mesh → A closed path for flow of current.

Kirchoff's voltage Law (KVL)

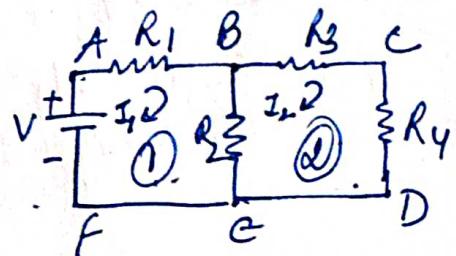The algebraic sum of voltages in a mesh is 0.



$$ABEF \Rightarrow I_1 R_1 + (I_1 - I_2) R_2 - V = 0.$$


$$BCDE \Rightarrow I_2 R_3 + I_2 R_4 + R_5 (I_2 - I_1) = 0. \quad ABCDEF \rightarrow \text{loop}.$$

$$\Rightarrow I_1 R_1 + I_1 R_2 - I_2 R_2 - V = 0.$$

$$\Rightarrow I_2 R_3 + I_2 R_4 + R_5 I_2 - R_5 I_1 = 0.$$

## Mesh Analysis Method

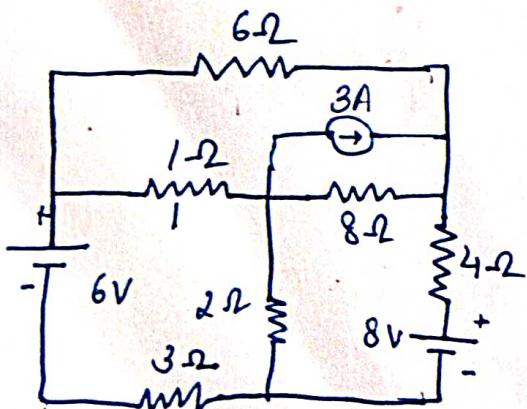
- (1) Transform all the current sources present in the circuit to the voltage sources.
- (2) Mark different currents in all the independent meshes of the given network.
- (3) Write KVL equations for these independent meshes.
- (4) Solve for the currents



Determine the power drawn by  $2\Omega$  resistor using mesh current analysis.

$$\text{Loop 1} \rightarrow 6 - 3I_1 - 2(I_1 - I_2) - 1(I_1 - I_3) = 0$$
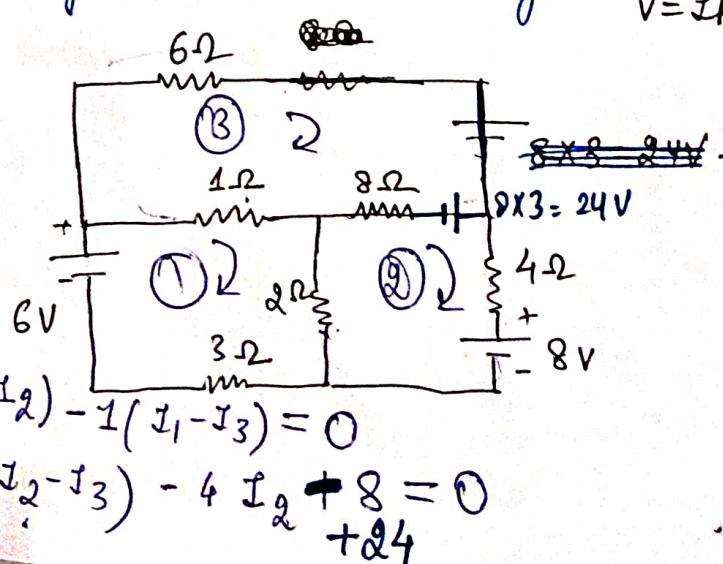
$$\text{Loop 2} \rightarrow -2(I_2 - I_1) - 8(I_2 - I_3) - 4I_2 + 8 = 0$$



$$\text{loop 3} \rightarrow -8(I_3 - I_2) - 1(I_3 - I_4) - 6I_3 + 24 = 0$$

Solving the equations

$$\rightarrow -8I_3 + 8I_2 - I_3 + I_4 - 6I_3 + 24 = 0$$

$$\rightarrow 6 - 3I_1 - 2I_1 + 2I_2 - I_4 + I_3 = 0$$

$$\rightarrow -2I_2 + 2I_1 - 8I_2 + 8I_3 - 4I_2 + 18 = 0$$

$$\rightarrow -15I_3 + 8I_2 + I_4 = +24$$

$$\rightarrow -6I_1 + I_3 + 2I_2 = -6$$

$$\rightarrow -14I_2 + 2I_4 + 8I_3 = +18$$

~~$$Q.59 \leftarrow I_4 = X = +90/77$$~~

~~$$Q.33 \leftarrow I_2 = Y = 214/77$$~~

~~$$-1.74 \leftarrow I_3 = Z = 250/77$$~~

$$I_4 =$$

~~$$15I_3 - 8I_2 - I_4 = 24$$~~

~~$$-I_3 - 2I_2 + 6I_4 = 6 \quad \times 4$$~~

~~$$19I_3 - 25I_4 = 0$$~~

~~$$\text{Power} = I^2 R$$~~

~~$$= (0.99 - 0.58)^2 R$$~~

~~$$= (0.41)^2 R$$~~

~~$$0.324 \text{ Watts} \quad 0.026 \text{ KW}$$~~

~~$$I_4 = 0.99 \text{ A}$$~~

~~$$I_2 = 0.58 \text{ A}$$~~

~~$$I_3 = -1.22 \text{ A}$$~~

~~$$-6I_4 + 2I_2 + I_3 = -6$$~~

~~$$3r \quad 24 - 14I_2 + 8I_3 = -8$$~~


~~$$-6I_4 + 2I_2 + I_3 = -6$$~~

~~$$6I_4 - 42I_2 + 24I_3 = -24$$~~

~~$$-40I_2 + 25I_3 = -30$$~~

~~$$-8I_2 + 5I_3 = -6$$~~

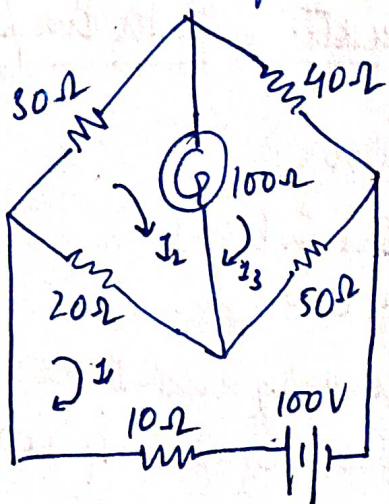Q2b Determine the current through the Galvanometer "G".



KVC Equations

$$\text{For } ① \rightarrow 10I_1 - 20(I_1 - I_2) + 50(I_1 - I_3) + 100 = 0$$

$$\text{For } ② \rightarrow 20(I_2 - I_1) + 30I_2 + 100(I_2 - I_3) = 0.$$

$$\text{For } ③ \rightarrow 40I_3 + 50(I_3 - I_1) + 100(I_3 - I_2) = 0.$$

$$\text{For } 1 \rightarrow -10I_1 - 20I_1 + 20I_2 - 50I_1 + 50I_3 + 100 = 0$$

$$\text{For } 2 \rightarrow 20I_2 - 20I_1 + 30I_2 + 100I_2 - 100I_3 = 0$$

$$\text{For } 3 \rightarrow 40I_3 + 50I_3 - 50I_1 + 100I_3 - 100I_2 = 0.$$

$$① \rightarrow -80I_1 + 20I_2 + 50I_3 = -100$$

$$② \rightarrow 150I_2 - 20I_1 - 100I_3 = 0$$

$$③ \rightarrow 190I_3 - 50I_1 - 100I_2 = 0$$

$$X = 2.023 = I_1$$

$$Y = 1.06 = I_2$$

$$Z = 1.14 = I_3$$

Current through G

$$100(I_3 - I_2)$$

$$I_G \rightarrow 1.14 - 1.06 = 0.08A$$

direction ↑ coz  $I_3$  is greater

Q3b How to write network equation with inspection

→ Referring to the previous question

loop 1

$$I_3 \Rightarrow \text{sum of all resistors in loop 1}$$

$$\rightarrow 20 + 50 + 10 = 80.$$

$I_2 \rightarrow$  Resistor between  $I_2$  and  $I_1$  loop  $\rightarrow 20$

$I_3 \rightarrow$  Resistor between  $I_3$  and  $I_1$  loop  $\rightarrow 50$

$$\therefore \text{equation} = 80I_1 - 20I_2 - 50I_3 = 100. \quad (\text{only } I_1 \text{ should be +ve.})$$

loop 2

$$I_2 = \text{sum of all resistors in loop 2}$$

$$\rightarrow 150 = 30 + 120 + 100$$

$I_1 =$  Resistor between  $I_1$  and  $I_2 = 20\Omega$

$I_3 =$  Resistor between  $I_2$  and  $I_3 = 100\Omega$

$$\therefore \text{equation} = -20I_1 + 150I_2 - 100I_3 = 0.$$

loop 3

$$I_3 = \text{sum of all resistors in loop 3}$$

$$\Rightarrow 40 + 100 + 50 = 190\Omega.$$

$I_1 =$  Resistor between  $I_1$  and  $I_3 = 50\Omega$ .

$I_2 =$  Resistor between  $I_2$  and  $I_3 = 100\Omega$

(only  $I_3$  should be +ve)

$$190I_3 - 50I_1 - 100I_2 = 0.$$

Polarity of V

→ When current enters (+ve terminal)  $\rightarrow V$  is (+ve)

→ When current leaves (+ve terminal)  $\rightarrow V$  is (-ve)

$$\begin{bmatrix} 80 & -20 & -50 \\ -20 & 150 & -100 \\ -50 & -100 & 190 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \\ 0 \end{bmatrix}$$

Q4) Realize the network defined by mesh current equations given below.

$$\begin{bmatrix} 30 & -20 & 0 \\ -20 & 50 & -20 \\ 0 & -20 & 20 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ -20 \end{bmatrix}$$

