



MANIPAL INSTITUTE OF TECHNOLOGY
MANIPAL

(A constituent institution of MAHE, Manipal)



Basic Electrical Technology

CLASS 11 – 01 DECEMBER 2021

Charging of a Capacitor through a Resistor

Applying KVL,

$$V - Ri - v_c = 0$$

where, $i = C \frac{dv_c}{dt}$


Initial Conditions,

$$\text{At } t = 0 \text{ sec, } V_c = 0 \text{ V}$$

Final current & voltage equation,


$$v_c = V \left(1 - e^{-\frac{1}{RC}t} \right)$$
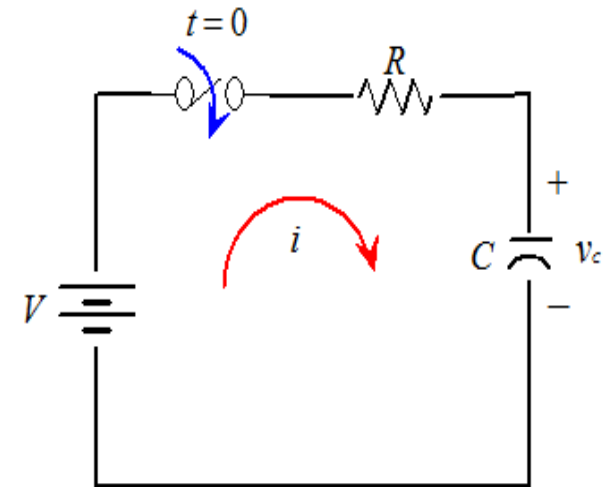
$$i_c = \left(\frac{V}{R} \right) e^{-\left(\frac{1}{RC} \right) t}$$



Time Constant (τ): Time taken by the voltage of the capacitor to reach its final steady state value, had the initial rate of rise been maintained constant

$$\tau = RC$$

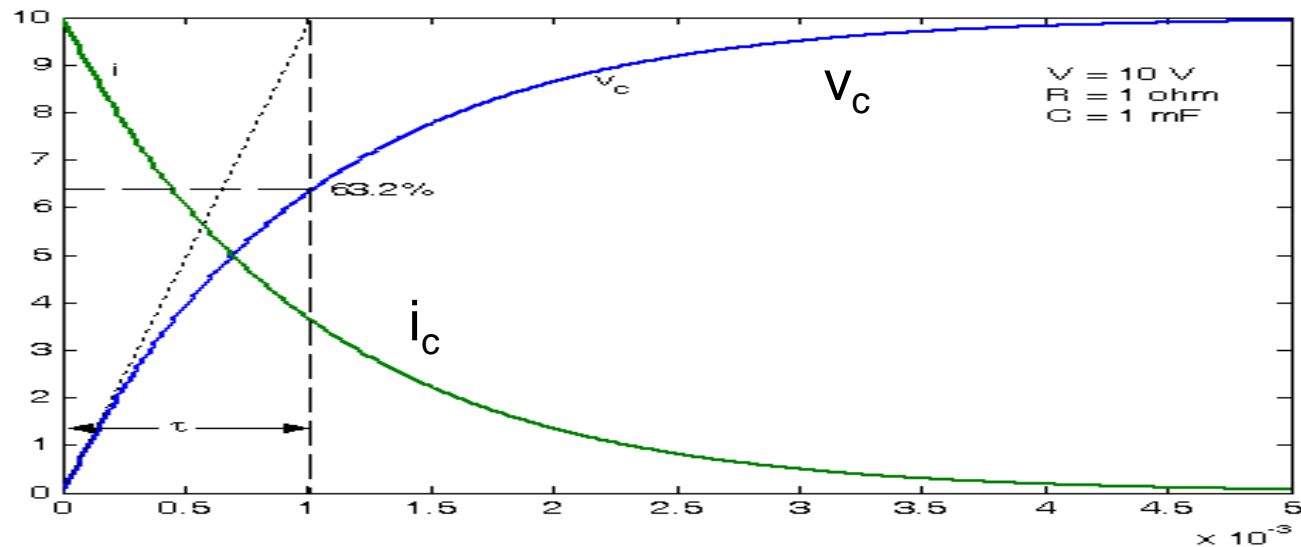

Discharging of a Capacitor through a Resistor

➤ Capacitor is initially charged to a voltage V

➤ At $t = 0$, switch is moved from position a to b

Applying KVL,


$$v_c - Ri = 0$$

Where, $i = -C \frac{dv_c}{dt}$

Using initial conditions and then solving

$$v_c = V e^{-\left(\frac{1}{RC}\right)t}$$
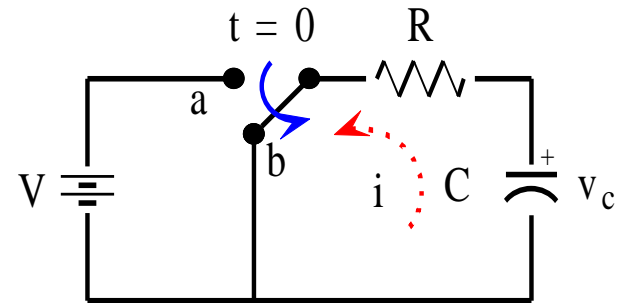
$$i_c = -I e^{-\left(\frac{1}{RC}\right)t}$$



Discharging of a Capacitor through a Resistor

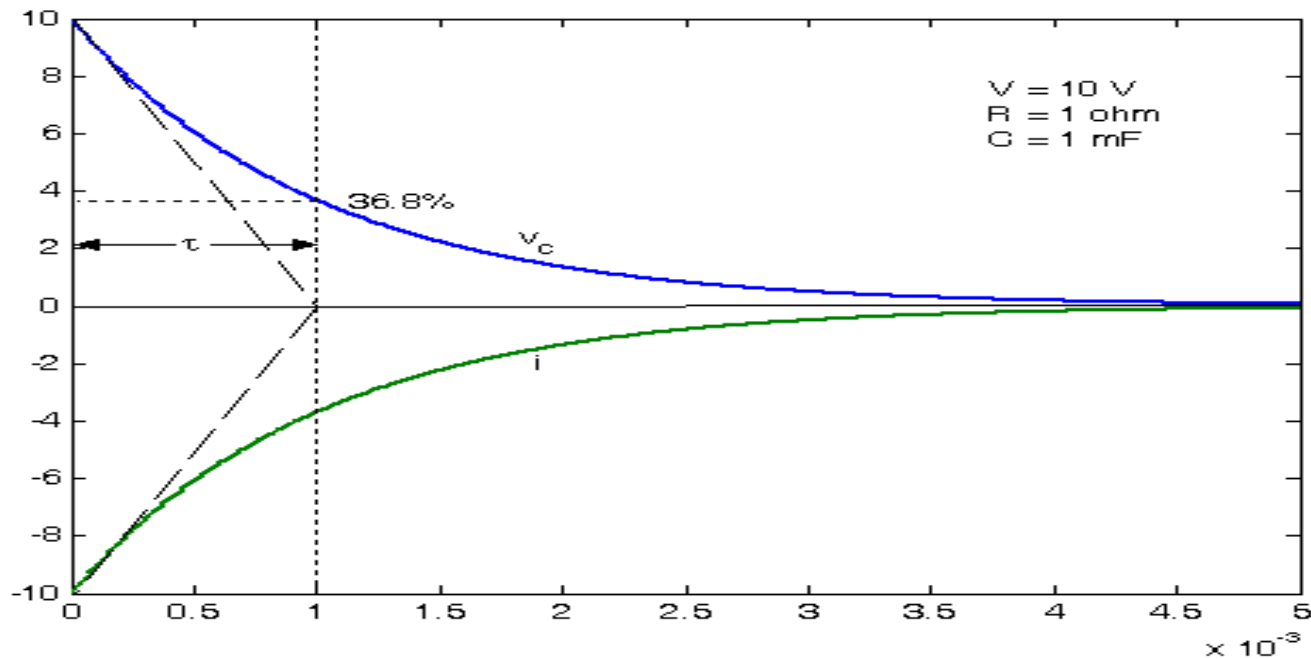


Illustration 1



An $8\ \mu\text{F}$ capacitor is connected in series with a $0.5\ \text{M}\Omega$ resistor, across a $200\ \text{V}$ dc supply through a switch. At $t=0$ sec, the switch is turned on. Calculate

- i. Time constant of the circuit
- ii. Initial charging current.
- iii. Time taken for the potential difference across the capacitor to grow to $160\ \text{V}$.
- iv. Current & potential difference across the capacitor 4.0 seconds after the switch is turned on.

Ans: (i) 4 seconds, (ii) $400\ \mu\text{A}$, (iii) 6.44 seconds (iv) $126.42\ \text{V}$ & $147.15\ \mu\text{A}$

Illustration 2



A $15\ \mu\text{F}$ uncharged capacitor is connected in series with a $47\ \text{k}\Omega$ resistor across a $120\ \text{V}$, d.c. supply.

a) Determine the capacitor voltage at a time equal to one time constant after being connected to the supply and also two seconds after being connected to the supply.

b) Find the time for the capacitor voltage to reach one half of its steady state value. Draw the capacitor voltage waveform.


Ans: a) 75.84 V, 112.97 V b) 0.49 s.

Illustration 3



In the network shown below, the switch is closed to position 1 at $t = 0$ & is moved to position 2 at $t = 0.4$ sec. Determine the voltage across the capacitor $v_c(t)$ & sketch it for $0 \leq t \leq 1$ sec

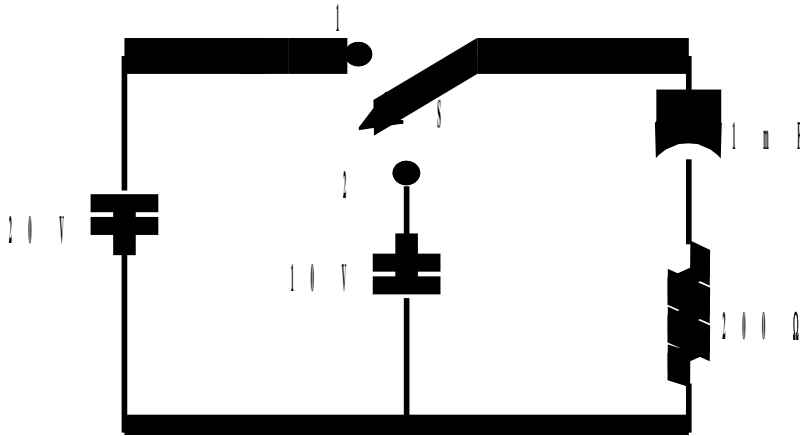Also find the value of 't' for which $v_c(t) = 0$



Ans: At $t = 0.6$ sec, $v_c = 0$ V

$$v_c = 20(1 - e^{-t/0.2})$$


At $t = 0.4 \text{ sec}$, $v_c = 17.29 \text{ V}$

After 0.4 second, the switch is in position 2

$$v_c = -10 + 27.29e^{-(t-0.4)/0.2}$$

At $t = 1 \text{ sec}$, $v_c = -8.64 \text{ V}$


Solution

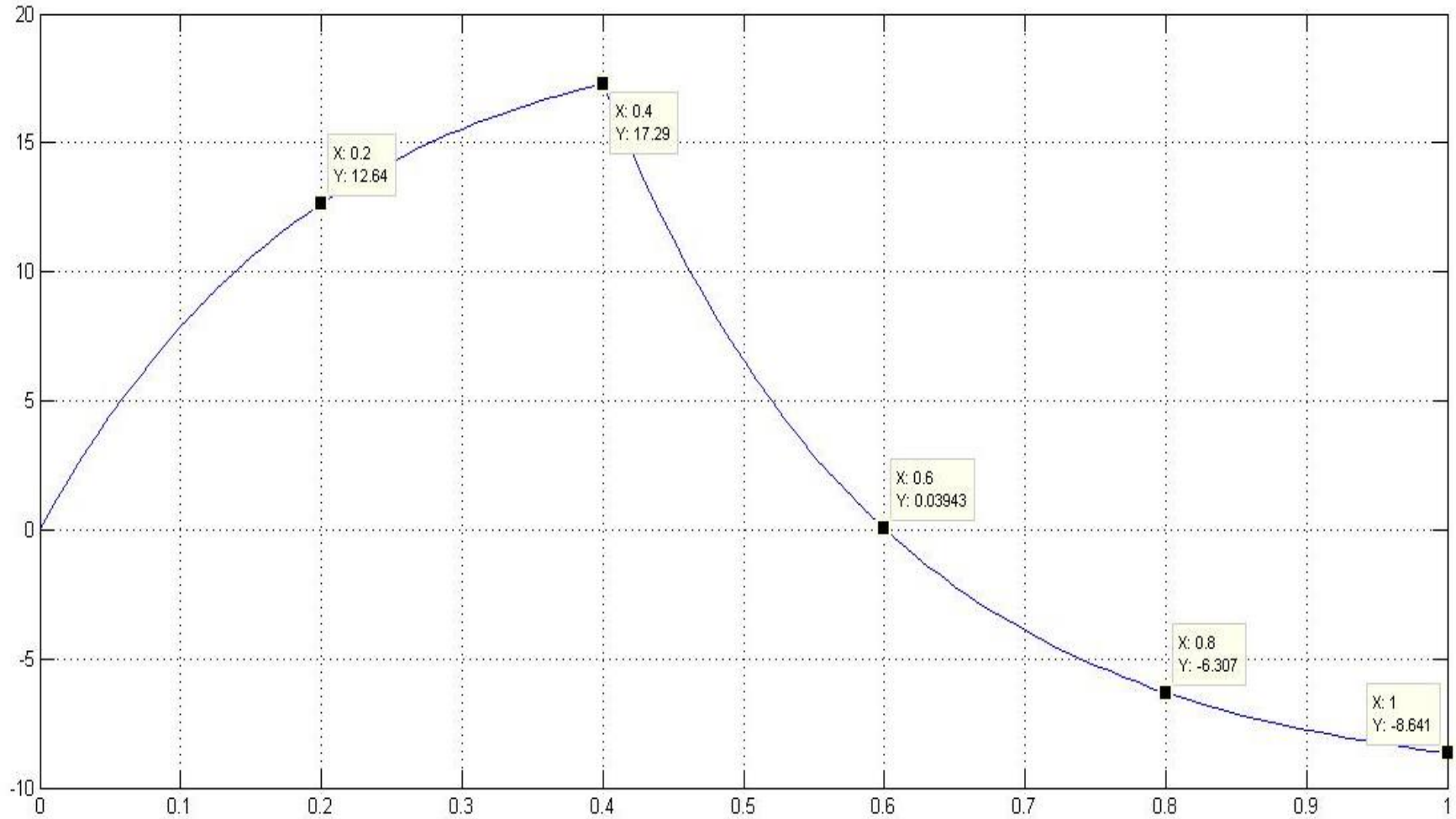

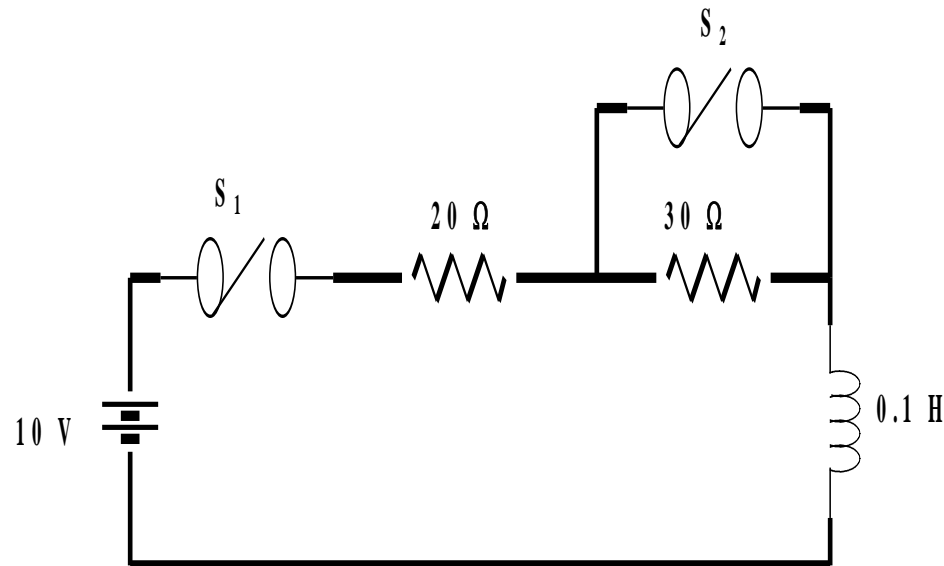
Question 01



In the circuit shown below, both the switches, S_1 & S_2 are open initially. At $t = 0$ sec, S_1 is closed (& S_2 remains open). At $t = 4$ ms S_2 is closed. Sketch the inductor current $i(t)$ for $0 \leq t \leq 25$ ms.



Solution

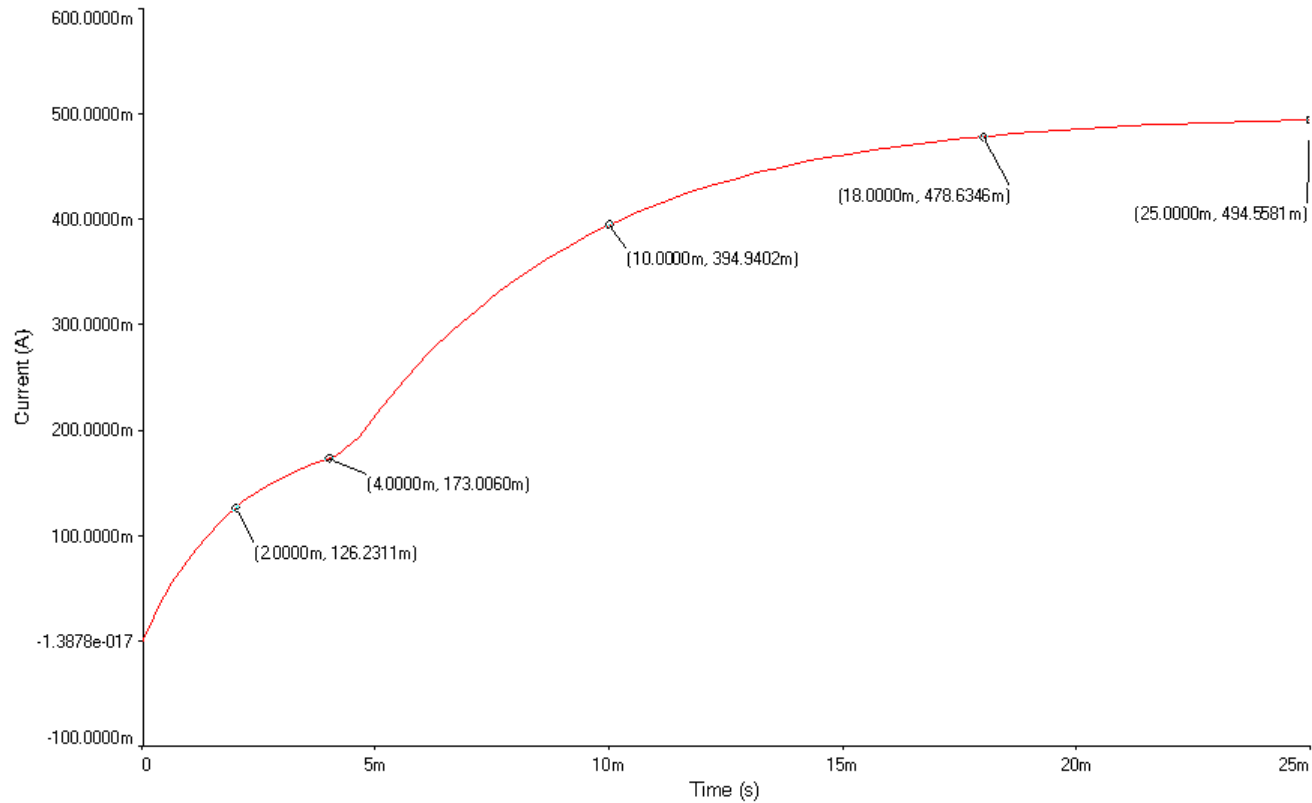

Question 02



For the circuit shown in figure below, the switch S has been closed for a long time and then opened at $t = 0$.

Find,

i. $v_{ab}(0^-)$

ii. $i_x(0^-)$

iii. $i_L(0^-)$


iv. $i_x(0^+)$

v. $v_{ab}(0^+)$

vi. $i_x(t = \infty)$

vii. $v_{ab}(t = \infty)$

viii. $i_x(t)$ for $t > 0$

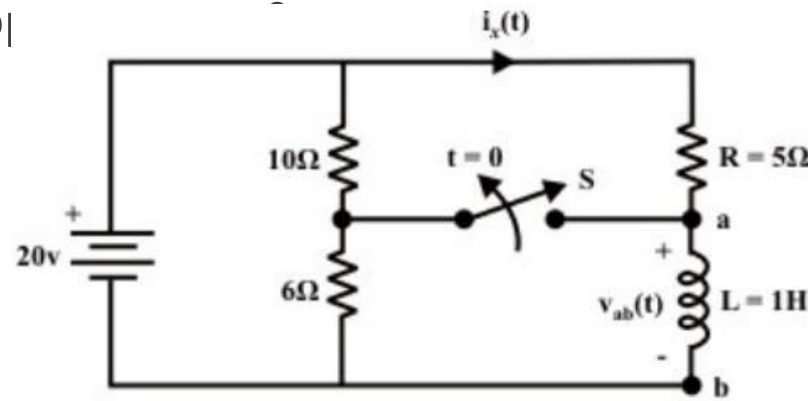

Answers:

i. $= 0 \text{ V}$

ii. $= 4 \text{ A}$

iii. $= 6 \text{ A}$

iv. $= 6 \text{ A}$

v. $= -10 \text{ V}$

vi. $= 4 \text{ A}$

vii. $= 0 \text{ V}$

viii. $20 - 5 i_x - \frac{di_x}{dt} = 0 \Rightarrow$
 $i_x(t) = 4 + 2e^{-5t} \dots$
 Initial condition: At $t = 0$, $i_x = 6 \text{ A}$

Question 03



For the circuit shown in figure below, the switch **S** has been kept open for a long time and then it is closed

Find,

i. $v_C(0^-)$


ii. $v_C(0^+)$

iii. $i_C(0^-)$

iv. $i_C(0^+)$

v. $\left. \frac{dv_C}{dt} \right|_{t=0^+}$

vi. $v_C(t = \infty)$

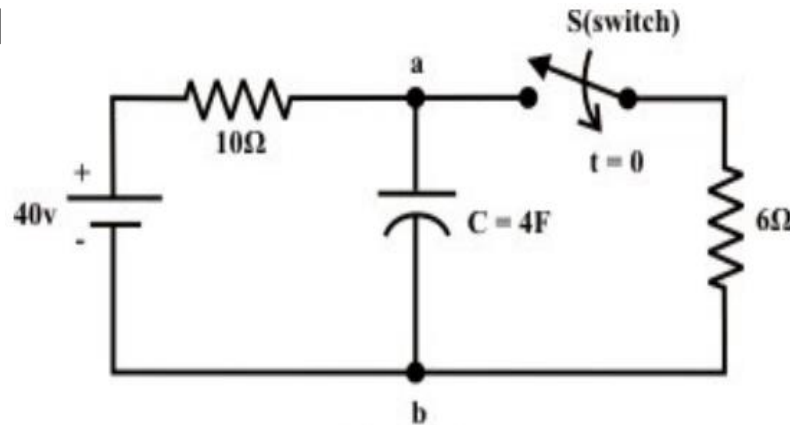

Answers:

i. $= 40 \text{ V}$

ii. $= 40 \text{ V}$

iii. $= 0 \text{ A}$

iv. $= \frac{20}{3} \text{ A}$

v. $= \frac{5}{3} \text{ V/s}$

vi. $= 15 \text{ V}$

vii. $\tau_1 = 40 \text{ s}, \tau_2 = 15 \text{ s}$ (To find τ_2 find the Thevenin's equivalent resistance)


vii. find the time constants of the circuit before and after

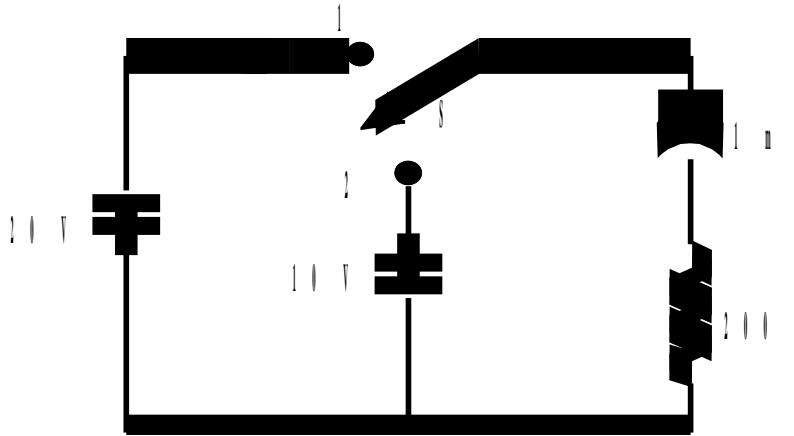Question 04



In the network shown below, the switch is closed to position 1 at $t = 0$ & is moved to position 2 at $t = 0.4$ sec. Determine the voltage across the capacitor $v_c(t)$ & sketch it for $0 \leq t \leq 1$ sec

Also find the value of 't' for which $v_c(t) = 0$



Solution



$$v_c = 20(1 - e^{-t/0.2})$$

At $t = 0.4 \text{ sec}$, $v_c = 17.29 \text{ V}$

After 0.4 second, the switch is in position 2

$$v_c = -10 + 27.29e^{-(t-0.4)/0.2}$$

At $t = 1 \text{ sec}$, $v_c = -8.64 \text{ V}$

Ans: At $t = 0.6 \text{ sec}$, $v_c = 0 \text{ V}$

