

47

1. Design a two bit multiplier using 74138 IC's and minimum universal gate.

→ Let  $A_1, A_0$  be one number and  $B_1, B_0$  be second number and  $F_3, F_2, F_1, F_0$  be output.

$A_1$	$A_0$	$B_1$	$B_0$	$F_3$	$F_2$	$F_1$	$F_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	01	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

$F_2$  :-

0	0	0	0
0	0	0	0
0	0	0	1
0	0	1	1

$F_1$  :-

0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0

$F_0$  :-

0	0	0	0
0	1	1	0
0	1	1	0
0	0	0	0


$$F_2 = \pi(10, 11, 14)$$

$$F_1 = \pi(6, 7, 13, 14, 9, 11)$$

$$F_0 = (6, 7, 13, 15)$$

$$F_3 = A_1 A_0 B_1 B_0 = \overline{A}_1 + \overline{A}_0 + \overline{B}_1 + \overline{B}_0$$


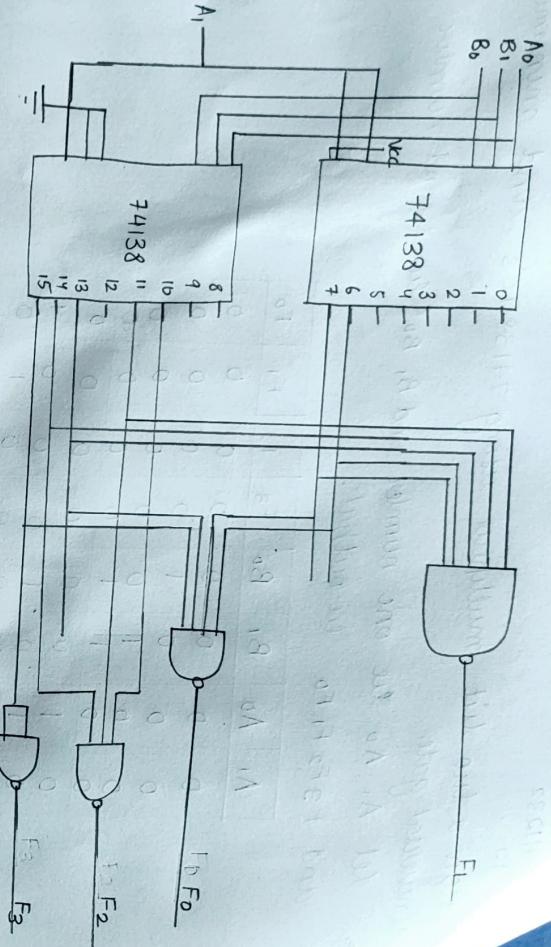
2. Design a 3-bit magnitude comparator using active high output decoders and minimum universal gates.



$$G = \sum (4, 8, 9, 12, 13, 14) = \sum (0, 1, 2, 3, 5, 6, 7, 10, 11, 15)$$

$$E = \sum (0, 5, 10, 15) = \sum (1, 2, 3, 4, 6, 7, 8, 9, 11, 12, 13, 14)$$
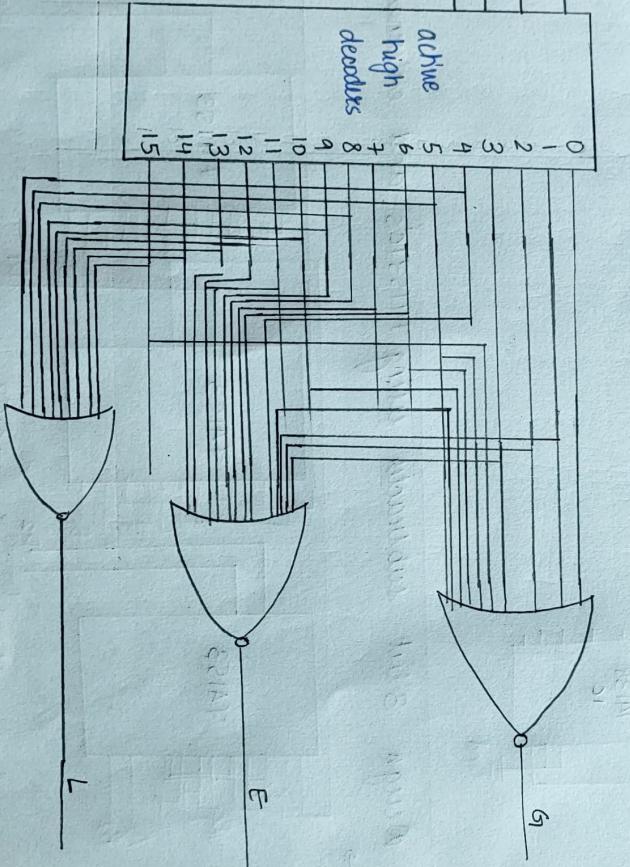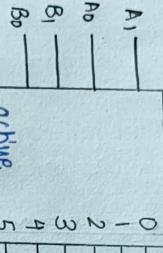
$$L = \sum (1, 2, 3, 6, 7, 11) = \sum (4, 5, 8, 9, 10, 12, 13, 14, 15, 16)$$




3. Implement the function  $F = (A'B'D + A'BC'D')$  using decoder and minimum external gates.

$$\rightarrow F = (A'B'D + A'BC'D')$$

$$= A' (B'D + BC'D')$$

	A <sub>1</sub>	A <sub>0</sub>	B <sub>1</sub>	B <sub>0</sub>	F
00	0	0	0	0	0
01	0	1	0	0	0
11	1	1	1	1	1
10	1	1	1	0	0

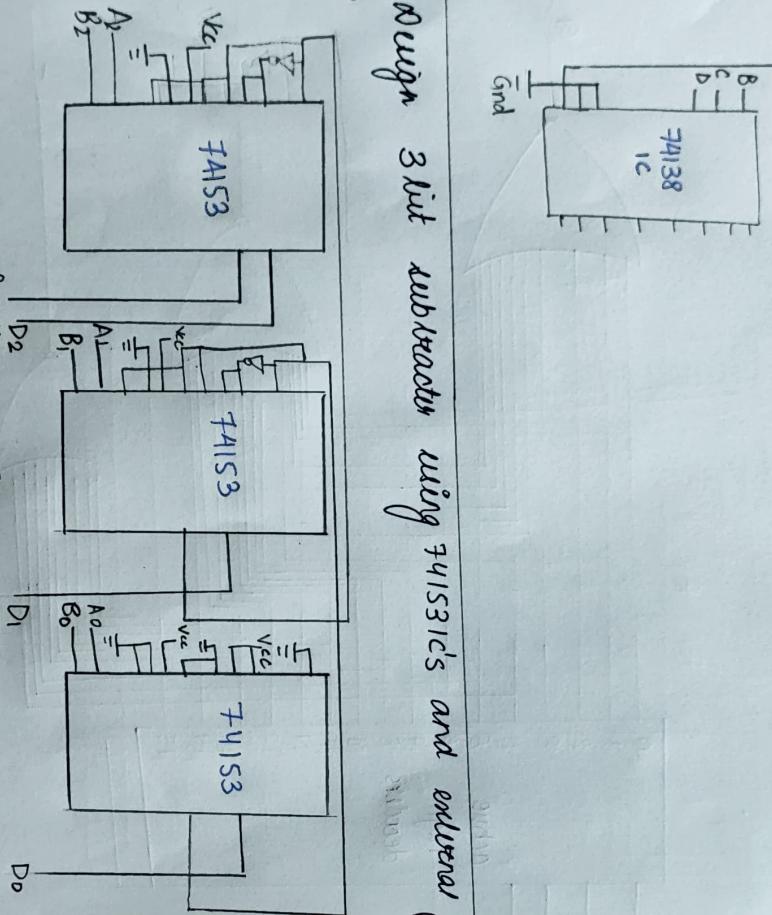4. Design 3 bit subtractor using 74153 ICs and universal gate



full subtractor using 74153

A	B	C	D	$D_B$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	0

Write the function (minterms) realised using following circuit.

(3)

w	x	y	z	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
1	1	0	0	1
1	1	1	0	1
1	1	1	1	1

$$F(w, x, y, z) = \sum(0, 1, 5, 6, 9, 10, 12, 13)$$

—	—	—	—	—
—	—	—	—	—
—	—	—	—	—
—	—	—	—	—
—	—	—	—	—

6. Design a BCD adder to add two single digit decimal numbers represented in excess-3 code the result also in excess-3

→ let one number represented as  $A_3 A_2 A_1 A_0$  and let Bbc represented as  $B_3 B_2 B_1 B_0$  in excess 3 code . result is represented in excess-3 and bcd i.e.  $A + B + g$  in excess 3

for sum<sub>Y</sub> 15 carry will be one and we need add 80  
 we can take 83525150 and find p and c from p directly

for sum>15 carry will be one and we need add 20  
 we can take  $S_3 S_2 S_1 S_0$  and find P and C from P directly


$$P_2 = S_3S_2 + S_3S_1 + C$$

V<sub>CC</sub>




7483

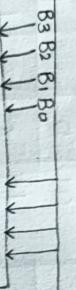A<sub>3</sub> A<sub>2</sub> A<sub>1</sub> A<sub>0</sub>



7483

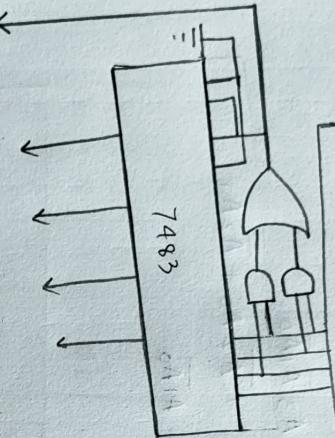

⑦ Design a code converter that converts a decimal digit from 84-2-1 code to BCD

→ Truth Table

	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	F <sub>3</sub>	F <sub>2</sub>	F <sub>1</sub>	F <sub>0</sub>
0	0	0	0	0	0	0	0
0	0	0	1	x	x	x	x
0	0	1	0	x	x	x	x
0	0	1	1	0	0	1	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	0	0
1	1	1	1	1	1	1	1

⑧

$A_3A_2$	$A_1A_0$	00	01	11	10
00	0	X	X	X	X
01	0	0	0	0	0
11	(X)	X	1	(X)	
10	1	0	0	0	0

$A_3A_2$	$A_1A_0$	00	01	11	10
00	0	X	X	X	X
01	1	0	0	0	0
11	(X)	X	0	X	
10	0	1	1	1	1

$A_3A_2$	$A_1A_0$	00	01	11	10
00	0	X	X	X	X
01	0	1	1	0	0
11	X	X	0	X	
10	0	1	1	1	0


$A_3A_2$	$A_1A_0$	00	01	11	10
00	0	(X)	X	(X)	(X)
01	0	1	0	1	1
11	X	X	0	X	
10	0	1	0	(X)	

$$F_3 = A_3A_2 + A_3\bar{A}_1\bar{A}_0$$

$$F_2 = A_2\bar{A}_1\bar{A}_0 + \bar{A}_2A_0 + \bar{A}_2A_1$$

$$F_1 = \bar{A}_1A_0 + A_1\bar{A}_0$$

$$F_0 = A_0$$

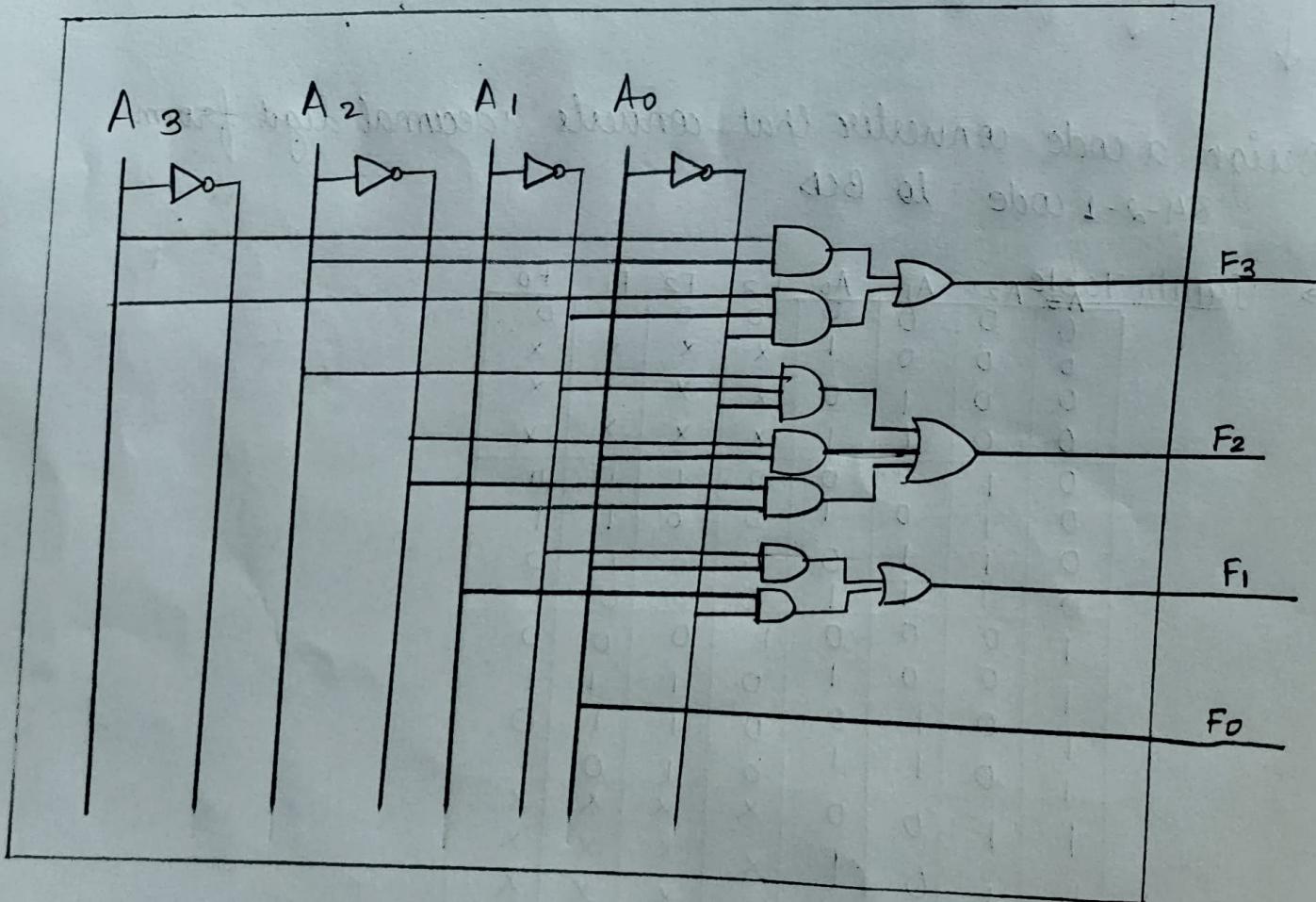

Use truth table and K-maps design the BCD to seven segment decoder using minimum number of gates. The six invalid combinations should result in a blank display. (5)

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	01	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	0	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	01	1	1	1	0	1	1
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

AB	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	0	0	0	0
10	1	1	0	0

AB	00	01	11	10
00	1	1	1	0
01	1	0	1	0
11	0	0	0	0
10	1	1	0	0

CD	00	01	11	10
AB	00	1	1	0
01	1	1	1	1
11	0	0	0	0
10	1	1	0	0

AB	00	01	11	10
00	1	0	1	1
01	0	1	0	1
11	0	0	0	0
10	1	1	0	0

$$A = (\bar{A} + \bar{B})(\bar{A} + \bar{C})(\bar{B} + C + D)(\bar{A} + B + C + \bar{D})$$

$$B = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C}\bar{D} + \bar{A}CD$$

$$C = \bar{A}B + \bar{B}\bar{C} + \bar{A}\bar{D}$$

$$D = (\bar{A} + \bar{B})(\bar{A} + \bar{C})(\bar{B} + \bar{C} + \bar{D})(\bar{B} + C + D)(A + B + C + \bar{D})$$

AB\CD	00	01	11	10
00	1	0	0	1
01	0	0	0	
11	0	0	0	0
10	1	0	0	0


AB\CD	00	01	11	10
00	1	0	0	0
01	1	1	0	1
11	0	0	0	0
10	1	1	0	0

AB\CD	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	0	0	0	0
10	1	1	0	0

$$e = \bar{B}\bar{C}\bar{D} + \bar{A}\bar{C}\bar{D}$$

$$f = \bar{A}\bar{C}\bar{D} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D}$$
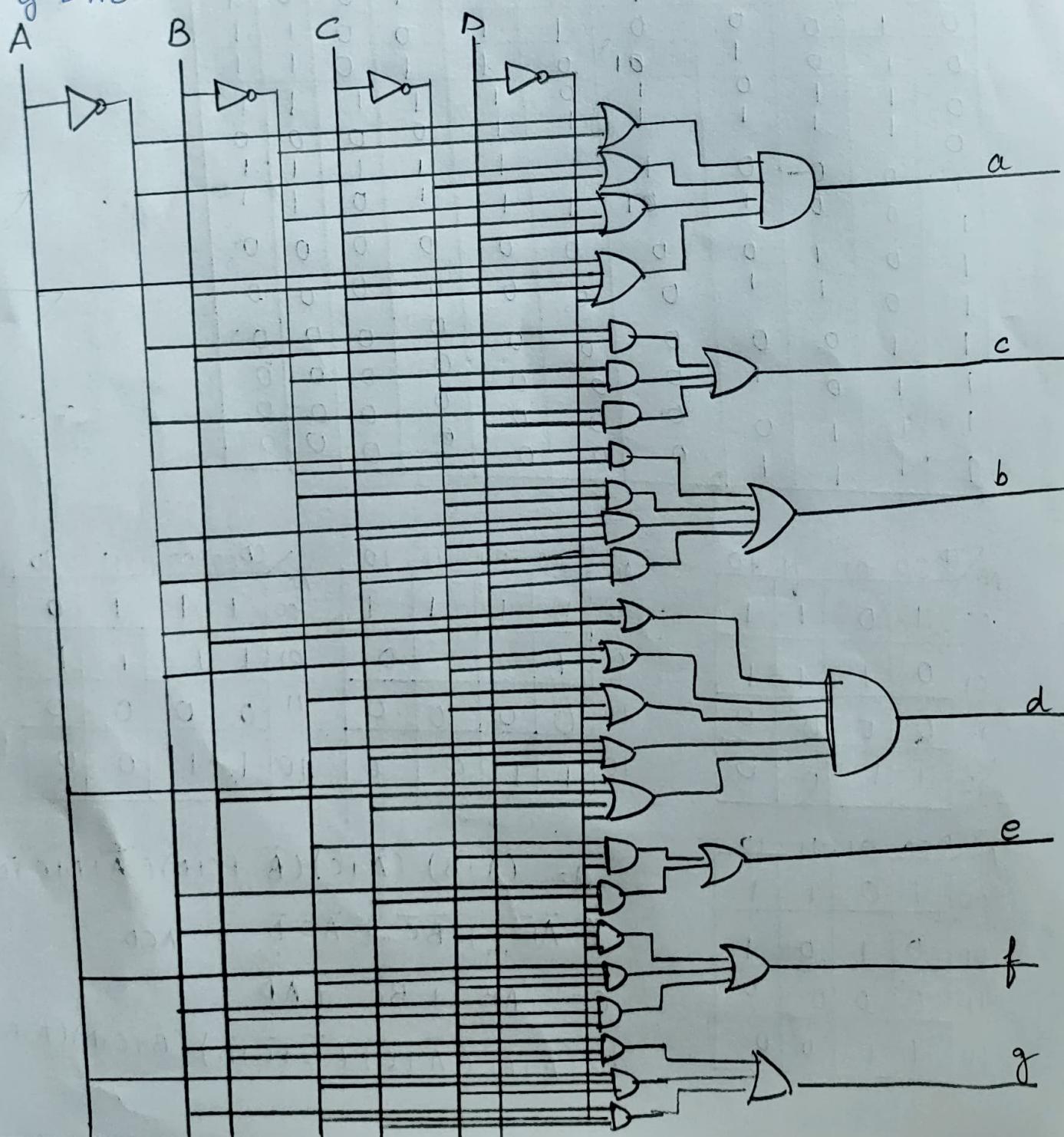
$$g = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C}\bar{D}$$



# Truth table

(6)


X	Y	$Q(t)$	$Q(t+H)$	Set	Reset
0	0	0	1	0	1
0	0	1	0	1	0
0	1	0	1	0	1
0	1	1	1	1	x
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	0	1	x
1	1	1	1	x	1

X	Y	Q	00	01	11	10
0	0	1	X			0
1	1	1	1	1	X	

$$\text{Set} = X + Q$$

X	Y	Q	00	01	11	10
0	1	0	1	0	1	1
1	0	0	X	0	X	1

$$\text{Reset} = \bar{Q} + Y$$

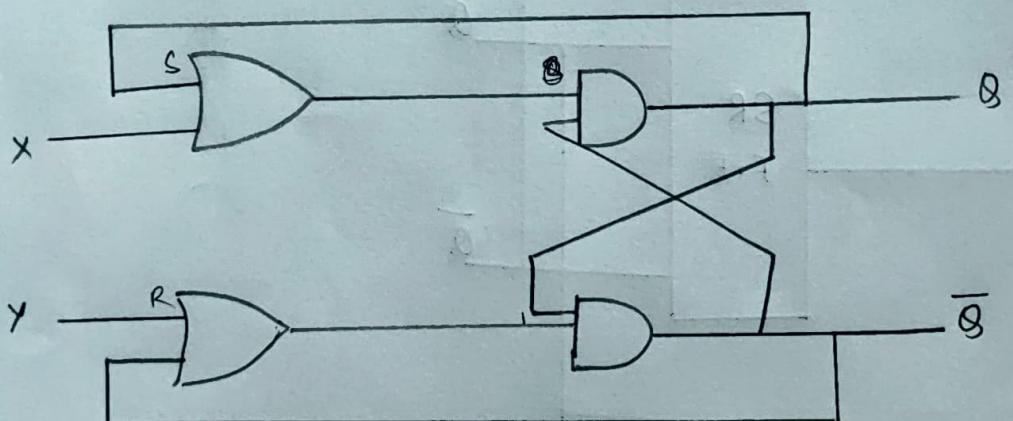

Q. 10. Convert the SR flip flop to XY flip flop.

CLASSMATE

$x$	$y$	$Q(t)$	$Q(t+1)$	$S$	$R$
0	0	0	1	1	0
0	0	1	0	0	1
0	1	0	1	1	0
0	1	1	1	X	0
1	0	0	0	0	X
1	0	1	0	0	1
1	1	0	0	0	X
1	1	1	1	X	0

$x^{48}$

	00	01	11	10
0	0	0	X	1
1	0	0	X	0

$s^{48}$

	00	01	11	10
0	0	1	0	0
1	X	1	0	X

