


23/10/21

→ Active Elements - Sources

• Voltage source :



1. Ideal (constant)
 - Maintains constant voltage irrespective of connected load
 - Internal resistance $R_s = 0$

Ideal voltage source (DC)

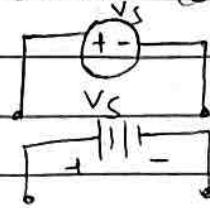

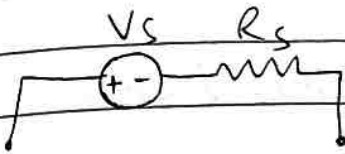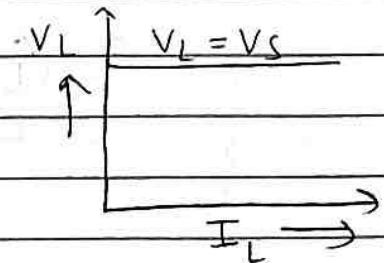
2. Practical : Real

- Terminal voltage changes based on the connected load
- Internal resistance $R_s \neq 0$



Practical voltage source

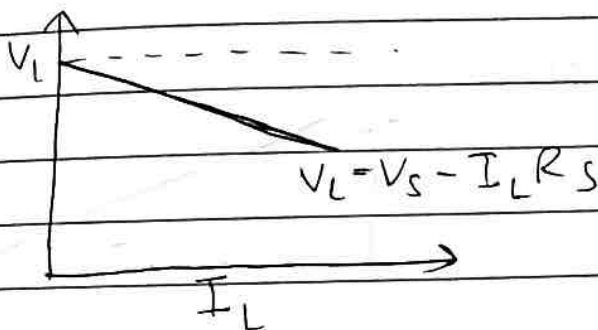(smaller the R_s , the closer to ideal voltage source)



23/10/21



classmate
Date
Page

• Current source

1. Ideal: constant

- Maintains constant current irrespective of the load connected
- Internal resistance $R_s = \infty$



Ideal current source (DC)

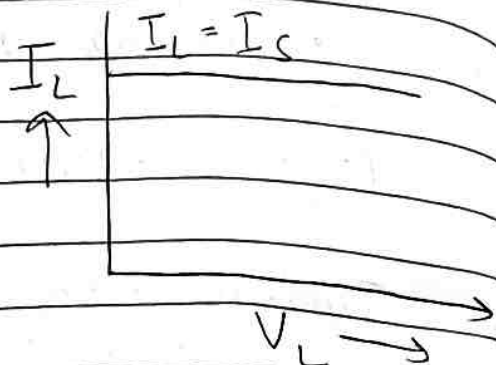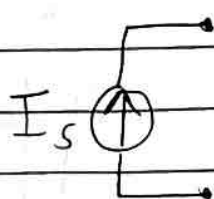

2. Practical: real

- Output current changes based on the connected load.
- Internal resistance ($R_s/R_i/R_{int}$) $< \infty$

Practical Current Source

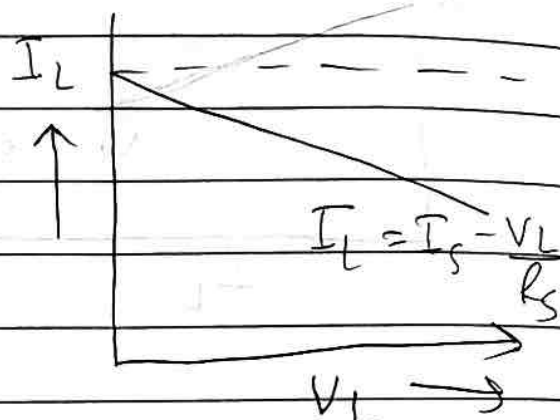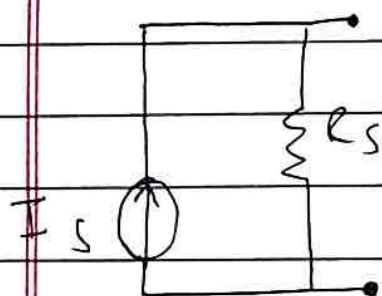

(The larger the value of R_s , the closer to ideal current source)


23/10/21

energy consuming element

→ Resistor:


- Passive electric device that dissipates energy
- Resistance: property which opposes flow of current
- Symbol: R
- Unit: Ohms (Ω)
- Power consumed $= I^2 R$
- Conductance:
 - reciprocal of resistance
 - Symbol: G
 - unit - Siemens (S)

→ Series connection of resistors

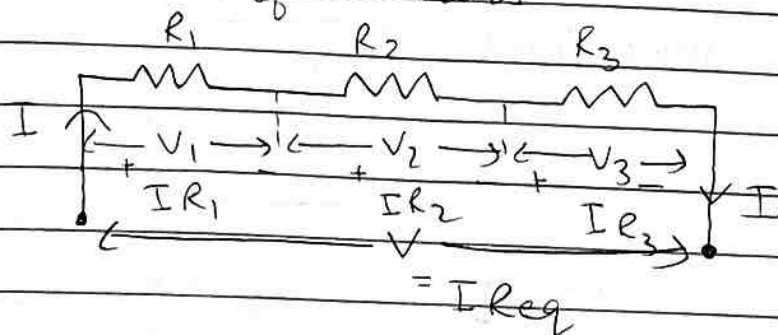

- Current (I) in all the resistors remains same
- $V = V_1 + V_2 + V_3$
- $R_{eq} = R_1 + R_2 + R_3$


→ Parallel connection of resistors

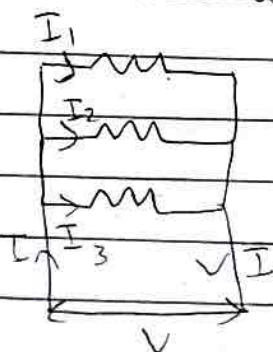

- Voltage (V) is same
- $I = I_1 + I_2 + I_3$
- $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

23/10/21


• Series resistors :

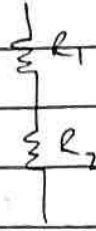

$$R_{eq} = R_1 + R_2$$

$$(V_S = V_1 + V_2)$$


• Voltage divider :

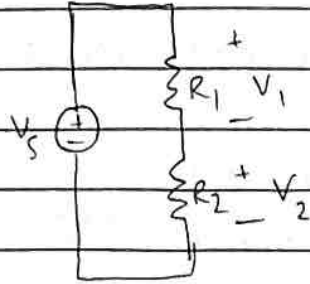

$$V_1 = \frac{R_1}{R_1 + R_2} V_S$$


$$V_2 = \frac{R_2}{R_1 + R_2} V_S$$

• Parallel resistors :

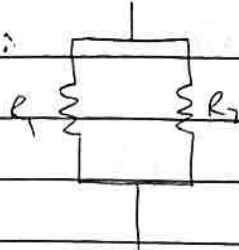

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

• Current divider :

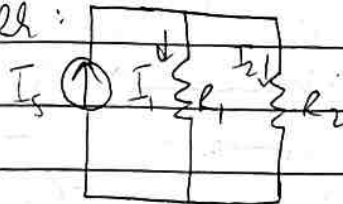

$$I_1 = \frac{R_2}{R_1 + R_2} I_S$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_S$$

→ Delivering and absorbing power by a source:



• A battery is discharging (delivering power/energy) if current is coming out from +ve terminal.

• A battery is charging (absorbing power/energy) if current is flowing into +ve terminal.



23/10/21

- When current flows through a resistor, power is dissipated.

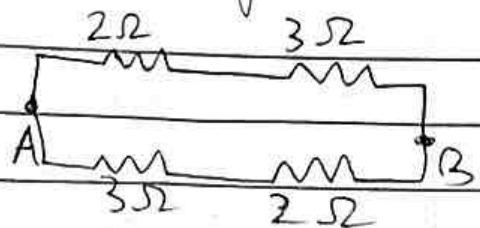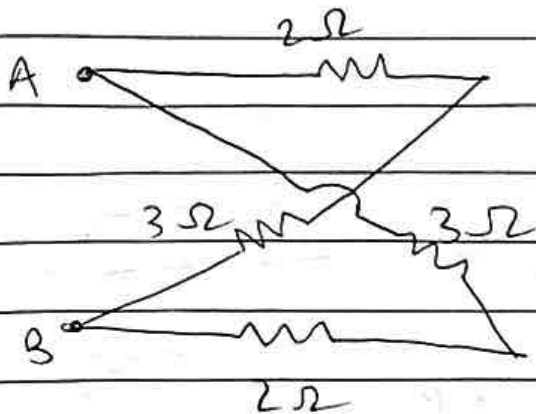Q. Find equivalent resistance of networks given below.



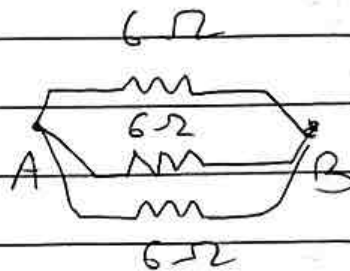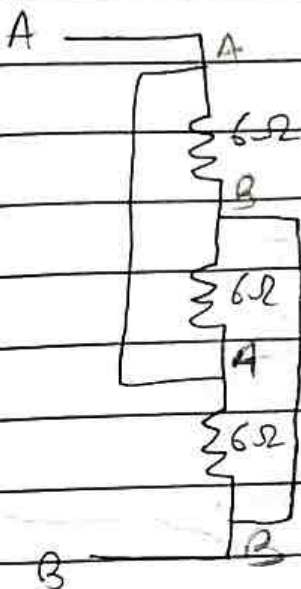
$$R_{\text{eff}} = \frac{5 \times 5}{5 + 5} \\ = \frac{25}{10} = 2.5 \Omega$$



$$\frac{1}{R_{\text{eff}}} = \frac{1}{6} + \frac{1}{6} + \frac{1}{6} \\ = \frac{3}{6} = \frac{1}{2}$$



$$R_{\text{eff}} = 2 \Omega$$

23/10/21

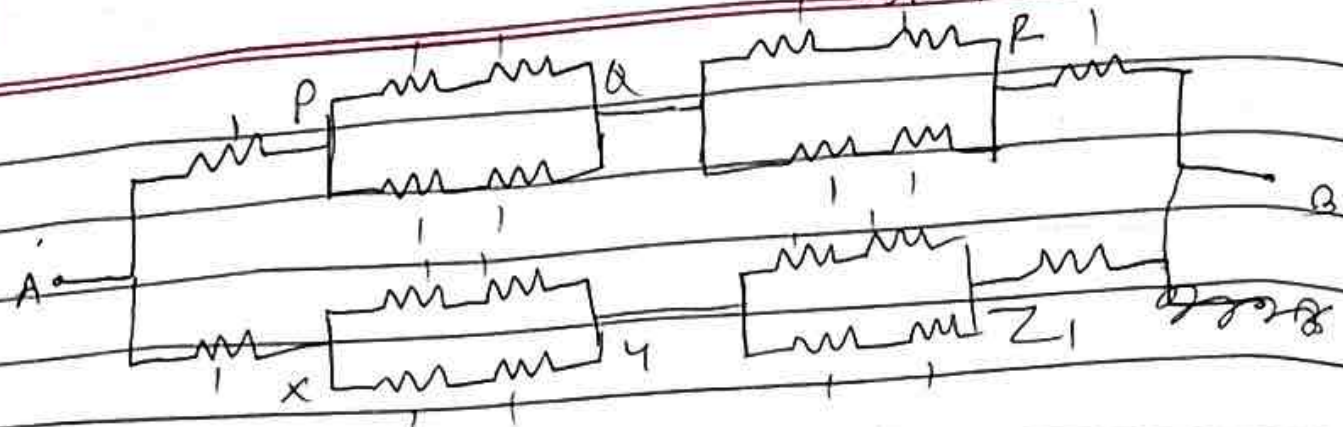

$R_{eff} = 1 + 2 + 2 + 2 \Omega$



Q.

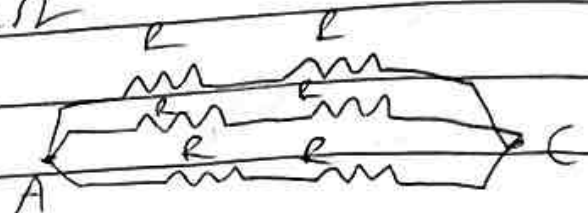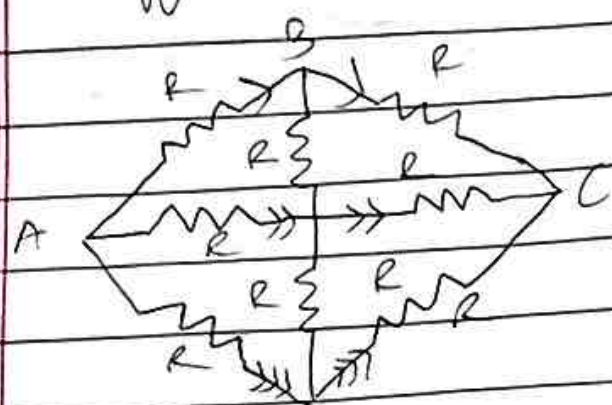

$$\frac{1}{R_p} = \frac{1}{2R} + \frac{1}{2R} + \frac{1}{2R}$$

$$R_p = \frac{2R}{3} \Omega$$

Q.

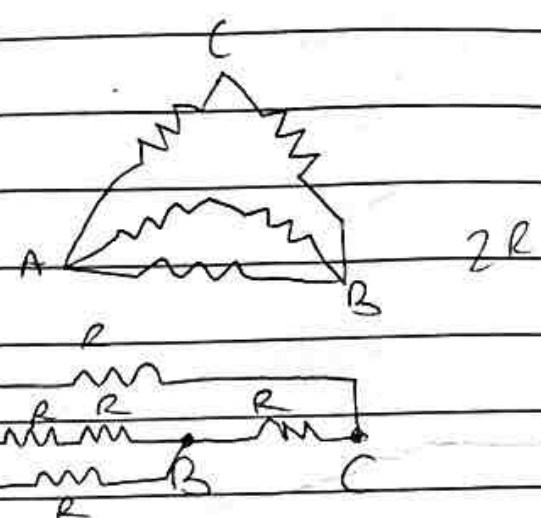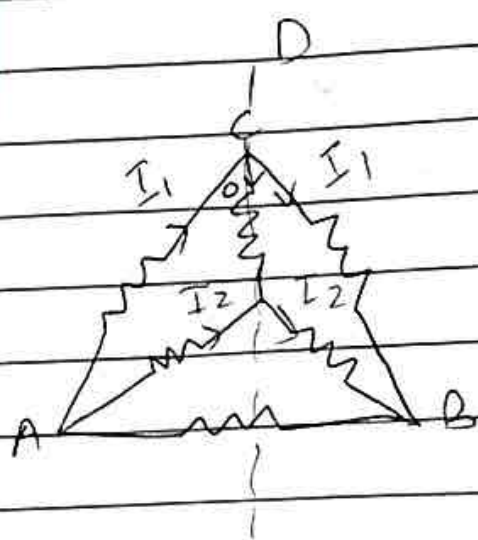

23/10/21

→ Inductor:

- Passive electric device that stores energy in its magnetic field when current flows through it.

- A coil of wire wound on a core

e.g.: air core or iron core inductor

- Inductance: property which opposes rate of change of current

Symbol: L

Unit: Henry (H)

- The voltage across inductor is proportional to the rate of change of current through it.

$$V_L = L \frac{di}{dt}$$

→ Inductive Circuit:

For a coil uniformly wound on an air-core of uniform cross section, self inductance is given by

$$L = \frac{\mu_0 AN^2}{l}$$

l = length of magnetic circuit in meter


A = cross sectional area in square meter

μ_0 = permeability of air = $4\pi \times 10^{-7}$

N = No. of turns in the coil


23/10/21

• Equivalent inductance

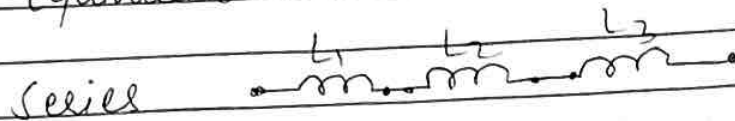

$$L_{eq} = L_1 + L_2 + L_3$$

Parallel

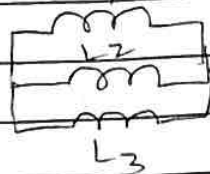

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

Energy stored in an inductor

• Instantaneous power,

$$p = v_L \cdot i = L i \frac{di}{dt}$$

• Energy absorbed in 'dt' time is

$$dw = L i di$$

• Energy absorbed by the magnetic field when current increases from 0 to I amperes is I

$$W = \int_0^I L i di = \frac{1}{2} L I^2$$

→ Capacitors :

- Passive electric device that stores energy in the electric field between a pair of closely spaced conductors

- Capacitance: property which opposes the rate of change of voltage

Symbol : C

Unit : Farad (F)

- The capacitive current is proportional to the rate of change of voltage across it

$$i_c = C \frac{dv_c}{dt}$$

- Charge stored in a capacitor whose plates are maintained at constant voltage

$$Q = CV$$

Terminologies :

- Electric field strength

$$E = \frac{V}{d} \text{ volts/m}$$

- Electric flux density

$$D = \frac{Q}{A} \text{ C/m}^2$$

- Permittivity of free space

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$


- Relative permittivity:

$$\epsilon_r$$

- Capacitance of parallel plate capacitor

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

23/10/21

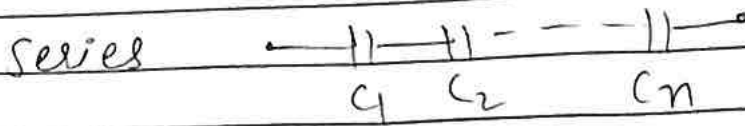Equivalent Capacitance

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

Parallel



$$C_{eq} = C_1 + C_2 + \dots + C_n$$

→ Energy stored in a capacitor

- Instantaneous power

$$p = v_c \times i = C v_c \frac{dv_c}{dt}$$

- Energy supplied during 'dt' time is :

$$dW = C v_c dv_c$$

- Energy stored in the electric field when potential rises from 0 to V volts is

$$W = \int_0^V C v_c dv_c = \frac{1}{2} C V^2 \text{ J}$$