

Node Voltage Analysis

NETWORK REDUCTION TECHNIQUE

Class 6 - 10 November 2021

Introduction



Kirchhoff's Current Law (KCL)


- At any node (junction) in a circuit, the algebraic sum of currents entering and leaving the node at any instant of time must be equal to zero

Node

- A point in an electric circuit where 3 or more elements are connected

Branch

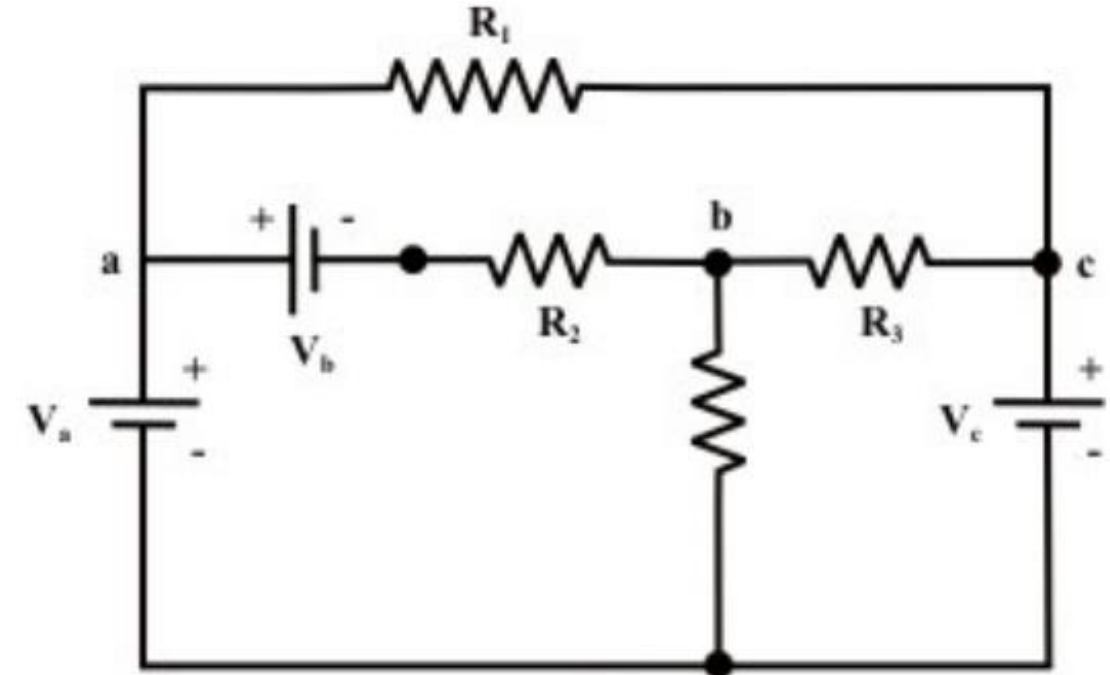- A conducting path between two nodes in a circuit containing circuit elements



Node Voltage Analysis Method

- Convert all the practical voltage sources to current sources
- Identify nodes in the circuit
- One of the nodes is taken as reference node
- Assign a voltage to each of the remaining nodes
- Write KCL equations for all the nodes (excluding the reference node)
- Solve for voltages

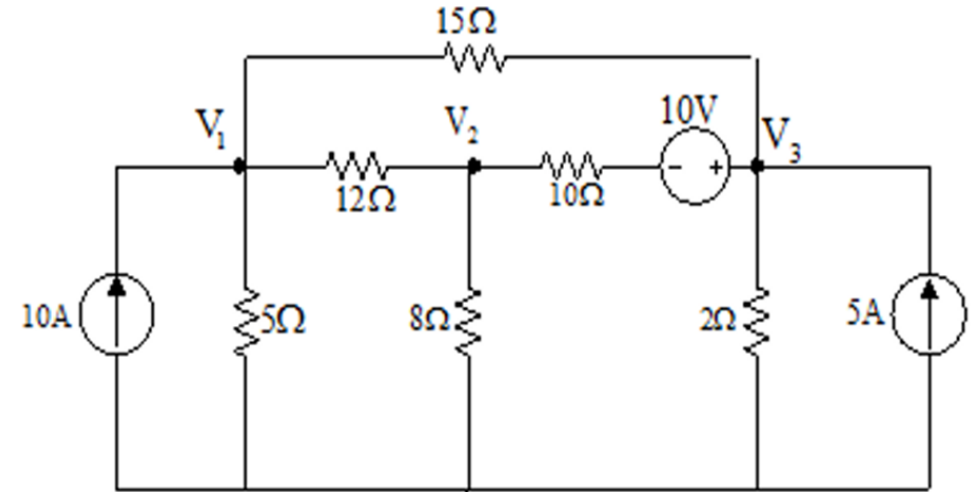


Illustration 1



Determine the current through the galvanometer “**G**”. Also, write network equations using inspection method

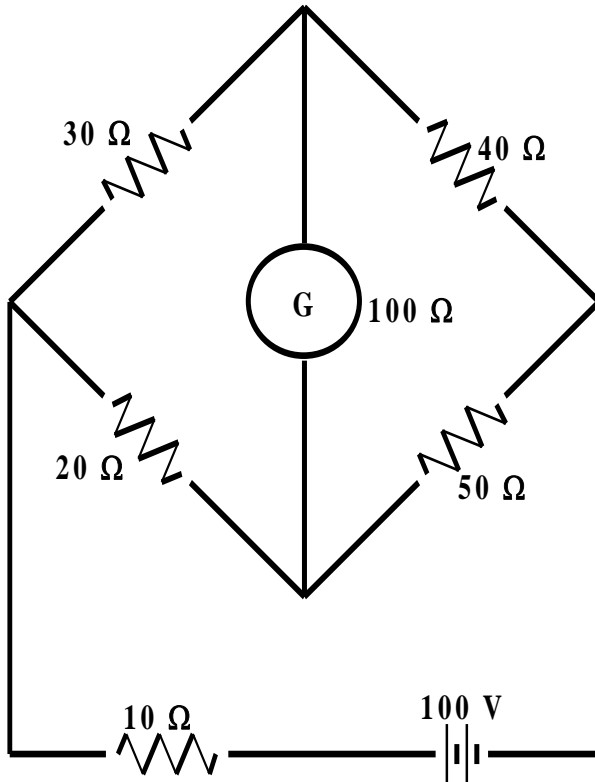


Illustration 2



Realize the network defined by node voltage equation


$$\begin{bmatrix} 1.55 & -0.5 & -0.05 \\ -0.5 & 0.875 & -0.25 \\ -0.05 & -0.25 & 0.4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 4 \\ -2 \\ 0 \end{bmatrix}$$

Quiz



The current I_s in amperes in voltage source and voltage V_s across the current source is

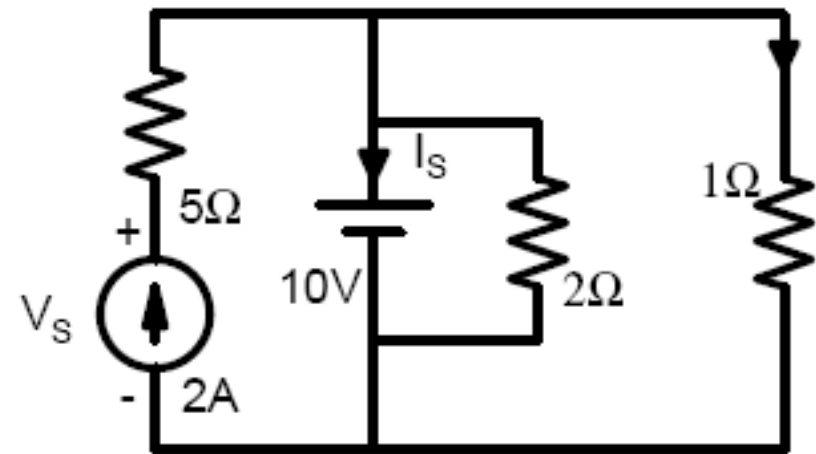
- a) -13, 20
- b) -13, 10
- c) 13, -10
- d) 13, -20



Supernode



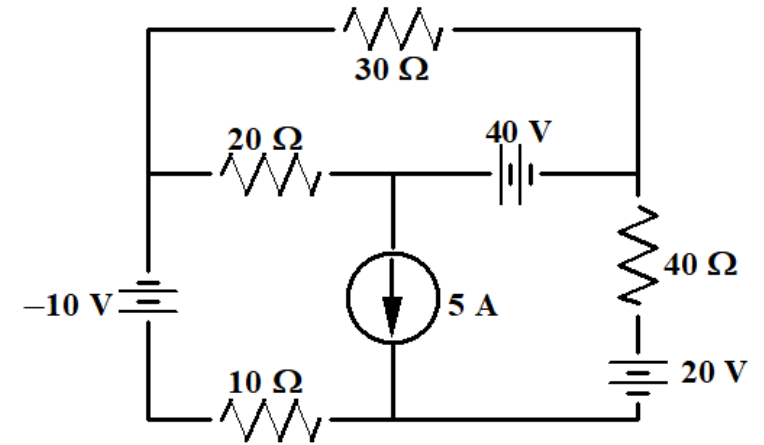Find the current through 40 V battery. Is the battery charging or discharging?



**Ans: 4.19 A,
Discharging**