

# LECTURE 5

---

KARNAUGH MAP (K – MAP)

### EXAMPLE 5:

DESIGN A COMBINATIONAL CIRCUIT WITH 4- INPUT LINES THAT REPRESENTS A DECIMAL DIGIT IN BCD AND 4- OUTPUT LINES THAT GENERATES 2'S COMPLEMENT OF INPUT DIGIT.

Decimal digit	8 4 2 1 A B C D	2's Complement $Y_3 Y_2 Y_1 Y_0$
0	0000	0000
1	0001	1111
2	0010	1110
3	0011	1101
4	0100	1100
5	0101	1011
6	0110	1010
7	0111	1001
8	1000	<del>0000</del> 1000
9	1001	0111

$0100 \Rightarrow 1's \text{ comp} = 1011$   
 $\uparrow (4)$

Sign bit = 0 = +ve  
 1 = -ve

$1100 \leftarrow 2's \text{ comp.}$   
 $\uparrow (-4) \text{ of } (0100)$

$0100 \leftarrow \text{LSB}$   
 $\uparrow$   
 $1100$  (circled)

4-bit  $\text{comp} = 2^4 = 16$  input combinations  
 $0000 - 1001$   
 = 10 combinations

4-bits = signed no.  
 $(-8)_{10} \leftarrow 0 \rightarrow (0111)_2 \leftarrow (+7)_{10}$

5-bits  
 $0 \rightarrow$

5-bits

Unsigned  $\Rightarrow$  00000 - 11111  $\Rightarrow$  (0) to (31)

Signed  $\Rightarrow$  ~~0000~~ <sup>10000</sup>  $\leftarrow$  00000  $\rightarrow$  01111 <sup>(+15)<sub>10</sub></sup>  
(-16)

unsigned short int A; 1 byte = 8 bits  $\Rightarrow 2^8 = 256$

0  $\rightarrow$  255

①

$A = -3;$

②

$A = 257; \rightarrow$

?

To find 2's complement contd:

$$Y_3 = \{ \pi M(0, 9) + d(10, 11, 12, 13, 14, 15) \}$$

$$Y_3 = \{ \Sigma m(1, 2, 3, 4, 5, 6, 7, 8) + d(10, 11, 12, 13, 14, 15) \}$$

$$Y_2 = \{ \pi M(0, 5, 6, 7, 8) + d(9, 10, 11, 12, 13, 14, 15) \}$$

$$Y_2 = \{ \Sigma m(1, 2, 3, 4, 5, 6, 7, 8) + d(9, 10, 11, 12, 13, 14, 15) \}$$

$$Y_1 = \{ \Sigma m(1, 2, 5, 6, 9) + d(10, 11, 12, 13, 14, 15) \}$$

$$Y_0 = \{ \Sigma m(1, 3, 5, 7, 9) + d(10, 11, 12, 13, 14, 15) \}$$

$Y_3$   $CD$


	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{C}$	0	1	1	1
$C$	1	1	1	1
$\bar{D}$	d	d	d	d
$D$	1	0	d	d

$Y_3 = B + C + \bar{A}D + A\bar{D}$

$$Y_2 = \bar{B} + \bar{C}D + B\bar{C} = B\bar{C}\bar{D} + \bar{B}D + \bar{B}C$$

$$Y_1 = ? \quad \bar{C}D + C\bar{D} = C \oplus D$$

$$Y_0 = D, \text{ from truth table}$$

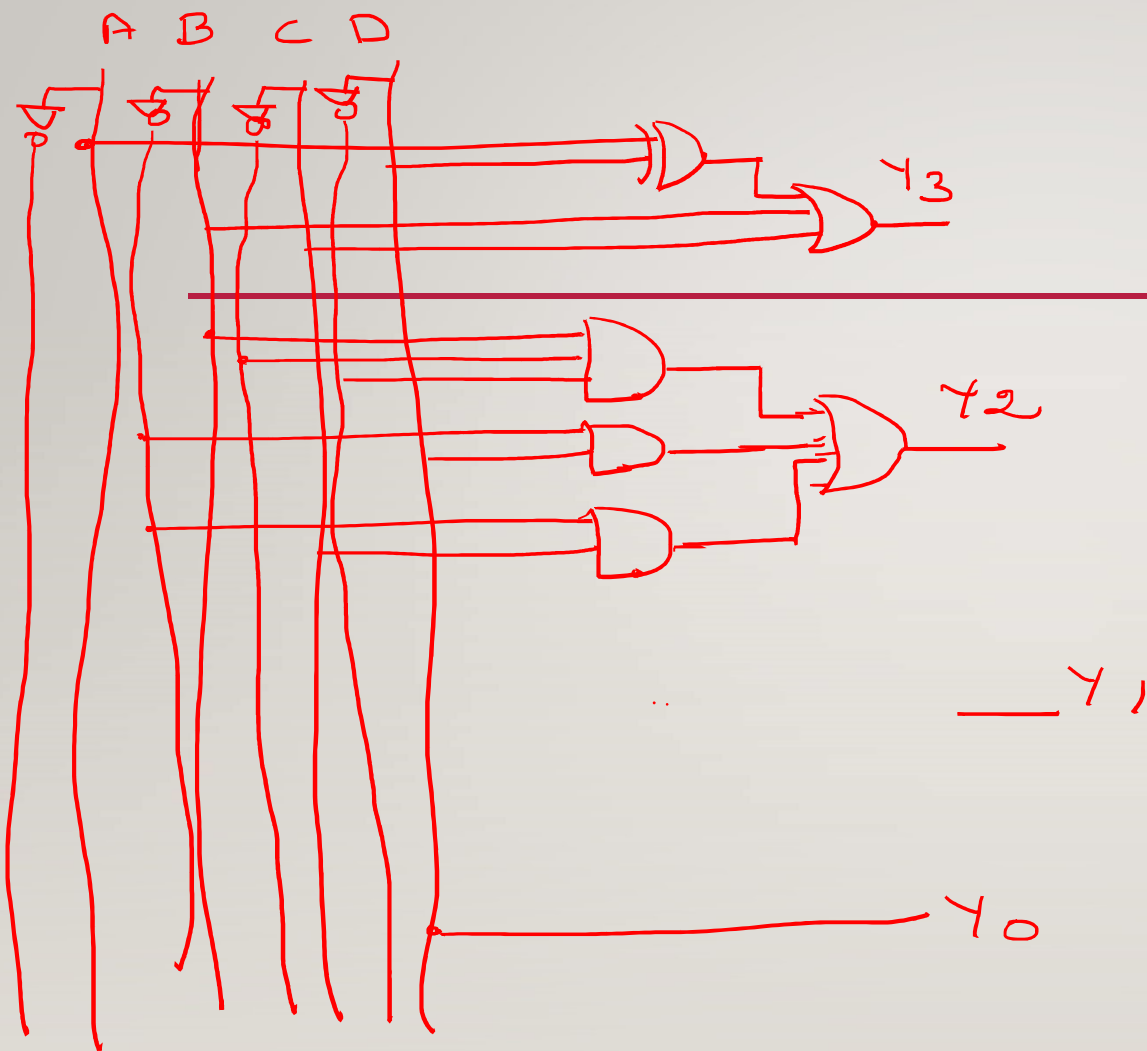

$$Y_3 = B + C + \underbrace{A\bar{D} + A\bar{D}}_{A \oplus D}$$

$$Y_2 = B\bar{C}\bar{D} + \bar{B}D + \bar{B}C$$

## EXAMPLE 6:

Design a combinational circuit to check for even parity of 4 bits. A logic '1' output is required when the 4 bits constitute an even parity.

---





## EXAMPLE 7:

Design a combinational circuit that multiplies by '5' an input decimal digit represented in BCD. The output is also in BCD.

---

Input :  $(0)_{10}$  to  $(9)_{10}$                        $(0000)$  to  $(1001)$  in BCD  
output :  $(0)_{10}$  to  $(45)_{10}$                        $(000000)$  to  $(0100\ 0101)$  in BCD