



# Basic Electrical Technology

## Thevenin's Theorem

---



# Definition

---

- Any **linear, bilateral** network may be replaced by a single voltage source (called Thevenin's equivalent voltage,  $V_{Th}$ ) in series with one resistance (called Thevenin's equivalent resistance,  $R_{Th}$ ) across the load terminals.
- Thevenin's equivalent voltage,  $V_{Th}$ , is the open circuit voltage at the load terminals.
- Thevenin's equivalent resistance,  $R_{Th}$ , is the equivalent resistance at the load terminals, after replacing the sources by their internal resistances.



# Procedure

---

## ➤ To find $V_{Th}$ :


- Remove the load and keep the terminals open circuited.
- Apply mesh current / node voltage method
- Find the voltage across the open circuited terminals.

## ➤ To find $R_{Th}$ :

- Keep the load terminals open.
- Replace all the sources by their internal resistances.
- Find the equivalent resistance with respect to open circuited load terminals.
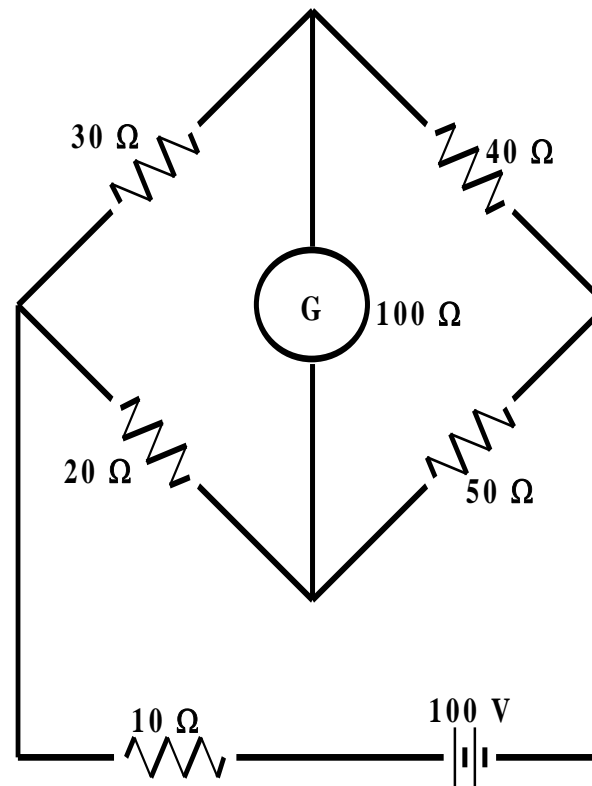
# Illustration 1


Determine the current through the galvanometer using Thevenin's Theorem



**Answer : 84 mA**
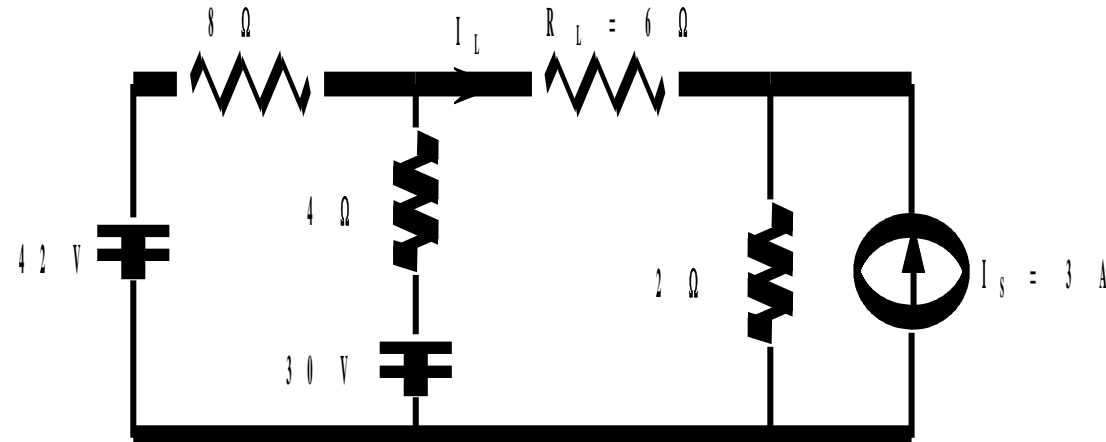
# Illustration 2

For the circuit shown find the current  $I_L$  through  $6\ \Omega$  resistor using Thevenin's theorem



**Ans:  $I_L = 2.625\text{ A}$**



# Illustration 3

The box shown in the adjacent figure consists of independent dc sources and resistances. Measurements are taken by connecting an ammeter in series with the resistor  $R_L$  and the results are shown in the table below. Find the value of  $R_L$  for which the current is 0.6 A




$R_L$	$I$
10 $\Omega$	2.0 A
20 $\Omega$	1.5 A
?	0.6 A

**Ans:  $R_L = 80 \Omega$**


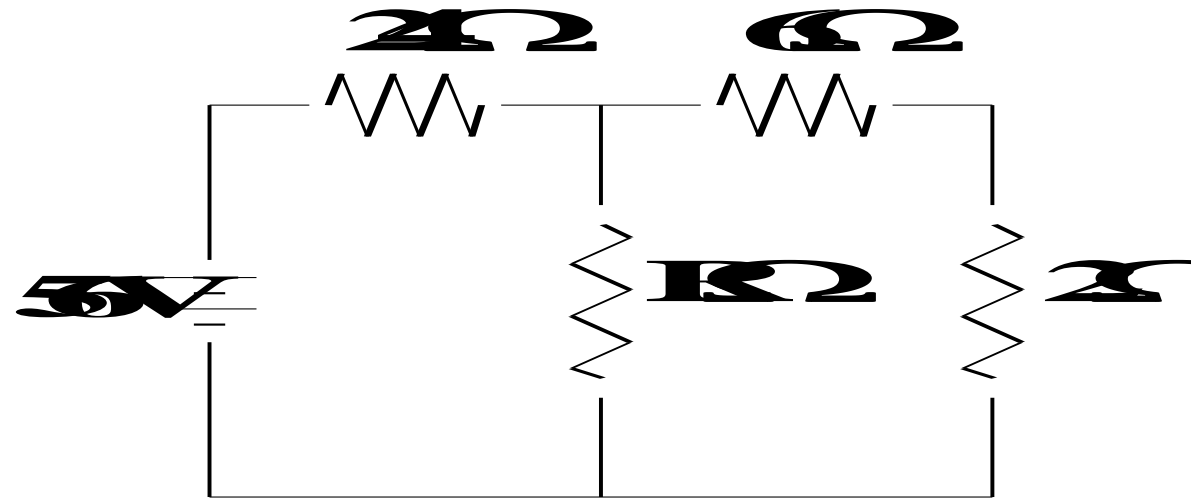
# Homework 1

Using Thevenin's theorem, find the value of  $R$  such that the current through  $2\ \Omega$  resistor is  $1\text{ A}$



**Ans:  $8\ \Omega$**