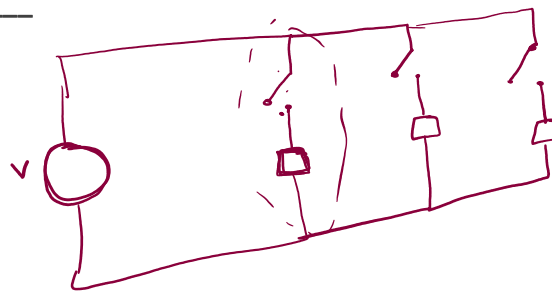



The domestic electrical installations are connected in _____

- A) 3-Phase Star
- B) 3-Phase Delta
- C) Parallel (Single-Phase) ✓
- D) Series (Single-Phase)



A network of resistors is connected to a 16 V battery with internal resistance of $1\ \Omega$, as shown below. The voltage drop V_{CD} is _____

- a) 4 V
- b) 2 V
- c) 8 V ✓
- d) 16 V

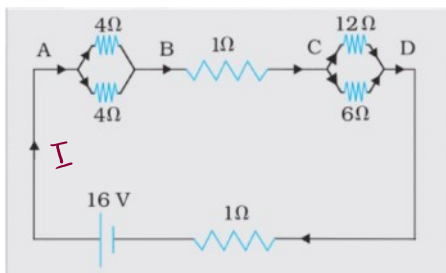

$$V_{CD} = 2 \times (12 \parallel 6)$$

$$= 2 \times 4 = 8V$$

$$V_{CD} = I \times R_{CD}$$


$$I = \frac{16}{R_{Total}}$$

$$I = \frac{16}{(4 \parallel 4) + 1 + (12 \parallel 6) + 1}$$

$$I = \frac{16}{2 + 1 + 4 + 1} = 2A$$

In the circuit shown, the equivalent resistance of the network is _____

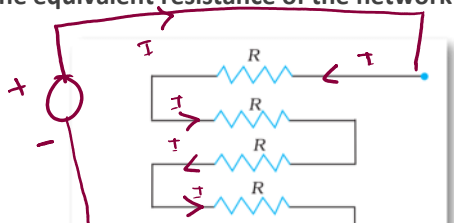
- A) $R/5\ \Omega$
- B) $5R\ \Omega$ ✓
- C) $6R/5\ \Omega$
- D) $2R\ \Omega$



$$R_{Total} = R + R + R + R + R = 5R$$

C) $6R/5 \Omega$

D) $2R \Omega$

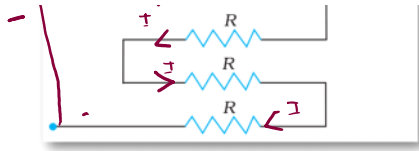


The equivalent resistance of the network shown is _____

A) 15Ω

B) $10/3 \Omega$

C) $16/3 \Omega$ ✓

D) $15/3 \Omega$

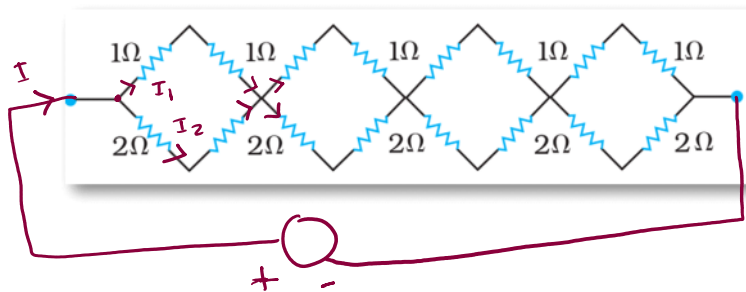


$$\begin{aligned}
 R_{\text{Total}} &= 4 \times \left((1+1) \parallel (2+2) \right) \\
 &= 4 \times (2 \parallel 4) \\
 &= 4 \times \frac{4}{3} \\
 &= \frac{16}{3}
 \end{aligned}$$

Two electric bulbs have filaments of same thickness. When connected to the same source, one of them consumes 60 W and other one consumes 100 W. Then

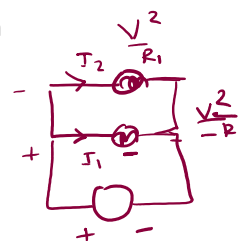- a) 60 W lamp filament has shorter length
- b) 100 W lamp filament has longer length
- c) 60 W lamp filament has longer length ✓
- d) Both have equal length

$$\begin{aligned}
 R_1 &= \rho \frac{l_1}{A} \\
 R_2 &= \rho \frac{l_2}{A}
 \end{aligned}$$



$$P = \frac{V^2}{R}$$

$$P \propto \frac{1}{R}$$

Since, $100\text{ W} > 60\text{ W}$, So $100\text{ W } R < 60\text{ W } R$
and $R \propto l$
 $\therefore 60\text{ W} \rightarrow \text{longer length}$