



# Basic Electrical Technology

[ELE 105 I]

---

## ***SINGLE PHASE AC CIRCUITS***

*LI 6, LI 7, RL, RC, RLC series circuit*





# Topics covered...

---

- AC response of
  - Series RL
  - Series RC
  - Series RLC

# RL circuit analysis

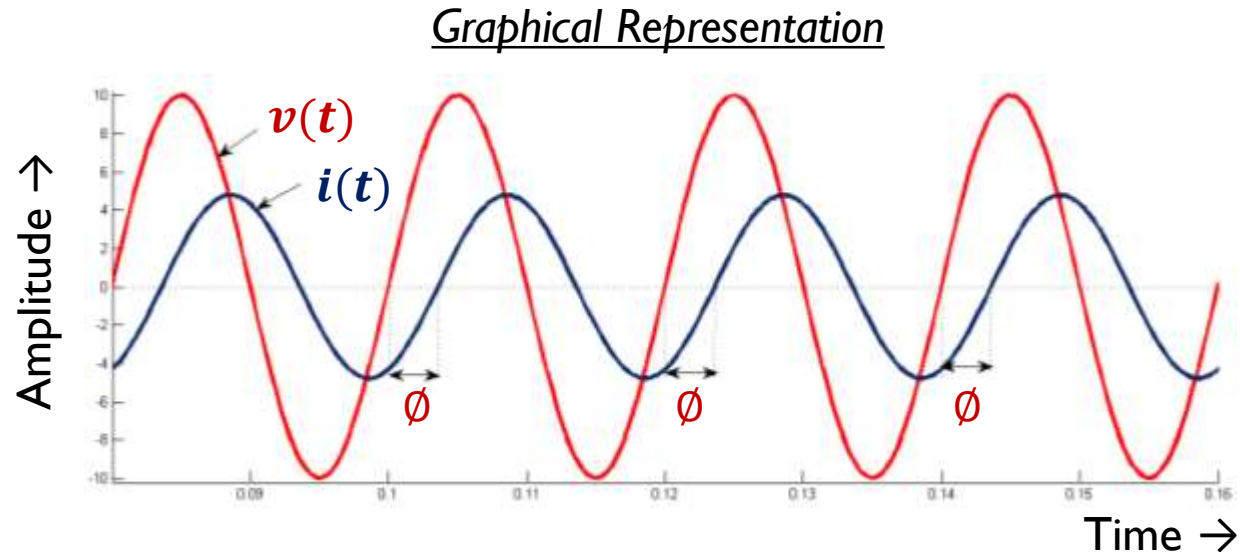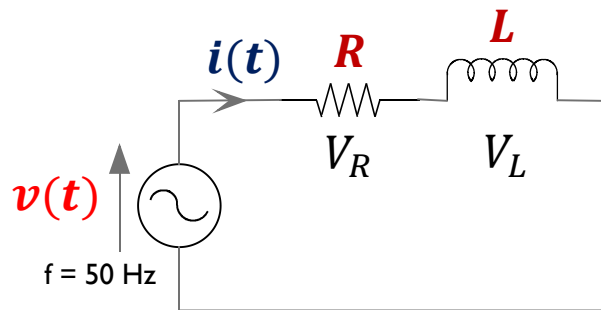


Let  $\bar{I}$  be along the reference

$$\bar{V}_R = \bar{I}R$$

$$\bar{V}_L = j\bar{I}X_L$$

$$\bar{V} = \bar{V}_R + \bar{V}_L = |V|\angle\phi$$

## Phasor Representation

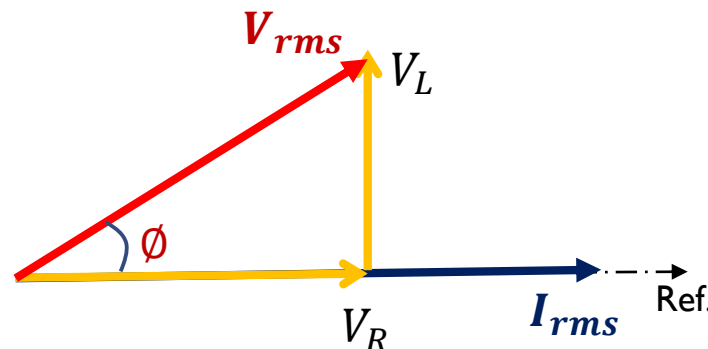

## Impedance

$$\frac{\bar{V}}{\bar{I}} = \frac{\bar{I}(R + jX_L)}{\bar{I}} = R + jX_L = |Z|\angle\phi$$

$Z$  – Impedance of the circuit

$$\therefore R = |Z| \cos \phi \quad X_L = |Z| \sin \phi$$

$$|Z| = \sqrt{R^2 + X_L^2} \quad \phi = \tan^{-1} \frac{X_L}{R}$$

## Mathematical Representation


$$i(t) = I_m \sin(\omega t)$$

$$v(t) = V_m \sin(\omega t + \phi)$$

$\phi$  – Phase Angle



# Power associated - RL circuit

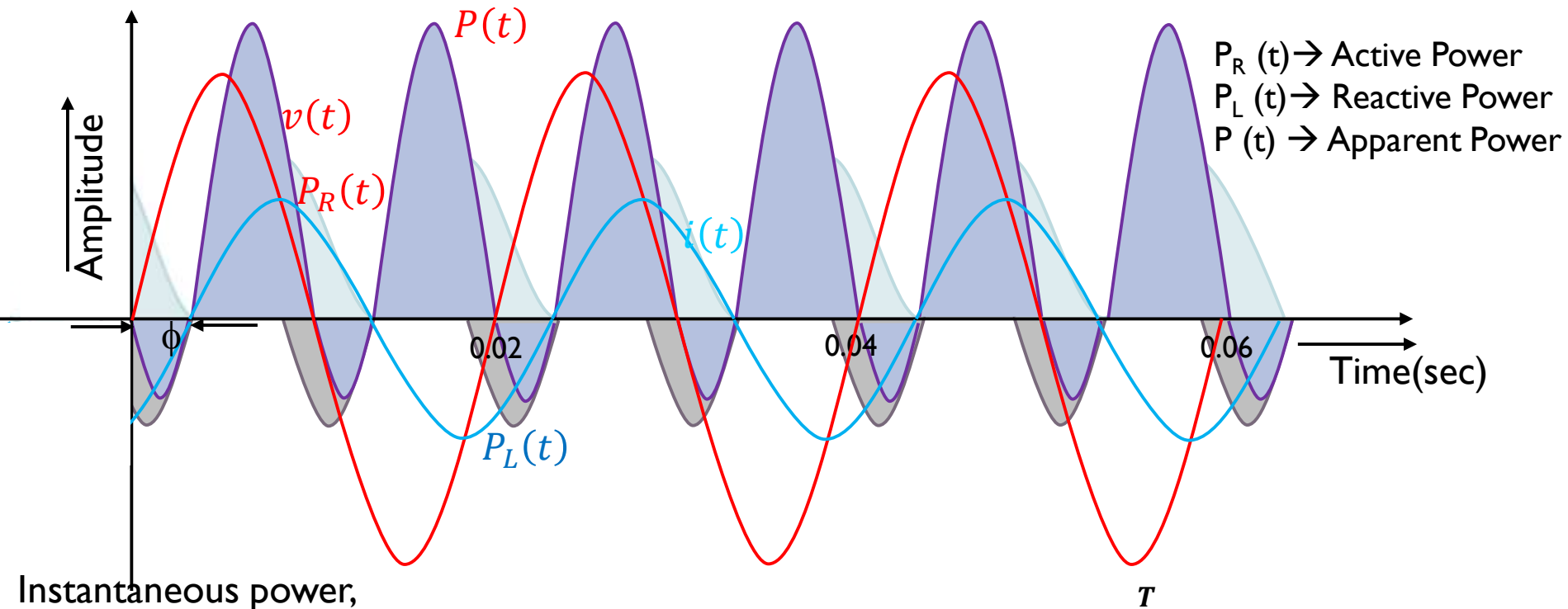

$P_R(t) \rightarrow$  Active Power  
 $P_L(t) \rightarrow$  Reactive Power  
 $P(t) \rightarrow$  Apparent Power

Instantaneous power,

$$p(t) = v(t) \cdot i(t)$$

$$= V_m I_m \sin \omega t \cdot \sin(\omega t + \phi)$$


$$= V_{rms} I_{rms} [\cos \phi - \cos(2\omega t + \phi)]$$

$$\text{Average Power, } P = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos \phi$$

$$\boxed{P_{avg} = V_{rms} I_{rms} \cos \phi}$$

**$\cos \phi$**  is called the **Power Factor**

# RC circuit analysis

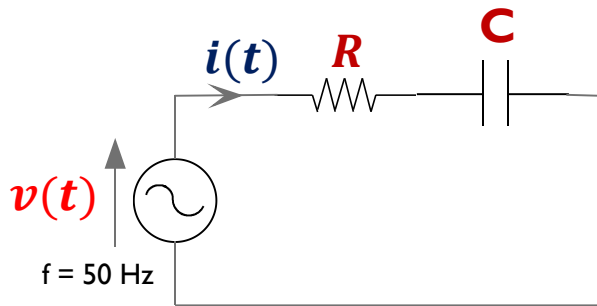

Let  $\bar{I}$  be along the reference

$$\bar{V}_R = \bar{I}R$$

$$\bar{V}_C = -j\bar{I}X_C$$

$$\bar{V} = \bar{V}_R + \bar{V}_C = |V|\angle -\phi$$


## Mathematical Representation

$$i(t) = I_m \sin(\omega t)$$


$$v(t) = V_m \sin(\omega t - \phi)$$

$\phi$  – Phase Angle

## Graphical Representation

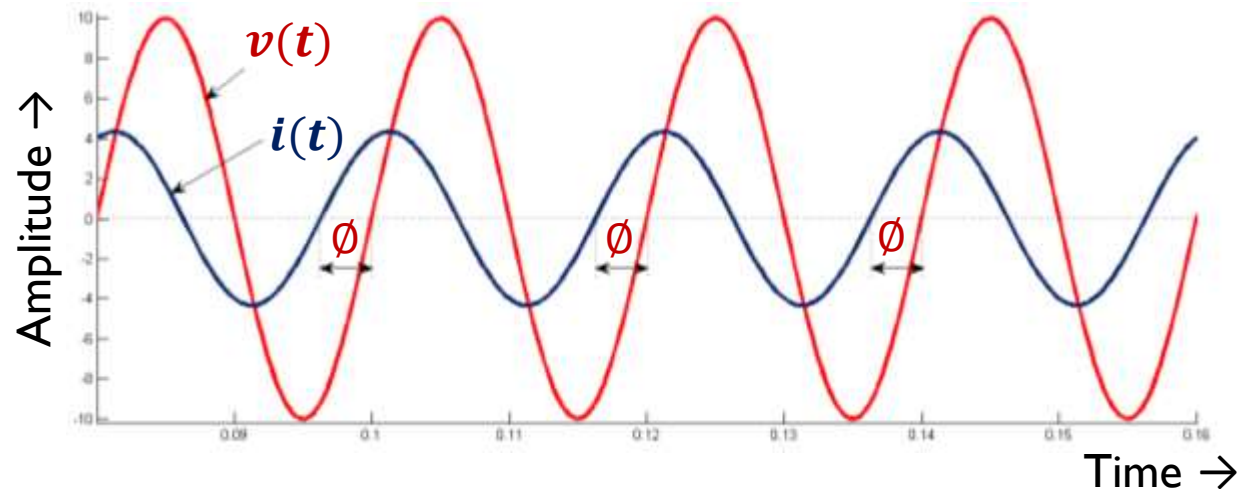

## Phasor Representation

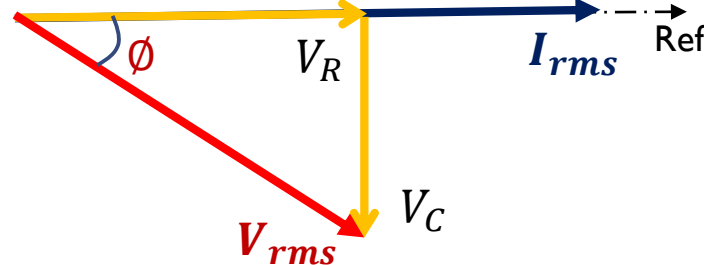

## Impedance

$$\frac{\bar{V}}{\bar{I}} = \frac{\bar{I}(R - jX_C)}{\bar{I}} = R - jX_C = |Z|\angle -\phi$$


$Z$  – Impedance of the circuit

$$\therefore R = |Z| \cos \phi \quad X_C = |Z| \sin \phi$$

$$|Z| = \sqrt{R^2 + X_C^2} \quad \phi = \tan^{-1} \frac{X_C}{R}$$



# Power associated - RC circuit

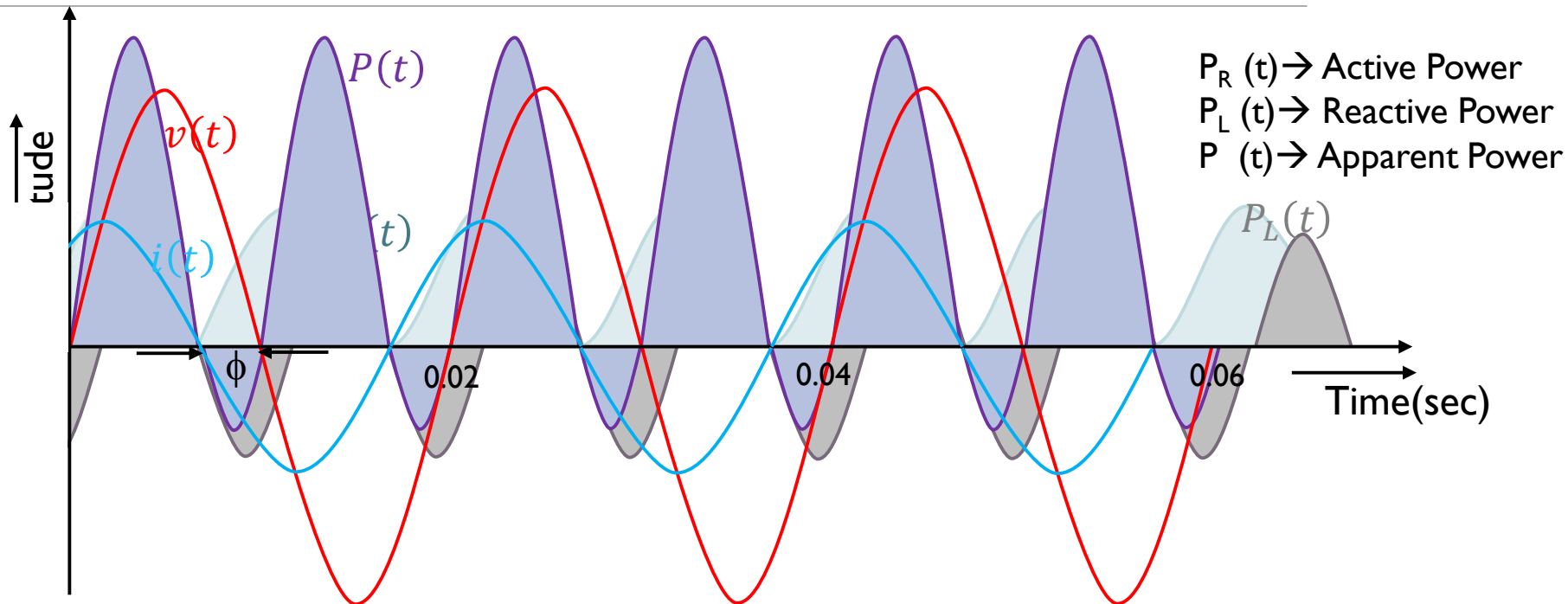

Instantaneous power,

$$p(t) = v(t) \cdot i(t)$$

$$= V_m I_m \sin \omega t \cdot \sin(\omega t - \phi)$$

$$= V_{rms} I_{rms} [\cos \phi - \cos(2\omega t - \phi)]$$


$$\text{Average Power, } P = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos \phi$$

$$\boxed{P_{avg} = V_{rms} I_{rms} \cos \phi}$$

Ratio of Active power to apparent power is called the **Power Factor**



# RLC circuit

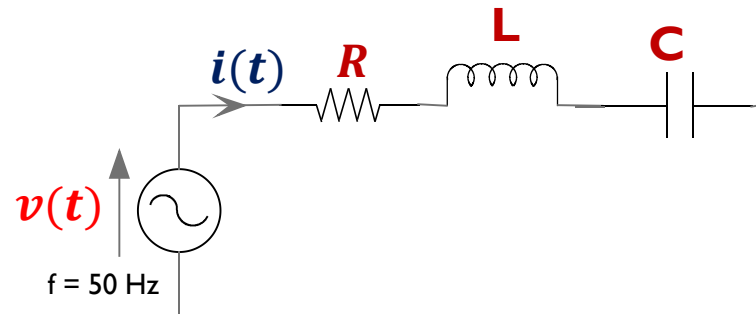

Let  $i(t)$  be the reference

**Impedance,  $Z = R + j(X_L \sim X_C)$**

*if  $X_L = X_C \Rightarrow$  Resistive circuit  
(Resonance condition)*

*if  $X_L > X_C \Rightarrow$  RL series circuit*

*if  $X_L < X_C \Rightarrow$  RC series circuit*




# Illustration I

A resistance of  $50\Omega$  is connected in series with an inductance of  $200\text{mH}$  and capacitance of  $101.321\mu\text{F}$  across a  $230\text{V}, 50\text{ Hz}$ , single phase AC supply. Obtain,

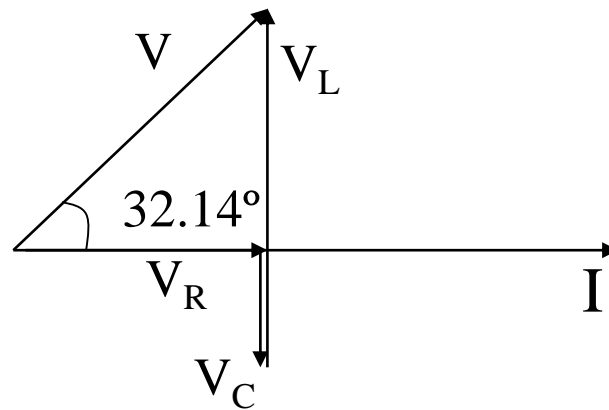- a) Impedance of the circuit
- b) Current drawn
- c) Power factor
- d) Power consumed
- e) Phasor diagram

**Ans:**  
 $59.050\angle 32.14^\circ \Omega$   
 $3.898\angle -32.14^\circ \text{ A}$   
 $0.846 \text{ lag}$   
 $759.15 \text{ W}$







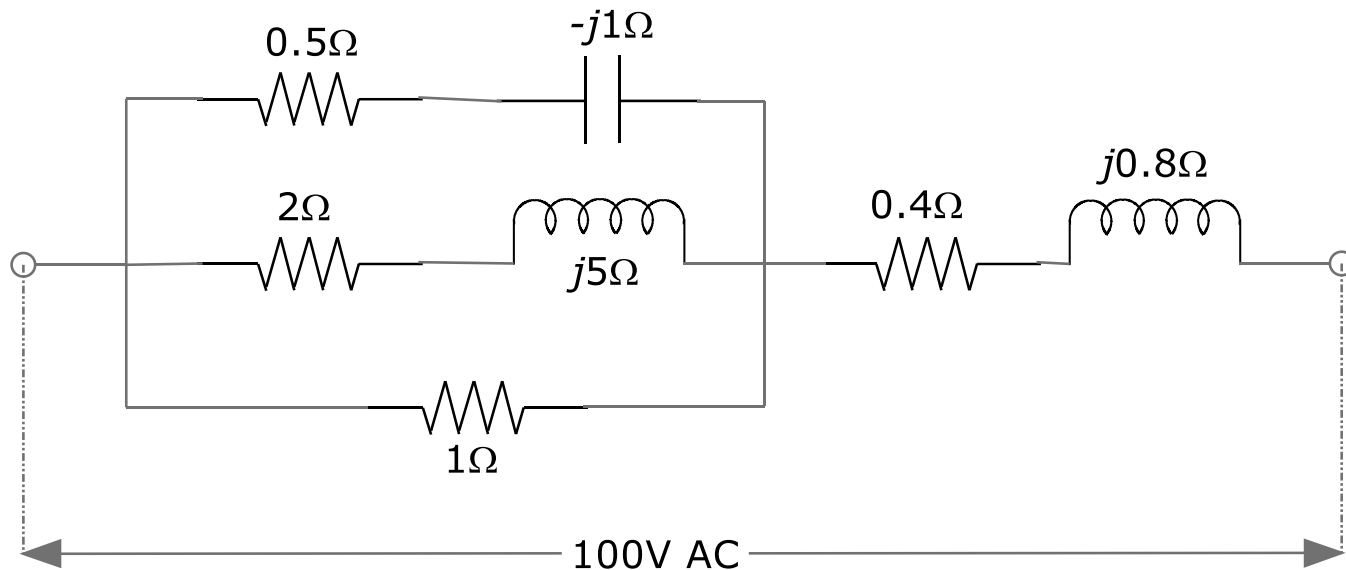
# Illustration 2

Determine the impedance of the circuit shown and the power consumed in each branch



*Ans:*  
 $Z = 1.12 \angle 29.5^\circ \Omega$   
 $1.25 \text{ kW}; 0.216 \text{ kW}; 3.12 \text{ kW}; 3.19 \text{ kW}$



# Summary

- **Define:** Impedance
- **Define:** Active Power; Reactive Power; Apparent Power; Power Factor

	RL	RC
Voltage, current relationship	$i(t)$ lags $v(t)$ by angle $\theta$	$i(t)$ leads $v(t)$ by angle $\theta$
Power associated	$S = VI$ $P = VI \cos \theta$ $Q = VI \sin \theta$	$S = VI$ $P = VI \cos \theta$ $Q = -VI \sin \theta$

# Basic Electrical Technology

[ELE 105 I]

---

## ***SINGLE PHASE AC CIRCUITS***

*L18 –Parallel circuits*




# Topics covered...

---

- Parallel circuit
  - Admittance
  - Conductance
  - Susceptance



# Impedance in parallel

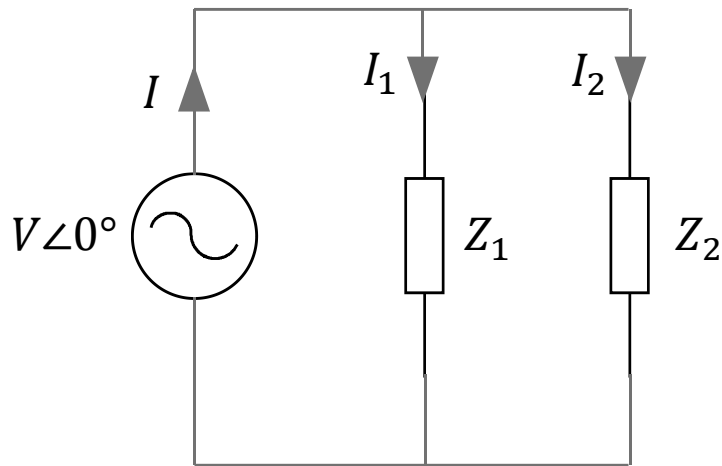

$$\text{Let } Z_1 = R_1 + jX_1 \quad Z_2 = R_2 + jX_2$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} \quad I_1 = I * \frac{Z_2}{Z_1 + Z_2} \quad I_2 = I * \frac{Z_1}{Z_1 + Z_2}$$

$$Y_{eq} = Y_1 + Y_2 \quad \textcolor{red}{Y: \textit{Admittance}}$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{R_1 + jX_1} = \frac{1}{(R_1 + jX_1)} * \frac{(R_1 - jX_1)}{(R_1 - jX_1)} = \frac{R_1}{(R_1^2 + X_1^2)} - j \frac{X_1}{(R_1^2 + X_1^2)} = G_1 - jB_1$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{R_2 + jX_2} = \frac{1}{(R_2 + jX_2)} * \frac{(R_2 - jX_2)}{(R_2 - jX_2)} = \frac{R_2}{(R_2^2 + X_2^2)} - j \frac{X_2}{(R_2^2 + X_2^2)} = G_2 - jB_2$$

$\textcolor{red}{G: \textit{Conductance}} \quad \textcolor{red}{B: \textit{Susceptance}}$

$$B_{eq} = \frac{X_1 + X_2}{(R_1^2 + X_1^2)(R_2^2 + X_2^2)}$$

$$\textcolor{red}{Y_{eq}} = (\textcolor{red}{G_1} + \textcolor{red}{G_2}) - j(\textcolor{red}{B_1} + \textcolor{red}{B_2}) = \textcolor{red}{G_{eq}} - j\textcolor{red}{B_{eq}} \quad G_{eq} = \frac{R_1 + R_2}{(R_1^2 + X_1^2)(R_2^2 + X_2^2)}$$


# Impedance in parallel

For 'N' impedances connected in parallel,

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_N}$$

$$Y_{eq} = Y_1 + Y_2 + Y_3 + \dots + Y_N$$

$$\mathbf{Y_{eq} = G_{eq} \pm jB_{eq}}$$

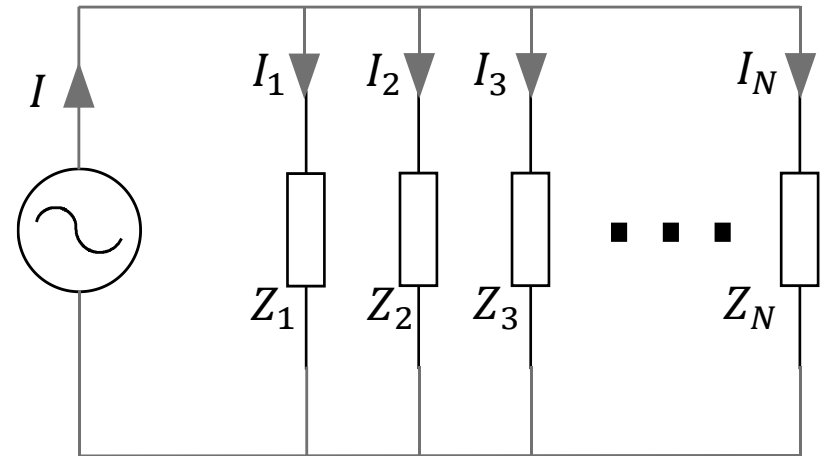

$$I_1 = VY_1; I_2 = VY_2; I_3 = VY_3; \dots \dots I_N = VY_N$$

$$I = I_1 + I_2 + I_3 + \dots + I_N = VY_{eq}$$



# Network equations for AC circuits

KVL Equation  
(Matrix form)

$$\begin{bmatrix} V_1 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & \cdots & Z_{1N} \\ \vdots & \ddots & \vdots \\ Z_{N1} & \cdots & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ \vdots \\ I_N \end{bmatrix}$$

$$[V] = [Z][I]$$


KCL Equation  
(Matrix form)

$$\begin{bmatrix} I_1 \\ \vdots \\ I_N \end{bmatrix} = \begin{bmatrix} Y_{11} & \cdots & Y_{1N} \\ \vdots & \ddots & \vdots \\ Y_{N1} & \cdots & Y_{NN} \end{bmatrix} \begin{bmatrix} V_1 \\ \vdots \\ V_N \end{bmatrix}$$

$$[I] = [Y][V]$$

All the other theorems are applicable to the AC circuits

# Maximum power transfer theorem

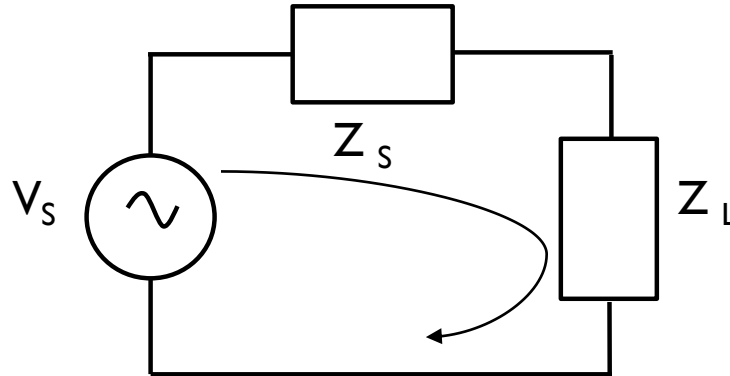

	Type of load	Condition of maximum power transfer
Case 1	Load is purely resistive	$R_L = \sqrt{R_s^2 + X_s^2}$
Case 2	Both $R_L$ & $X_L$ are variable	$Z_L = Z_{TH}^*$
Case 3	$X_L$ is fixed & $R_L$ is variable	$R_L = \sqrt{R_s^2 + (X_s + X_L)^2}$





# Crammers rule

$$\begin{bmatrix} V_1 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & \cdots & Z_{1N} \\ \vdots & \ddots & \vdots \\ Z_{N1} & \cdots & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ \vdots \\ I_N \end{bmatrix}$$

Solution for the linear simultaneous equations above is as follows

Step 1: finding the determinant

$$\Delta = \begin{vmatrix} Z_{11} & \cdots & Z_{1N} \\ \vdots & \ddots & \vdots \\ Z_{N1} & \cdots & Z_{NN} \end{vmatrix}$$

Step 2: finding the determinant after substituting first column with RHS column matrix


$$\Delta_1 = \begin{vmatrix} V_1 & \cdots & Z_{1N} \\ \vdots & \ddots & \vdots \\ V_N & \cdots & Z_{NN} \end{vmatrix}$$

Step 3 :Solution for  $I_1$        $I_1 = \frac{\Delta_1}{\Delta}$


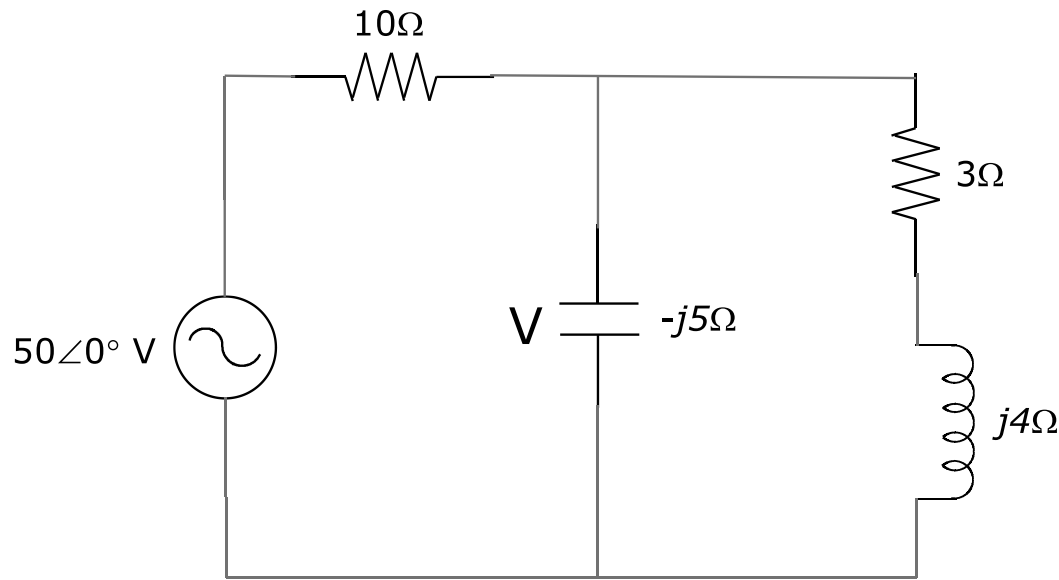
# Illustration I

Assigning two mesh currents, find the voltage  $V$  across the capacitor in the following circuit




*Ans:*

$$V = 22.36 \angle -10.30^\circ \text{ V}$$


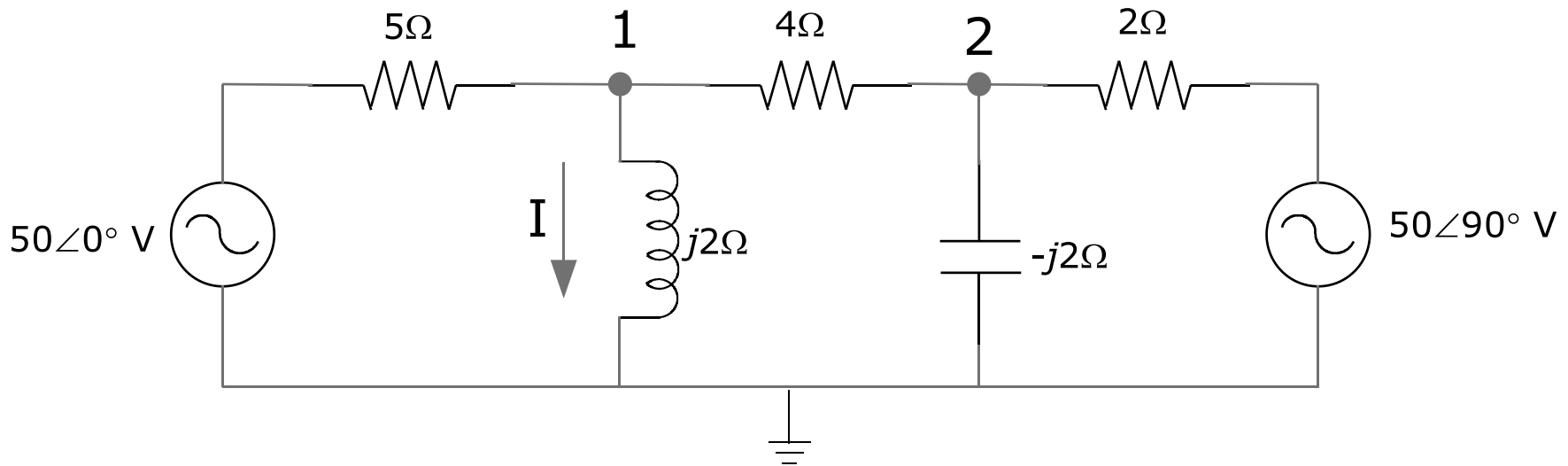
# Illustration 2

Use node voltage method to obtain the current  $I$  in the network



*Ans:*

$$I = 12.38 \angle -17.75^\circ \text{ A}$$



# Summary

---

- **Define:** Conductance; Susceptance; Admittance
- All network equations & theorem are applicable to AC circuits