



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)



Basic Electrical Technology

LECTURE 2 – 23 OCTOBER 2021

- ACTIVE & PASSIVE ELEMENTS



Active Elements - Sources

Voltage Source

➤ Ideal:

- Maintains constant voltage irrespective of connected load
- Internal resistance $R_s = 0$



Ideal Voltage Source (DC)

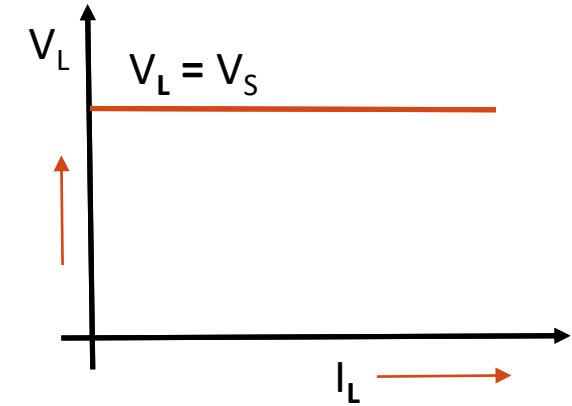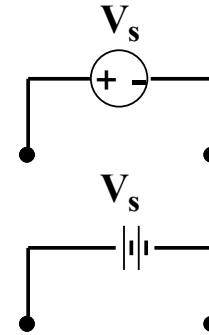

➤ Practical:

- Terminal voltage changes based on the connected load
- Internal resistance $R_s \neq 0$

Practical Voltage Source

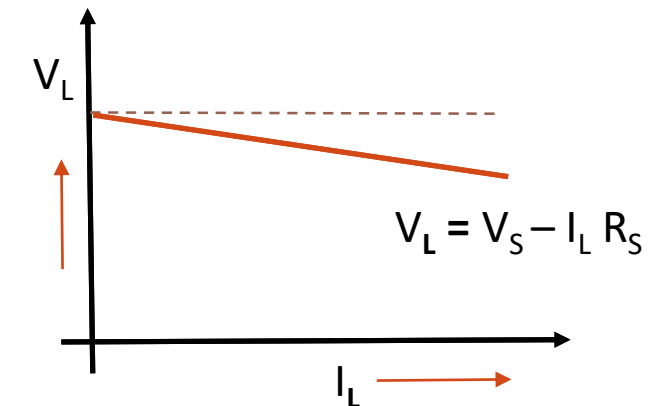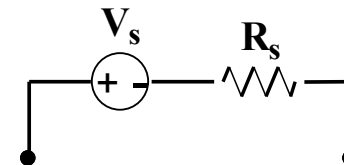



Active Elements - Sources

Current Source

➤ Ideal:

- Maintains constant current irrespective of the load connected
- Internal resistance $R_s = \infty$



Ideal Current Source (DC)

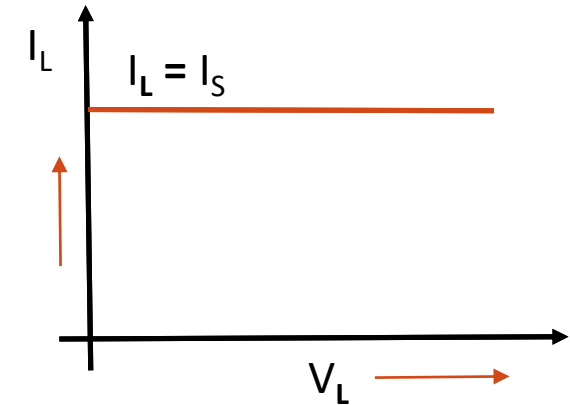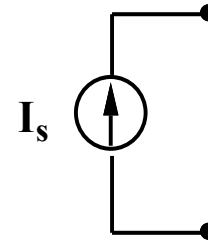

➤ Practical:

- Output current changes based on the connected load
- Internal resistance $R_s < \infty$

Practical Current Source

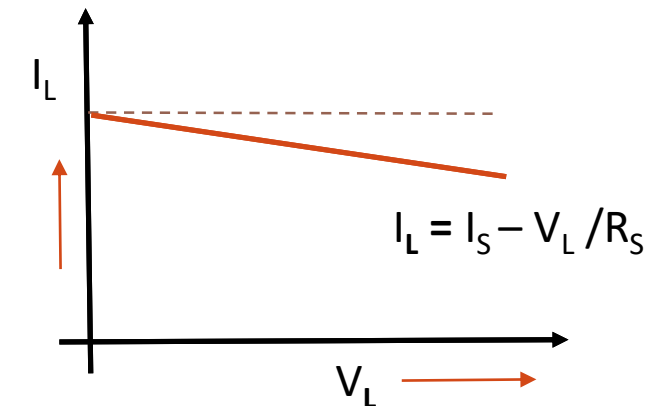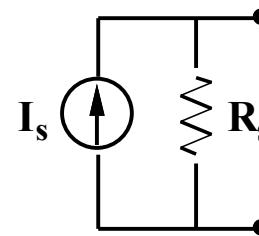

Resistor

Energy Consuming Element

Resistor




- **Passive electric device** that **dissipates energy**
- **Resistance:** property which opposes flow of current
 - Symbol: **R**
 - Unit: Ohms (Ω)
 - Power Consumed = $I^2 R$
- **Conductance**
 - Reciprocal of resistance
 - Symbol: **G**
 - Unit – Siemens (S)



Resistors




Series connection of Resistors

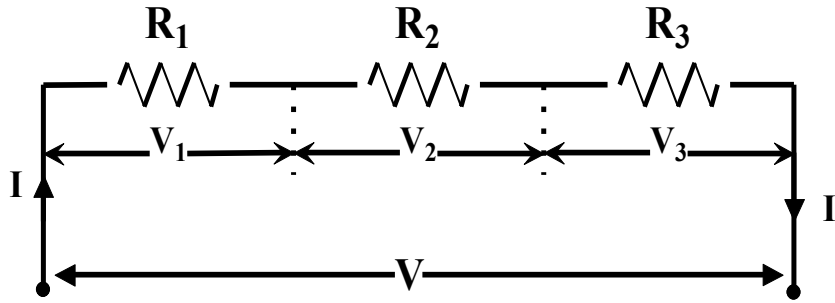

- Current (I) in all the resistors remains same
- $V = V_1 + V_2 + V_3$
- $R_{eq} = R_1 + R_2 + R_3$

Parallel connection of Resistors

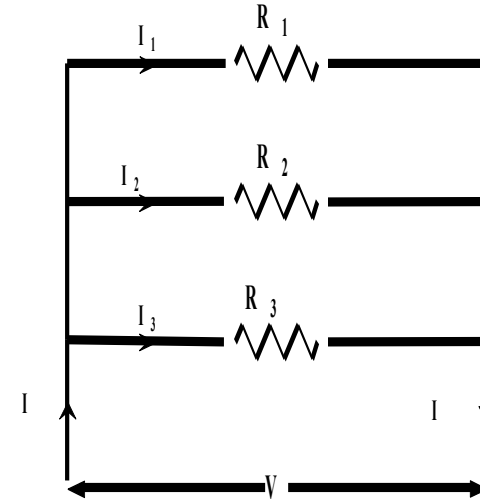


- Voltage (V) is same
- $I = I_1 + I_2 + I_3$
- $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

Resistors




Series Resistors

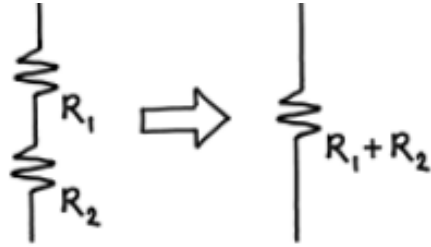


$$\text{Equivalent resistance} = R_1 + R_2$$

Voltage Divider

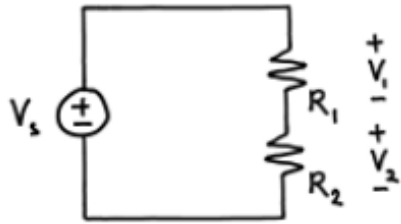


$$V_1 = \frac{R_1}{R_1 + R_2} V_s \quad V_2 = \frac{R_2}{R_1 + R_2} V_s$$

Parallel Resistors

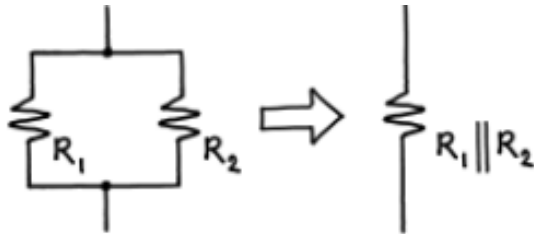

$$\text{Equivalent resistance} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


Current Divider

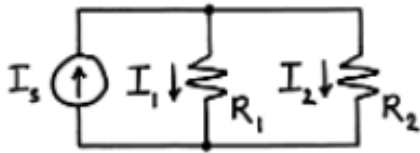

$$I_1 = \frac{R_2}{R_1 + R_2} I_s \quad I_2 = \frac{R_1}{R_1 + R_2} I_s$$

Delivering and absorbing power by a source

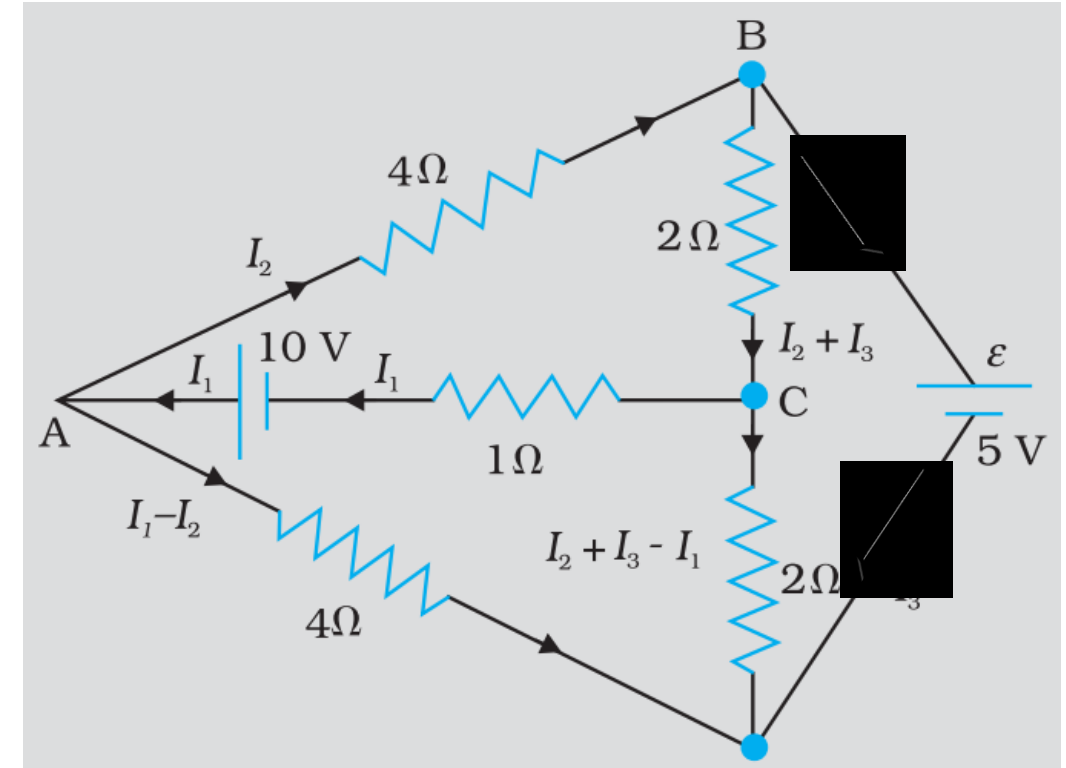- A battery is **discharging (delivering power/energy)** if,
 - Current **coming out from positive (+) terminal**
- A battery is **charging (absorbing power/energy)** if,
 - Current **flowing into positive (+) terminal**
- When current flows through a resistor,
 - Power is dissipated




10 V battery is **discharging**
 5V battery is **charging**


Illustration 1



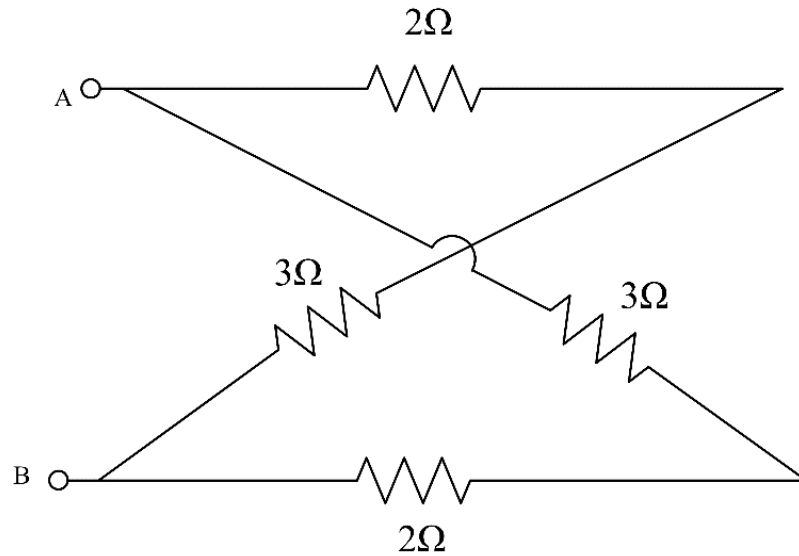Find the equivalent resistance of the networks given below.



Ans: 2.5 Ohms

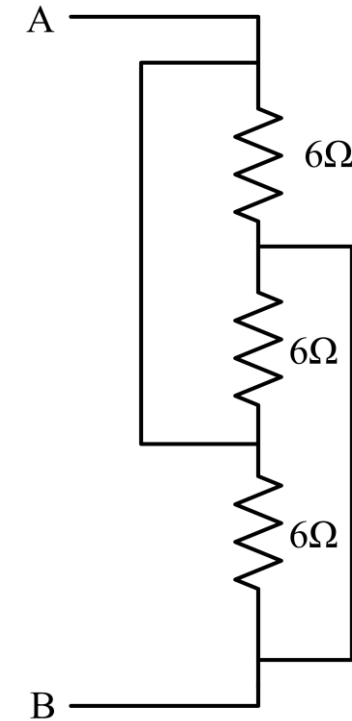


Ans: 2 Ohms

Illustration 2



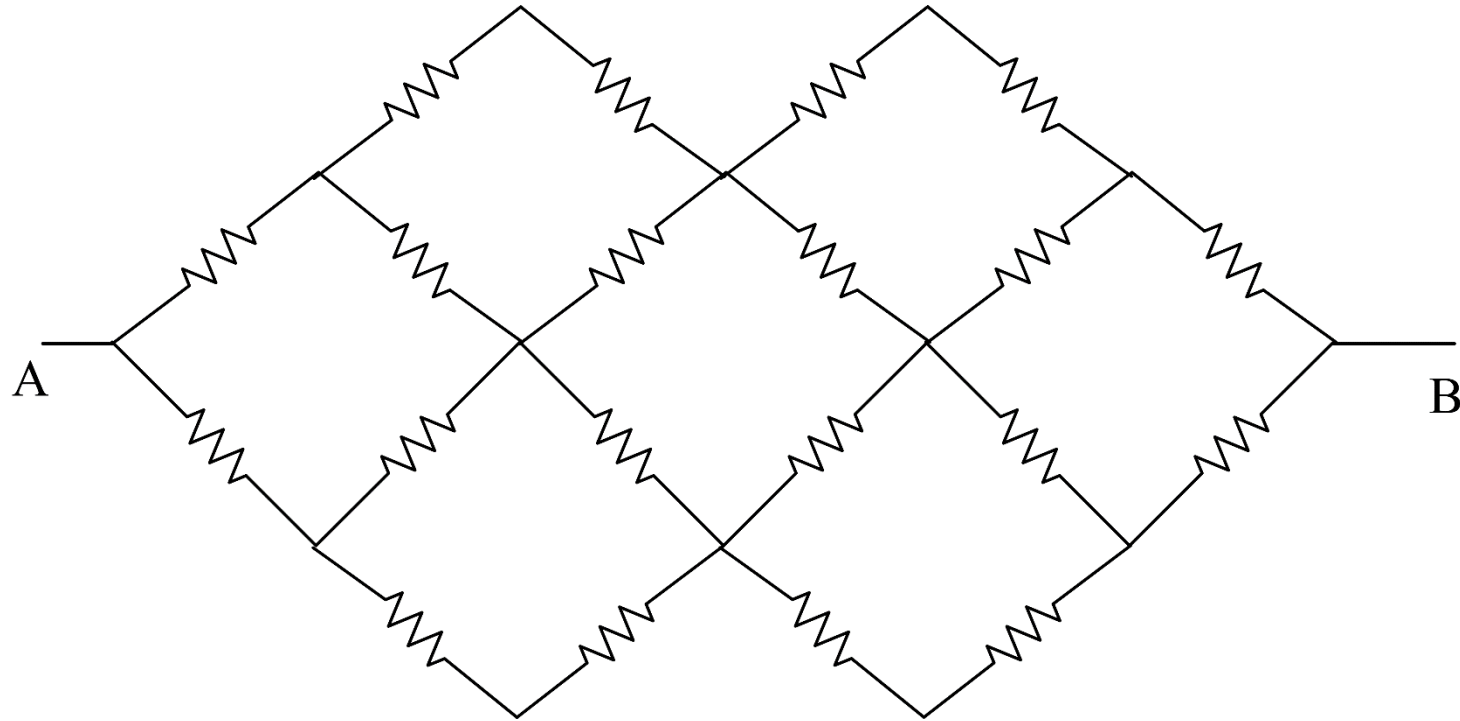Determine the equivalent resistance between the points A and B for the given resistive network with $1\ \Omega$ resistors




Ans: 2 Ohms


Illustration 3



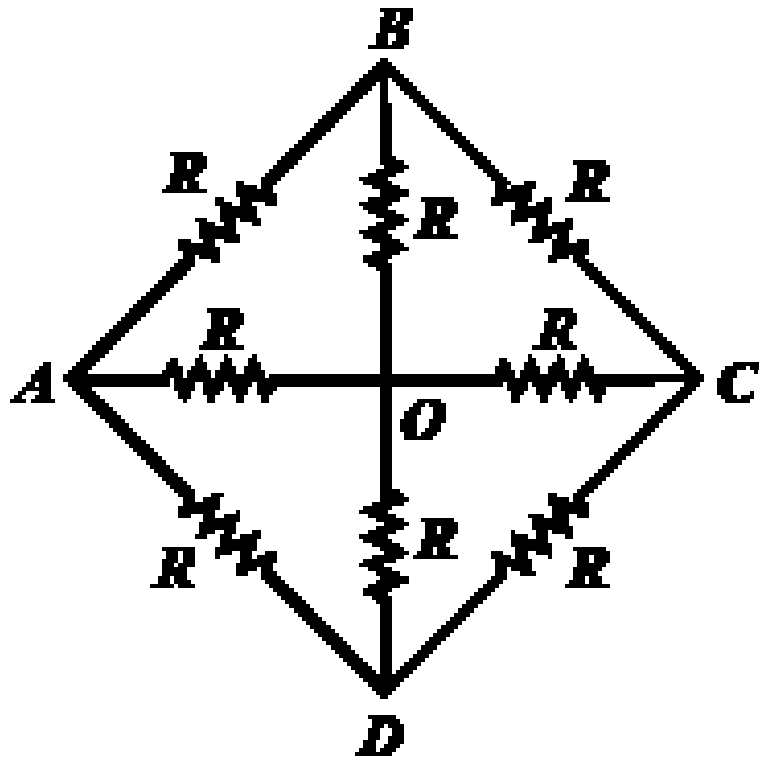Determine the equivalent resistance between the points **A & C** and **a & b**, respectively for the given resistive network. Each resistance is R Ohms.



Ans: $2R/3$ Ohms

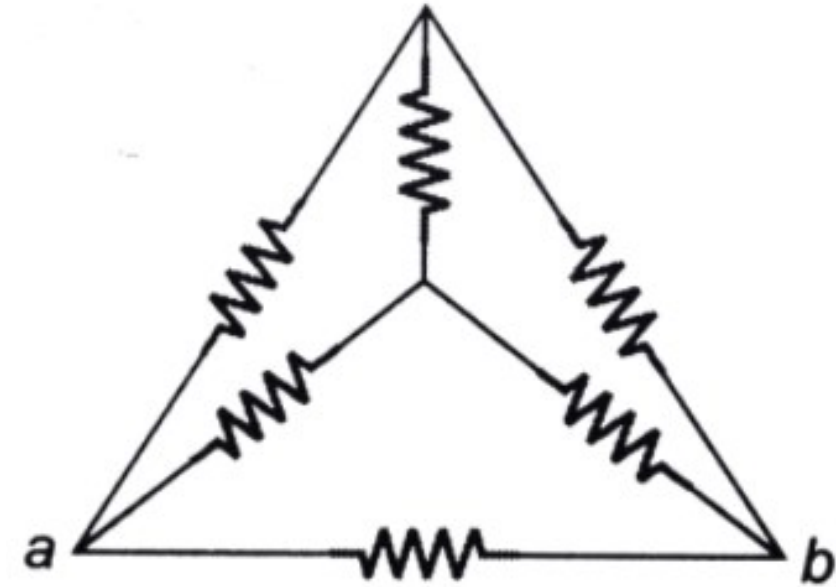

Ans: $R/2$ Ohms

Inductor

Energy Storing Element

Inductor

- **Passive** electric device that **stores energy in its magnetic field** when current flows through it
- A coil of wire wound on a core
 - Example: Air core Inductor, iron core inductor
- **Inductance**: property which opposes rate of change of current
 - Symbol: **L**
 - Unit: Henry (H)
- The voltage across inductor is proportional to the rate of change of current through it



$$v_L = L \frac{di}{dt}$$

Inductive Circuit

For a coil uniformly wound on a **non-magnetic core** of uniform cross section, self-inductance is given by

$$L = \frac{\mu_0 AN^2}{l}$$

where,

l = length of the magnetic circuit in meters

A = cross sectional area in square meters


μ_o = Permeability of air = $4\pi \times 10^{-7}$

N = *No. of turns in the coil*

Equivalent Inductance


Inductors in series

$$L_{eq} = L_1 + L_2 + \dots + L_n$$

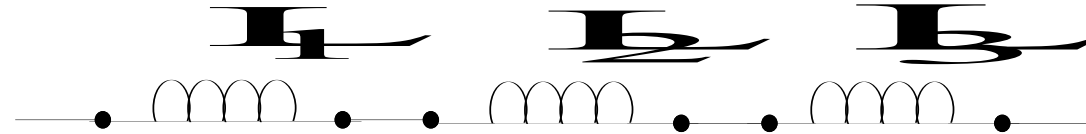

Inductors in Parallel
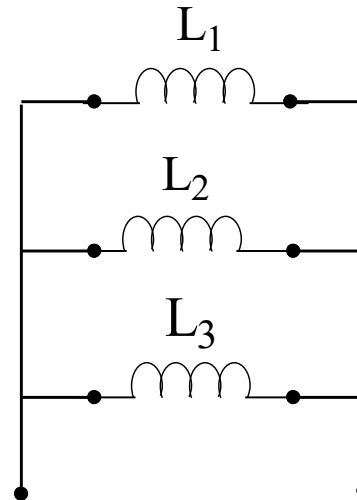
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$



Energy Stored in an Inductor

- Instantaneous power,

$$p = v_L \cdot i = L i \frac{di}{dt}$$

- Energy absorbed in ' dt ' time is

$$dw = L i di$$

- Energy absorbed by the magnetic field when current increases from **0** to **I** amperes, is

$$W = \int_0^I L i di = \frac{1}{2} L I^2$$

Capacitor

Energy Storing Element

Capacitors




- **Passive electric device** that **stores energy in the electric field** between a pair of closely spaced conductors
- **Capacitance:** Property which opposes the rate of change of voltage
 - Symbol: **C**
 - Unit: Farad (F)
- The capacitive current is proportional to the rate of change of voltage across it

$$i_c = C \frac{dv_c}{dt}$$

- Charge stored in a capacitor whose plates are maintained at constant voltage:

$$Q = CV$$

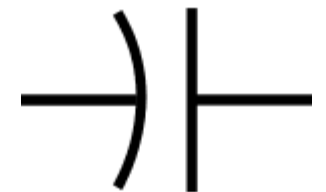

Terminologies



- Electric field strength,

$$E = \frac{V}{d} \text{ volts/m}$$

- Electric flux density,

$$D = \frac{Q}{A} \text{ C/m}^2$$


- Permittivity of free space,

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

- Relative permittivity, ϵ_r

- Capacitance of parallel plate capacitor

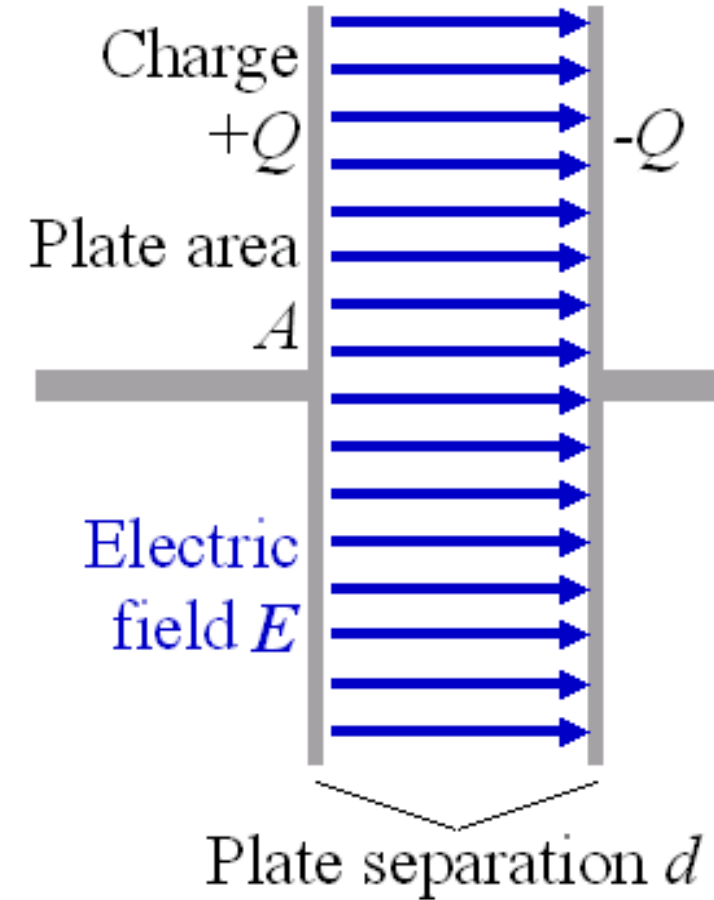
$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$



Equivalent Capacitance


Capacitors in Series
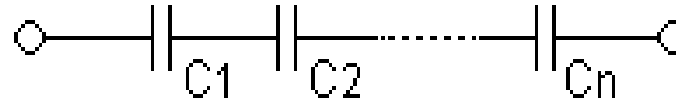
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$



Capacitors in Parallel

$$C_{eq} = C_1 + C_2 + \dots + C_n$$

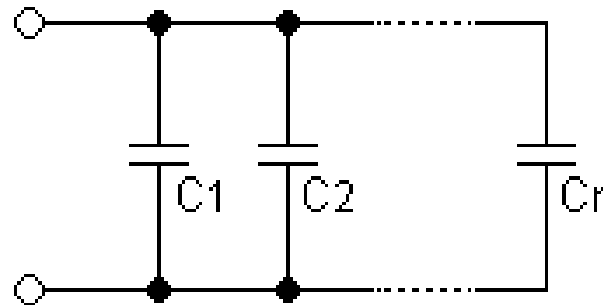

Energy stored in a Capacitor

- Instantaneous power

$$p = v_c \times i = C v_c \frac{dv_c}{dt}$$

- Energy supplied during ' dt ' time is:

$$dw = C v_c dv_c$$

- Energy stored in the electric field when potential rises from 0 to V volts is,

$$W = \int_0^V C v_c dv_c = \frac{1}{2} CV^2 \text{ Joules}$$



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)



Quiz Time


UNGRADED

An inductor and a resistor opposes _____ & _____ respectively

- a) flow of current, rate of change of current
- b) rate of change of current, flow of current**
- c) rate of change of current, rate of change of current
- d) flow of current, flow of current

The source voltage is ____

- a) 10 V
- b) 20 V
- c) 30 V
- d) 40 V

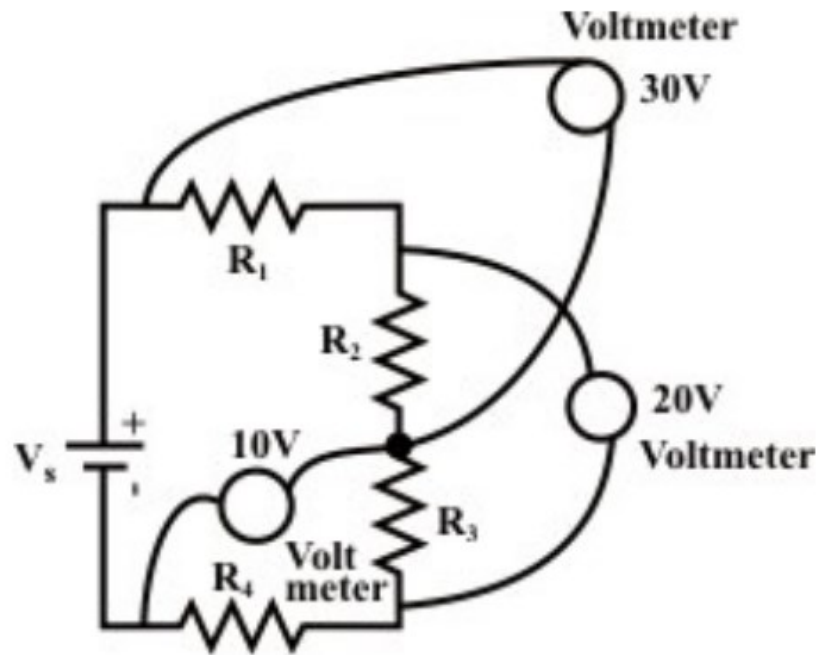

Two incandescent bulbs of 40 W and 60 W ratings are connected in series across the mains. Assuming the voltage rating of both the bulbs to be same, which of the following statement(s) is (are) correct?

- a) The bulbs together will consume 100 W
- b) The bulbs together will consume 50 W
- c) The 60 W bulb glows brighter
- d) **The 40 W bulb glows brighter**

Resistors in the following circuit are connected in

- a) Series
- b) **Parallel**
- c) Combination of series and parallel
- d) None of the above

