



Basic Electrical Technology

[ELE 105 I]

SINGLE PHASE AC CIRCUITS

L19 – Power in AC circuits




Topics covered...

- Impedance, phasor & Power Diagram
- Concept of power factor and its significance
- Need for power factor improvement

Power associated in RL load

For RL load:

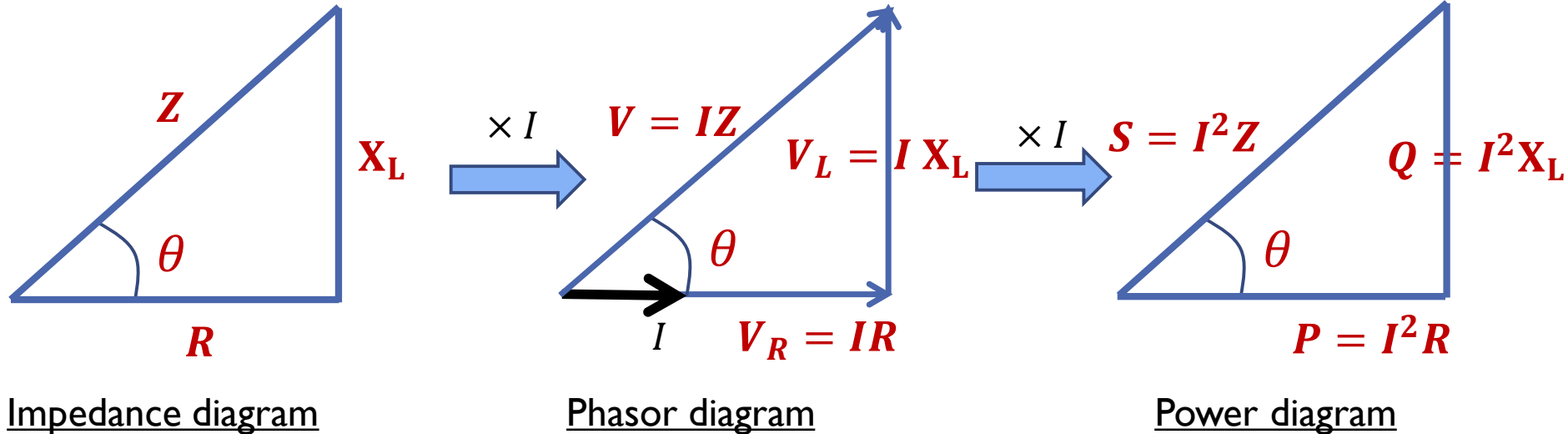

$$S = P + jQ$$

Where,

S = Apparent Power (VA)

P = Active Power (W)

Q = Reactive Power (var)

$$S = VI$$


$$P = VI \cos \phi$$

$$Q = VI \sin \phi$$



Power associated in RL load

For RC load:

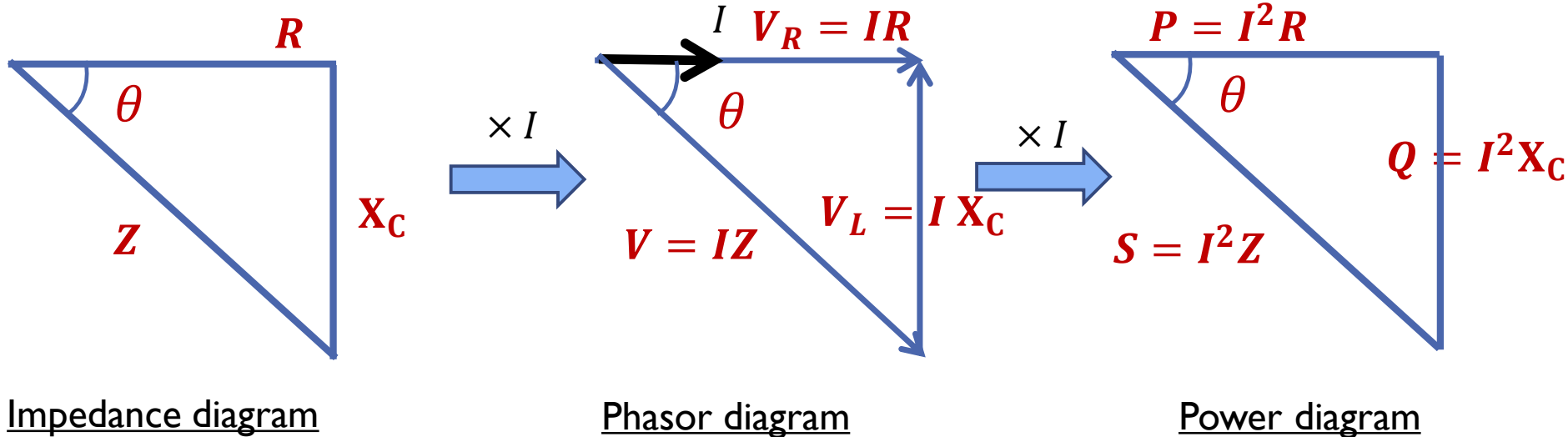

$$S = P - jQ$$

Where,

S = Apparent Power (VA)

P = Active Power (W)

Q = Reactive Power (var)

$$S = VI$$

$$P = VI \cos \phi$$

$$Q = VI \sin \phi$$



Power Factor

$$\text{Power Factor} = \frac{\text{Active Power } P \text{ in watts}}{\text{Apparent Power } S \text{ in voltamperes}}$$

$$\cos \theta = \frac{P}{S} = \frac{P}{VI}$$

- For an impedance Z ,

$$\cos \theta = \frac{IR}{V} = \frac{IR}{IZ} = \frac{\text{resistance}}{\text{impedance}}$$

- Power factor is *lagging* when the *current lags the supply voltage*
- Power factor is *leading* when the *current leads the supply voltage*
- For a resistive load, power factor is Unity



Disadvantages of Low Power Factor



- 1) Draws more reactive power
 - 2) For supplying a certain amount of active power (consumed), the apparent power to be supplied increased
 - 3) Cost of supply increases
 - 4) Voltage drop occurs in the vicinity of consumer
- Increased transmission losses
 - Hence bulk consumers are advised to maintain the power factor close to unity by power utilities.

Remedial Measures

- Most of the industrial loads are inductive in nature
- Reactive power demand of Inductive loads can be compensated with capacitive loads
- Hence it is possible to localise reactive power requirement by connecting parallel capacitors across the load

Power Triangle

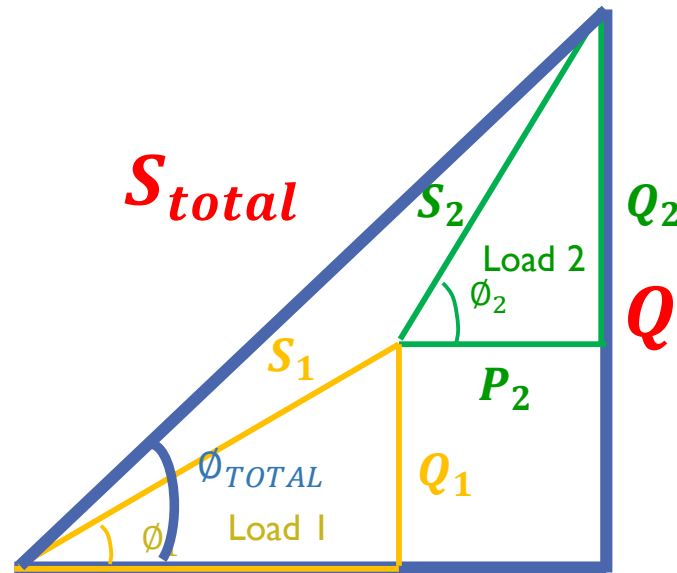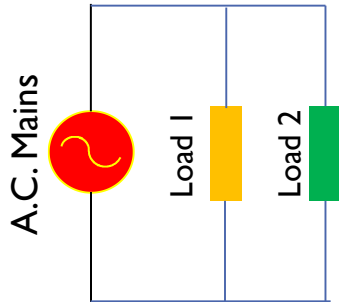- Practically, loads are in connected parallel
- Majority of the loads are inductive in nature




$$Q_{total} = Q_1 + Q_2$$

$$P_{total} = P_1 + P_2$$

$$S_{total} = P_{total} + jQ_{total}$$

Power Factor Improvement

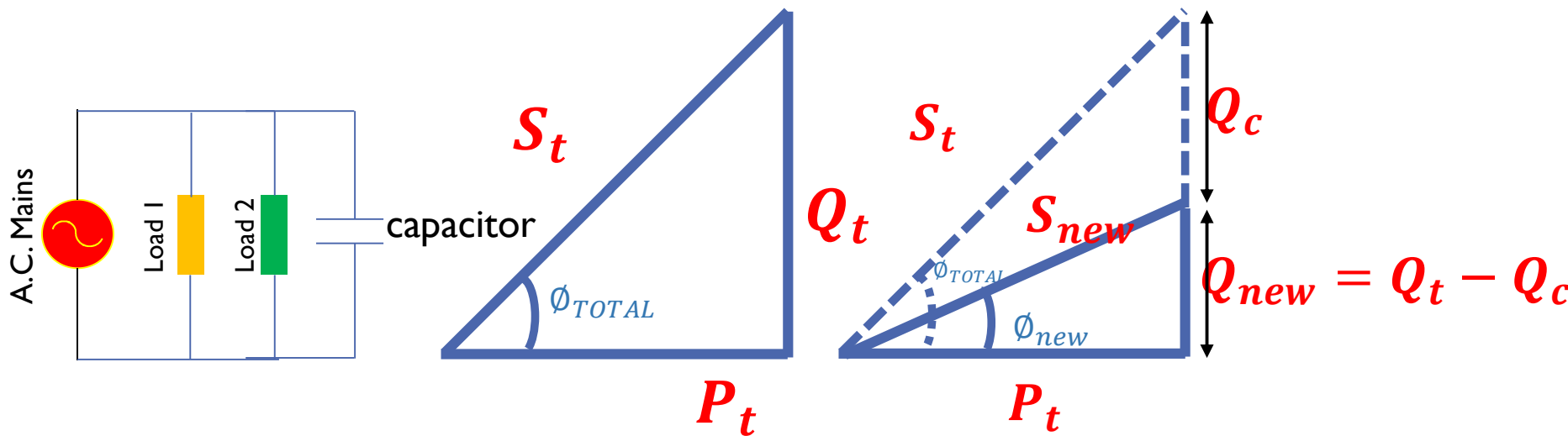- Connect capacitor parallel to the load
- Energy stored by the capacitor provides the required reactive power by the load



Calculation of capacitor value

- Calculate Q_c needed to improve power factor to $\cos\phi_{new}$
- Calculate $X_c = \frac{V^2}{Q_c}$ & $c = \frac{X_c}{2\pi f}$

Power Factor Improvement

Since most of the loads are inductive in nature, a capacitor connected in parallel to the inductive load improves the power factor

Determination of Capacitor Value:

- ϕ_T is the over all power angle
- ϕ_F is the final power angle after connecting the capacitor across the load
- $S_T = P_T / \cos \phi_T$ & $S_F = P_T / \cos \phi_F$
- $Q_T = (P_T / \cos \phi_T) * \sin \phi_T$
- $Q_F = (P_T / \cos \phi_F) * \sin \phi_F$
- $Q_C = (Q_T - Q_F) = P_T (\tan \phi_T - \tan \phi_F)$
- $X_C = V^2 / Q_C$


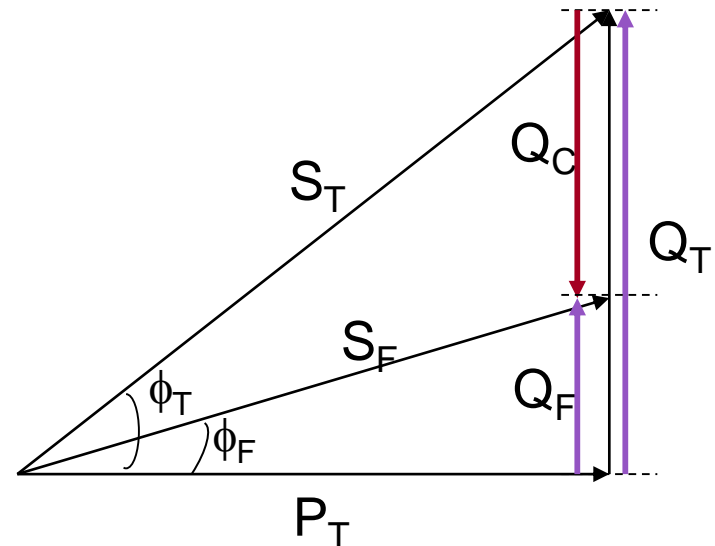


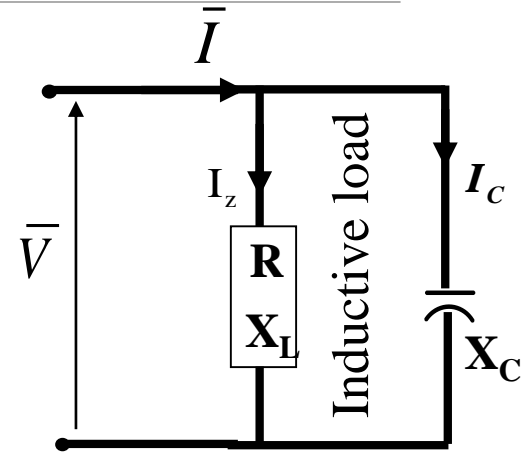

Illustration I

A single-phase motor takes **8.3 A** at a power factor of **0.866 lagging** when connected to a **230 V, 50 Hz supply**. Capacitance bank is now connected in parallel with the motor to raise the power factor to **unity**. Determine the capacitance value

Ans: 57.4 μF



Illustration 2


A single-phase load of **5 kW** operates at a power factor of **0.6 lagging**. It is proposed to improve this power factor to **0.95 lagging** by connecting a capacitor across the load. Calculate the kvar rating of the capacitor

Ans: 5.02 kvar




Summary

Impedance diagram

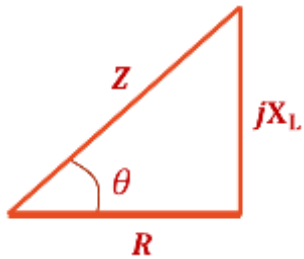


RL Load

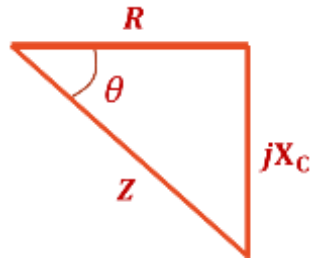


RC Load

Power diagram

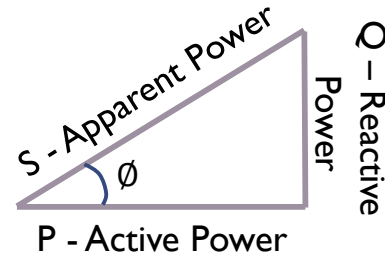

RL Load

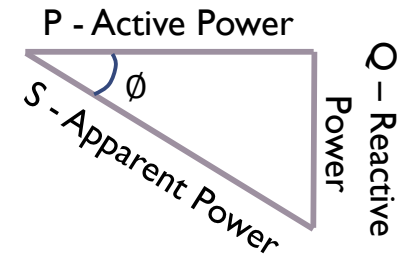

RC Load

- Power in AC circuit is given by, $S = VI$
- For any load with impedance Z ,
 - Active Power (watt), $P = VI \cos \theta = I^2 Z \cos \theta = I^2 R$
 - Reactive Power (var), $Q = VI \sin \theta = I^2 Z \sin \theta = I^2 X$
 - Apparent Power (VA), $S = VI = I^2 Z$
- $\text{Power Factor} = \frac{\text{Active Power}}{\text{Apparent Power}} = \frac{P}{S} = \frac{R}{Z} = \cos \theta$



Summary

- Low power factor loads must be avoided

- Capacitor bank connected parallel to the load serves as the source of reactive power for the load
 - Improves load power factor
 - Reduces transmission and distribution losses