

## Department of Information & Communication Technology

(Manipal Institute of Technology, Manipal 576104.)

Subject: Digital Systems ICT – 2102

3<sup>rd</sup> Sem . B.Tech Information Technology

Date: 18/08/2015

Assignment – 1

1. Simplify the logical expressions  $F(A,B,C,D) = \sum M(0,1,2,4,5,6,7,8,9) + d(10,12,15)$  using K-Map and implement using (i) NOR gates only. (ii) NAND gates only
2. Simplify the logical expressions  $F(A,B,C,D) = \prod m(1,5,10,14) + d(0,4,9,11,13)$  using K-Map and implement using (i) NOR gates only. (ii) NAND gates only.
3. Using K-map, find the simplest **sum** of products form for the function  $F(V,W,X,Y,Z) = \sum m(0,1,2,3,6,7,11,15,16) + D(17,19,23,27,31)$  and implement using NOR gates only.
4. Using K-map, find the simplest sum of products form for the function  $F(V,W,X,Y,Z) = \prod M(0,1,2,3,6,7,11,15,16) \cdot D(17,19,23,27,31)$  and implement using NAND gates only.
5. Write the (i) simplified SOP & POS and  
(ii) Sum of minterms and product of maxterms logical expressions for the circuit given below

