



Basic Electrical Technology

Source Transformation & Star-Delta Transformation



Source Transformation


**Practical
Voltage
Source**




**Practical
Current
Source**

Source Transformation

Practical Voltage source

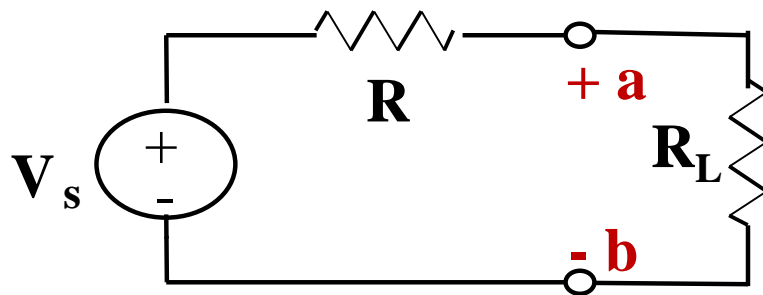


Practical Current source

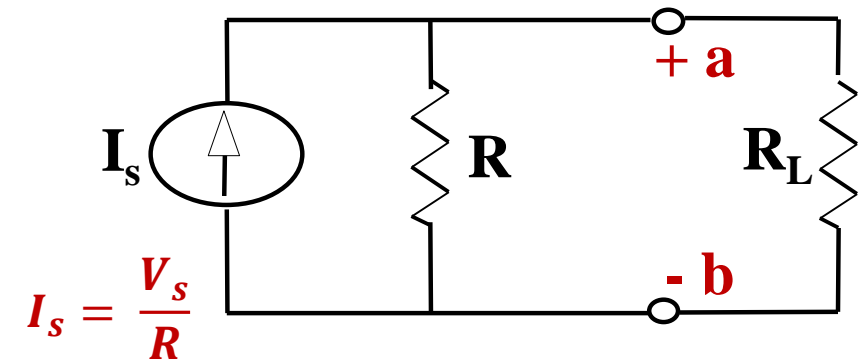

Source Transformation


Practical Voltage source

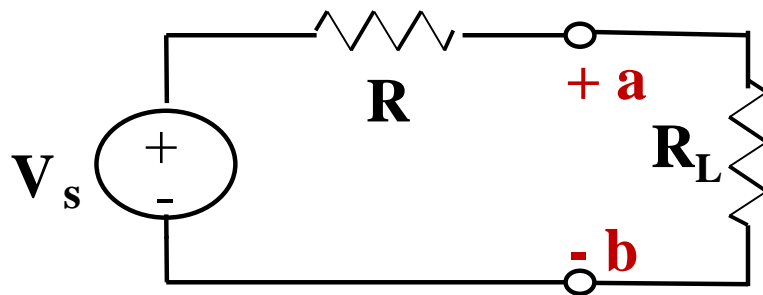


$$V_s = R \times I_s$$




Practical Current source

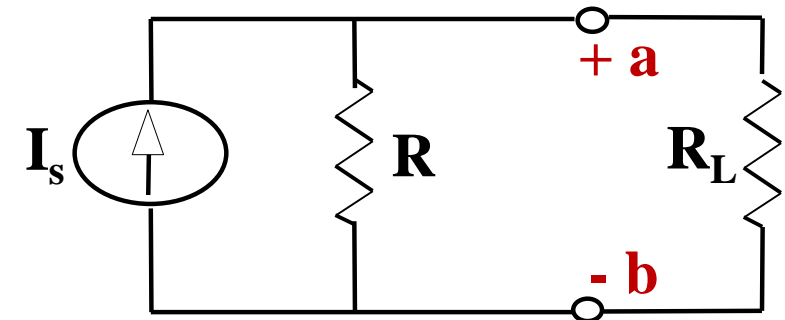

Star & Delta Connections

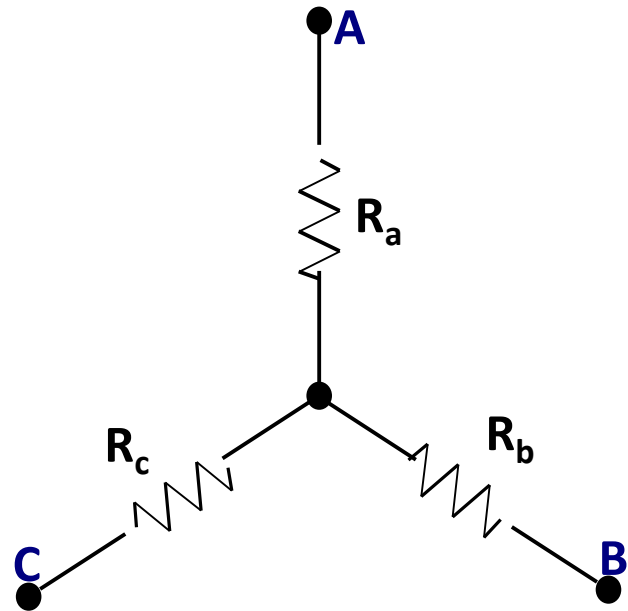



Star Connection

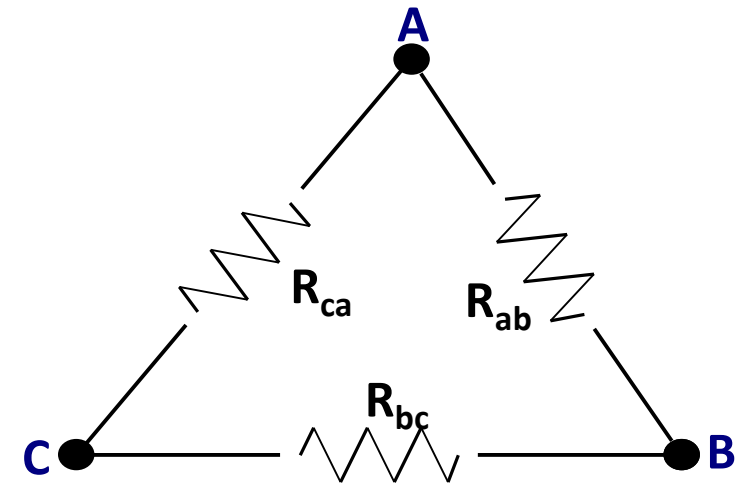

Delta Connection

Star-Delta Transformation

Delta to Star Transformation

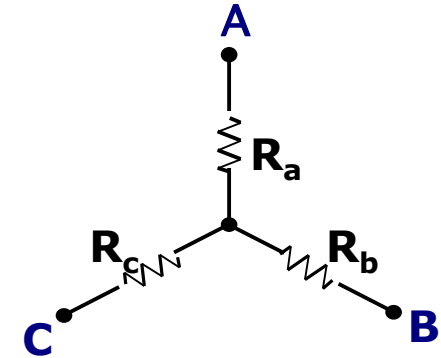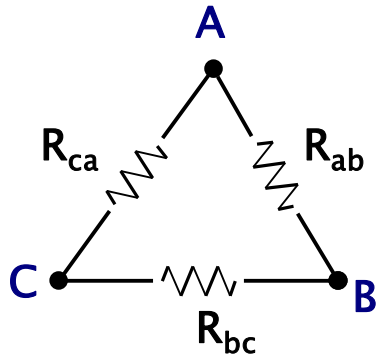



$$R_a = \frac{R_{ab} R_{ca}}{R_{ab} + R_{bc} + R_{ca}} = \frac{R_{ab} R_{ca}}{\sum R_{ab}}$$

$$R_b = \frac{R_{bc} R_{ab}}{R_{ab} + R_{bc} + R_{ca}} = \frac{R_{bc} R_{ab}}{\sum R_{ab}}$$

$$R_c = \frac{R_{ca} R_{bc}}{R_{ab} + R_{bc} + R_{ca}} = \frac{R_{ca} R_{bc}}{\sum R_{ab}}$$

Star-Delta Transformation

Star to Delta Transformation

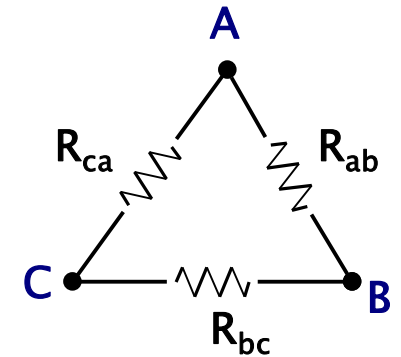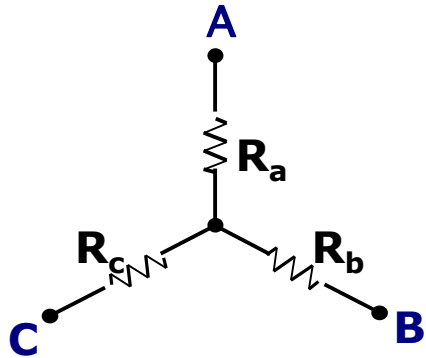


$$R_{ab} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c} = \frac{\sum R_a R_b}{R_c}$$

$$R_{bc} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a} = \frac{\sum R_b R_c}{R_a}$$

$$R_{ca} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b} = \frac{\sum R_c R_a}{R_b}$$

Illustration 1

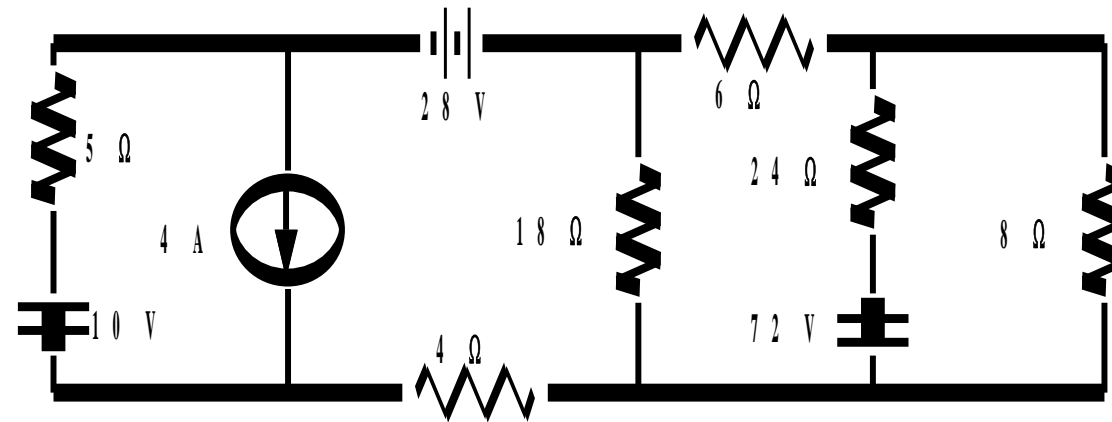
Find the current through $8\ \Omega$ resistor by source transformation method.



Ans: 1 A

Illustration 2

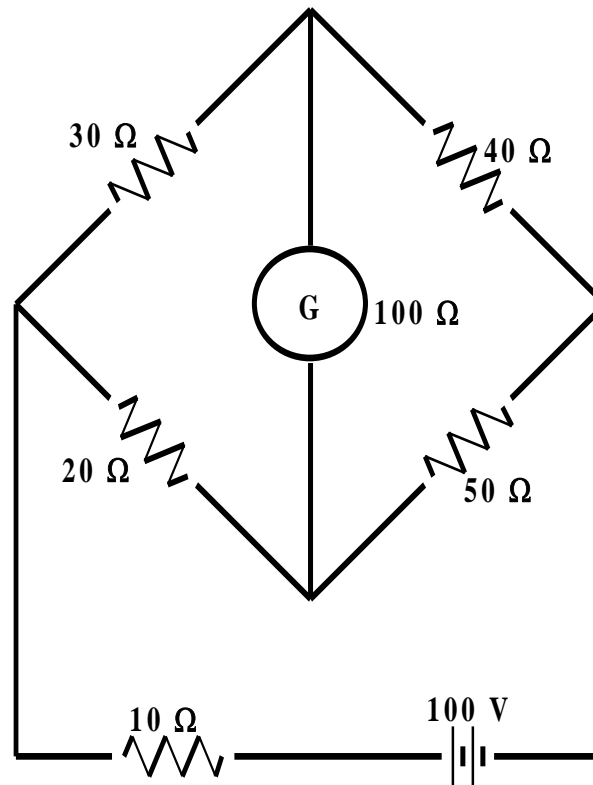For the circuit shown, determine the total power supplied by the source using star-delta transformation




Ans: $P_{\text{supplied}} = 223.12 \text{ W}$



Illustration 3

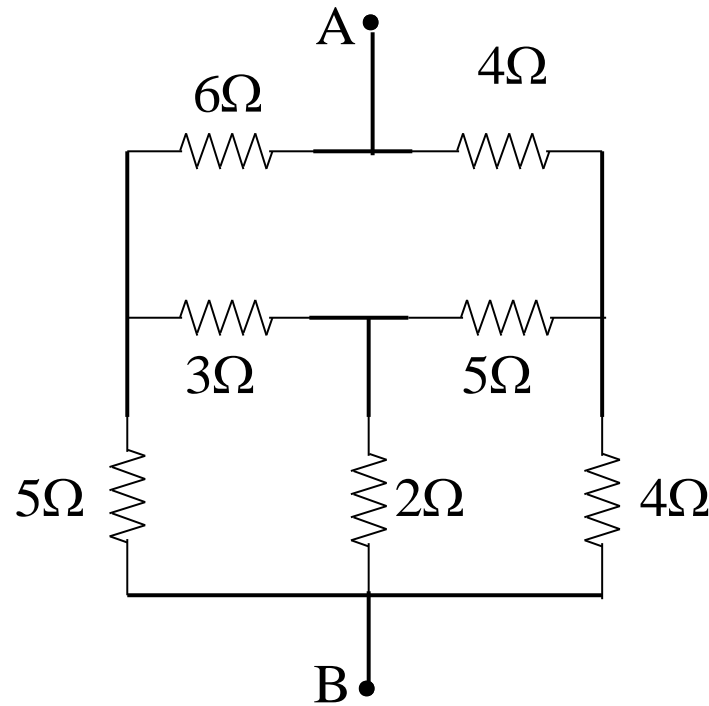Determine the equivalent resistance between the terminals A and B.




Ans: 3.85 Ω



Homework 1

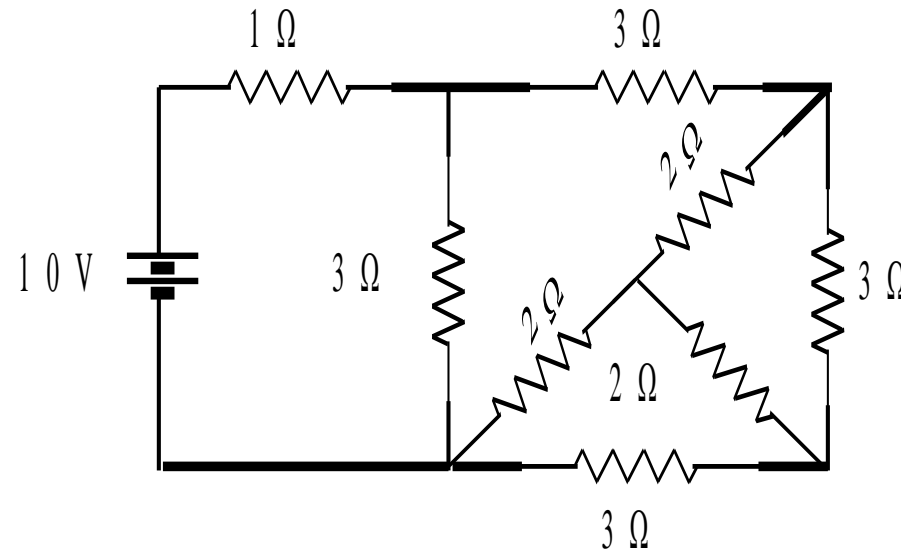Find the power dissipated in 1Ω resistor and the power delivered by $10V$ source using network reduction technique



Ans: $P_{1\Omega} = 11.65 \text{ W}$, $P_{10V} = 34.2 \text{ W}$