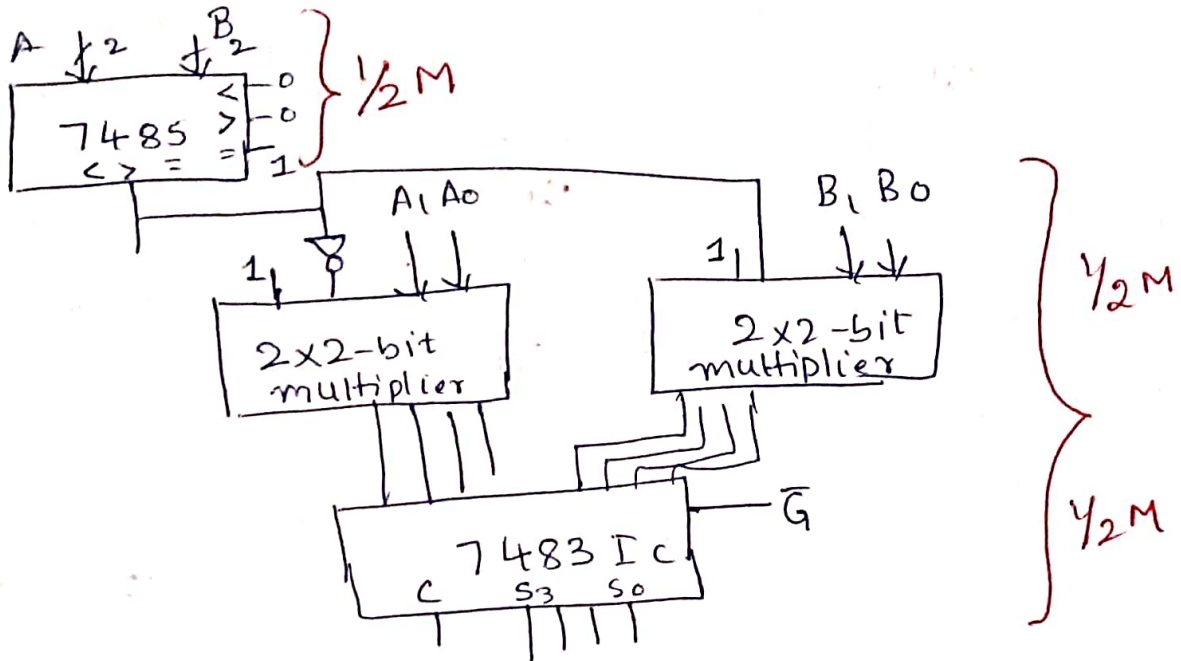


91. If $A > B$, $F = 2A + 3B$

else



$$F = 3A - 2B$$

A & B are 2-bit binary numbers.



$$\begin{aligned} 2 &= 10 \\ 3 &= 11 \end{aligned}$$

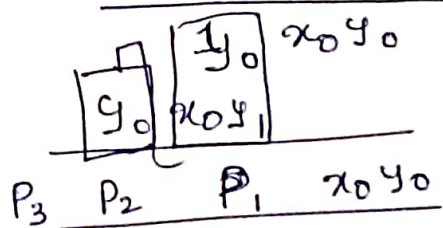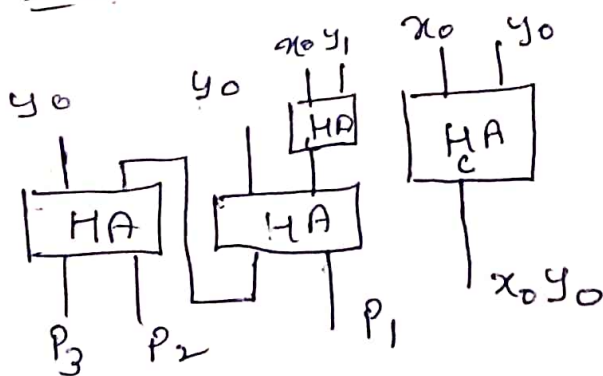2x2-bit multiplier: $x_1x_0 \times y_1y_0$



HA as AND gate: $\frac{1}{2}M$.
 Multiplier design using HAs } $1M$