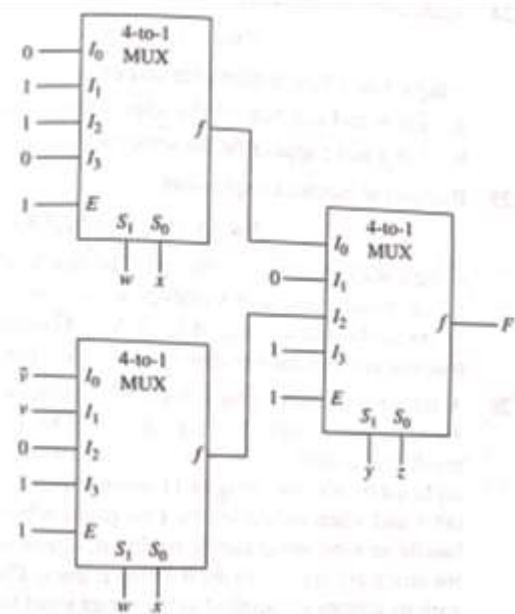


ICT 2154 Digital Systems / ICT 2171 Digital Systems and Computer Organization

Note: Students are required to submit handwritten assignment in A4 Sheet on or before 2pm,

5th November 2022. Design should use minimum number of components/gates

Q. No.	Questions									
1.	Design 2 – bit X 2 – bit binary multiplier using 74138ICs and minimum universal gates.									
2.	Design 2 – bit magnitude comparator using active high output decoders and minimum universal gates.									
3.	Implement the function $F = (A'BD + AB'C' + A)$ using decoders and minimum external gates.									
4.	Design a 3-bit subtractor using 74153 ICs and external gates									
5.	Write the function (minterms) realized using following circuit. <div></div>									
6.	Design a BCD adder to add two single digit decimal numbers represented in excess-3 code. The result should also be in excess-3 code form.									
7.	Design a code converter that converts a decimal digit from 8 4 –2 –1 code to BCD.									
8.	Using truth table and K-maps design the BCD to seven segment decoder using minimum number of gates. The six invalid combinations should result in a blank display.									
9.	Design a XY flip flop using NAND latch and EXTERNAL gates according to the truth table given below. <table><tr><th>X</th><th>Y</th><th>OUTPUT</th></tr><tr><td>0</td><td>0</td><td>toggle</td></tr><tr><td>0</td><td>1</td><td>set</td></tr></table>	X	Y	OUTPUT	0	0	toggle	0	1	set
X	Y	OUTPUT								
0	0	toggle								
0	1	set								

	1	0	reset	
	1	1	Same as previous output	
10	Convert the SR flip flop to XY flip flop. Truth table of XY flip flop is given in question 9.			