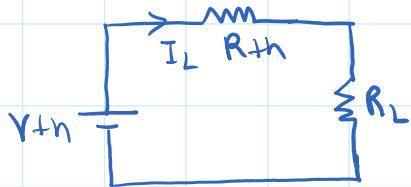


# Network Theorems ✓

Tuesday, November 23, 2021 9:36 PM

prove  
 $R_{th} = R_L$



$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$\begin{aligned} P &= I_L^2 R_L \\ &= \frac{V_{th}^2 \times R_L}{(R_{th} + R_L)^2} \end{aligned}$$

$$\frac{dP}{dR_L} = V_{th}^2 \left( \frac{(R_{th} + R_L)^2 - 2(R_{th} + R_L)R_L}{(R_{th} + R_L)^4} \right)$$


$$\frac{dP}{dR_L} = 0$$

$$(R_{th} + R_L)^2 - 2(R_{th} + R_L)R_L$$

$$R_{th}^2 + R_L^2 + 2R_{th}R_L - 2R_{th}R_L - 2R_L^2$$

$$R_{th}^2 = R_L^2$$

\*  
 $R_L = R_{th}$

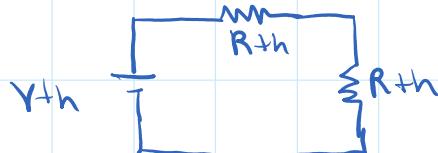

$$I = \frac{V_{th}}{2R_{th}}$$


$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

$P_{max} = \frac{V_{th}^2}{4R_{th}}$

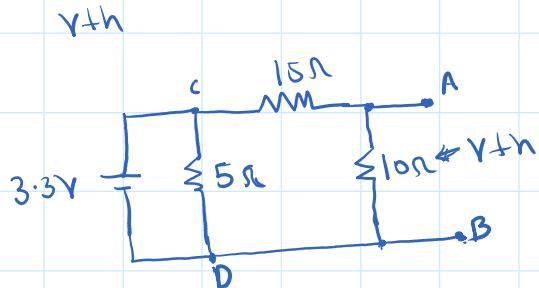
## Illustration 1

Tuesday, November 16, 2021 3:40 PM


Using Thevenin's theorem, find the value of  $R$  such that the current through it is 120 mA


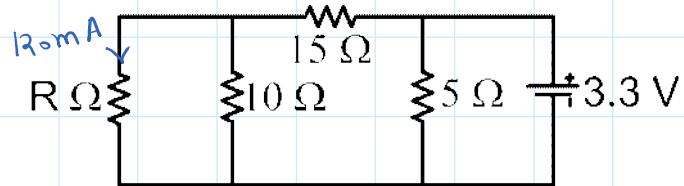
$$V_{th} = \frac{3.3 \times 10}{10 + 15} = 1.32V$$


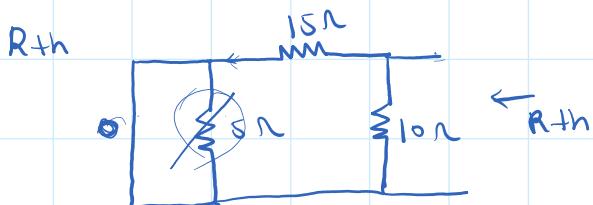
$$R_{eq} = \frac{0 \times 5}{0 + 5} = 0$$



$$R_{th} = \frac{10 \times 15}{10 + 15} = 6\Omega$$






$$\begin{aligned} I &= \frac{V_{th}}{R_{th} + R} \\ 120 \times 10^{-3} &= \frac{1.32}{6 + R} \\ R &= 5\Omega \end{aligned}$$
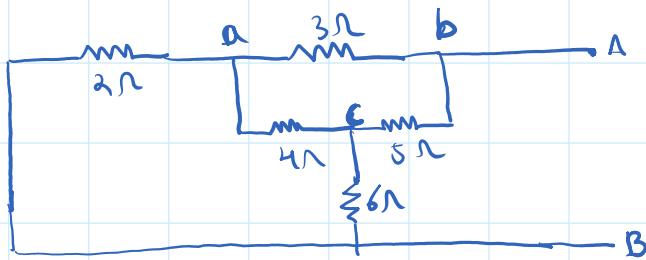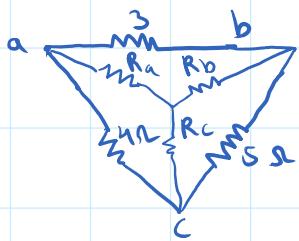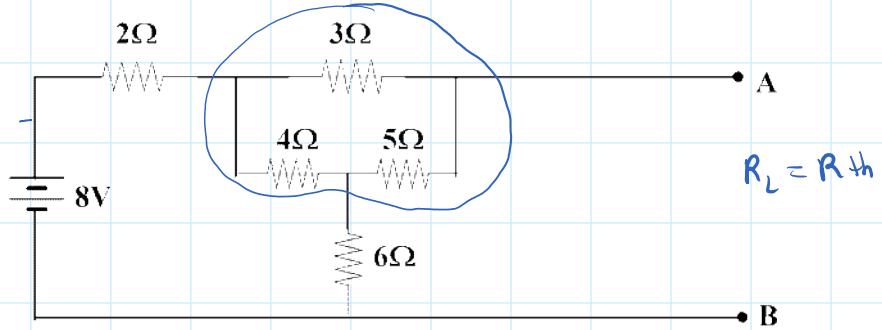
## Illustration 2

Tuesday, November 16, 2021 3:41 PM



Determine the value of resistor to be connected across the terminals A & B such that maximum power is transferred to that resistor. Also, find the value of maximum power.



$$R_a = \frac{3 \times 4}{3+4+5} = 1$$


$$R_b = \frac{3 \times 5}{3+5+4} = 1.25$$
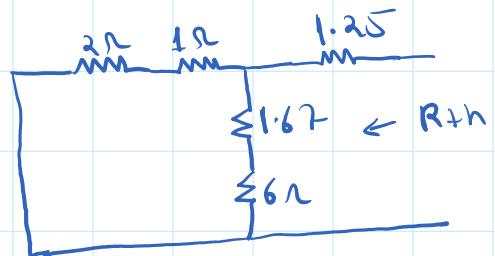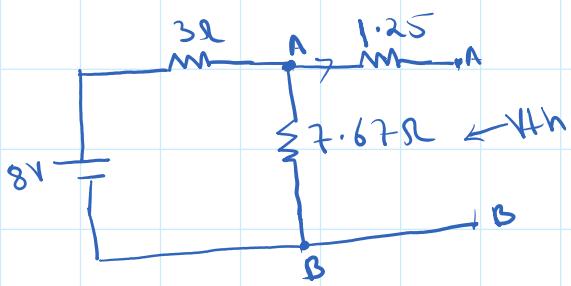
$$R_c = \frac{4 \times 5}{3+5+4} = 1.67$$



$$V_{th} = \frac{8 \times 7.67}{10.67} = 5.75V$$
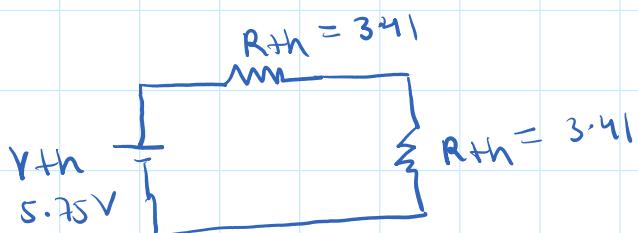
$$R_{th} = \frac{3 \times 7.67}{10.67} + 1.25 \\ = 3.41\Omega$$




$$P_{max} = \frac{V^2}{4R + h} = \frac{(5.75)^2}{4 \times 3.41} = 2.43W$$

### Illustration 3

Tuesday, November 16, 2021

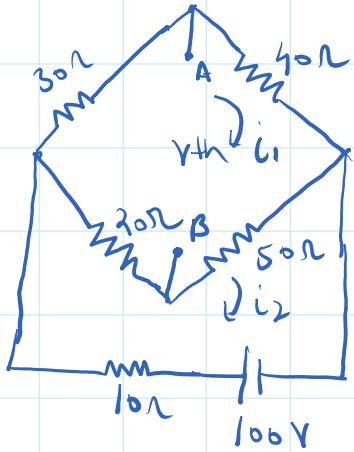3:40 PM

Determine the current through the galvanometer using Thevenin's Theorem



$$V_{th} = V_{AB}$$

$$V_A - 40i_1 - 50(i_1 - i_2) = V_B$$

$$V_A - V_B = V_{th} = 40i_1 + 50(i_1 - i_2)$$

$$V_{th} = -\frac{100}{9} V$$

$$100 - 10i_2 - 20(i_2 - i_1) - 50(i_2 - i_1) = 0$$



$$-70i_1 + 80i_2 = 100 \quad \text{--- (1)}$$

$$-30i_1 - 40i_1 - 50(i_1 - i_2) - 20(i_1 - i_2) = 0$$

$$140i_1 - 70i_2 = 0 \quad \text{--- (2)}$$

$$i_1 = \frac{10}{9}$$


$$i_2 = \frac{20}{9}$$

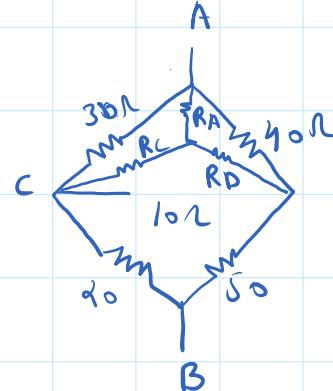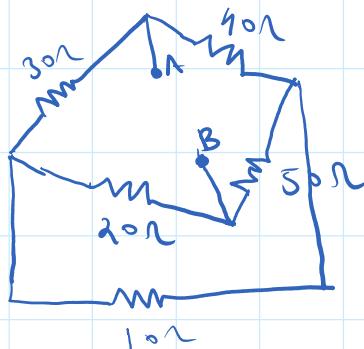

$$R_A = 15$$

$$R_C = \frac{15}{4}$$

$$R_D = 5$$

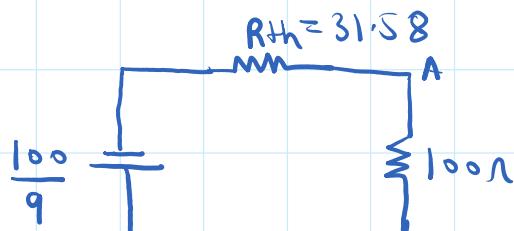



$$R_{th} = 31.58$$

$$I = \frac{100/9}{31.58 + 100} = 84.44 \text{ mA}$$

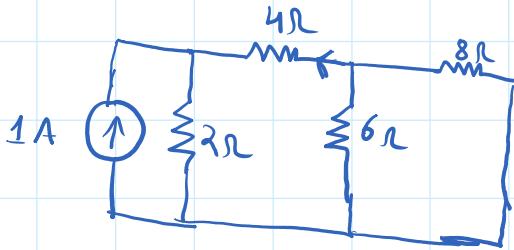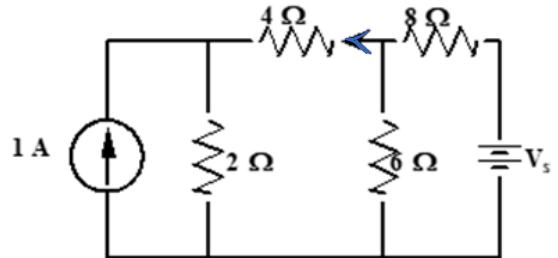
## Question 1

Tuesday, November 23, 2021 10:00 PM


- Using Superposition theorem, find the value of  $V_s$  if the current in  $4\Omega$  is  $0.515 \text{ A}$  and the direction is as shown in the diagram below.




$$R = \frac{8 \times 6}{14} \Omega$$

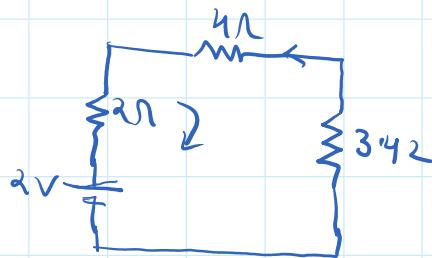

$$I = \frac{2}{9.42} = 0.212$$

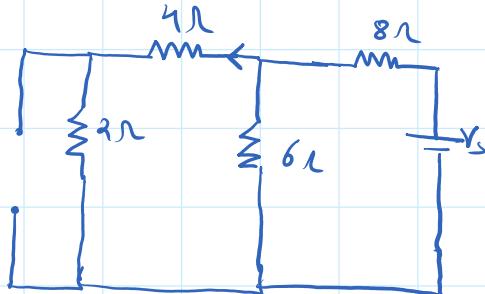

$$I_{4\Omega} = -0.212$$

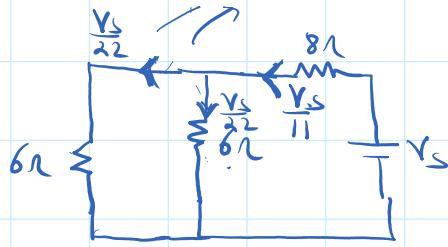

$$I = I_{4\Omega} + I_{4\Omega}$$

$$0.515 = -0.212 + \frac{V_s}{22}$$

$$\boxed{V_s = 16 \text{ V}}$$

$$I = \frac{V_s}{8+3} \quad I = \frac{V_s}{11}$$






$$I_{4\Omega} = \frac{V_s}{22}$$

$$\boxed{V_s = 16 \text{ V}}$$
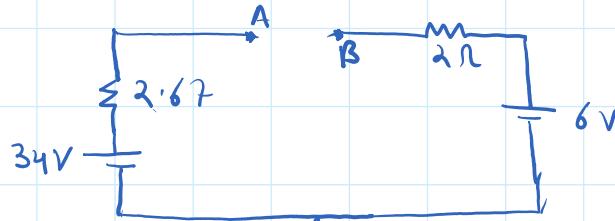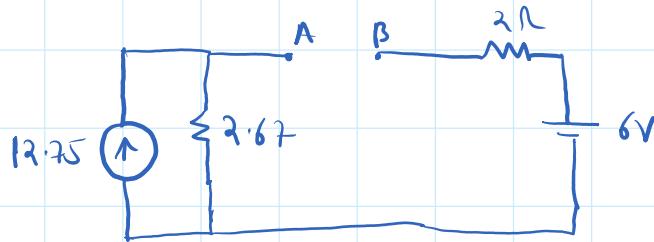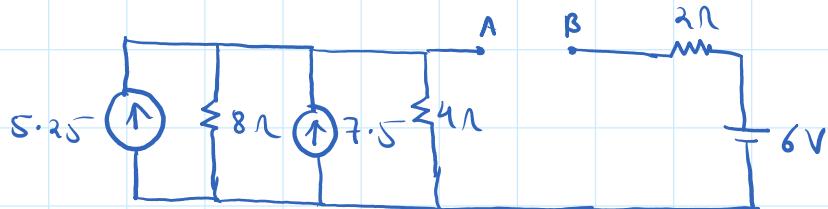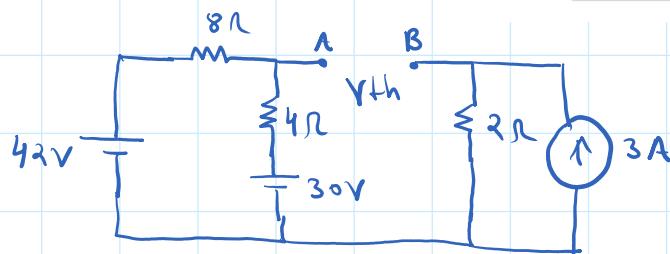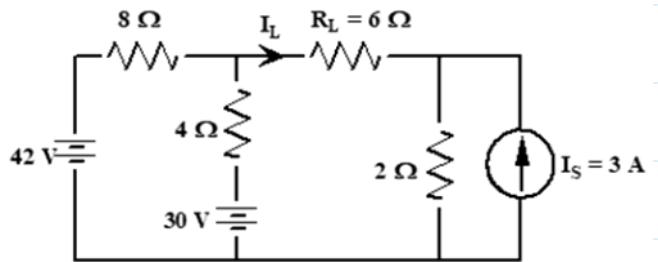
## Question 2


Tuesday, November 23, 2021 10:00 PM

- For the circuit shown find the current  $I_L$  through  $6\Omega$  resistor using Thevenin's theorem



$$V_{AB} = 34 - 6 \\ = 28V$$

$$R_{th} = 4.67$$





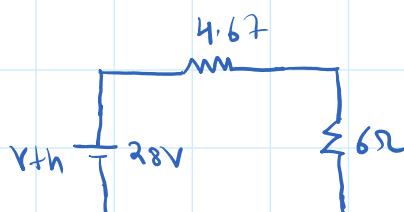


$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{28}{10.67} \\ = 2.624A$$
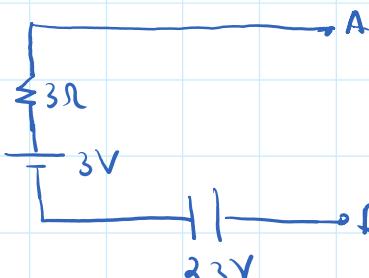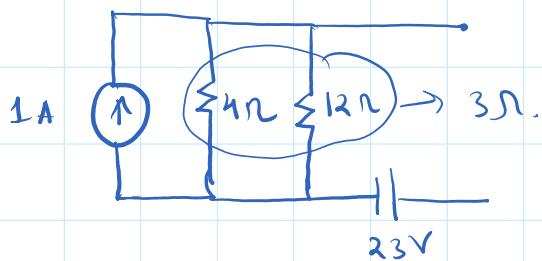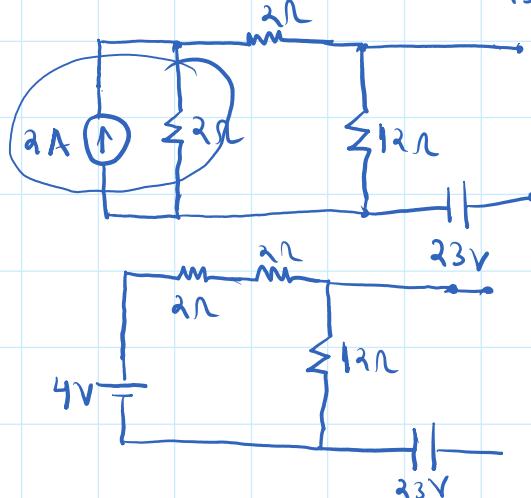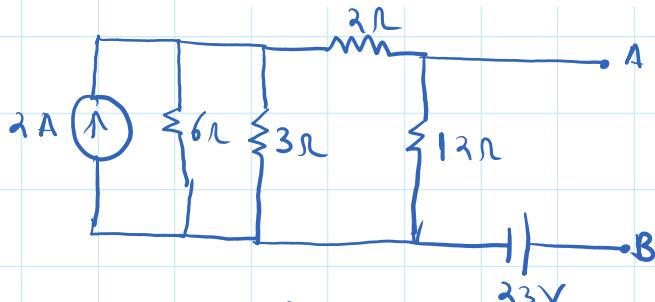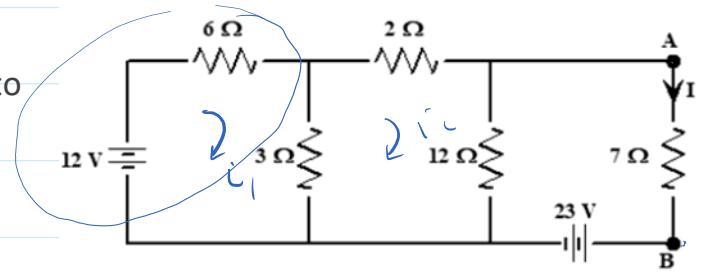
### Question 3

Tuesday, November 23, 2021 10:00 PM

- In the figure shown below replace the network to the left of terminals A & B by its Thevenin's equivalent circuit. Hence, determine I



$$V_{AB} = -20V$$

$$R_h = 3\Omega$$



$$I = -3A$$

$$V_{th} = \frac{1}{20\Omega} \times 7$$

$$I = \frac{-20}{10}$$


$$\boxed{I = -2A}$$

#### Question 4

Tuesday, November 23, 2021 10:00 PM

- The box shown in the adjacent figure consists of independent dc sources and resistances. Measurements are taken by connecting an ammeter in series with the resistor  $R_L$  and the results are shown in the table below. Find the value of  $R_L$  for which the current is 0.6 A

$R_L$	I
10Ω	2.0A
20Ω	1.5A
?	0.6A

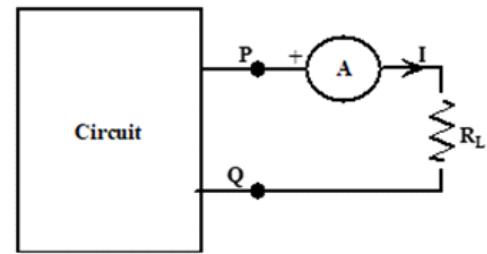

## Question 5

Tuesday, November 23, 2021 10:04 PM

Find the value of  $R$  such that maximum power is transferred to  $8\Omega$  resistor

