





# Binary adders and subtractors

- Half adder, full adder, parallel adder
- Half subtractor , full subtractor, parallel subtractor
- Subtraction using complements, parallel adder/subtractor
- Carry Look ahead adder, Decimal adder

# Binary Addition


## Arithmetic Operation

Example: Addition of two 4-bit Numbers

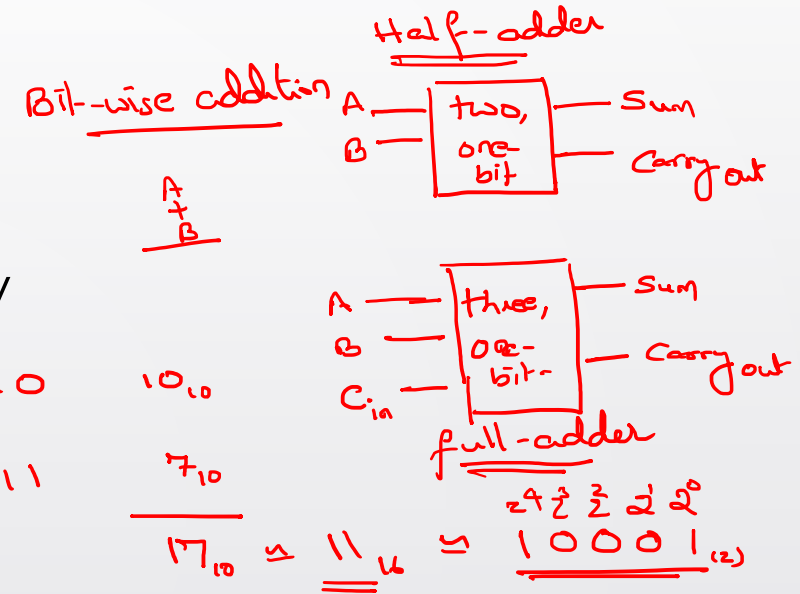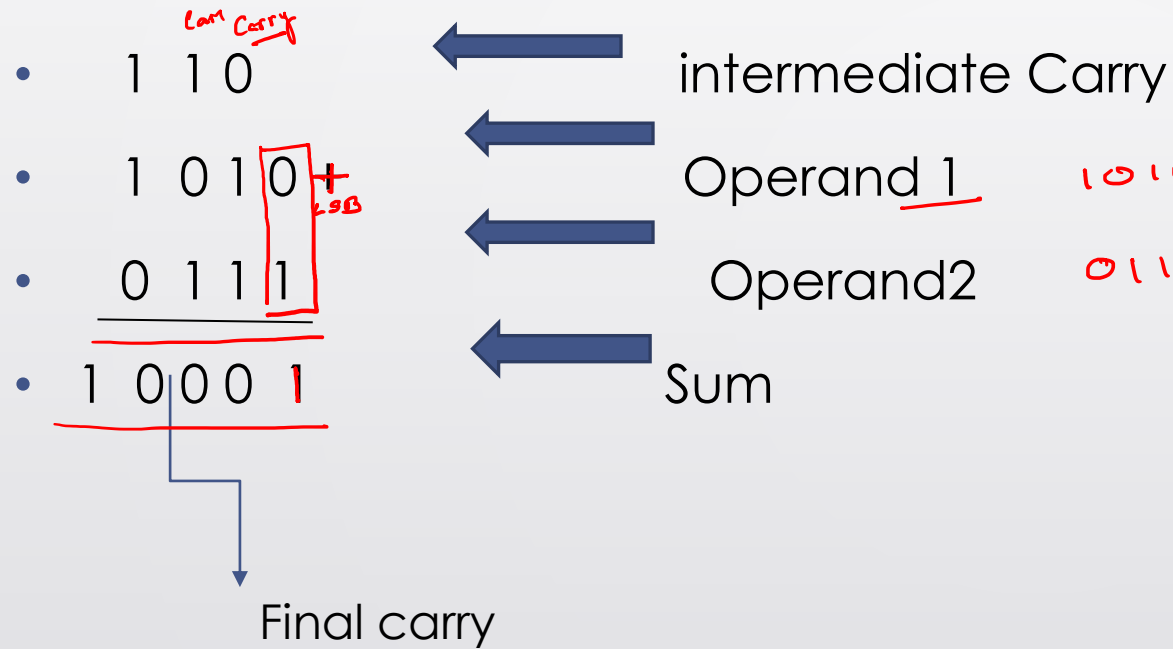
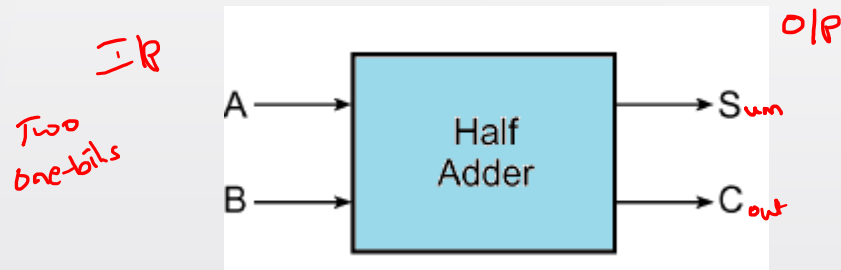
# Half adder(HA)

- Adds 2, 1-bit numbers A and B , generated two outputs sum(S) and carry (C).




Expression for sum and carry :

$$\begin{array}{r}
 A \quad 0 \quad 0 \quad 1 \quad 1 \\
 +B \quad 0 \quad 1 \quad 0 \quad 1 \\
 \hline
 \hline
 \quad 00 \quad 01 \quad 01 \quad 10
 \end{array}$$

$$\begin{aligned}
 S_{\text{sum}} &= \sum_{j=1,2} = \prod_{m=0,3} \\
 C_{\text{out}} &= \sum_{j=3} = \prod_{m=0,1,2}
 \end{aligned}$$

SOP POS

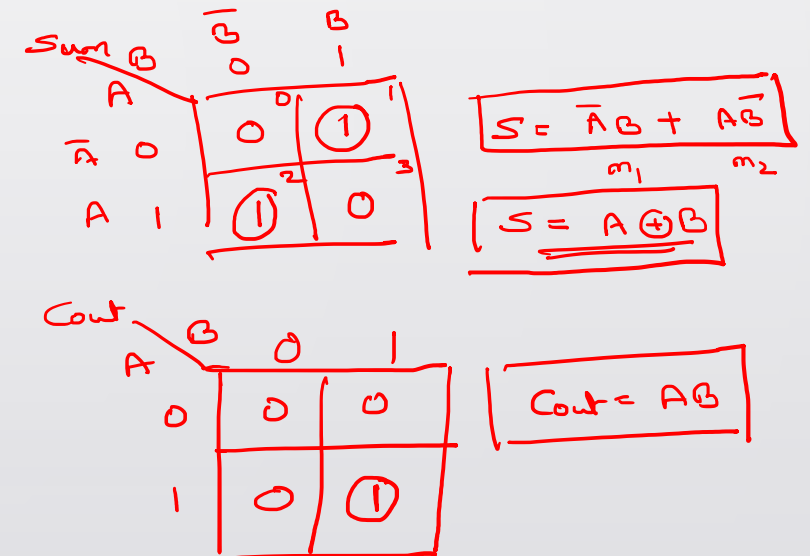


I/P O/P

A	B	Sum	Cout
0	0	0	0
0	1	1 ✓	0
1	0	1 ✓	0
1	1	0	1

$m_0$   $\bar{A}\bar{B}$  MSB  
 $m_1$   $\bar{A}B$   
 $m_2$   $A\bar{B}$   
 $m_3$   $AB$   
 4 combinations

# HA circuit


Using basic logic gates

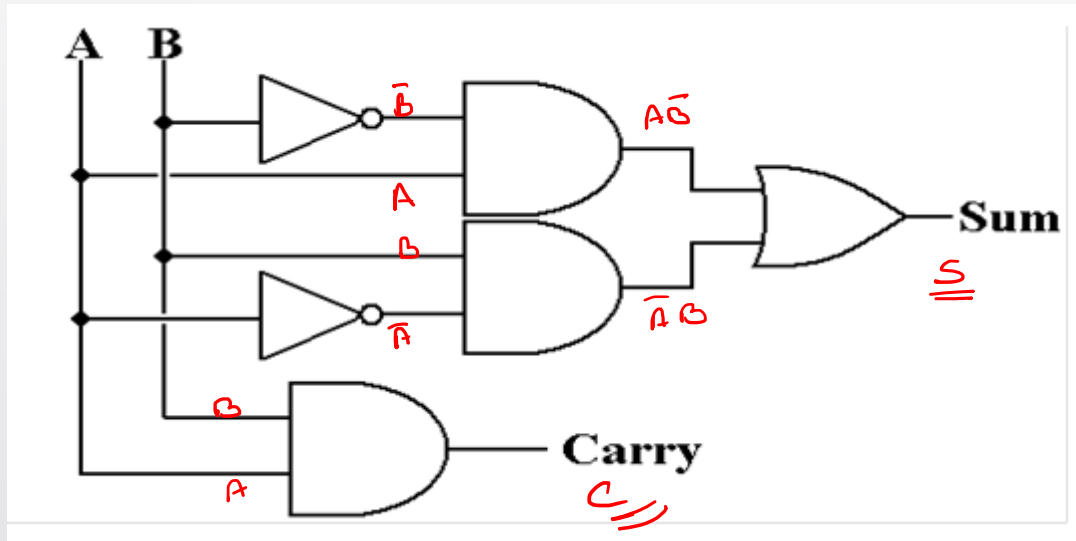

$$S = \bar{A}B + A\bar{B}$$

$$C = AB$$


Using XOR and AND gate

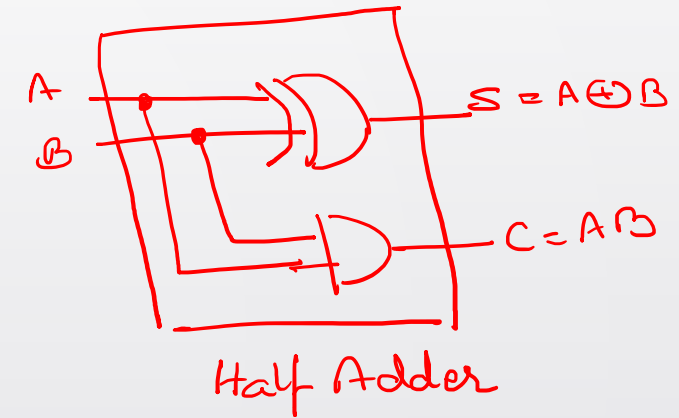

# Full adder

Truth Table

A B C	msb	lsb	Carry	Sum
0 0 0	$m_0$		0	0
0 0 1	$m_1$		0	1
0 1 0	$m_2$		0	1
0 1 1	$m_3$		1	0
1 0 0	$m_4$		0	1
1 0 1	$m_5$		1	0
1 1 0	$m_6$		1	0
1 1 1	$m_7$		1	1

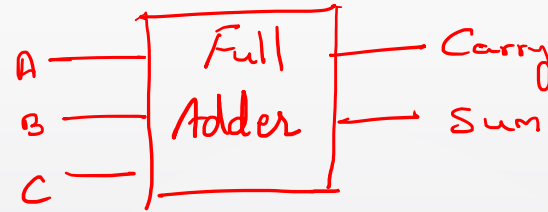

$$\text{Carry} = \sum_m 3, 5, 6, 7 = \prod_m 0, 1, 2, 4$$

$$\text{Sum} = \sum_m 1, 2, 4, 7 = \prod_m 0, 3, 5, 6$$

Sum	BC	00	01	11	10
A	0	0	1	0	1
1	1	1	0	1	0



	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$\begin{aligned}
 \text{Sum} &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\
 &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC) \\
 &= \bar{A}(B \oplus C) + A(\overline{B \oplus C}) \\
 &= \underline{\underline{A \oplus B \oplus C}}
 \end{aligned}$$

$$\text{Carry} = \underline{\underline{BC + AC + AB}}$$

$$\begin{array}{r}
 0+0+1 \rightarrow \\
 \hline
 01
 \end{array}$$

# FA circuit using basic logic gates

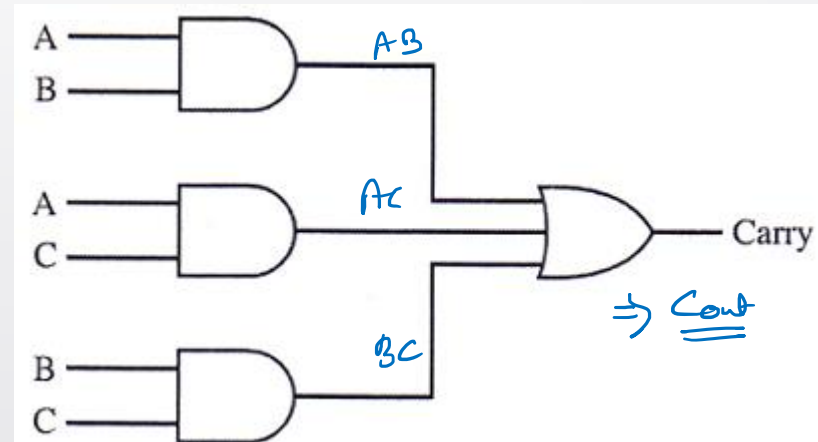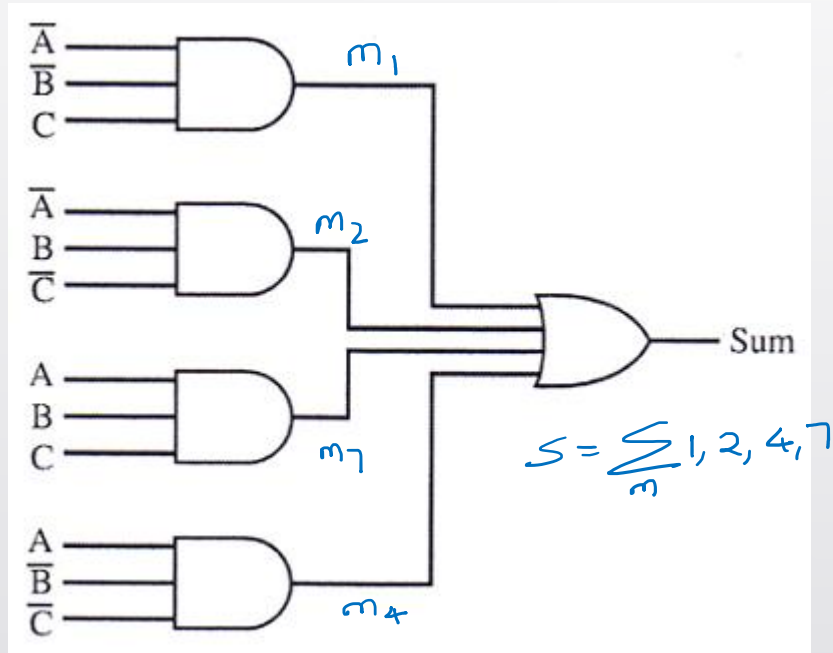





# Full adder circuit using XOR operations

FA will XOR

$$\text{Sum} = \underline{A \oplus B \oplus C}$$
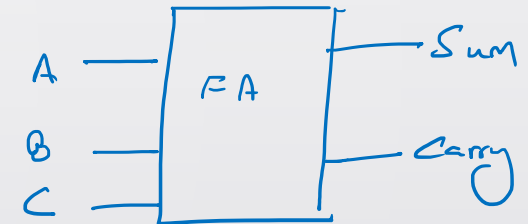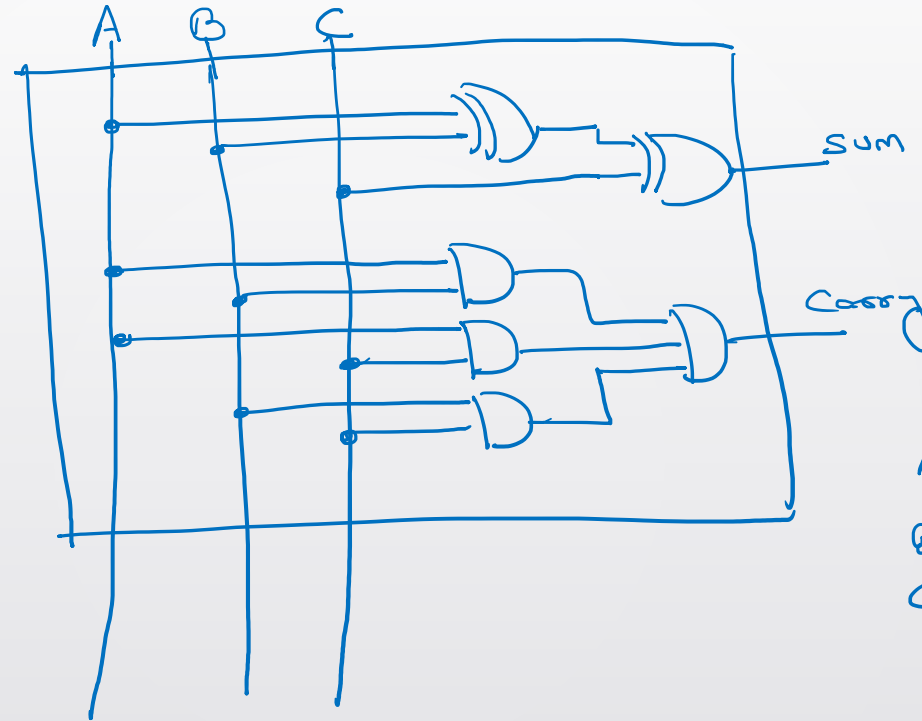
$$\text{Carry} = \underline{AB + AC + BC}$$



# FA using 2 HA s and one external gate



Half Adder

$$S = A \oplus B$$

$$C = A \cdot B$$



Full Adder

S of HA1

$$\text{Sum} = (A \oplus B) \oplus C$$

$$\text{Carry} = \underline{AB + AC + BC} = \sum_m 3, 5, 6, 7 = \left( \overset{\text{OR}}{\bar{A}BC + A\bar{B}C} \right) + \left( \overset{\text{OR}}{AB\bar{C} + ABC} \right)$$



$m_3 \quad m_5 \quad m_6 \quad m_7$

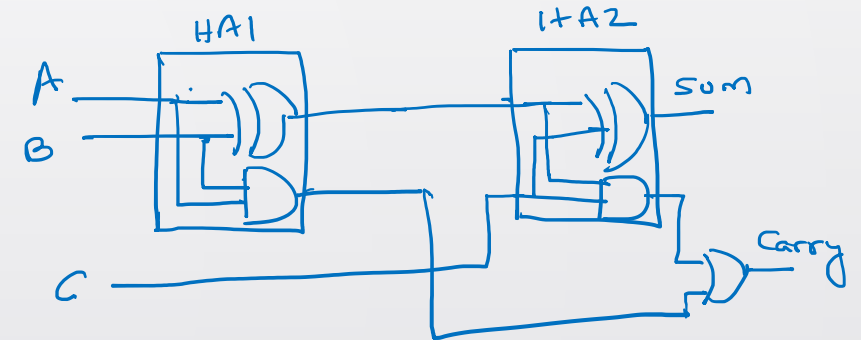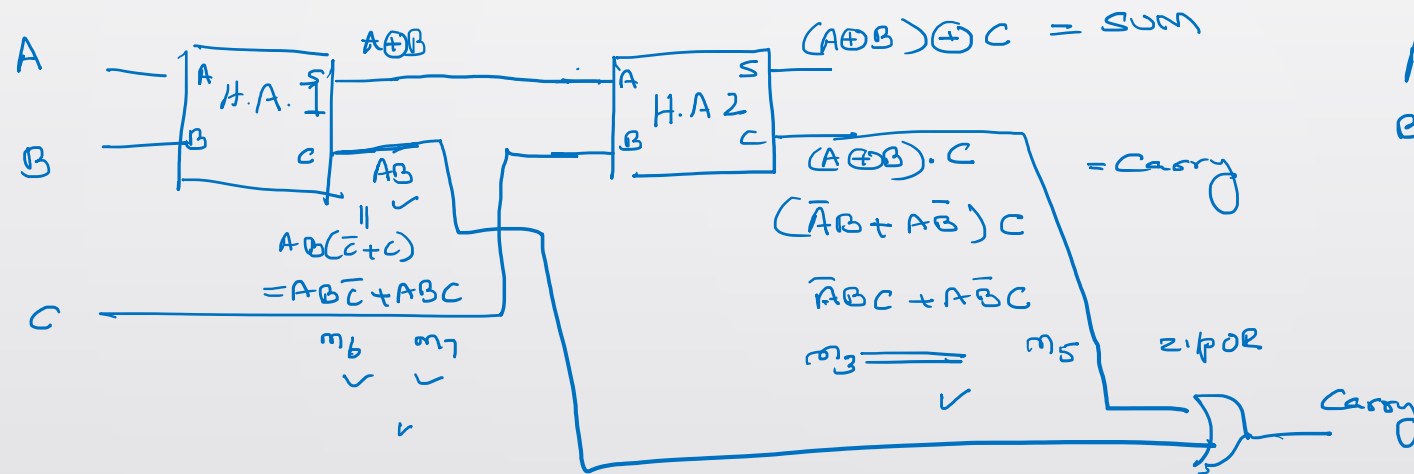


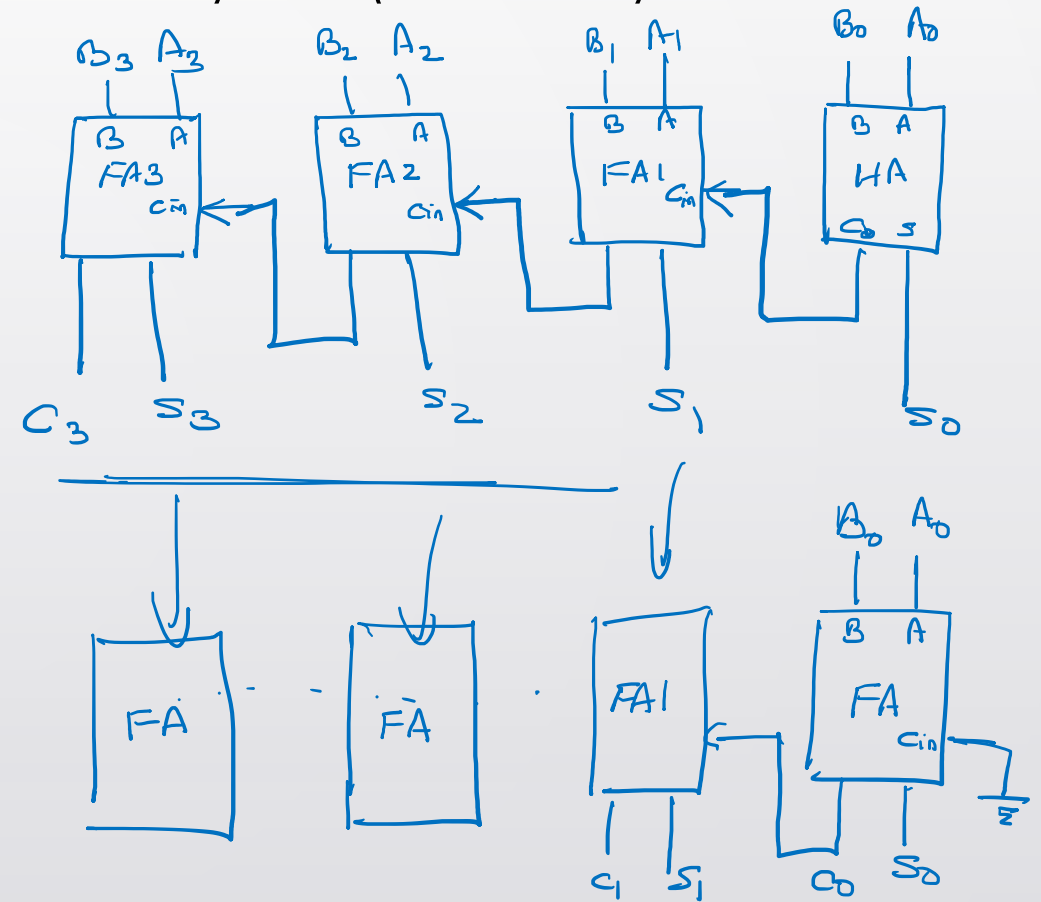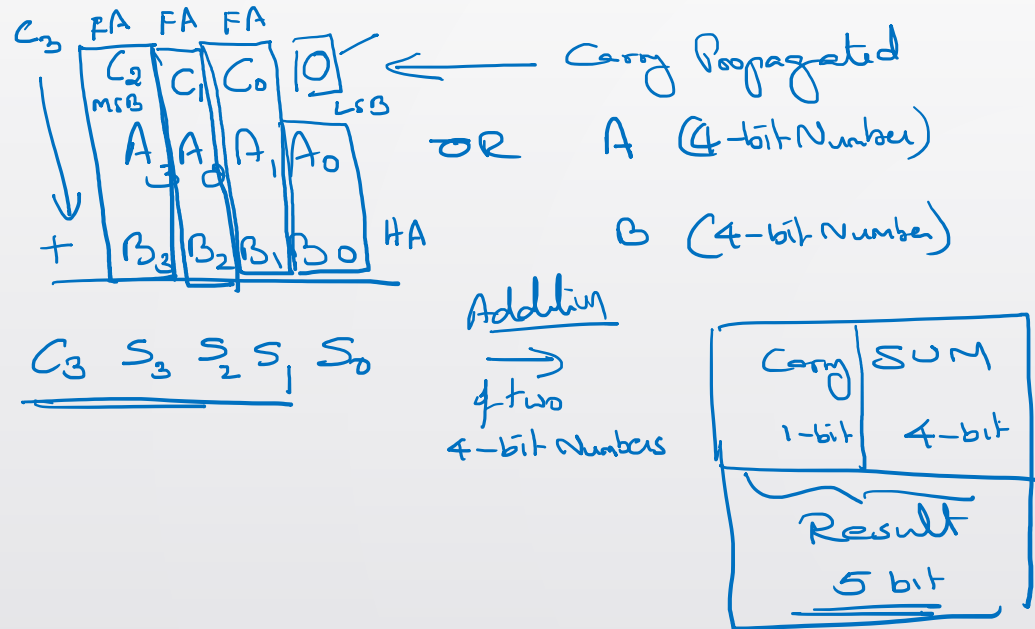
# 4-bit Parallel adder using FA blocks

- Consider addition of 2, 4-bit numbers:  $(A_3 A_2 A_1 A_0)$  and  $(B_3 B_2 B_1 B_0)$




# 4-bit parallel adder

Also called as Carry Propagation Adder (CPA)


MS FA

LS, FA


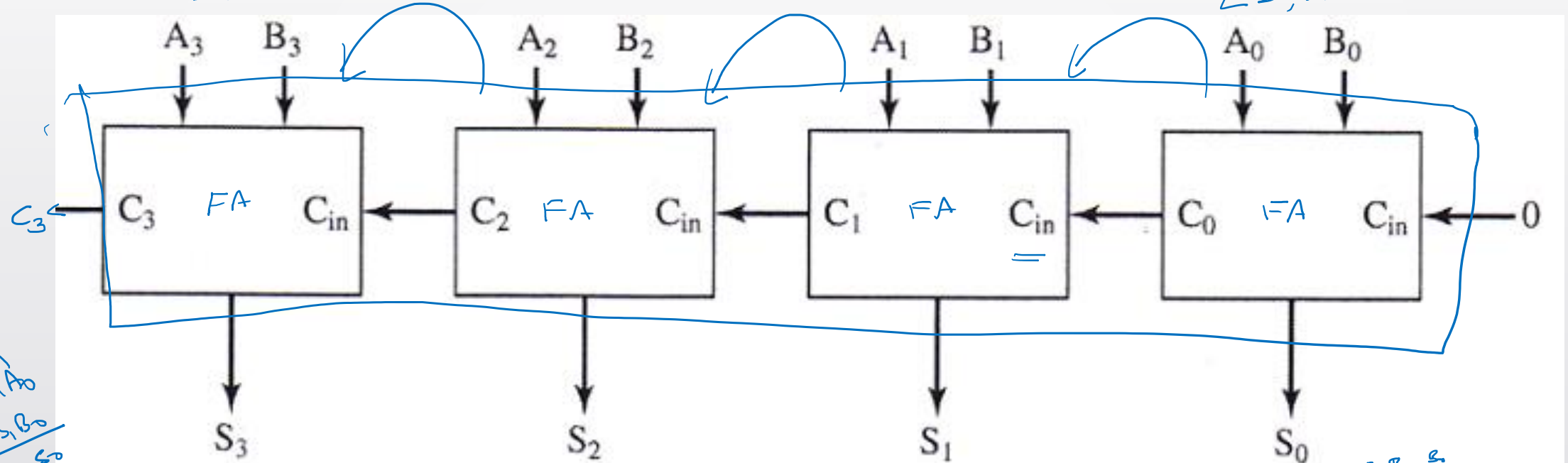


$C_2, C_1, C_0$   
 $A_3, A_2, A_1, A_0$   
 $B_3, B_2, B_1, B_0$   
 $C_3, S_3, S_2, S_1, S_0$

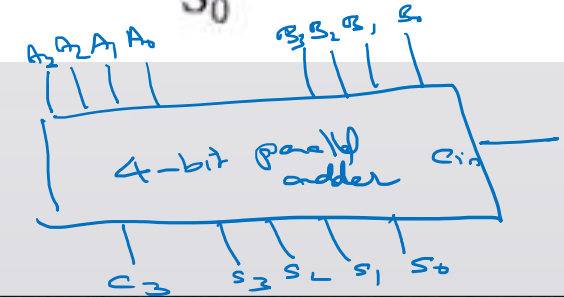Each Gate : Response time  $\propto$  Gate propagation delays



# 7483 IC : 4-BIT PARALLEL ADDER

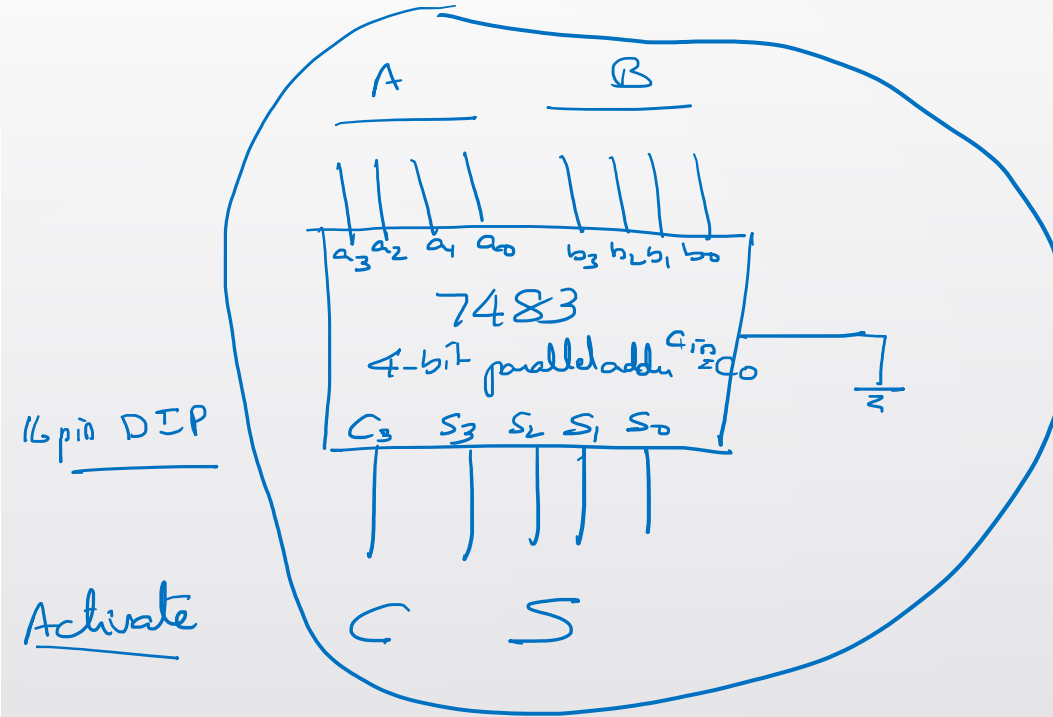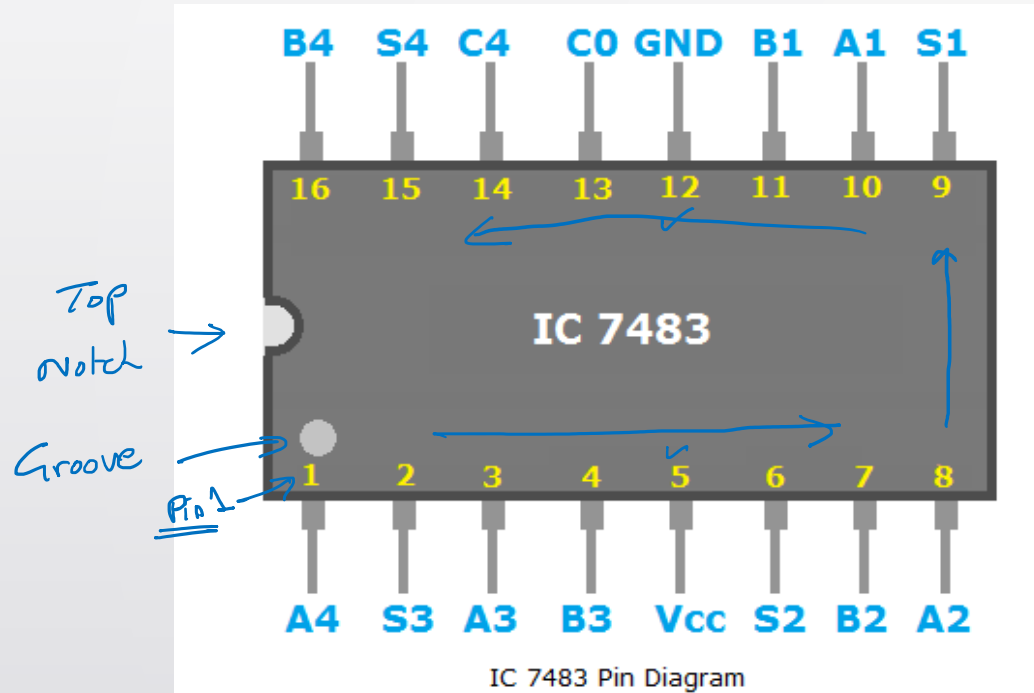

# Half subtractor

- Write the truth table and circuit for half subtractor

$$\begin{array}{r} A \\ -B \\ \hline A-B \end{array}$$

bit wise subtraction

A → 1-bit 0 or 1

B → 1-bit 0 or 1

10

10

01

00

10

10

$$\text{Difference} = \sum_{i=1,2} = \prod_{i=0,3}$$

$$\text{Borrow} = \sum_{i=1} = \prod_{i=0,2,3}$$


A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\text{Difference} = \bar{A}B + A\bar{B} = A \oplus B$$


A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\text{Borrow} = \bar{A}B$$

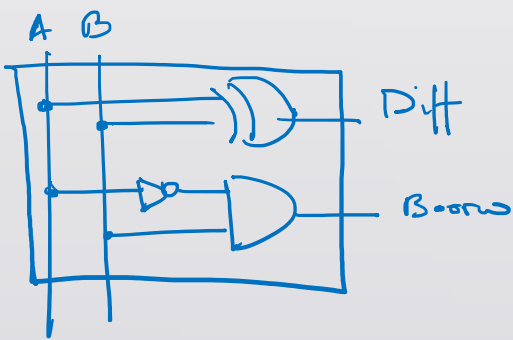

# Full subtractor

DIFFERENCE (D) = X-Y-Z, Borrow (B)

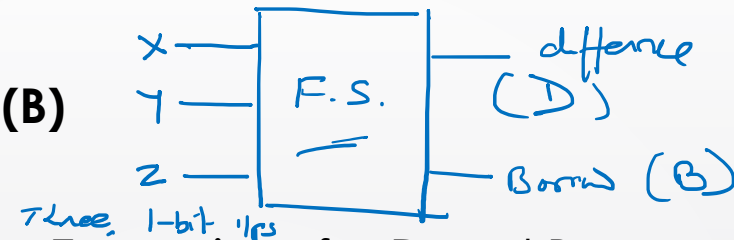


Expressions for D and B:

X	Y	Z	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


$$D = \sum_3 1, 2, 4, 7 = \prod_3 0, 3, 5, 6$$
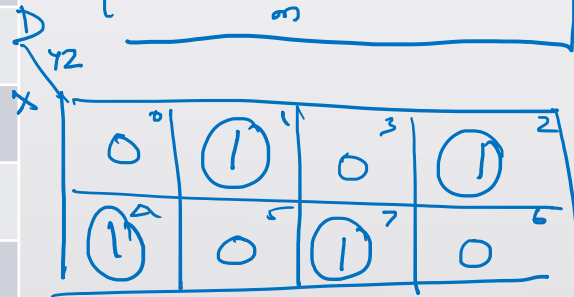
$$B = \sum_3 1, 2, 3, 7 = \prod_3 0, 4, 5, 6$$



$$\bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$$

$$D = \underline{x \oplus y \oplus z}$$

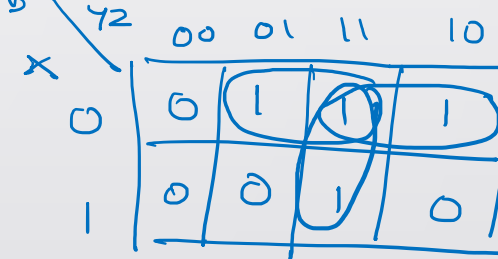

$$B = \underline{\bar{x}z + \bar{x}y + yz}$$




# FS circuit

- Draw the circuit for FS using
- (i) basic logic gates only
- (ii) XOR and basic logic gates

$$D = X \oplus Y \oplus Z = \sum 1, 2, 4, 7 = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$
$$B = \bar{X}Y + \bar{X}Z + YZ$$

PRACTICE

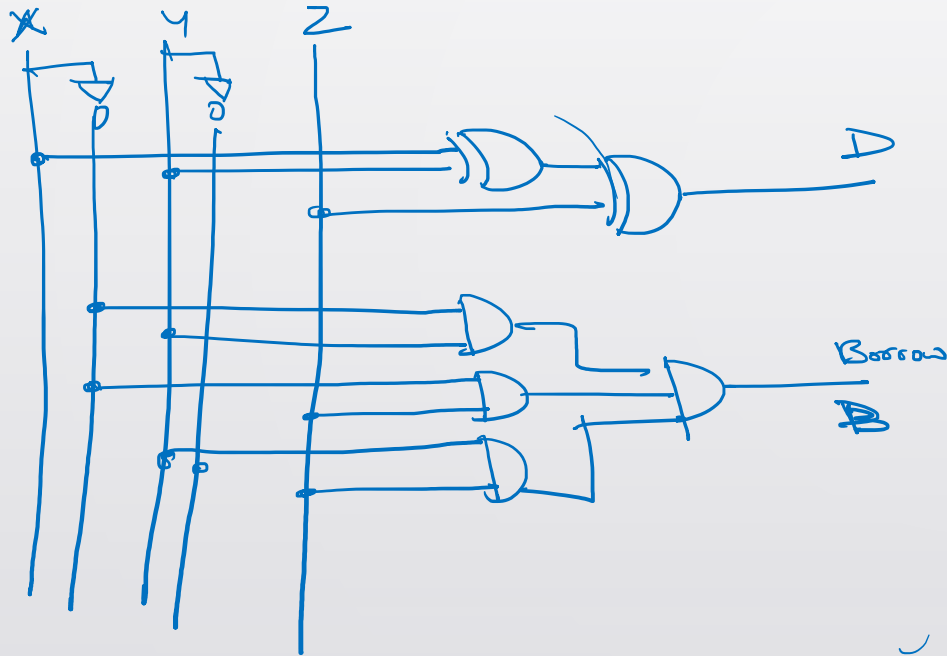




# Full subtractor using 2 HS s and one external gate

HS

$$\text{Diff} = X \oplus Y$$



$$\text{Borrow} = \bar{X}Y$$

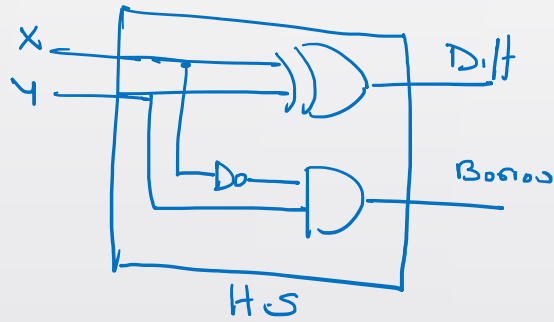

F.S


$$D = \underline{X \oplus Y \oplus Z} = \underbrace{(X \oplus Y)}_{\text{HS1 Diff term}} \oplus Z$$
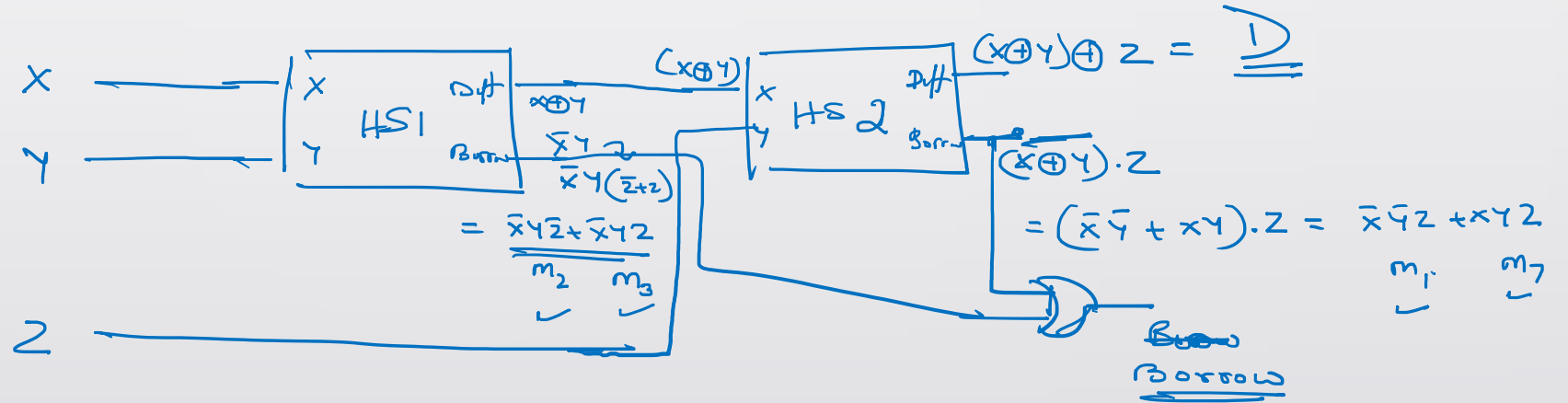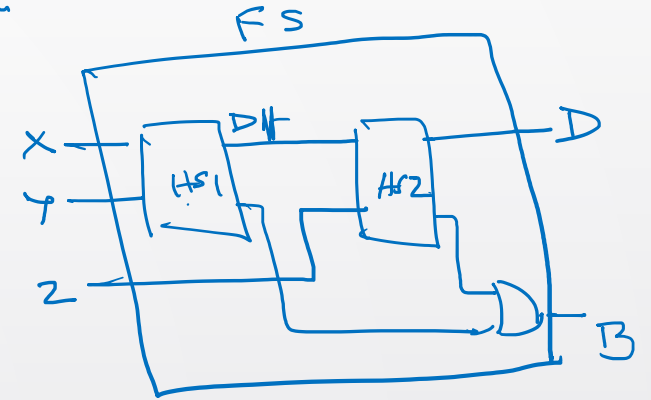
$$B = \sum_{j=1,2,3,7} = (m_1) + (m_2) + (m_3) + (m_7)$$


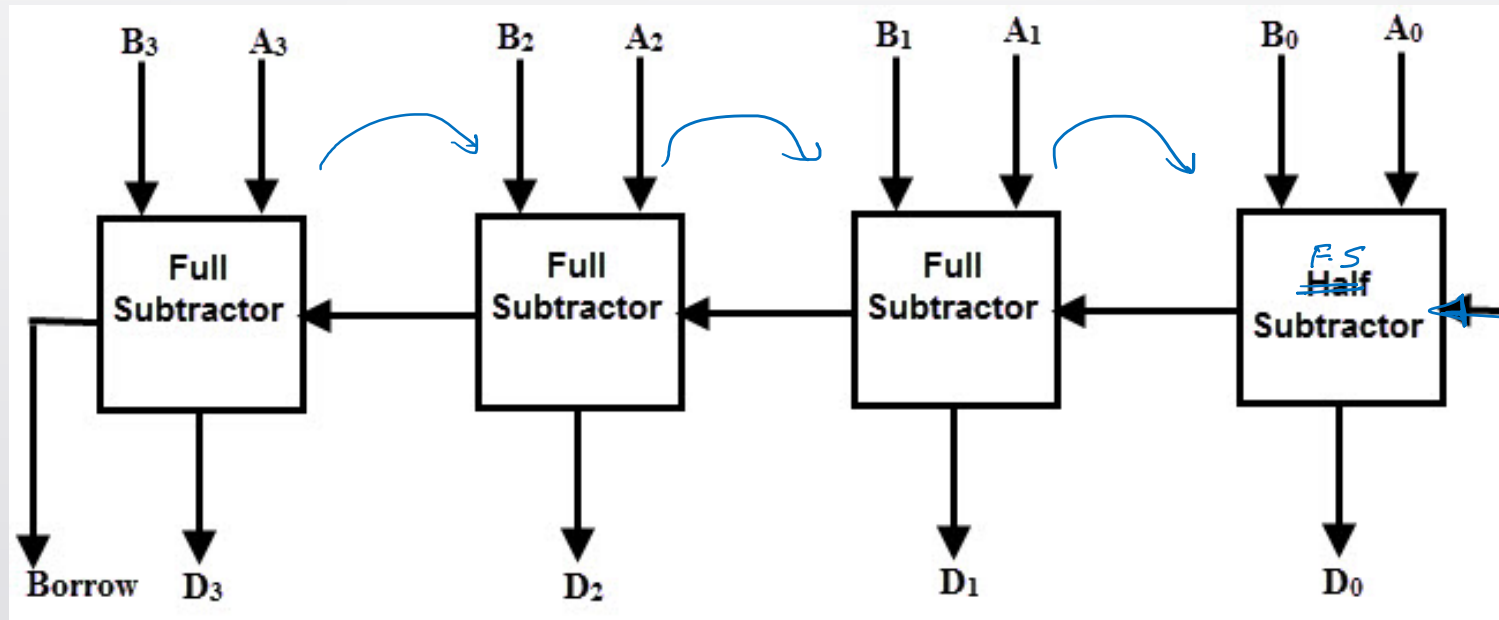
# 4-bit parallel subtractor using FS blocks

Consider subtraction of 2, 4-bit numbers:  $(A_3 A_2 A_1 A_0)$  and  $(B_3 B_2 B_1 B_0)$



$$\begin{array}{r} A_3 A_2 A_1 A_0 \\ - B_3 B_2 B_1 B_0 \\ \hline \end{array}$$

$$\begin{array}{r} 1000 \\ 246 \\ 683 \\ - 563 \\ \hline \end{array} \quad \begin{array}{r} 1000 \\ 2999 \\ - 8001 \\ \hline \end{array}$$

$$\begin{array}{r} 1000 \rightarrow \\ 1111 \\ \hline 001 \\ 246 \rightarrow 246 \\ - 683 \rightarrow 316 \quad 317 \\ \hline 3 \quad 0563 \\ \hline \end{array}$$

999 - 4 = 995

$$\begin{array}{r} 683 \\ 317 \\ \hline 1000 \end{array}$$

ve 563, 437<sup>10'</sup>

# Subtraction using complements

use 4 bit parallel adders or use 7483

## Using 2's complement method

### Using 1's complement method

Example

$$\begin{array}{r} 8 \\ - 2 \\ \hline + 6 \\ \hline \end{array}$$

$$\begin{array}{r} 8 \rightarrow 1000 \\ - 2 \rightarrow 0010 \\ \hline \end{array}$$

Let us use 2's complement addition

$$\begin{array}{r} 1000 \\ + 0010 \\ \hline 1001 \\ \hline \end{array}$$

$$\begin{array}{r} 1101 \\ + 1 \\ \hline 0110 \\ \hline \end{array}$$

the sign

if the carry

6 Difference

retain only sum terms → Difference

Retain

$$\begin{array}{r} 0111 \\ 0010 \\ \hline \end{array}$$

2's comp

$$\begin{array}{r} 0111 \\ + 1 \\ \hline 0100 \\ \hline \end{array}$$


1's comp + 1

if Cout = 0

sign -ve

$$\begin{array}{r} 0100 \\ + 1 \\ \hline 0101 \\ \hline \end{array}$$

2's complement

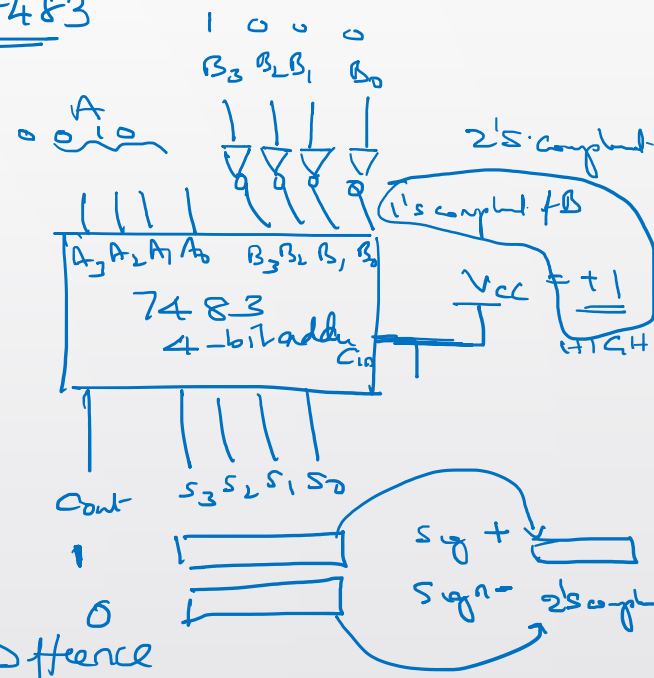

$$\begin{array}{r} 1010 \rightarrow 0101 \\ \hline 0110 \\ \hline \end{array}$$

# Subtraction using complements

Using 2's complement method

Using 1's complement method

$$\begin{array}{r}
 8 \rightarrow 1000 \rightarrow 1'000 \\
 -2 \rightarrow -0010 \xrightarrow{\text{1's comp}} 1101 \\
 \hline
 \end{array}
 \xrightarrow{\text{Carry}}
 \begin{array}{r}
 10101 \\
 \hline
 \end{array}
 \rightarrow \text{Carry +ve sign}$$

$$\begin{array}{r}
 2 \rightarrow 0010 \\
 -8 \rightarrow 1000 \\
 \hline
 \end{array}$$


$$\begin{array}{r}
 2 \quad 0010 \rightarrow 011 \\
 -8 \quad -1000 \xrightarrow{\text{1's comp}} 0111 \\
 \hline
 \end{array}
 \xrightarrow{\text{Add}}
 \begin{array}{r}
 01001 \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 0101 \\
 + \quad 1 \\
 \hline
 0110
 \end{array}$$

also use carry to add to sum

Carry or Carry is 0  
 $\downarrow$   
-ve number

Ans is in its complement form  
is

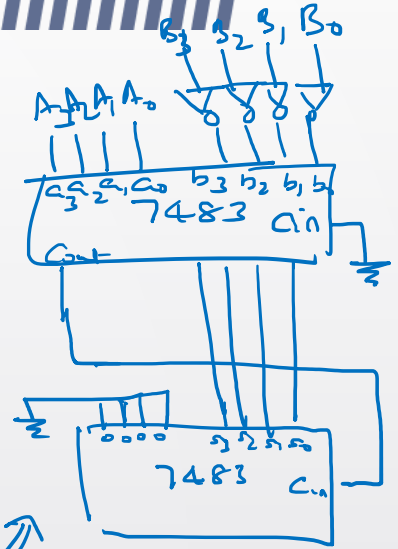

Sum  
 Add  
 Carry to Least bit

2nd level  
 if Cout = 1

9

Cout = 0

$$\begin{array}{r}
 1001 \rightarrow 0110 \\
 \hline
 \hline
 \end{array}
 = 6$$



**Questions?**