



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)



Basic Electrical Technology

LECTURE 3 – 27 OCTOBER 2021

- NETWORK REDUCTION

Illustration 1

Two incandescent bulbs have the following ratings:

Bulb-1: 120 V, 60 W;

Bulb-2: 240 V, 480 W

- a) Both of them are connected in series across a voltage source.
 - i. Which bulb will glow brighter and why?
 - ii. What is the maximum voltage that can be applied so that none of the bulbs fuse?

- b) Now both of them are connected in parallel across a voltage source.
 - i. Which bulb will glow brighter and why?
 - ii. What is the maximum voltage that can be applied so that none of the bulbs fuse?


Assume that the incandescent bulbs are purely resistive.

Ans: (a) – (i) Bulb 1 will glow brighter as $P_1 > P_2$, (ii) Max. voltage = 180 V
(b) – (i) Bulb 2 will glow brighter as $P_2 > P_1$, (ii) Max. voltage = 120 V

Illustration 2



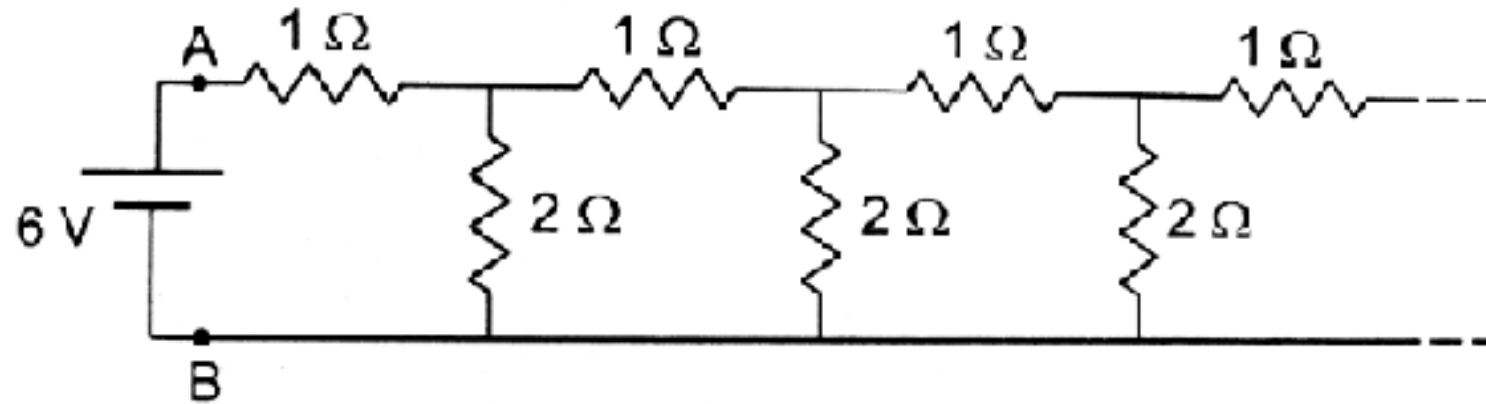What is the equivalent resistance across the terminals A & B in the network shown?



Ans: 2 Ohms


Illustration 3



15 resistors are connected as shown in the diagram. Each of the resistors has resistance $1\ \Omega$.

- a) Find the equivalent resistance of the network between A & B.
- b) What will be the equivalent resistance of this network if the resistors arranged in the sequence extends to infinity?


Ans: (a) 1.875 Ohms, and (b) 2 Ohms

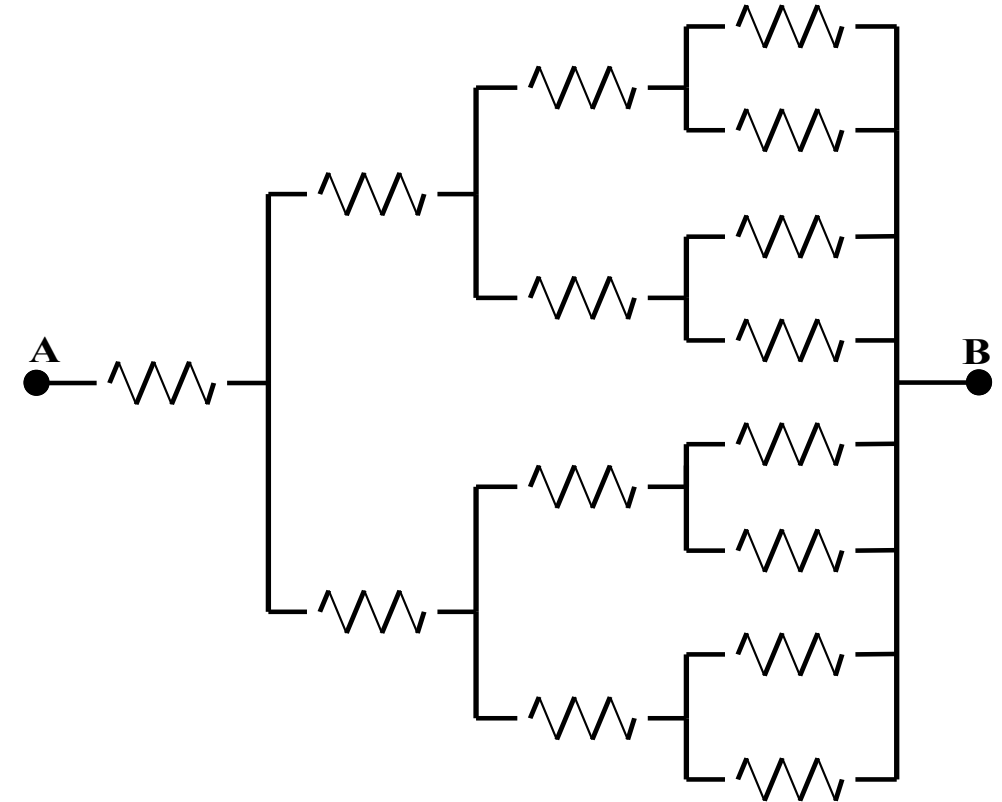

Home Work 1



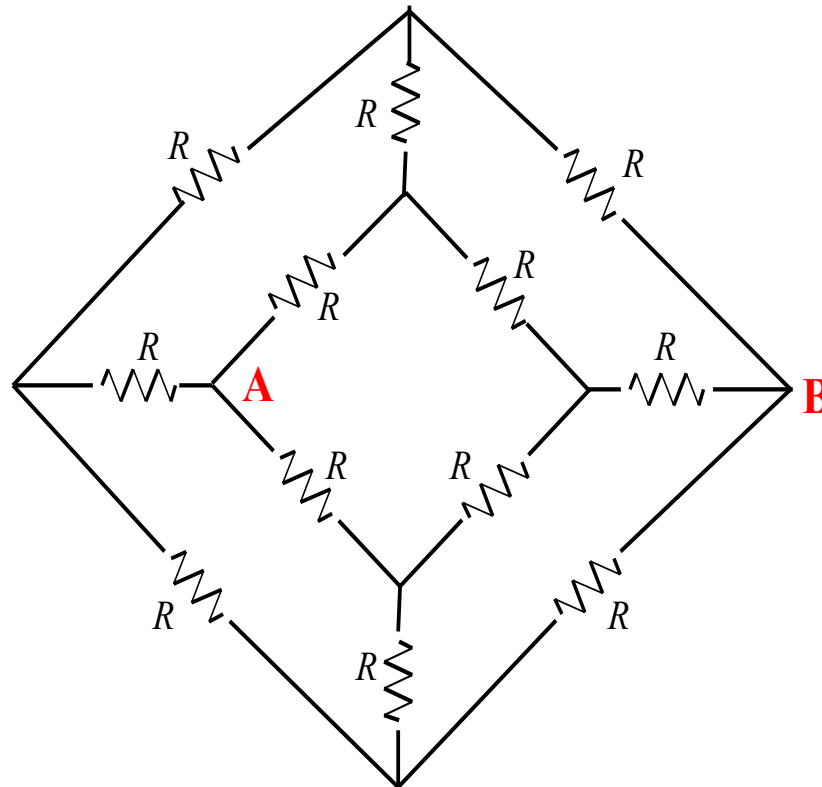Reduce the network to its equivalent resistance between terminals A and B



Ans: $5R/6$



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL



(A constituent institution of MAHE, Manipal)



Star - Delta Transformation

NETWORK REDUCTION TECHNIQUE


Star & Delta Connections

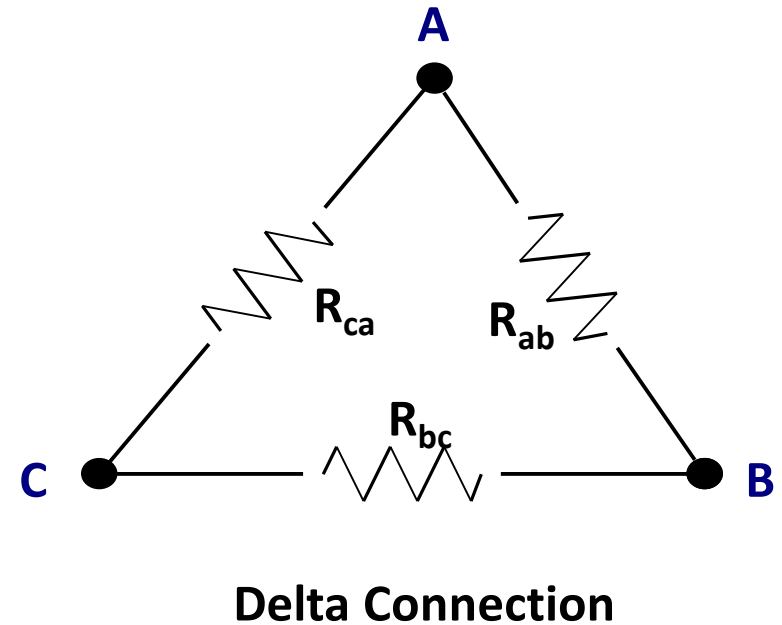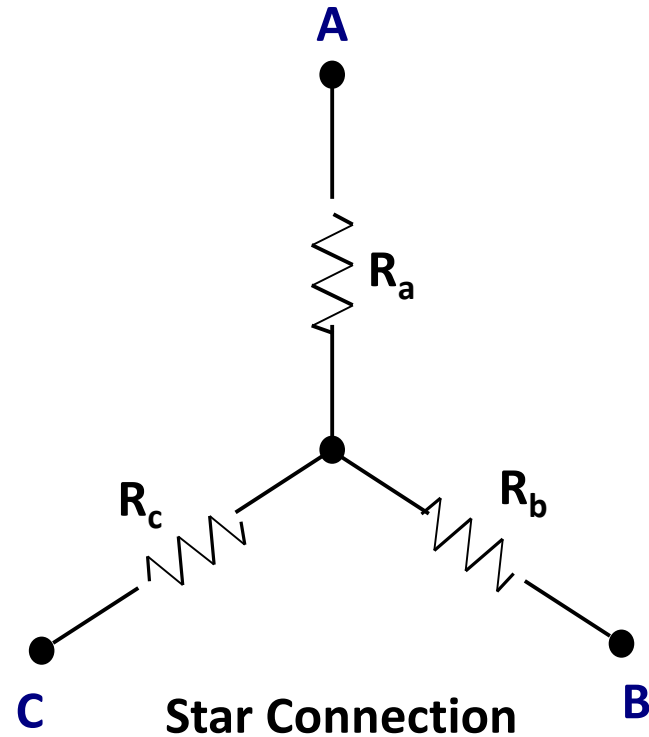


Link for the formula derivation:

[https://nptel.ac.in/content/storage2/courses/108105053/pdf/L-06\(GDR\)\(ET\)%20\(\(EE\)NPTEL\).pdf](https://nptel.ac.in/content/storage2/courses/108105053/pdf/L-06(GDR)(ET)%20((EE)NPTEL).pdf)

Delta - Star Transformation

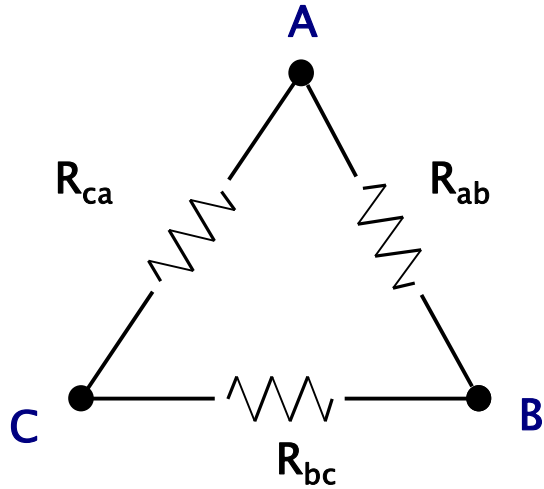

Delta to Star Transformation

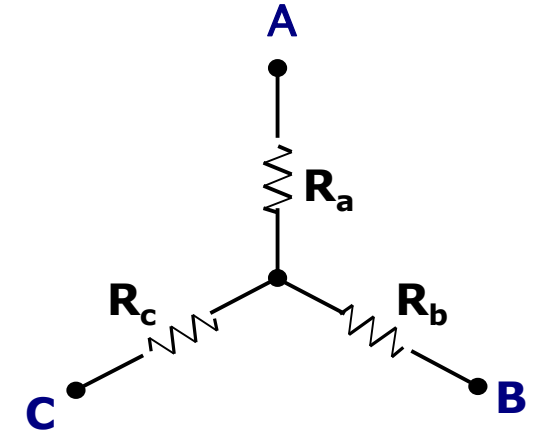



$$R_a = \frac{R_{ab} R_{ca}}{R_{ab} + R_{bc} + R_{ca}} = \frac{R_{ab} R_{ca}}{\sum R_{\Delta}}$$

$$R_b = \frac{R_{bc} R_{ab}}{R_{ab} + R_{bc} + R_{ca}} = \frac{R_{bc} R_{ab}}{\sum R_{\Delta}}$$

$$R_c = \frac{R_{ca} R_{bc}}{R_{ab} + R_{bc} + R_{ca}} = \frac{R_{ca} R_{bc}}{\sum R_{\Delta}}$$

Star - Delta Transformation

Star to Delta Transformation

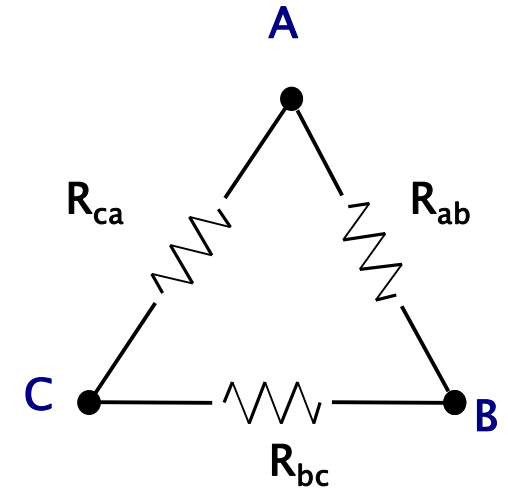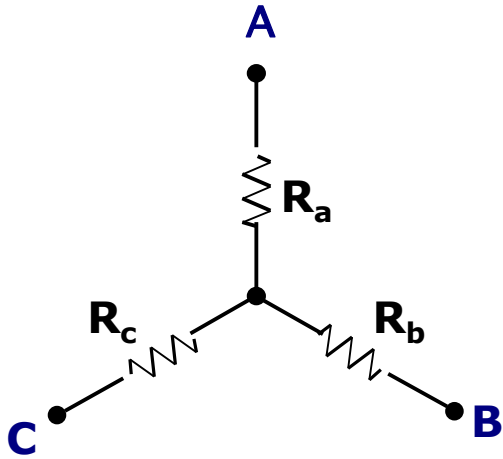

$$R_{ab} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c} = R_a + R_b + \frac{R_a R_b}{R_c}$$


$$R_{bc} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a} = R_b + R_c + \frac{R_b R_c}{R_a}$$

$$R_{ca} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b} = R_c + R_a + \frac{R_a R_c}{R_b}$$

Illustration 4



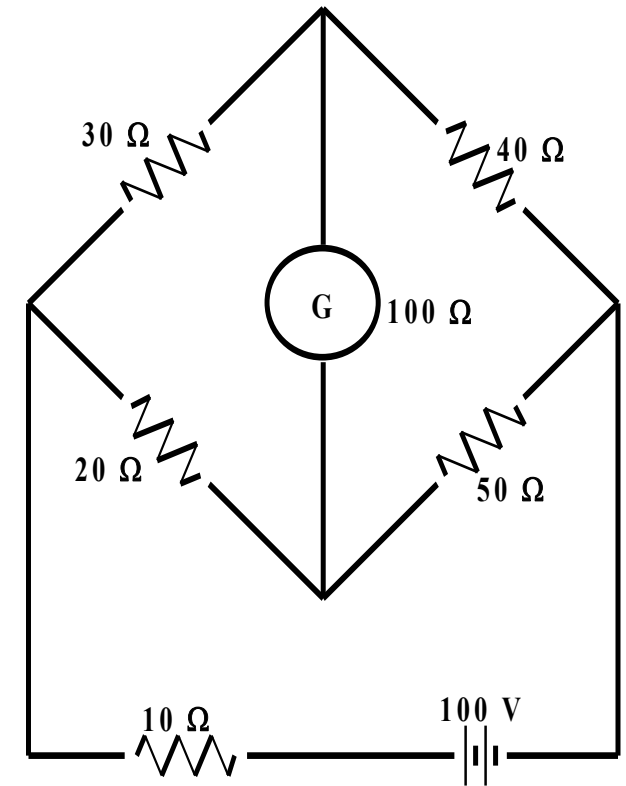For the circuit shown, determine the total power supplied by the source using star-delta transformation




Ans: $P_{\text{supplied}} = 223.1608 \text{ W}$

Illustration 5



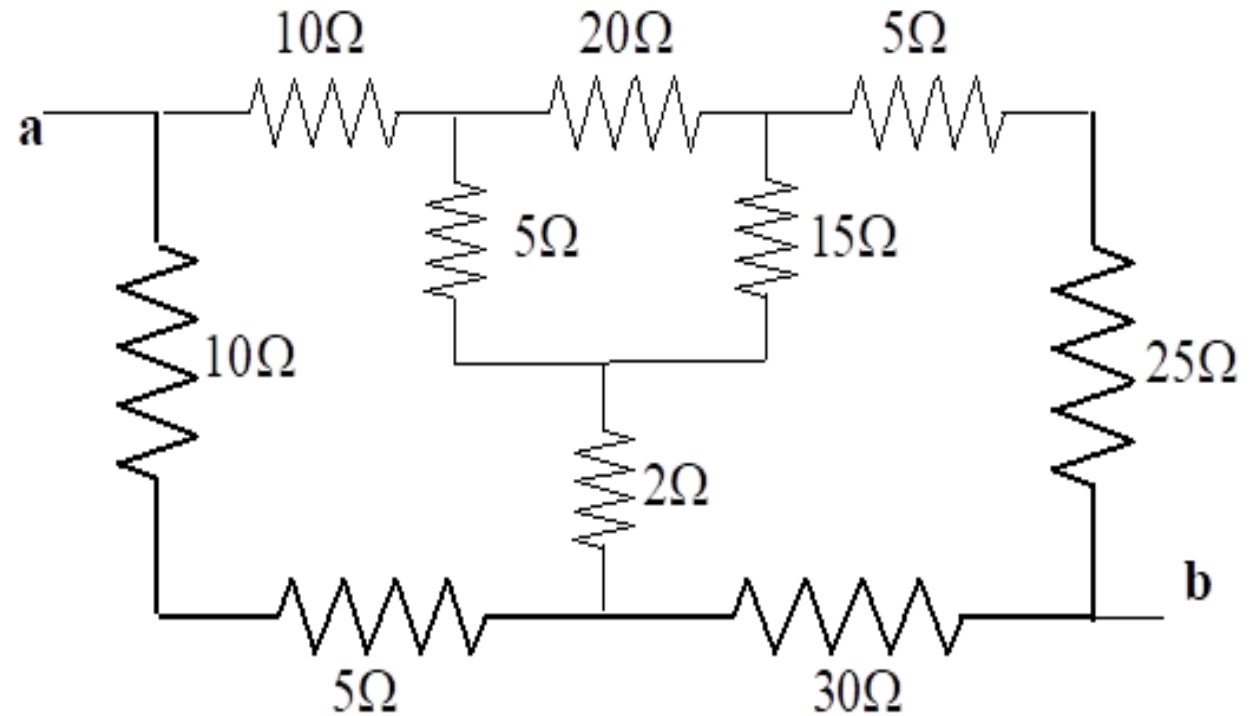Determine the resistance between terminals a & b of the network shown in figure, using Star-Delta transformation.




Ans: 23.518 Ω

Homework 2



Find R_{AB}

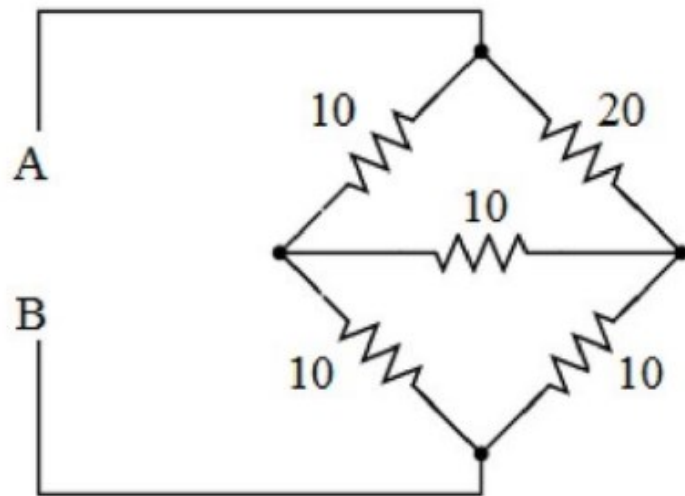

Ans: 11.818 Ohms