
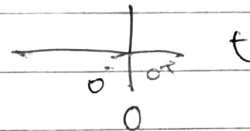


## \* Transient Analysis

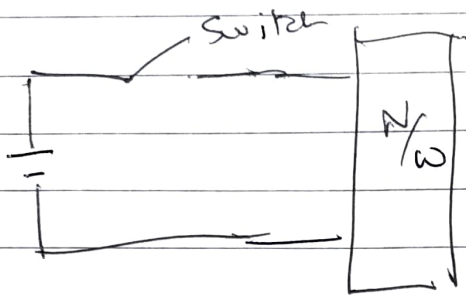

$t = 0^- \rightarrow$  Just before switch is opened / closed

$t = 0^+ \rightarrow$  Just after " " " "


\* The current in the inductor cannot change instantaneously

$$i_L(0^-) = i_L(0^+)$$

\* The voltage in the capacitor cannot change instantaneously

$$V_C(0^-) = V_C(0^+)$$

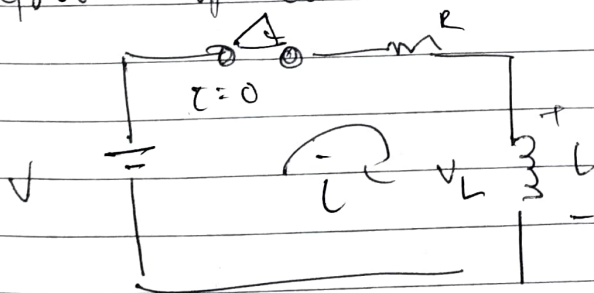① Growth of current in an Inductive circuit.



$t = 0^- \rightarrow$  switch was open

\*  $i_L(0^-) = i_L(0^+) = 0 \rightarrow$  initial condition

KVL  $\rightarrow$  closed switch

$$V - V_R - V_L = 0$$

$$V - iR - L \frac{di}{dt} = 0 \quad \Rightarrow V = iR + L \frac{di}{dt}$$

(First order LDE)

$$i(t) = i_h(t) + i_p(t)$$

Homogeneous sol<sup>n</sup>      Particular sol<sup>n</sup>

$\rightarrow$  Homogeneous sol<sup>n</sup>  
Characteristic eq<sup>n</sup>

$$DL + R = 0$$

$$\Rightarrow D = -R/L$$

$\hookrightarrow$  Roots of char: eq<sup>n</sup>

$$i_h = A e^{-R/L t} \quad \rightarrow \text{homo sol}^n$$

$$\left( \begin{aligned} \frac{di}{dt} &= D \\ \frac{d^2 i}{dt^2} &= D^2 \end{aligned} \right) \rightarrow \text{so on}$$

$\rightarrow$  Particular sol<sup>n</sup>  $\rightarrow$  Same form as the input

$$i_p(t) = c \quad \text{const}$$

$$\Rightarrow \frac{dc}{dt} = 0$$

$$V = iR + L \frac{di}{dt} \Rightarrow V = (R + L/0)$$

$$\Rightarrow c = V/R$$

$$\Rightarrow i_p(t) = V/R$$


$$\Rightarrow i(t) = A e^{-R/L t} + V/R$$

Using  $i=0$  @  $t=0$

$$\frac{+V}{R} = 0 \Rightarrow A = -V/R$$

$$\Rightarrow i(t) = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$\Rightarrow i(t=\infty) = V/R$$

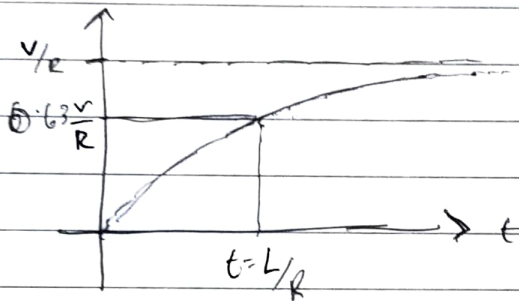


$$\begin{aligned} t &= L/R \\ \Rightarrow i &= \frac{V}{R} (1 - e^{-1}) \\ i\left(\frac{L}{R}\right) &= 0.63 \frac{V}{R} \end{aligned}$$

$L/R \rightarrow$  time const.

$$V_L(t) = L \frac{di}{dt} = \frac{V}{R} \times \frac{R}{L} \times L e^{-R/L t}$$

$$= V e^{-R/L t}$$

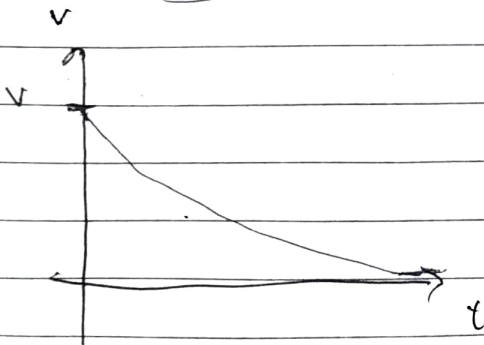

$$\Rightarrow V_R = i_L(t) R$$


A coil of inductance  $0.04\text{H}$  &  $R=10$  is connected to a  $120\text{V}$  dc. Determine

a  $\rightarrow$  final value of current

b  $\rightarrow$  time const

c  $\rightarrow$   $i$  @  $t = \text{time const.}$

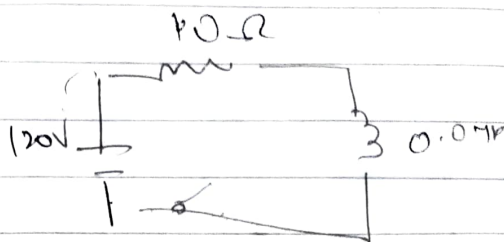d  $\rightarrow$  Expected time for the current to rise within  $1\%$  of its final value



a  $I(\infty) = V/R = 12\text{ A}$

b  $\tau = L/R = 0.04/10 = 0.004\text{ sec}$

c  $I(\tau) = 0.63 \times 12 = 7.56$

d  $1\% \text{ of final value} = \frac{12}{100} = 0.12$

$$\frac{V}{R \times 100} = \frac{V}{R} (1 - e^{-t/0.004})$$

$$\frac{1}{100} = 1 - e^{-t/0.004}$$

$$\frac{99}{100} = e^{-t/0.004}$$

$$\ln \frac{99}{100} = -\frac{t}{0.004} \Rightarrow t = -0.004 \ln \left( \frac{99}{100} \right)$$

$$t = 18.421\text{ msec}$$

Q An RL series circuit is designed for a steady current of 250 mA. A current of 120 mA flows in the circuit at an instant 0.1 sec after connecting from supply voltage. Calc.

- Time const
- Time from closing the circuit at which the current has reached 200 mA.

$$i = \frac{V}{R} = 250 \text{ mA}$$

$$i(0.1 \text{ s}) = 120 \text{ mA}$$

$$\frac{120}{250} = \frac{250}{250} (1 - e^{-t/\tau})$$

$$\frac{12}{25} = 1 - e^{-t/\tau}$$

$$e^{-t/\tau} = \frac{13}{25}$$

$$\frac{t}{\tau} = \ln\left(\frac{25}{13}\right)$$

$$\Rightarrow \tau = 0.1529 \text{ sec.}$$

$$200 \text{ mA} = 250 \text{ mA} (1 - e^{-t/0.1529})$$



$$\frac{4}{5} = e^{-t/0.1529}$$

$$\Rightarrow t = 0.1529 \ln 5$$

$$= 0.2461 \text{ sec}$$


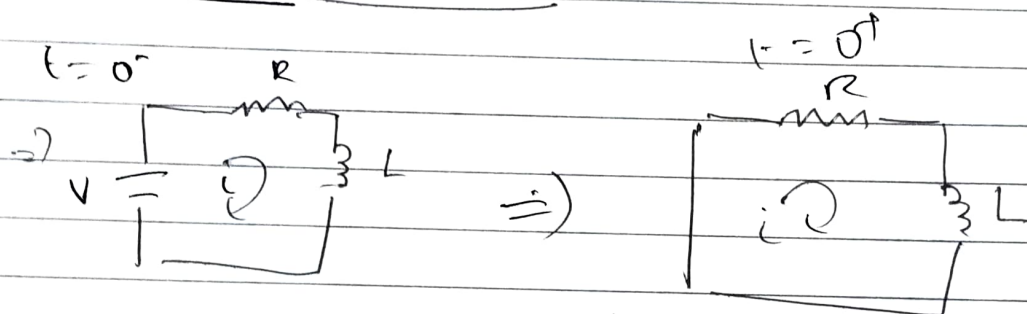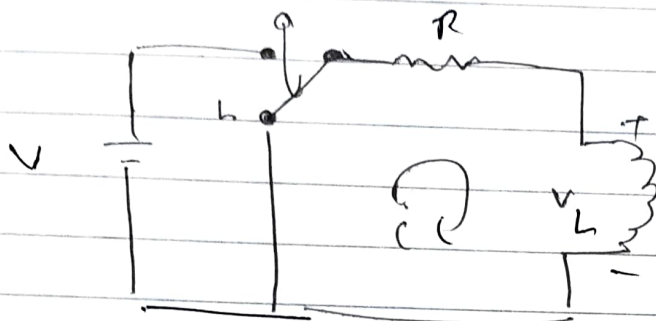
# Decay of current in an Inductive circuit



$$i(0^-) = \frac{V}{R}$$

$$i(0^+) = \frac{V}{R}$$

$$-iR - L \frac{di}{dt} = 0$$

$$iR + L \frac{di}{dt} = 0 \rightarrow \text{First order LDI}$$

$$i_h(t) = i_h(t) \quad \text{particular} = 0 \quad (V=0)$$

$$\Rightarrow DL + R = 0 \Rightarrow D = -R/L$$

$$\Rightarrow i_h(t) = A e^{-\frac{R}{L}t}$$

$$\Rightarrow i(t) = A e^{-\frac{R}{L}t}$$

$$A = \frac{V}{R}$$

$$t=0^+ \quad i(0^+) = \frac{V}{R}$$

$$\Rightarrow i(t) = \frac{V}{R} e^{-\frac{R}{L}t}$$



$$V_L(t) = L \frac{di_L}{dt} \Rightarrow \frac{L}{R} \times \frac{-R}{L} \times e^{-R/L t}$$

$$V_L(t) = -V e^{-R/L t}$$

- Q In network, switch is closed to position 1 @  $t=0$  & is moved to position 2 @ 10ms. Determine  
 a)  $i_L(t)$  → sketch it

$$0 < t < 10 \text{ ms}$$

$$i_L(0^-) = 0 = i_L(0^+)$$

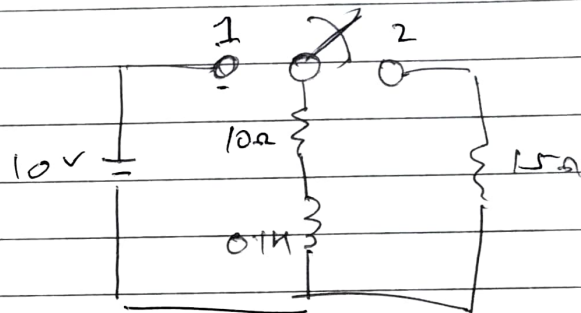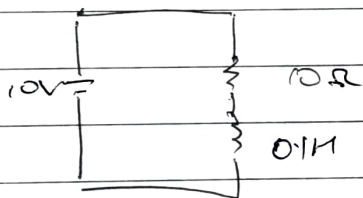

$$i = \frac{10}{10} V \left( 1 - e^{-\frac{R}{L} t} \right) = \frac{10}{10} \left( 1 - e^{-\frac{10}{0.1} \times t} \right)$$

$$= \boxed{1 - e^{-100t}} \quad \text{at } t =$$

when  $t \geq 10 \text{ ms}$

$$i(t_{\text{trans}}) = 1 - e^{-\left(\frac{100 \times 10}{10}\right)} = 1 - \frac{1}{e} = \boxed{0.63}$$

$$R = 25 \Omega \quad \Rightarrow \quad i = 0.63 e^{-(25/0.1)(t-10\text{ms})} = 0.63 e^{-250(t-10\text{ms})}$$

$$i(t) = 1 - e^{-100t}$$

$$0.63 e^{-250(t-10\text{ms})}$$

$$0 \leq t < 10 \text{ ms}$$

$$t \geq 10 \text{ ms}$$