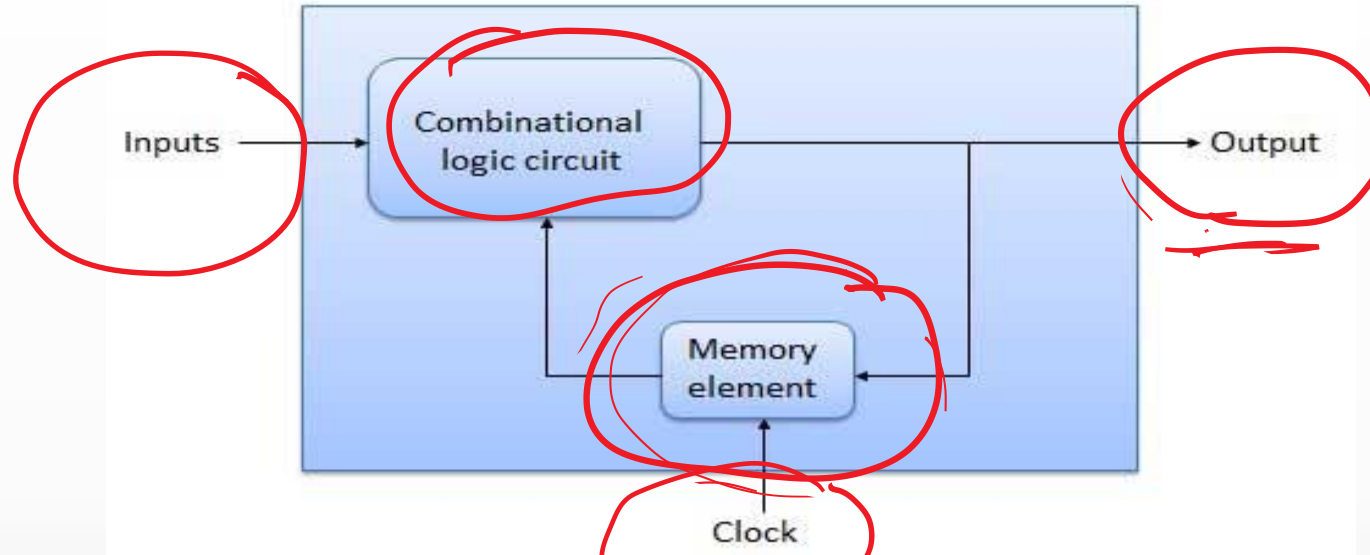


SEQUENTIAL CIRCUITS


- NAND Latch
- NOR Latch
- SR, D, JK, T flip flop

Sequential circuits:

- Outputs are dependent on current inputs and previous outputs.



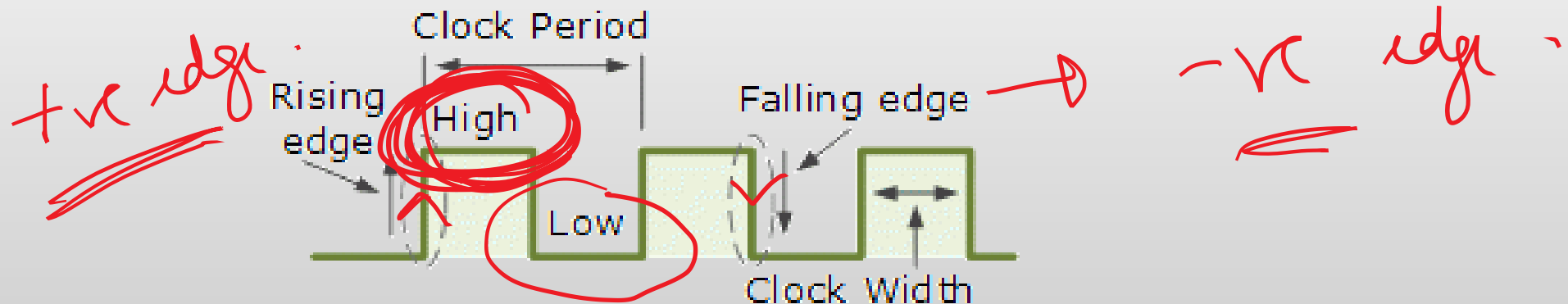- Storage elements : Devices capable of storing binary information
- Clock Signal: Is a periodic rectangular pulse train or a square wave.



■ Two types of sequential circuits:

- Asynchronous sequential circuits: The output of the logic circuits can change state at any time when one or more of the inputs change.
- Synchronous sequential circuits: The exact times at which any output can change states are determined by a signal called the clock.

4-bit → 4 FF

■ Flip Flop:



clock.

= Is a binary storage element capable of storing one bit of information

■ Latch:

= Basic type of flip flop is referred as Latch

NAND Latch (Active Low latch)

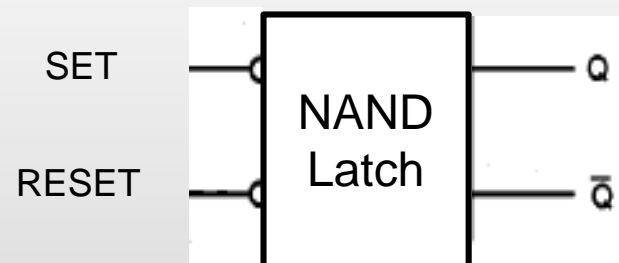
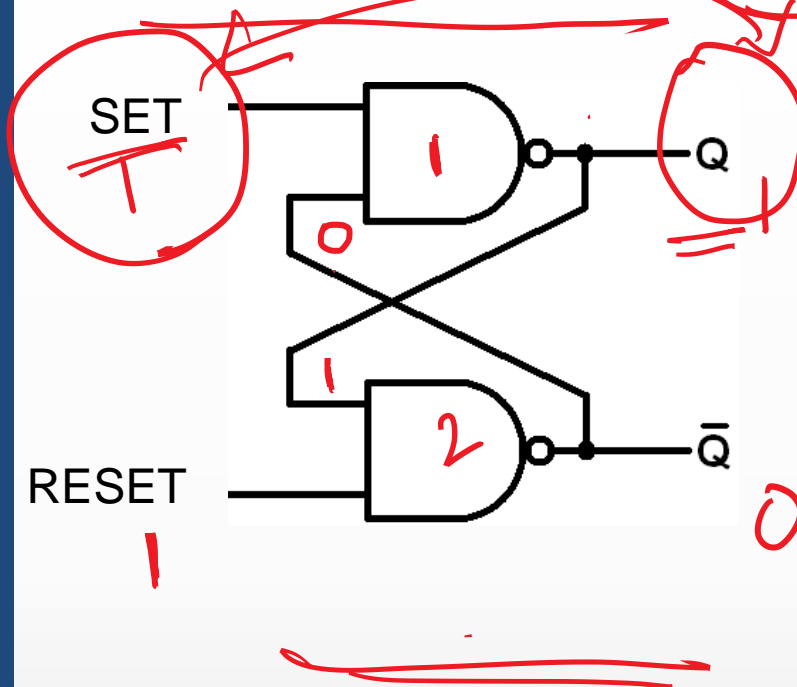


SET	RESET	Q(t)	Q(t+1)	Q'(t+1)
0	0	0	1 ✓	1 ✓
0	0	1	1 ✓	1 ✓
0	1	0	1 ✓	0 ✓
0	1	1	1 ✓	0 ✓
1	0	0	0 ✓	1 ✓
1	0	1	0 ✓	1 ✓
1	1	0	0 ✓	1 ✓
1	1	1	1 ✓	0 ✓

Function table		
SET	RESET	Output
0	0	Indeterminate
0	1	Set
1	0	Reset
1	1	No Change

undefined, invalid

NOR Latch (Active high Latch)

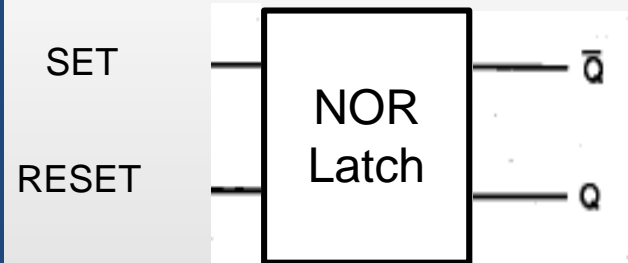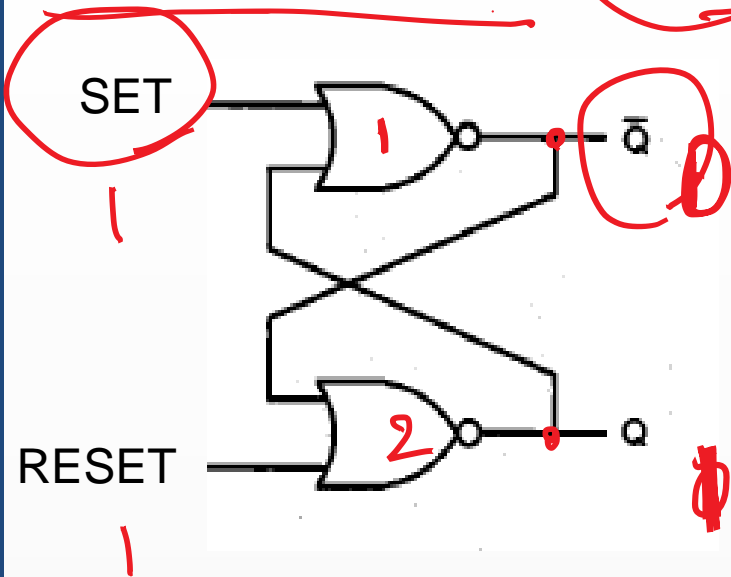

SET	RESET	Q(t)	Q(t+1)	Q'(t+1)
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	0	0
1	1	1	0	0

Function table		
SET	RESET	Output
0	0	No Change
0	1	Reset
1	0	Set
1	1	Indeterminate

invalid or undefined