


DECODERS AND ENCODERS CONTD

STUDENTS ARE ADVISED TO WRITE DOWN THE NOTES FOR EVERY LECTURE

NOV. 2ND 2021 (10.30 AM TO 12.30 PM)

Realize $f_1(x,y,z) = \prod M(1,3,6,7)$ using $= \sum m(0,2,4,5) \Rightarrow \text{OR}$

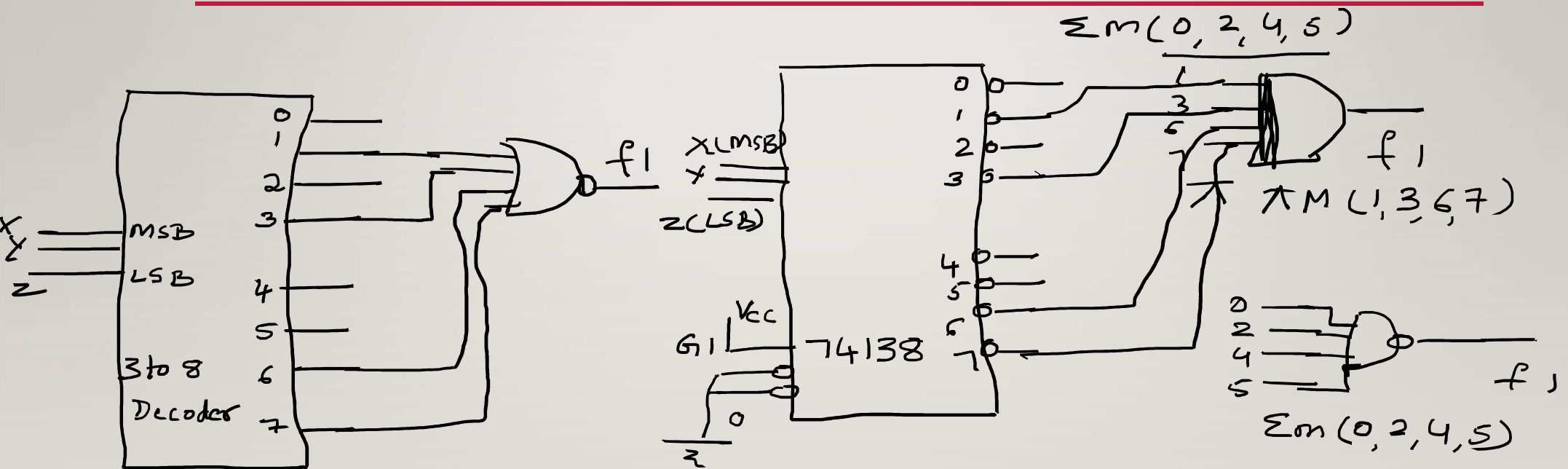- 3-to-8 line decoder with active high output and suitable gates
- 74138 decoder and suitable gates



Design a code converter to convert a decimal digit represented in 84-2-1 code to a decimal digit represented in excess-3 code using 74138 decoder and external gates..

→ complete the truth table

84-2-1 A B C D	Excess-3 e3 e2 e1 e0
0 0 0 0 0	0 0 1 1
0 1 1 1 7	0 1 0 0
0 1 1 0 6	0 1 0 1
0 1 0 1 5	0 1 1 0
0 1 0 0 4	0 1 1 1
1 0 1 1 11	1 0 0 0
1 0 1 0 10	1 0 0 1
1 0 0 1 9	1 0 1 0
1 0 0 0 8	1 0 1 1
1 1 1 1 15	1 1 0 0

$$e_3 = A$$

$$e_3 = \sum m(\overset{8,9,10,11,15}{\cancel{0,1,2,3,4}}) = \pi M(5 \text{ terms})$$






$$e_2 = \sum m(\overset{4,5,6,7,15}{\cancel{0,1,2,3,8}}) = B$$

$$e_1 = \sum m(\overset{0,4,5,8,9}{\cancel{1,2,3,6,7}}) = \bar{C}$$

$$e_0 = \sum m(\overset{0,4,6,8,10}{\cancel{1,3,5,7,9}}) = \bar{D}$$

$$e_3(A, B, C, D)$$

Code converter design....

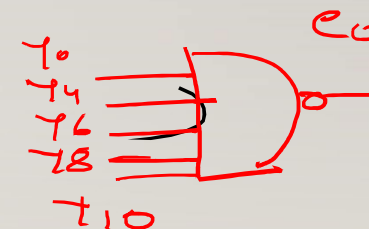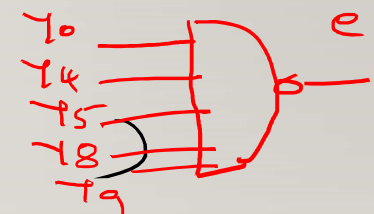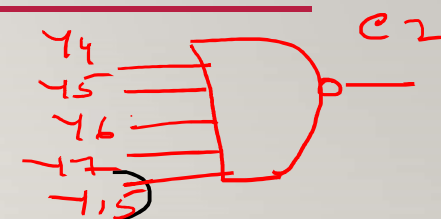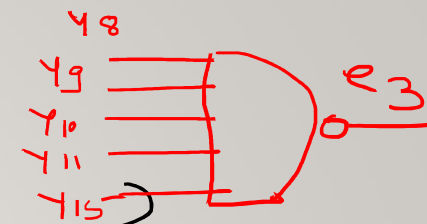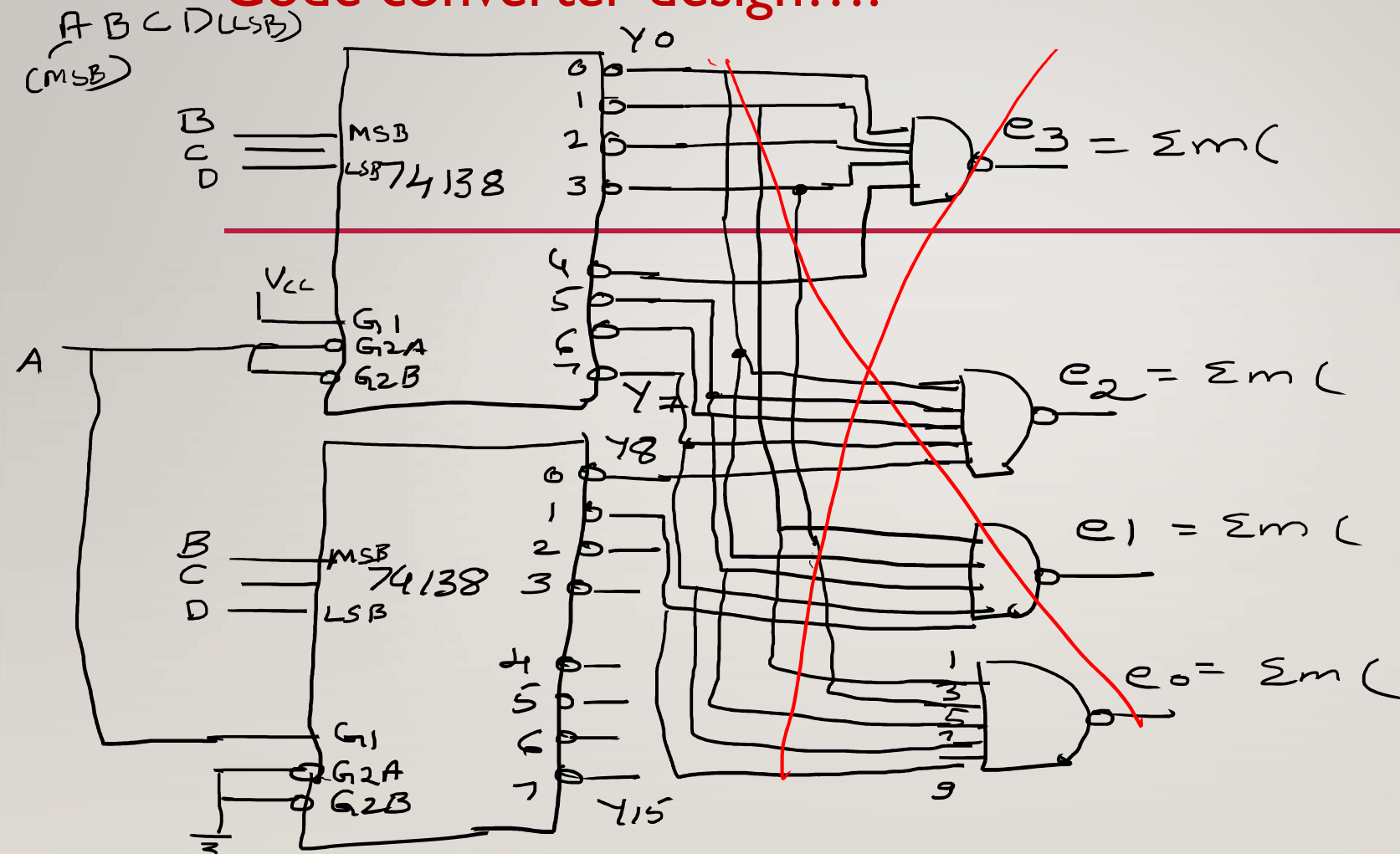

Code converter design...

Design $f(x,y,z) = x' + y'z$ using 3-to-8 line decoder and external gates.

$$f(x,y,z) =$$


assumed as active high o/p

Minterms for x' ($x=0$, y,z -don't care) = $\sum m(0,1,2,3)$

$$\begin{array}{ccc} x & y & z \\ 0 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \end{array} \quad \bar{y}z (x=0 \text{ or } 1, y=0 \text{ \& } z=1) = 1, 5$$

$$f(x,y,z) = \bar{x} + \bar{y}z = \sum m(0,1,2,3,5) = \pi m(4,6,7)$$

Can also be written from truth table

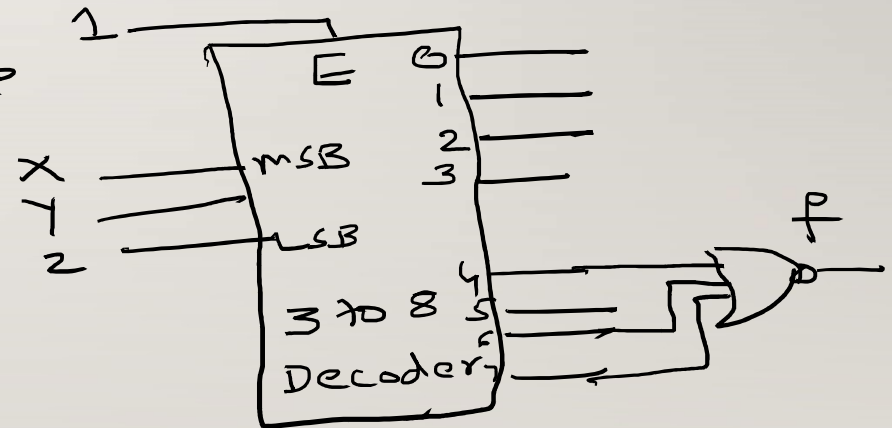

ENCODER:

- Combinational circuit that performs inverse operation of a decoder.
- Encoder has 2^n (or fewer) input lines and n output lines. Ex: 4-to-2 line, 8-to-3 line...etc
- 4-to-2 encoder is given below:
 2^2 to 2


Truth table

Inputs				Outputs	
D_0	D_1	D_2	D_3	x	y
1	0	0	0	0	0
0	1	0	0	0	1 ✓
0	0	1	0	1 } ✓	0 ✓
0	0	0	1	1 } ✓	1 ✓

$$X = D_2 + D_3$$

$$Y = D_1 + D_3$$

Circuit

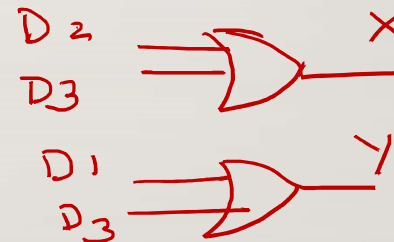



Write the truth table and circuit for 8-to-3 line encoder

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	X	Y	Z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$X = D_4 + D_5 + D_6 + D_7$$

$$Y = D_2 + D_3 + D_6 + D_7$$

$$Z = D_1 + D_3 + D_5 + D_7$$

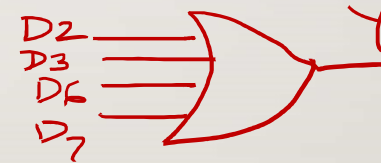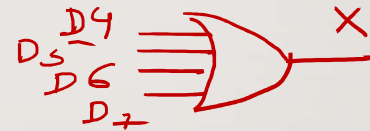

Design a 4-to-2 line priority encoder


$$D_0 < D_1 < D_2 < D_3$$

D_0	D_1	D_2	D_3	X	Y	V (Valid)
0	0	0	0	0	0	0
1	0	0	0	0	0	1
0	1	0	0	0	1	1
0	0	1	0	1	0	1
0	0	0	1	1	1	1


$$V = D_0 + D_1 + D_2 + D_3$$

$$X = D_3 + D_2 \overline{D_3} = D_2 + D_3$$
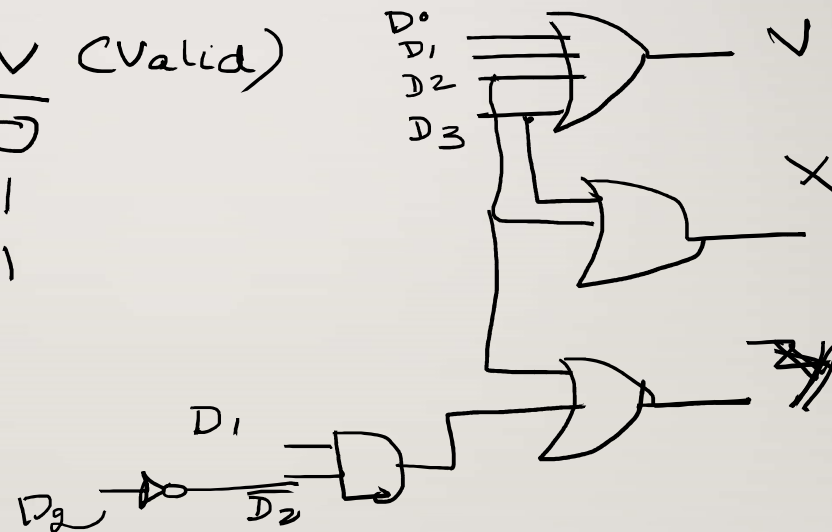
$$Y = D_1 \overline{D_2} \overline{D_3} + D_3 = D_3 + D_1 \overline{D_2}$$



4-to-2 line priority encoder contd...

 

-
- Any questions?