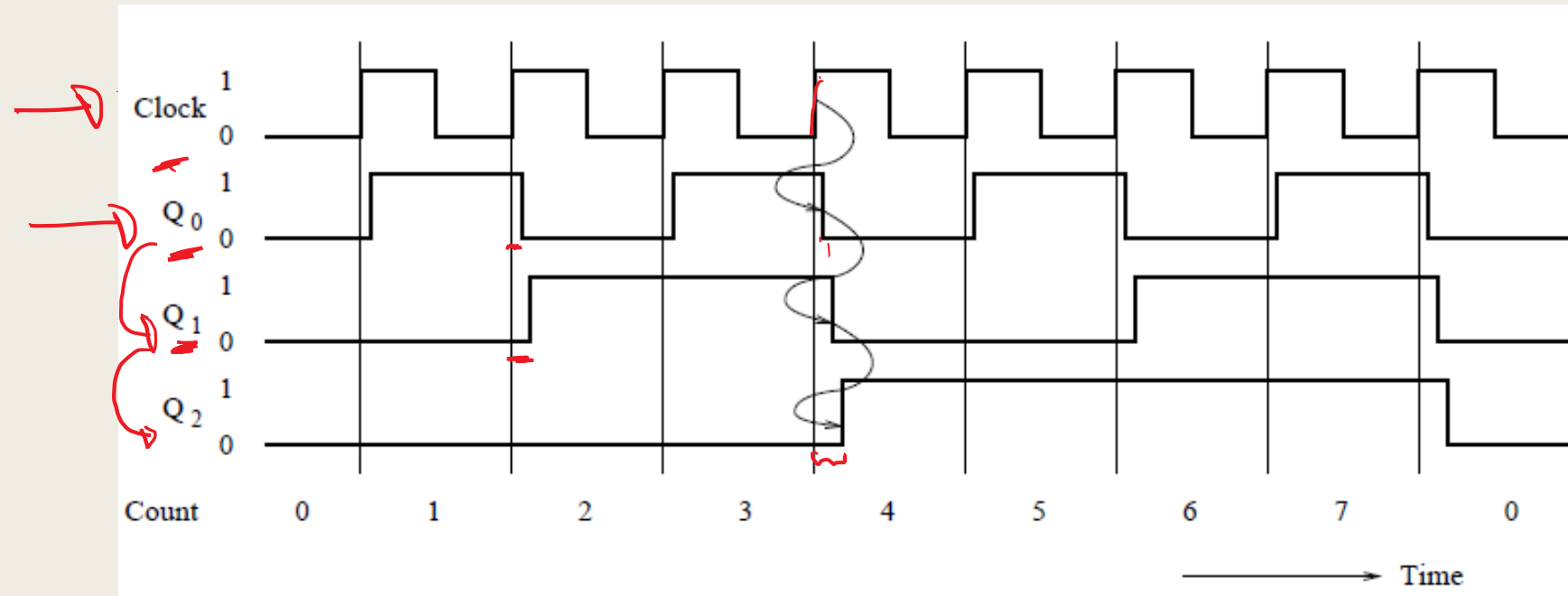


Synchronous counters

- Limitations of asynchronous counters
- Synchronous counter design
- Synchronous counter IC

Limitation of asynchronous counters



- Limitations:
1. Not suitable for high frequency applications
 2. Not suitable for higher mod counters


Synchronous counter design

- All the flip flops are clocked simultaneously using same clock.
- Suitable for high frequency applications
- Designed using sequential circuit design process which can be used for any synchronous circuit designs

1. Design 2-bit synchronous binary UP counter using T ffs

- Counter states: 00 → 01 → 10 → 11

State diagram

 


State table


Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

$$TA_1 = A_0$$


$$TA_0 = 1$$

 

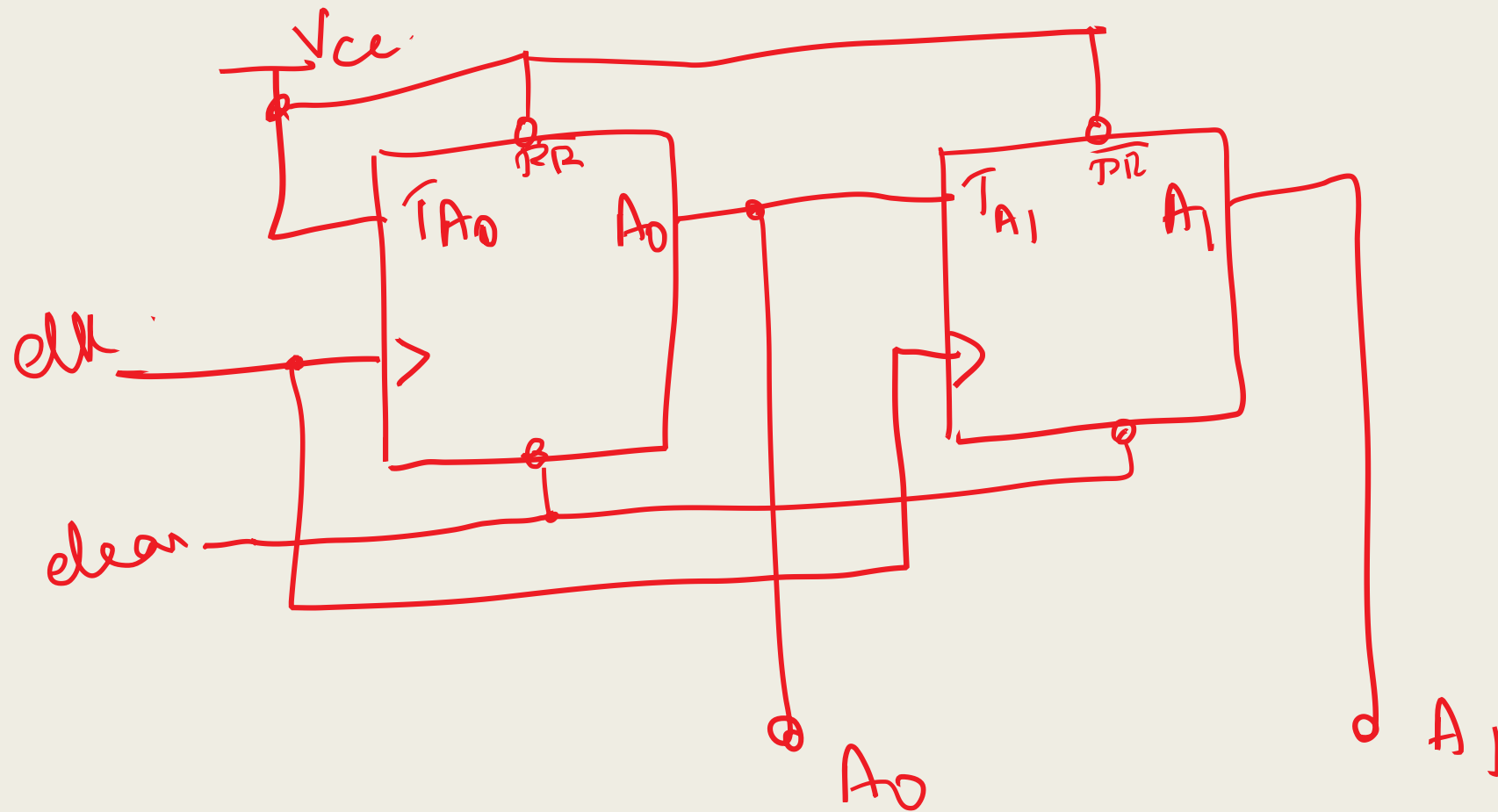2-bit synchronous binary UP counter using T ffs : circuit diagram



 2. Design 2-bit synchronous binary UP counter using JK ffs



$J_1 = Q_0$

Q_1	0	1
Q_0	0	1
	0	1
	X	X

$J_1 = Q_0$

$K_1 = Q_0$

Q_1	0	1
Q_0	0	1
	0	1
	X	X

$K_1 = Q_0$


$J_0 = 1$ $K_0 = 1$

P.S.	N.S	$J_1 K_1$	$J_0 K_0$
$Q_1 Q_0$	$Q_1 Q_0$		
0 0	0 1	0 X	1 X
0 1	1 0	1 X	X 1
1 0	1 1	X 0	1 X
1 1	0 0	X 1	X 1

FT of JK FF.

P.S	N.S	$J K$
0 → 0	0 0	0 X
0 → 1	1 0	1 X
1 → 0	0 1	X 1
1 → 1	1 1	X 0

 2-bit synchronous binary UP counter using JK ffs contd..



3. Design 3-bit synchronous binary UP counter (MOD 8) using SR ffs



FT of SR FF

P.S.	N.S.	S_2	R_2	S_1	R_1	S_0	R_0
$Q_2 Q_1 Q_0$	$Q_2 Q_1 Q_0$						
0 0 0	0 0 1	0	X	0	X	1	0
0 0 1	0 1 0	0	X	1	0	0	1
0 1 0	0 1 1	0	X	X	0	1	0
0 1 1	1 0 0	1	0	0	1	0	1
1 0 0	1 0 1	X	0	0	X	1	0
1 0 1	1 1 0	X	0	1	0	0	1
1 1 0	1 1 1	X	0	X	0	1	0
1 1 1	0 0 0	0	1	0	1	0	1

	S	R
0 → 0	0	0
0 → 1	0	1
1 → 1	0	0
1 → 0	1	0

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	0	0	1	0
1	X	X	0	X

$$S_2 = \overline{Q_2} Q_1 Q_0$$

$$R_2 = Q_2 Q_1 Q_0$$

3-bit synchronous binary UP counter (MOD 8) using SR ffs

$$S_2 =$$

$$R_2 =$$

$$S_1 =$$

$$R_1 =$$



$$S_0 =$$

$$R_0 =$$

4. Draw the circuit of 3-bit synchronous binary up counter (MOD 8) using T ffs

- Analyse the previous examples and draw the circuit directly without the design steps.

  5. Design 2-bit synchronous binary down counter (MOD 4) using D ffs




P.S	N.S		
$Q_1 Q_0$	$Q_1 Q_0$	D_1	D_0
00	11	1	1
01	00	0	0
10	01	0	1
11	10	1	0

$$D_1 =$$

$$D_0 =$$

 2-bit synchronous binary down counter (MOD 4) using D ffs



6. Design 3-bit synchronous binary down counter (MOD 4) using D ffs

P.S.	N.S.			
$Q_2 Q_1 Q_0$	$Q_2 Q_1 Q_0$	D_2	D_1	D_0
000	111	1	1	1
001	000	0	0	0
010	001	0	0	1
011	010	0	1	0
100	011	0	1	1
101	100	1	0	0
110	101	1	0	1
111	110	1	1	0

D_2 :-

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	1	0	0	0
1	0	1	1	1

$$D_2 = \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 + Q_2 Q_0 + Q_2 Q_1$$

D_1 :-

$Q_2 \backslash Q_1 Q_0$	00	01	10	11
0	1	0	1	0
1	1	0	1	0

$$D_1 = \bar{Q}_1 \bar{Q}_0 + Q_1 \bar{Q}_0$$

D_0 :-

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	1	0	0	1
1	1	0	0	1

$D_0 = \bar{Q}_0$

7. Design decade (BCD) synchronous up counter (MOD 10) using T ffs

■ (0→1→2→3→4→5→6→7→8→9→0)

4-bits -
FFs T-FF

P.S				N.S				T ffs				
Q_3	Q_2	Q_1	Q_0	Q_3	Q_2	Q_1	Q_0	T_3	T_2	T_1	T_0	
0	0	0	0	0	0	0	1	0	0	0	1	$T_3 =$
0	0	0	1	0	0	1	0	0	0	1	1	
0	0	1	0	0	0	1	1	0	0	0	1	$T_2 =$
0	0	1	1	0	1	0	0	0	1	1	1	
0	1	0	0	0	1	0	1	0	0	0	1	$T_1 =$
0	1	0	1	0	1	1	0	0	0	1	1	
0	1	1	0	0	1	1	1	0	0	0	1	$T_0 =$
0	1	1	1	1	0	0	0	1	1	1	1	
1	0	0	0	1	0	0	1	0	0	0	1	
1	0	0	1	0	0	0	0	1	0	0	1	

Decade (BCD) synchronous up counter contd..

$Q_3 \backslash Q_2 \quad Q_1 \quad Q_0$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	0	1	X	X

$$T_3 = \underline{Q_3 Q_0 + Q_1 Q_0}$$


$Q_3 \backslash Q_2 \quad Q_1 \quad Q_0$	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	X	X	X	X
10	0	0	X	X

$Q_3 \backslash Q_2 \quad Q_1 \quad Q_0$	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	X	X	X	X
10	0	0	X	X

$$T_2 = Q_1 Q_0$$

$$T_1 = \underline{\underline{\overline{Q_3} Q_0}}$$

$$T_0 = \underline{\underline{1}}$$

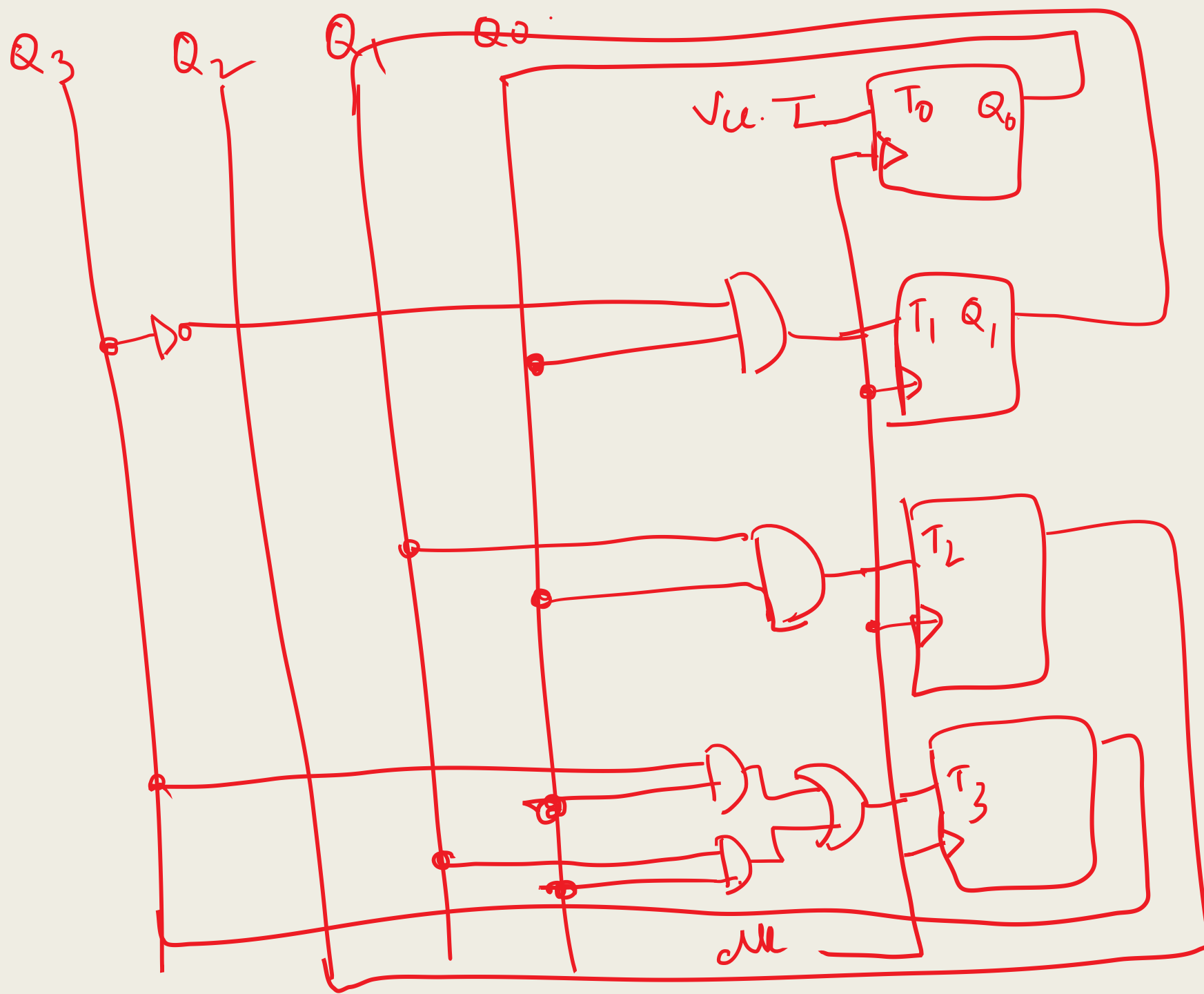

- Questions: ?