
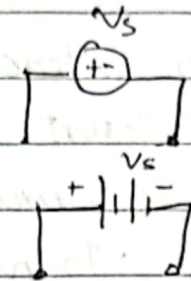


## ACTIVE ELEMENTS
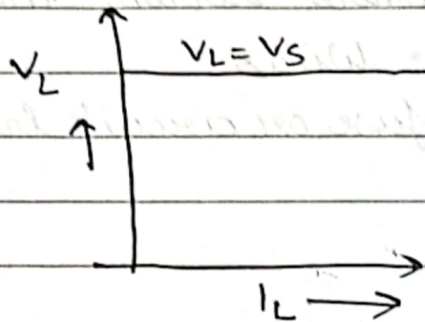
### Voltage Source



→ Ideal: Constant

- maintains constant terminal voltage irrespective of current load.
- Internal Resistance  $R_s = 0$ .



→ Practical: Real.

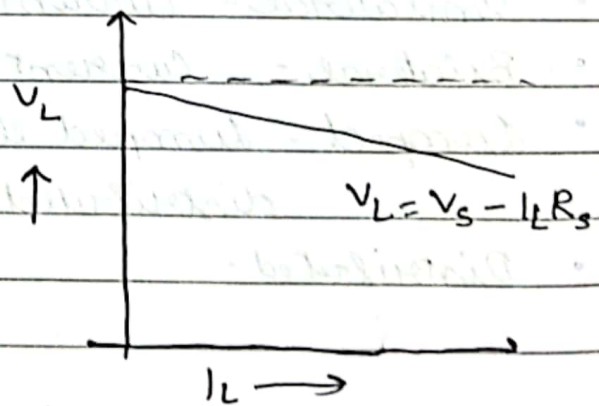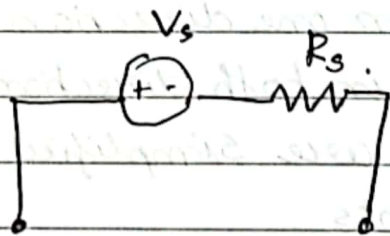
- Terminal voltage changes based on connected load.
- Internal Resistance  $R_s \neq 0$



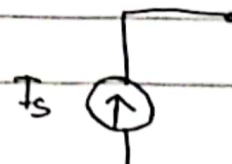
### Current Source

→ Ideal: Constant.



- Maintains constant current irrespective of load connected.
- Internal Resistance  $R_s = \infty$



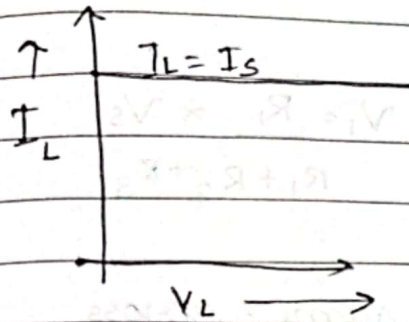

→ Practical: Real.

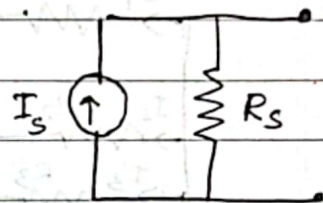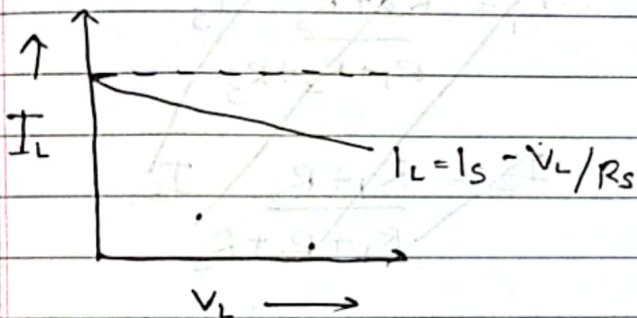- Output current changes based on connected load.
- Internal Resistance  $R_s < \infty$ .



## PASSIVE ELEMENTS

### RESISTOR.

- Passive electric device that dissipates energy.

- Resistance

Symbol:  $R$

Unit:  $\Omega$

Power consumed:  $I^2 R$ .

- Conductance


- Reciprocal of resistance

- Symbol:  $G$ .

- Unit:  $S$ ,  $\Omega^{-1}$



## Series Resistance.

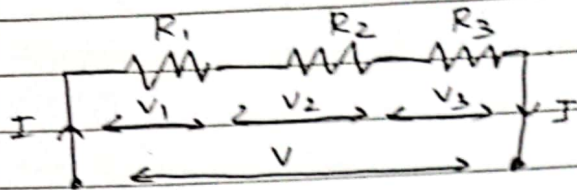


$$V_1 = \frac{R_1}{R_1 + R_2 + R_3} \times V_s$$

$$V = V_1 + V_2 + V_3$$

I is same across

$$R_{eq} = R_1 + R_2 + R_3$$

## Parallel Resistances

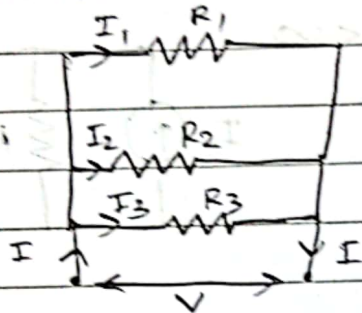

$$I_1 = \frac{R_2 + R_3}{R_1 + R_2 + R_3} I_s$$

$$I_2 = \frac{R_1 + R_3}{R_1 + R_2 + R_3} I_s$$


V is same

$$I = I_1 + I_2 + I_3$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
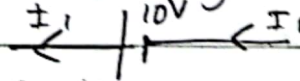
## DELIVERING AND ABSORBING POWER BY A SOURCE

- A battery is discharging (delivering power/energy) if current is coming out through +ve terminal.



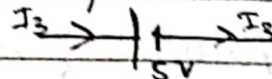- A battery is charging (absorbing power/energy) if current flowing into positive (+ve) terminal.



- When current flows through a resistor, power is dissipated.

- Horizontal plane and vertically plane of symmetry for solving resistance circuits.


## INDUCTOR.

stores electrical energy in magnetic field when current flows through it. A coil of wire wound around a core.

Inductance - property opposing rate of change of current.

Symbol:  $L$

Unit: Henry (H).

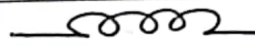

Voltage across inductor  $\propto$  rate of change of current.

$$V_L = L \frac{dI}{dt}$$

Inductive circuit:

$$L = \frac{\mu_0 AN^2}{l} \quad (\text{Self inductance of air core inductor})$$

$l$  = length of the magnetic circuit in m.

$A$  = cross sectional area in sq. m.

$\mu_0$  = permeability of air =  $4\pi \times 10^{-7}$

$N$  = number of turns in the coil.

Series.

$$L_{eq} = L_1 + L_2 + L_3$$

Parallel.

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$



- Instantaneous Power.

$$p = V_L i = L \frac{di}{dt}$$

- Energy absorbed in dt time

$$dw = L i di$$

- Energy absorbed when current inc from 0 to I (by the magnetic circuit)

$$W = \int_0^I L i di = \frac{1}{2} L I^2$$

## CAPACITOR.

Stores energy in the electric field.

Capacitance: Property opposing rate of change of voltage.

Symbol: C

Unit: Farad (F)

Capacitive current  $\propto$  rate of change of voltage.

$$i_c = C \frac{dv_c}{dt}$$

Charge stored when plates are at const voltage.

$$Q = CV$$

- Electric field strength.

$$E = \frac{V}{d} \text{ V/m}$$

- Capacitance of parallel plate capacitor.

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

- Electric flux density.

$$D = \frac{C}{A} \text{ C/m}^2$$

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

Series .

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

Parallel

$$C_{eq} = C_1 + C_2 + C_3$$

- Instantaneous Power.

$$p = V_c \times i = C V_c \frac{dV_c}{dt}.$$

- Energy supplied during 'dt' time.

$$dW = C V_c dV_c.$$

- Energy stored when potential rises from 0 to V  
 $W = \int_0^V C V_c dV = \frac{1}{2} C V^2 \text{ joules.}$