

Illustration 1


Two incandescent bulbs have the following ratings:

Bulb-1: 120 V, 60 W

Bulb-2: 240 V, 480 W

- a) Both of them are connected in series across a voltage source.
- Which bulb will glow brighter and why?
 - What is the maximum voltage that can be applied so that none of the bulbs fuse?
- b) Now both of them are connected in parallel across a voltage source.
- Which bulb will glow brighter and why?
 - What is the maximum voltage that can be applied so that none of the bulbs fuse?

Assume that the incandescent bulbs are purely resistive.

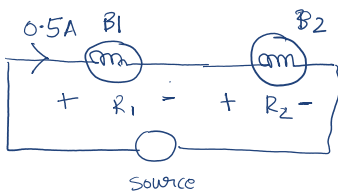(a) Series Connection


max. current permitted = 0.5A

$$P_1 = (0.5)^2 \times R_1 = (0.5)^2 \times 240 = 60 \text{ W}$$

$$P_2 = (0.5)^2 \times R_2 = (0.5)^2 \times 120 = 30 \text{ W}$$

(i) $\therefore P_1 > P_2$, B1 will glow brighter

$$\begin{aligned} \text{(ii)} \quad V_{\text{Total}} &= (0.5 \times R_1) + (0.5 \times R_2) \\ &= (0.5 \times 240) + (0.5 \times 120) \\ &= 180 \text{ Volts} \end{aligned}$$

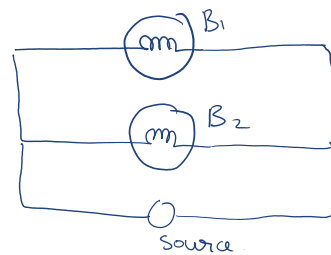(b) Parallel Connection

(i) \rightarrow max. voltage permitted = 120V \rightarrow rating of B1

$$P_1 = \frac{120^2}{240} = 60 \text{ W}$$


$$P_2 = \frac{120^2}{120} = 120 \text{ W}$$

(ii) $\rightarrow \therefore P_2 > P_1$, B2 will glow brighter

Bulb 1: 120V, 60W	Bulb 2: 240V, 480W
$P = VI$	
$P = I^2 R$	
$P = \frac{V^2}{R}$	
$I_1 = \frac{P_{r1}}{V_{r1}} = \frac{60}{120} = 0.5 \text{ A}$	$I_{r2} = \frac{P_{r2}}{V_{r2}} = \frac{480}{240} = 2 \text{ A}$
$R_1 = \frac{V_{r1}^2}{P_{r1}} = \frac{120^2}{60} = 240 \Omega$	$R_2 = \frac{V_{r2}^2}{P_{r2}} = \frac{240^2}{480} = 120 \Omega$
or $R_1 = \frac{P_{r1}}{I_{r1}^2} = \frac{60}{(0.5)^2} = 240 \Omega$	or $R_2 = \frac{P_{r2}}{I_{r2}^2} = \frac{480}{(2)^2} = 120 \Omega$

Illustration 2

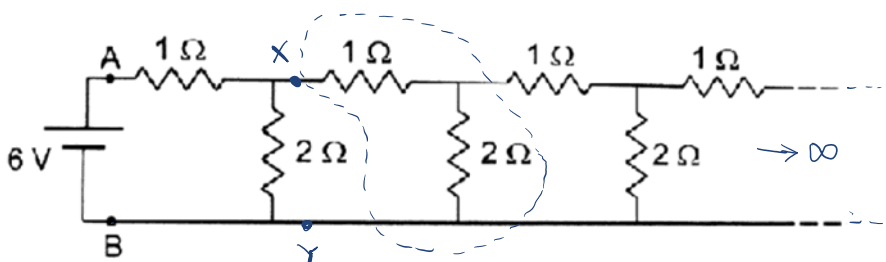What is the equivalent resistance across the terminals A & B in the network shown?




$$\text{Let } R_{AB} = x \Omega$$

$$\text{Then } R_{XY} = x \Omega$$

Replace the circuit XY onwards with $x \Omega$

$$R_{AB} = 1 \Omega \text{ in series with } (2 \parallel x) \Omega$$

$$R_{AB} = 1 + \frac{2x}{2+x}$$

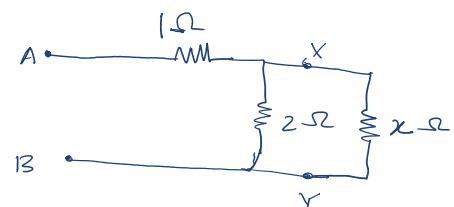

$$x = \frac{1 + \frac{2x}{2+x}}{2+x} \quad \text{or} \quad x^2 - x - 2 = 0$$


$$x^2 - 2x + x - 2 = 0 \quad \text{or} \quad x = 2 \quad \text{and} \quad x = -1 \rightarrow \text{Neglected}$$

$$R_{AB} = x \Omega = 2 \Omega$$

Illustration 3

15 resistors are connected as shown in the diagram. Each of the resistors has resistance 1Ω .

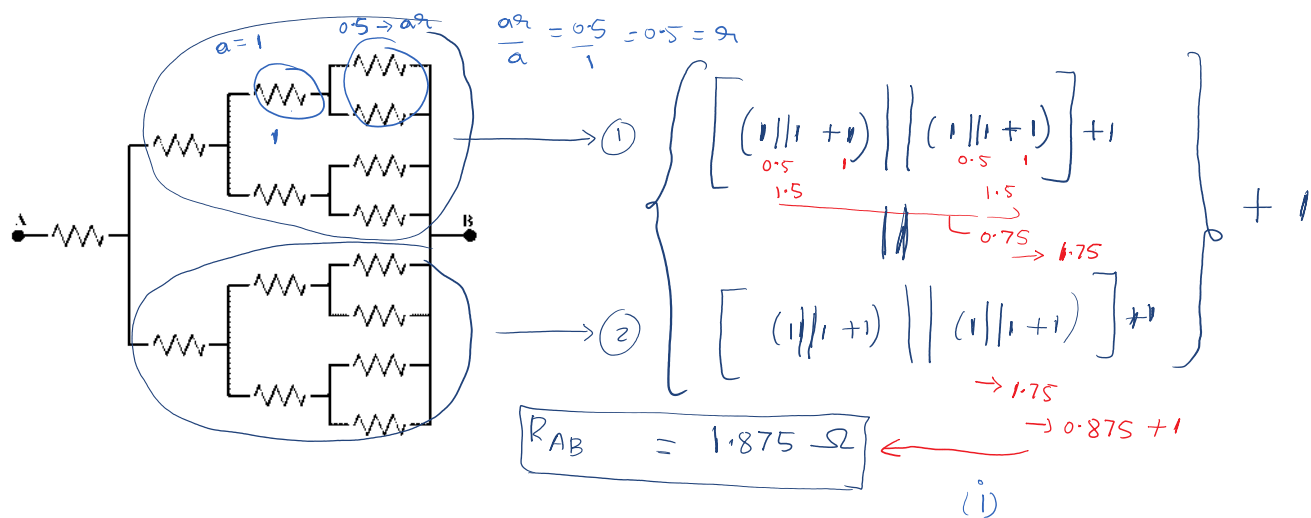- Find the equivalent resistance of the network between A & B.
- What will be the equivalent resistance of this network if the resistors arranged in the sequence extends to infinity?



Geometric Sequence or progression

$$a, ar, ar^2, ar^3, \dots, ar^{n-1}$$

$$1^{\text{st}} \text{ term} = a$$

$$n^{\text{th}} \text{ term} = ar^{n-1}$$

$$\text{Sum of } n \text{ terms} = \frac{a(1-r^n)}{1-r}$$

Sum up to ∞

$$S_{\infty} = \frac{a}{1-r}$$


Here, $a = 1$

$$r = \frac{1}{2}$$

$$S_{\infty} = \frac{1}{1 - \frac{1}{2}} = 2 \Omega \quad \text{(ii)}$$

Illustration 4

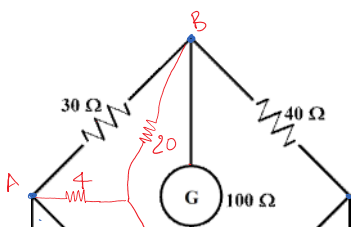For the circuit shown, determine the total power supplied by the source using star-delta transformation.





$$R_{AB} = 30 \Omega$$

$$R_{BC} = 100 \Omega$$

$$R_{CA} = 20 \Omega$$
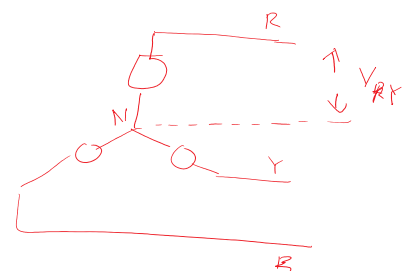
$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{BC} + R_{CA}} = \frac{30 \times 20}{30 + 100 + 20} = \frac{600}{150} = 4 \Omega$$




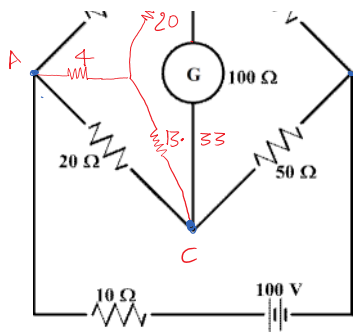

$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{BC} + R_{CA}} = \frac{30 \times 20}{30 + 100 + 20} = \frac{600}{150} = 4 \Omega$$

$$R_B = \frac{R_{AB} \times R_{BC}}{R_{AB} + R_{BC} + R_{CA}} = \frac{30 \times 100}{150} = 20 \Omega$$
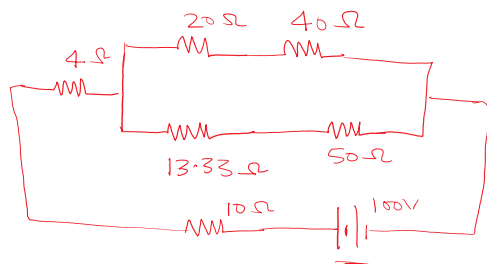
$$R_C = \frac{R_{CA} \times R_{BC}}{R_{AB} + R_{BC} + R_{CA}} = \frac{20 \times 100}{150} = 13.33 \Omega$$



$$R_{Total} = (4 + 10) + ((20 + 40) \parallel (13.33 + 50))$$

$$R_{Total} = 44.8107 \Omega$$





$$P = \frac{V^2}{R} = \frac{100^2}{44.8107} = 223.1608 \text{ Watts}$$

$$= I^2 R = \left(\frac{100}{44.8107} \right)^2 \times 44.8107 = 223.1608 \text{ W}$$

$$= VI = (100) \times \left(\frac{100}{44.8107} \right) = 223.1608 \text{ W}$$

Illustration 5

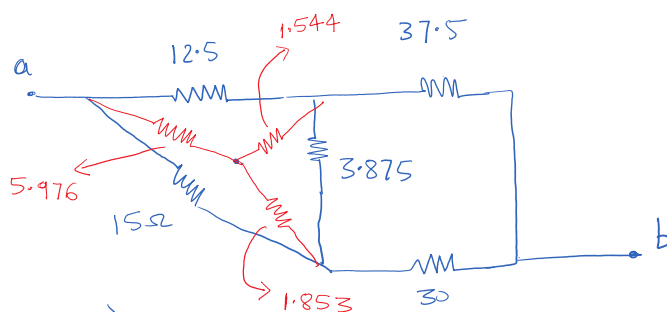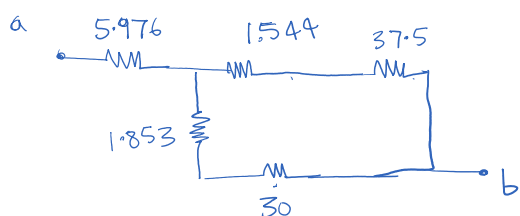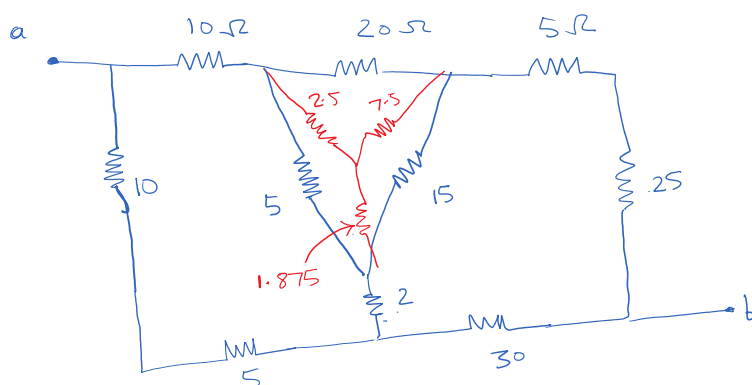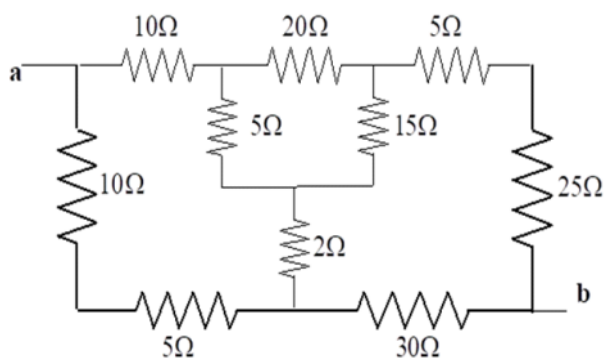Determine the resistance between terminals a & b of the network shown in figure, using Star-Delta transformation.



$$R_{ab} = 5.976 + ((15.44 + 37.5) \parallel (1.853 + 30))$$

$$R_{ab} = 23.518 \Omega$$