
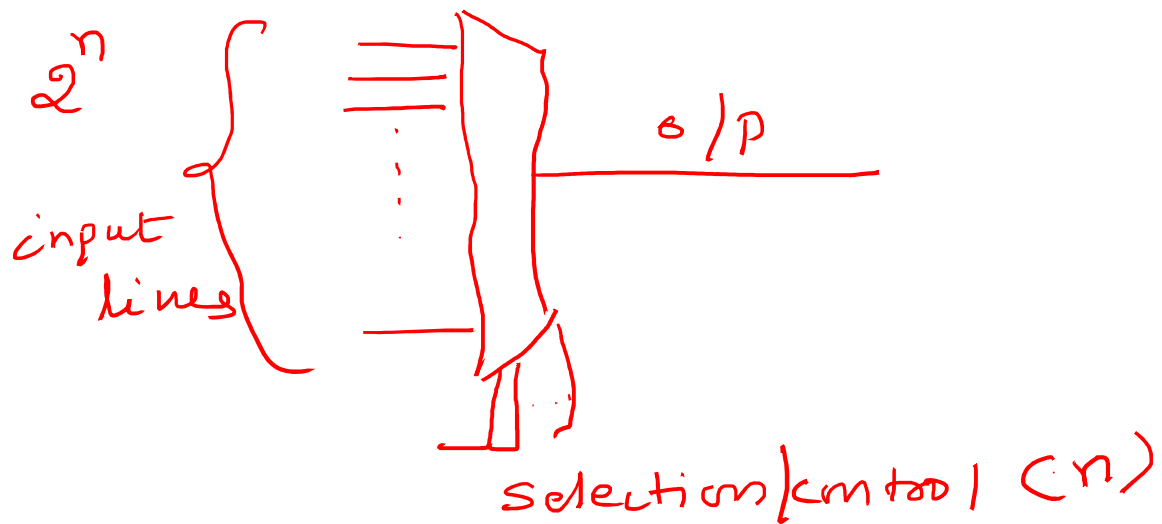


Multiplexers

Students are advised to write down the notes for every lecture

Multiplexer

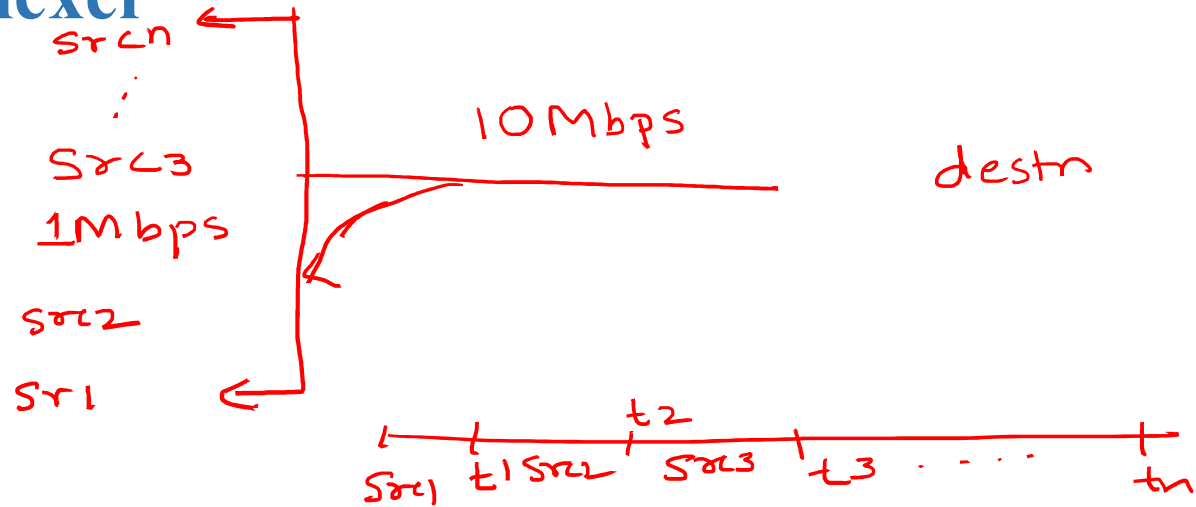

Multiplexer

- Multiplexer is an useful MSI device and are also called as data selectors.
- Multiplexer selects one of its 2^n input line and directs it to a single output line .
- n-bit select lines decide which input line is to be selected.
- Examples: 2-to-1 line MUX, 4-to-1 line MUX, 8-to-1 line MUX, 16-to-1 line MUX.

2^n : $n \Rightarrow$ select lines

2 : 1



4 : 1

8 : 1

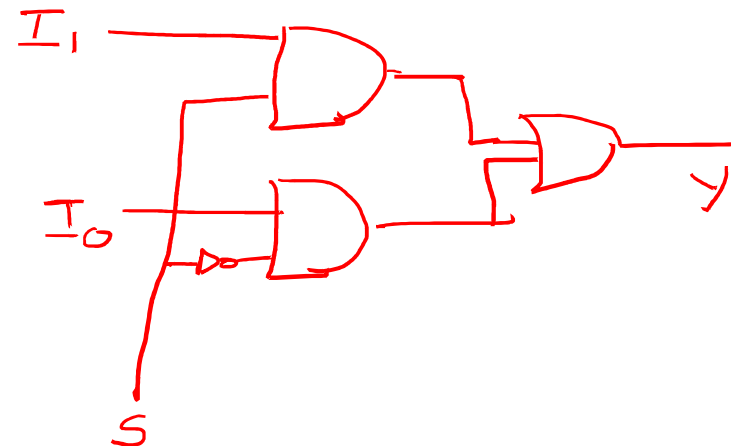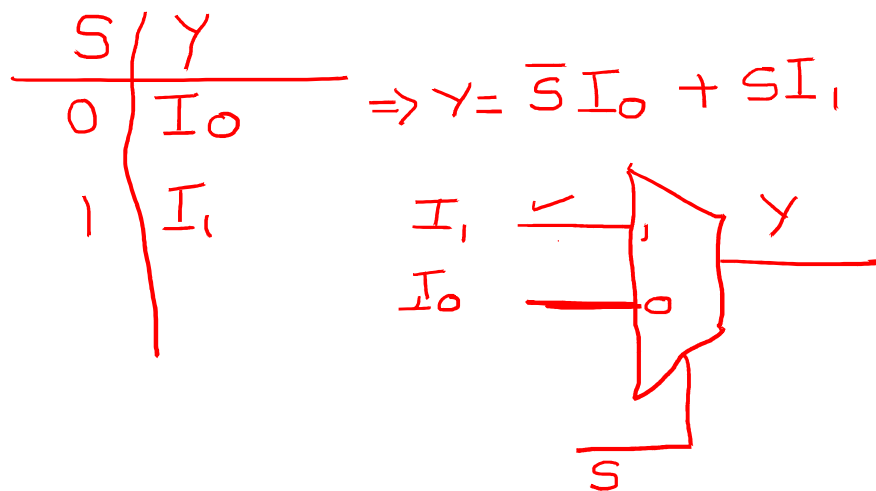
16 : 1

2-to-1 line MUX


- S- selection input, y is the output, I1 and I0 are inputs
- Symbol/block diagram, function table, output expressions and circuit is given :



2-to-1 line MUX

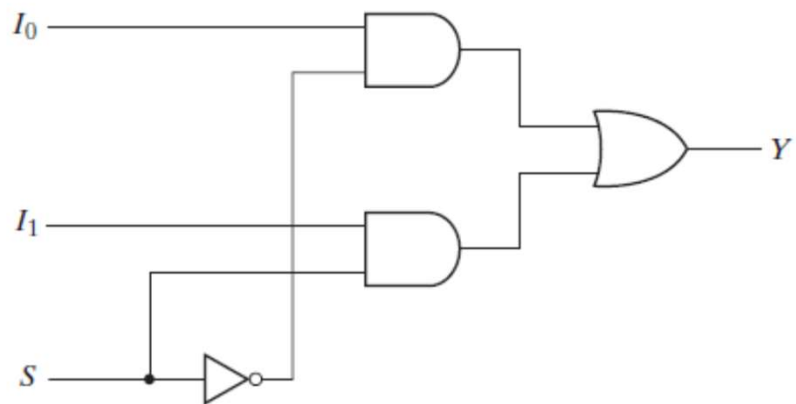


(a) Logic diagram

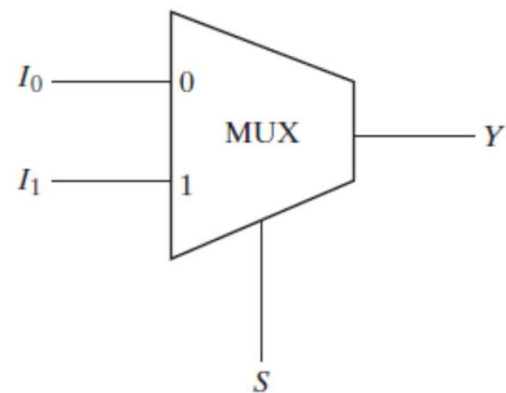

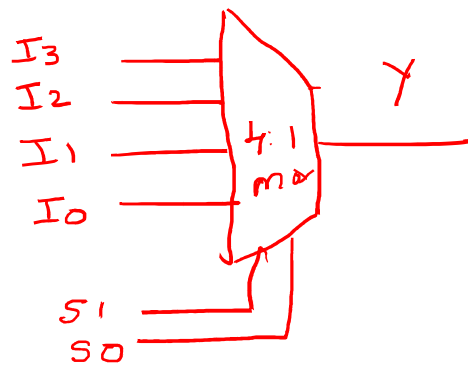(b) Block diagram

4-to-1 line multiplexer

- Write the Symbol/block diagram, Function table, output expressions and circuit.



S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


Assume

$$I_3 = 1 \quad \textcircled{I_2 = 1} \quad I_1 = 0 \quad I_0 = 0$$

$$S_1, S_0 = 10, \quad Y = ? \quad \underline{1}$$

$$Y = \bar{S}_1 \bar{S}_0 \cdot I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 \cdot I_2 + S_1 S_0 I_3$$

4-to-1 line multiplexer

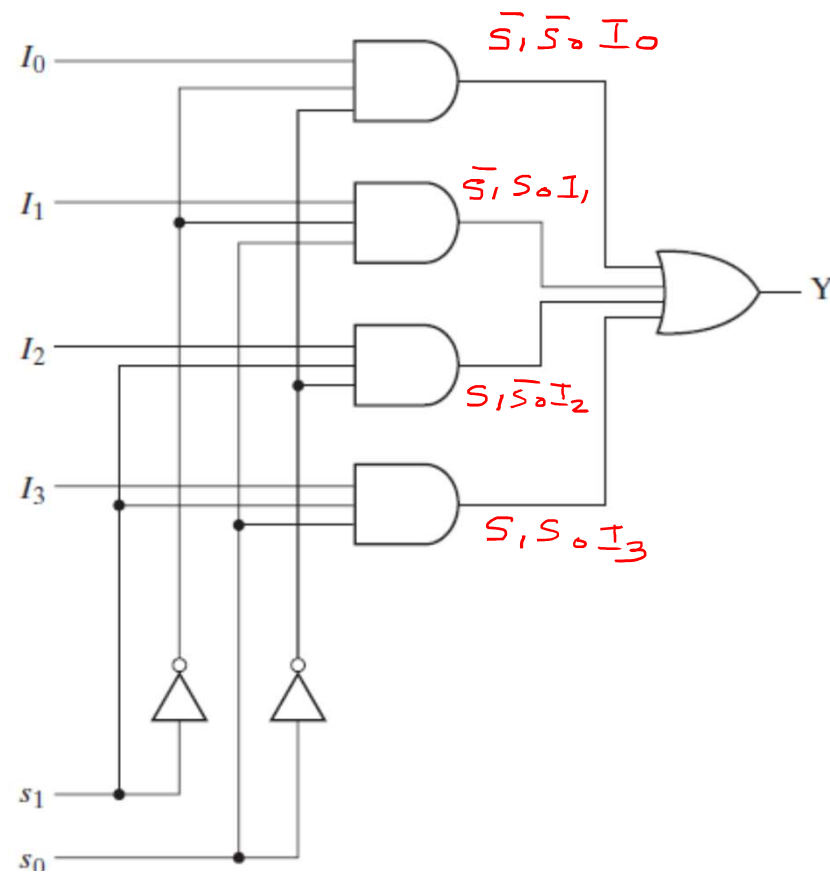

8-to-1 line multiplexer

- Write the Symbol/block diagram, function table, output expressions and circuit

select lines: S_2, S_1, S_0

$$Y = \bar{S}_2 \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_2 \bar{S}_1 S_0 I_1 + \bar{S}_2 S_1 \bar{S}_0 I_2 + \bar{S}_2 S_1 S_0 I_3 \\ S_2 \bar{S}_1 \bar{S}_0 I_4 + S_2 \bar{S}_1 S_0 I_5 + S_2 S_1 \bar{S}_0 I_6 + S_2 S_1 S_0 I_7$$

→ Draw 8:1 mux circuit

Realize 4:1 using only 2:1 MUXs (Multiplexer tree)


For 4:1 mux

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

For 2:1 MUX


$$y = \bar{S}_0 I_0 + S_0 I_1$$
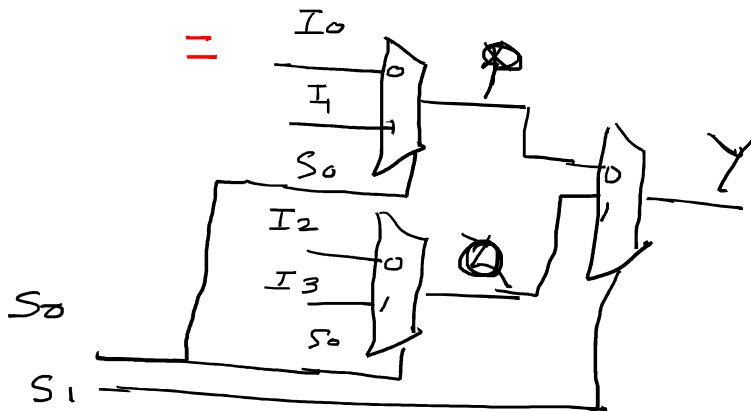
$$\rightarrow Y = \bar{S}_1 (\underbrace{\bar{S}_0 I_0 + S_0 I_1}_{2:1 \text{ mux}}) + S_1 (\underbrace{\bar{S}_0 I_2 + S_0 I_3}_{2:1 \text{ mux}}) = \bar{S}_1 \cdot \text{mux} + S_1 \cdot \text{mux}$$



3, 2:1 muxs

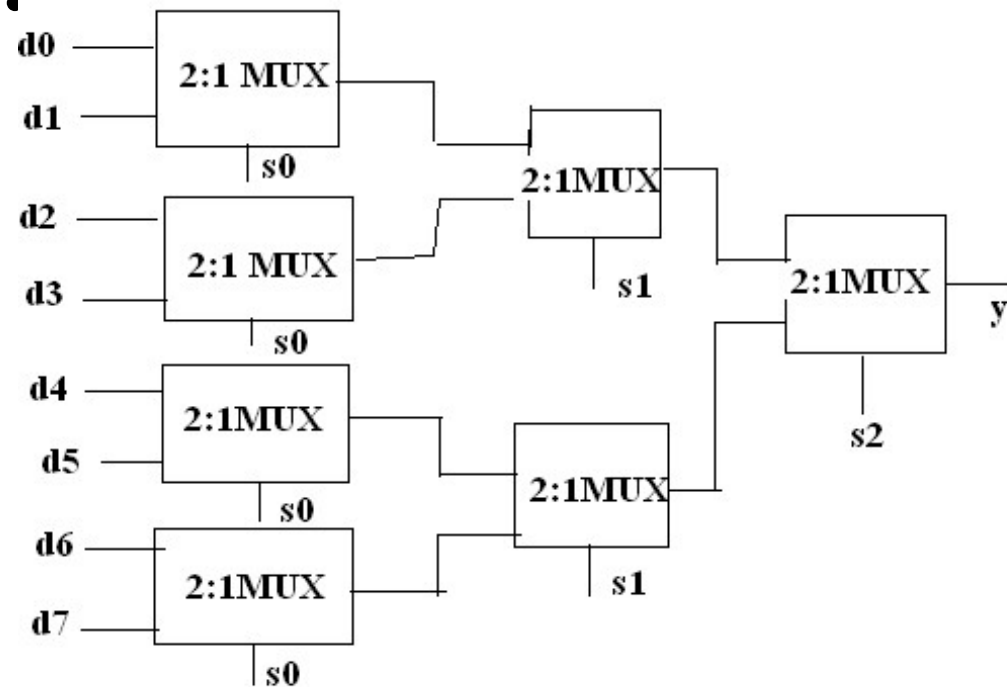Realize 8:1 using only 2:1 MUXs (Multiplexer tree)



$(4 + 2 + 1)$, 2:1 MUXs

2^n :1 MUX using
2:1 MUX
how many 2:1 MUX?
 $2^n - 1$ ← Ans?

Realize 8:1 using only 4:1 MUXs and 2:1 MUX

- select lines: $S_2S_1S_0$

$$Y = \bar{S}_2 \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_2 \bar{S}_1 S_0 I_1 + \bar{S}_2 S_1 \bar{S}_0 I_2 + \bar{S}_2 S_1 S_0 I_3 + S_2 \bar{S}_1 \bar{S}_0 I_4 + S_2 \bar{S}_1 S_0 I_5 + S_2 S_1 \bar{S}_0 I_6 + S_2 S_1 S_0 I_7$$


~~→ Draw 8:1 mux circuit~~ ^{4:1 mux} A

$$= \bar{S}_2 (\bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3) +$$

$$S_2 (\underbrace{\bar{S}_1 \bar{S}_0 I_4 + \bar{S}_1 S_0 I_5 + S_1 \bar{S}_0 I_6 + S_1 S_0 I_7}_{B})$$

$$= \overline{S_2} A + S_2 B$$


2:1 MUX

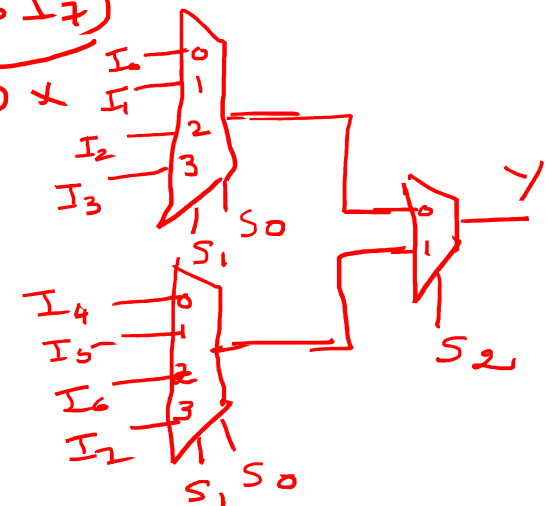

Realize each of the basic logic gates using 2:1 MUX

NOT $\Rightarrow Y = \bar{A}$

A	Y
0	1
1	0

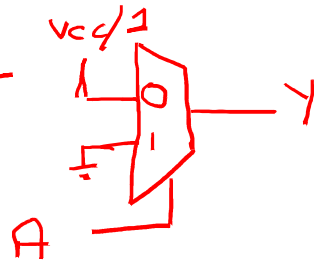


OR gate $Y = A + B$

if $A=0$ $Y=B$

A	B	Y
A=0 {	0 0	0
	0 1	1
A=1 {	1 0	1
	1 1	1

$Y=B$ for $A=0$, $Y=1$ for $A=1$


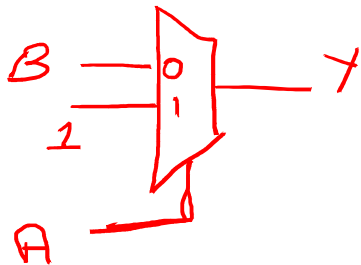


AND

$Y = AB$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$Y=0$ for $A=0$, $Y=B$ for $A=1$

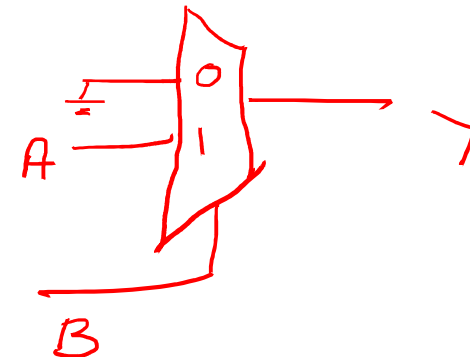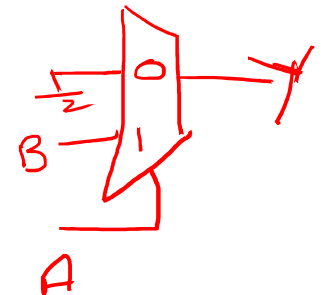


NAND gate using 2:1 MUXs

$$Y = \overline{A \cdot B}$$

A	B	Y
0	0	1
0	1	1
1	0	0
1	1	0

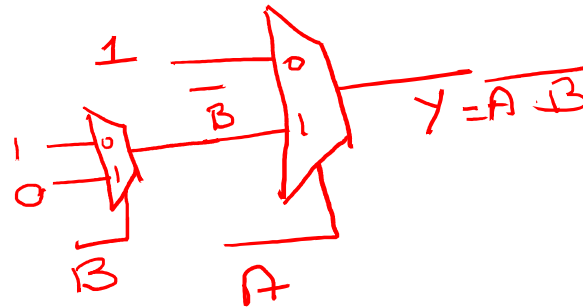
$\left. \begin{matrix} 1 & 1 \\ 1 & 1 \end{matrix} \right\} Y = 1$
 $\left. \begin{matrix} 0 & 0 \\ 0 & 0 \end{matrix} \right\} Y = \overline{B}$



Realize NOR, XOR

16-to-1 line multiplexer---Exercise for you

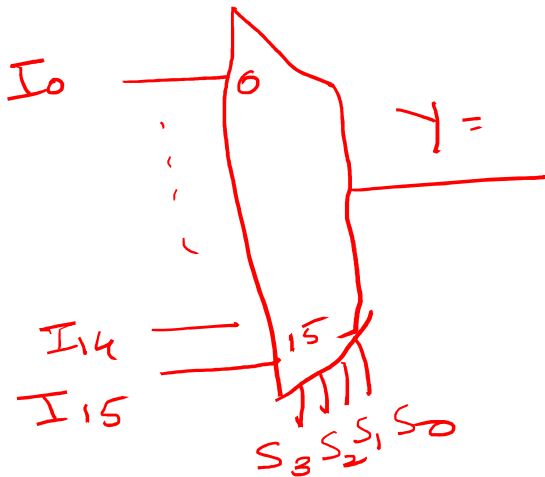- Write the Symbol/block diagram, function table, output expressions and circuit



Multiplexer application in logic design

- Implement the function $F(a,b,c) = \sum m(0,1,3,6,7)$ using

- 8:1 MUX only ✓



Equal to the no. of select lines

- ✓ Minimum no. of 4:1 MUXs only ~~is extra~~

4:1 MUX

	a	b	c	F
ab=00	0	0	0	1
	0	0	1	1
ab=01	0	1	0	0
	0	1	1	1
ab=10	1	0	0	0
	1	0	1	0
ab=11	1	1	0	1
	1	1	1	1

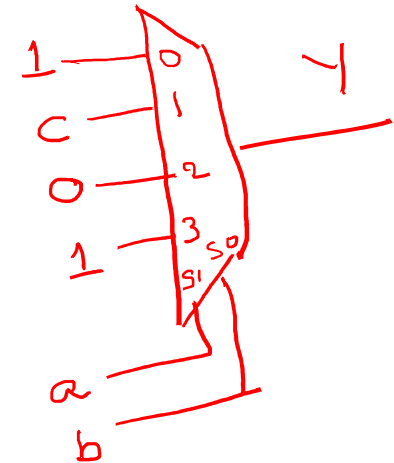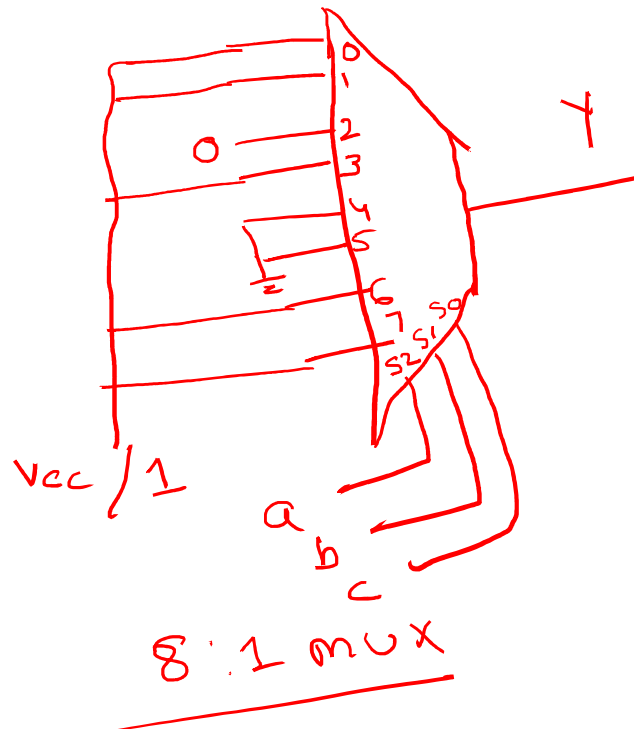Handwritten groupings from table:
 ab=00: F=1
 ab=01: F=c
 ab=10: F=0
 ab=11: F=1




Implement the function $F(a,b,c) = \sum m(0,1,3,6,7)$
using bc as selection lines for 4:1 mux

	$\bar{b}\bar{c}$	$\bar{b}c$	$b\bar{c}$	bc
\bar{a}	0 1	1 1	2 0	3 1
a	4 0	5 0	6 1	7 1
	$bc=00$	01	10	11

$$Y = \bar{a} \quad \bar{a} \quad a \quad 1$$




TT is new written

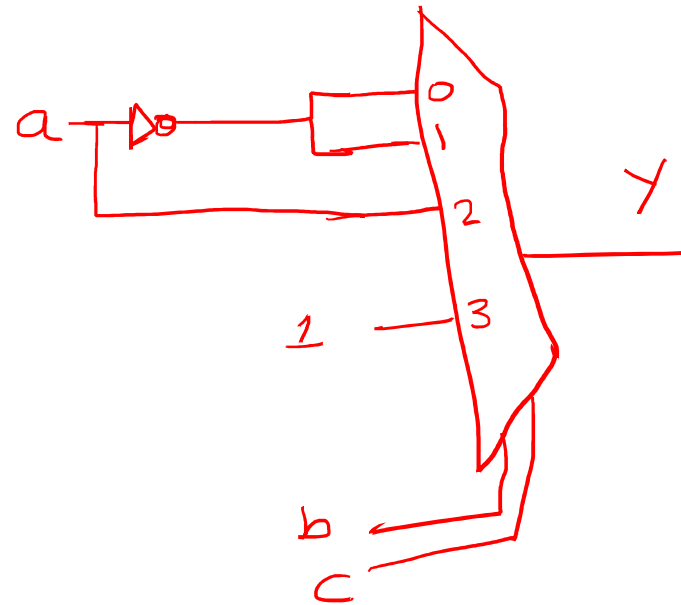

Implement the function $F(a,b,c,d) = \sum m(2,4,6,8, 9,11,14,15)$

• using

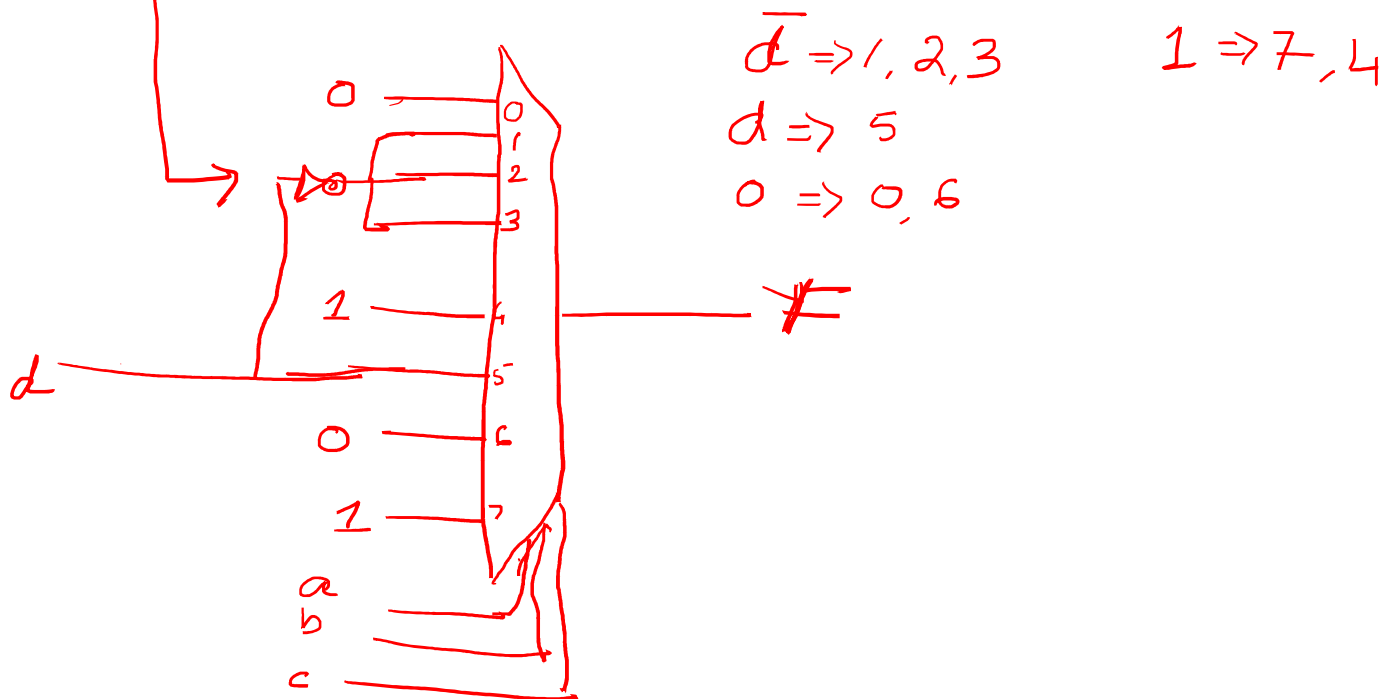- ✓ 8:1 MUX and one NOT gate ✓ *a, b, c as the selection inputs*
- . 4:1 MUX and external gates
- . 4:1 MUX and 2:1 MUXs only



$$F(a,b,c,d) = \sum m(2,4,6,8, 9,11,14,15)$$

a	b	c	d	F
$ab = 00$	0	0	0	0
	0	0	1	0
	0	1	0	1
	0	1	1	0
$ab = 01$	0	1	0	1
	0	1	1	0
	1	0	0	1
	1	0	1	1
	1	0	1	0
	1	1	0	0

$abc = 000$
 $F = \bar{c}$
 $ab = 10$
 $F = \bar{c}d$
 $F = \bar{d}$
 $ab = 11$
 $F = \bar{d}$
 $F = d$
 $F = \bar{d}$
 $F = \bar{d}$
 $F = 1$
 $\bar{c} + d$

a	b	c	d	F
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1


$8:1 \text{ mux}$
 $F = d$
 $F = 0$
 $F = 1$


$F(a,b,c,d) = \Sigma m(2,4,6,8, 9,11,14,15)$ realization contd...

Nibble Multiplexer

- A and B are two 4-bit numbers. Design a combinational circuit using suitable multiplexers according to following requirements.

- If $\text{cntrl_ip} == 0$
Output = A
- Else
Output = B

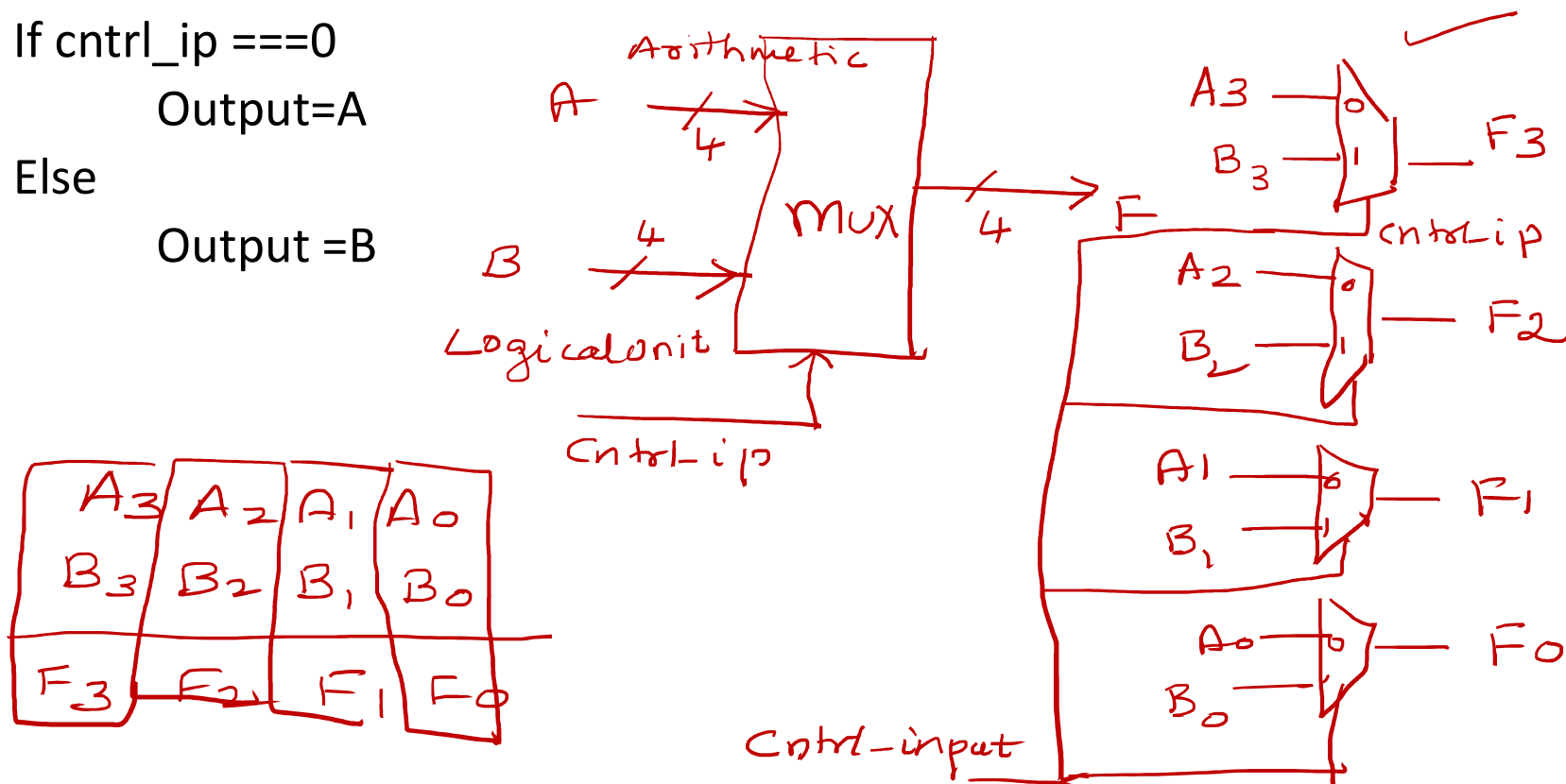


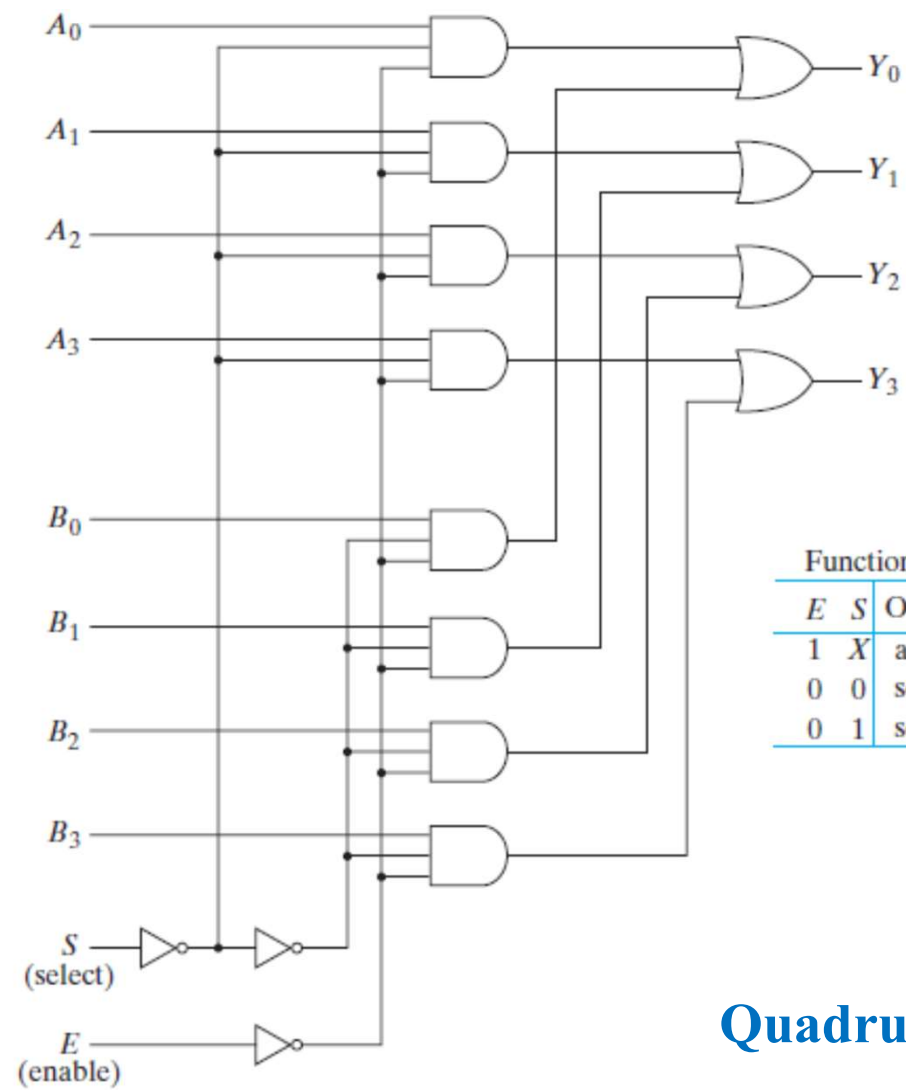

Quadruple 2:1 MUX or Nibble MUX


Multiplexer ICs :

74151- 8:1 MUX

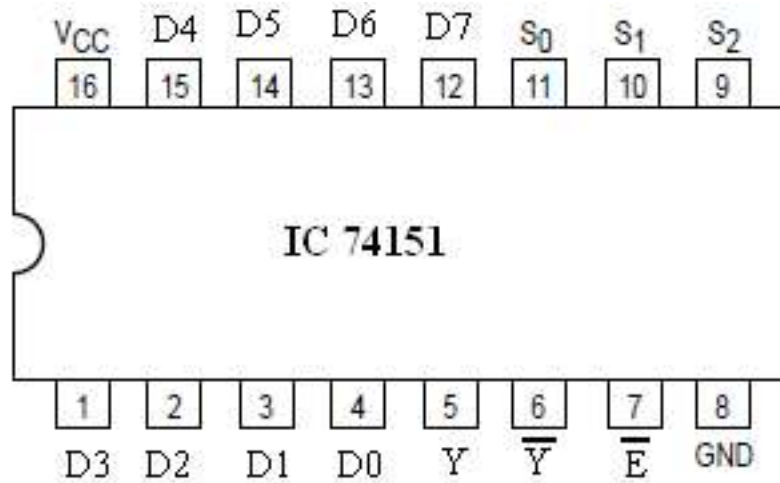



$\overline{E}=0$

74153- 4:1 MUXs

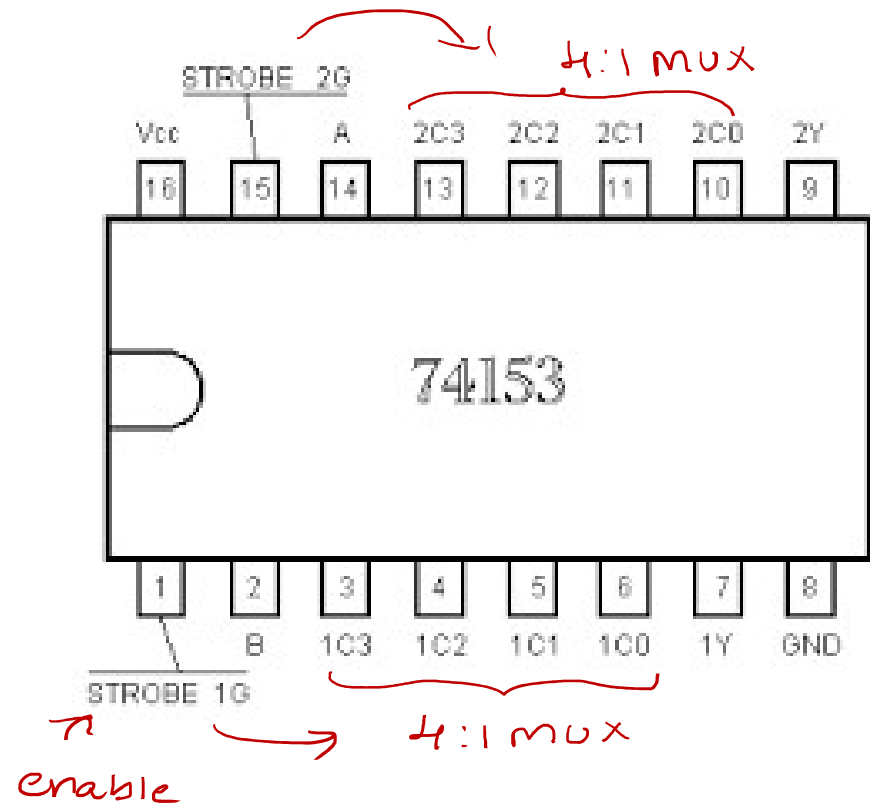

74157 Quad 2:1 MUX IC

4 ,

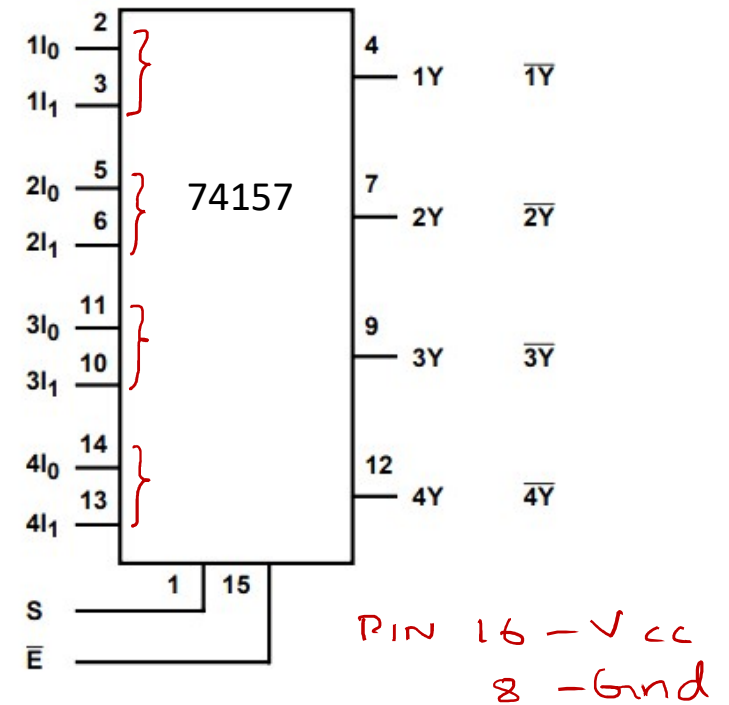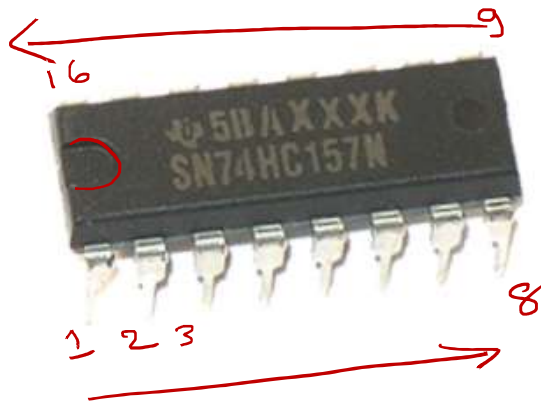

Design a full subtractor using 74153 IC and one external gate.

(a, b, c)

$$D = \sum m(1, 2, 4, 7) \quad B = \sum m(1, 2, 3, 7)$$

Truth Table for Difference (D):


ab	00	01	10	11
c=0	0	1	1	0
c=1	1	0	0	1

$D = C \bar{C} \bar{C} C$

Truth Table for Borrow (B):

ab	00	01	10	11
c=0	0	1	0	0
c=1	1	1	0	1

$B = C \quad 1 \quad 0 \quad C$

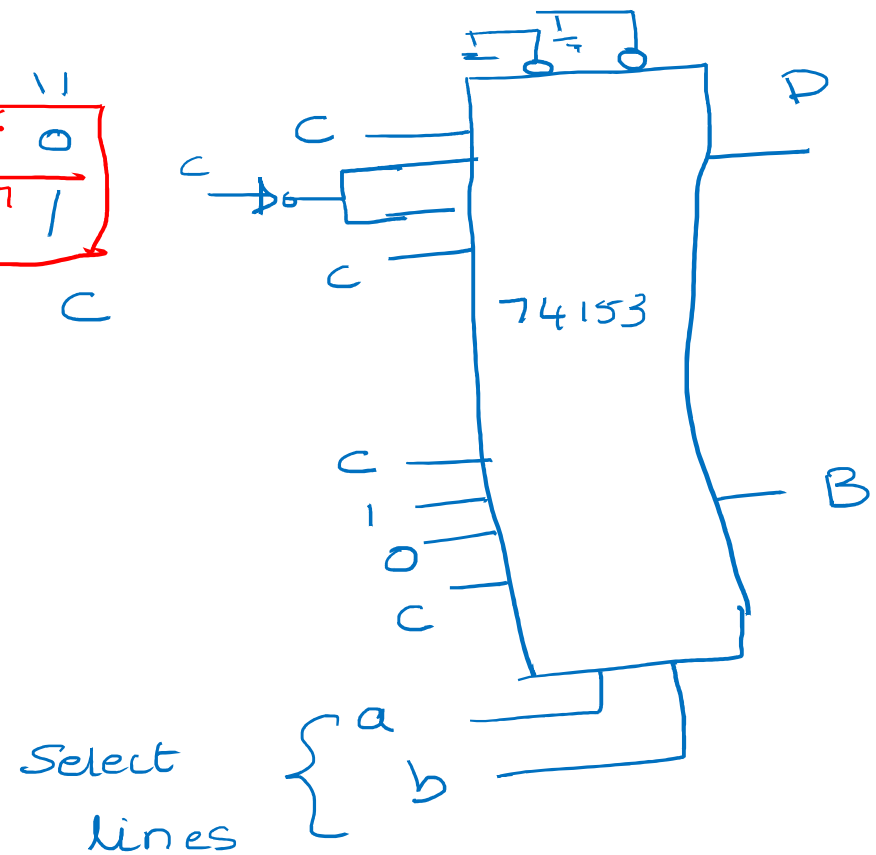

**Full subtractor using 74153 IC and one external gate
contd...**

Design a full adder/ subtractor using 74153 IC and two external gates

if $m = 0$ adder $F = a + b + C_{in} = 0$

else

subtractor $F = a - b$
 ~~$= a + b$~~

$$FA \Rightarrow S = \sum m(1, 2, 4, 7)$$

$$FS \Rightarrow D = \sum m(1, 2, 4, 7)$$

$$C = \sum m(3, 5, 6, 7)$$


$$B = \sum m(1, 2, 3, 7)$$

Full adder/subtractor using 74153 IC and two external gates contd...

Choose bc as selection ^{CP}

bc	00	01	10	11
a=0	0	1	1	0
a=1	1	0	0	1
	a	\bar{a}	\bar{a}	a

Sum/Diff =

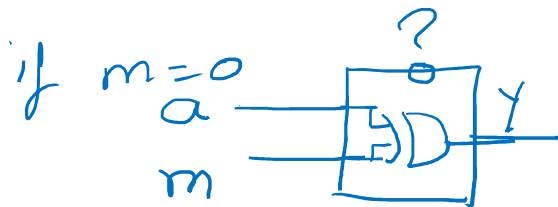

m	a	Y
0	0	0
0	1	1


m	a	Y
1	0	1
1	1	0

bc	00	01	10	11
a=0	0	0	0	1
a=1	0	1	1	1
Carry =	0	a	a	1

bc	00	01	10	11
a=0	0	1	1	1
a=1	0	0	0	1

borrow = \bar{a} \bar{a} 1

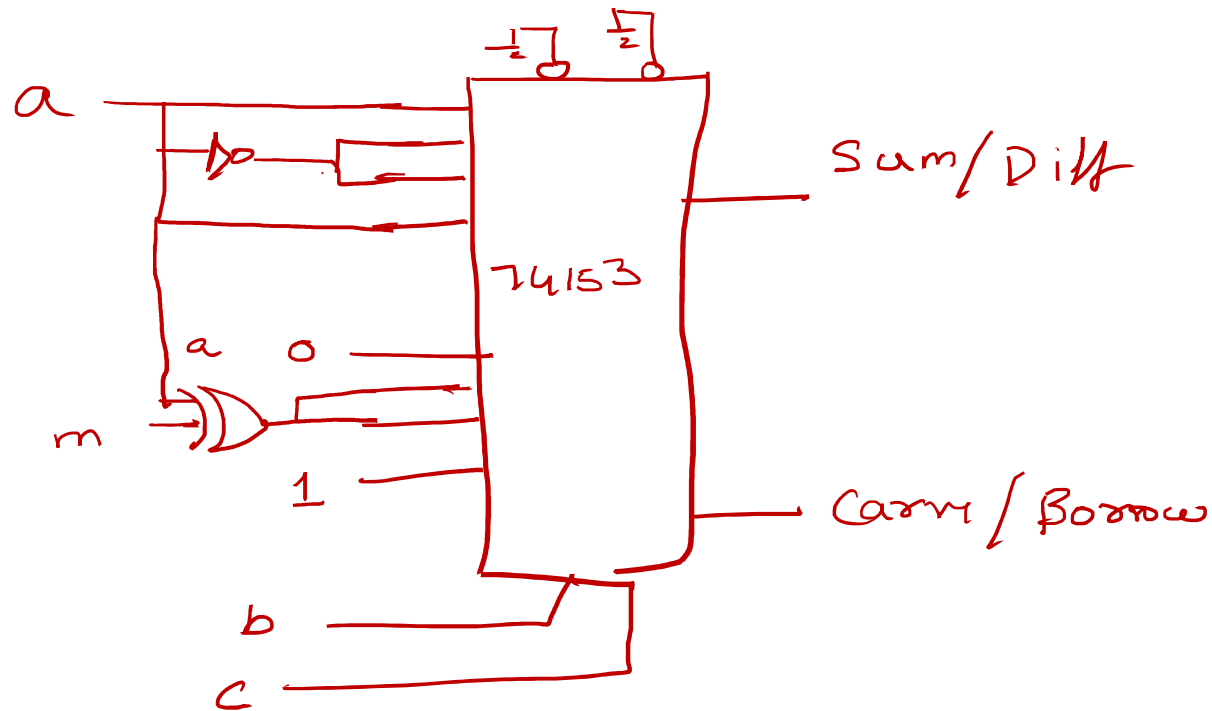Full adder/subtractor using 74153 IC and two external gates contd..



Exercise:

- Realize the Boolean expression $f(w,x,y,z) = \sum m(4,5,7,8,10,12,15)$ using
 - 74151 multiplexer and external gate
 - 74153 IC and external gates
- Refer the prescribed book for additional problems

Question?