

Binary adders and subtractors

- Half adder, full adder, parallel adder
- Half subtractor, full subtractor, parallel subtractor
- Subtraction using complements, parallel adder/subtractor
- Carry Look ahead adder, Decimal adder

Subtraction using complements

 

 

Subtraction.


Az Az Aj Ho 7483IL

4-bit parallel adder/subtractor:


 Design a 4-bit adder/ subtractor using FA blocks or 7483 IC and minimum external gates, i.e. if the control input bit K=0, the circuit should add the input numbers or if K=1, the circuit should subtract the two numbers using 2's complement method.

 Note: Unless and otherwise mentioned assume subtraction to be using 27s complement method.

4-bit parallel adder/subtractor:

 


4-bit parallel adder/subtractor:

 

Carry Look Ahead (CLA) Adder

• Propogation delay in Full Adder is $3T_g$ with respect to following circuit, where T_g is the propagation delay of a gate. All the gates are assumed to have a propagation delay of T_g .

 • Pi is the carry propagate term and Gi is the carry generate term



Ci

Ai

Bi

Pi = Ai ⊕ Bi

rast

Gi = Ai. Bi

+dan 3) 4+3A:

CLA continued



• Carry generation in CLA from Ai, Bi, and Co

Coe input carry

C1 =
$$COP_0 + K_0 = Co(A_0 + B_0) + A_0 + C_0$$

C2 = $C_1P_1 + K_1 = (C_0P_0 + K_0) + K_1$
 $C_2P_1 + K_2 = (C_1P_0 + P_1P_0 + P_$

CLA Continued

• Expressions for sum

Expressions for sum
$$S0 = A B B B C$$

$$S1 = A B B C$$

$$S2 = A B B C$$


$$S3 = A B B C$$

$$C4 = A$$

CLA: Carry look ahead generator circuit


• Draw the combinational circuit to generate C1, C2 and C3 from Pi, Gi and C0 terms.

CLA: Carry look ahead generator circuit

 

Time required to generate C1,C2,C3 in terms of Tg?

4-bit CLA

 

Time required to generate S1,S2,S3,C4 in terms of Tg?

D+2D+D

Comparison

•CLA or CPA...which is better? than

4-1st Cla is 3 fines

4-1st Pipple Carry


4-1st Pipple


BCD addur

Decimal adder: Used to add decimal numbers represented in binary coded form

Decimal adder:

 
• Design a decimal adder to add two, single digit decimal numbers input in 8421 code using 4-bit parallel adder and basic logic gates. Output should



 

BCD ADDER: TRUTH TABLE


Decimal		m	CD Su	BO		Binary Sum				
	S ₁	S ₂	S ₄	S ₈	c	Z ₁	Z ₂	Z_4	Z ₈	k)
0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	1	0	0	0	0
2	0	1	0	0	0	0	1	0	0	0
3	1	1	0	0	0	1	1	0	0	0
4	0	0	1	0	0	0	0	1	0	0
5	1	0	1	0	0	1	0	1	0	0
6	0	1	1	0	0	0	1	1	0	0
7	1	1	1	0	0	1	1	1	0	0
8	0	0	0	1	0	0	0	0	1	0
9	1	0	0	1	$\supset 0$	1	0	0	1	0
10	0	0	0	0	1	0	1	0	1	0
11	1	0	0	0	1	1	1	0	1	0
12	0	1	0	0	1	0	0	1	1	0
13	1	1	0	0	1	1	0	1	1	0
14	0	0	1	0	1	0	1	1	1	0
15	1	0	1	0	1	1	1	1	1	0
16	0	1	1	0	1	0	0	0	0	1
17	1	1	1	0	1	1	0	0	0	1
18	0	0	0	1	1	0	1	0	0	1
19	1	0	0	1	1	1	1	0	0	1

 

BCD ADDER

- Binary sum can be converted to BCD by adding 6 to binary sum.
- 6 needs to be added only when binary sum is > 9 or $(1001)_2$
- Referring the truth table, write the expression for F such that, F=1 if binary sum is > 9
 else F=0

Block diagram of BCD adder

 

1- digit BCD adden B7-134 H7-14 (4-lit broad

Reference:

- Digital design , third edition by morris mano, chapter 4
- . Slides are used only as a supporting material to teach the subject.
- . Students should write down the notes and read the text book.

Questions?