



MANIPAL INSTITUTE OF TECHNOLOGY  
MANIPAL  
*(A constituent institution of MAHE, Manipal)*



# Basic Electrical Technology

[ELE 105 I]

---

***SINGLE PHASE AC CIRCUITS***

*L20 -Resonance*




# Topics covered...

---

- Resonance in series RLC circuit
- What is half power frequency, bandwidth and quality factor in series RLC circuit?
- Resonance in parallel circuits




# Series Resonance

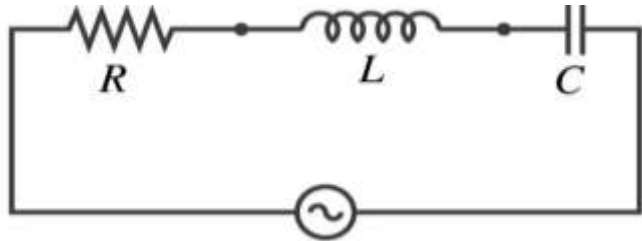

$v(t)$ , variable frequency

$$Z = R + j(X_L \sim X_C)$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

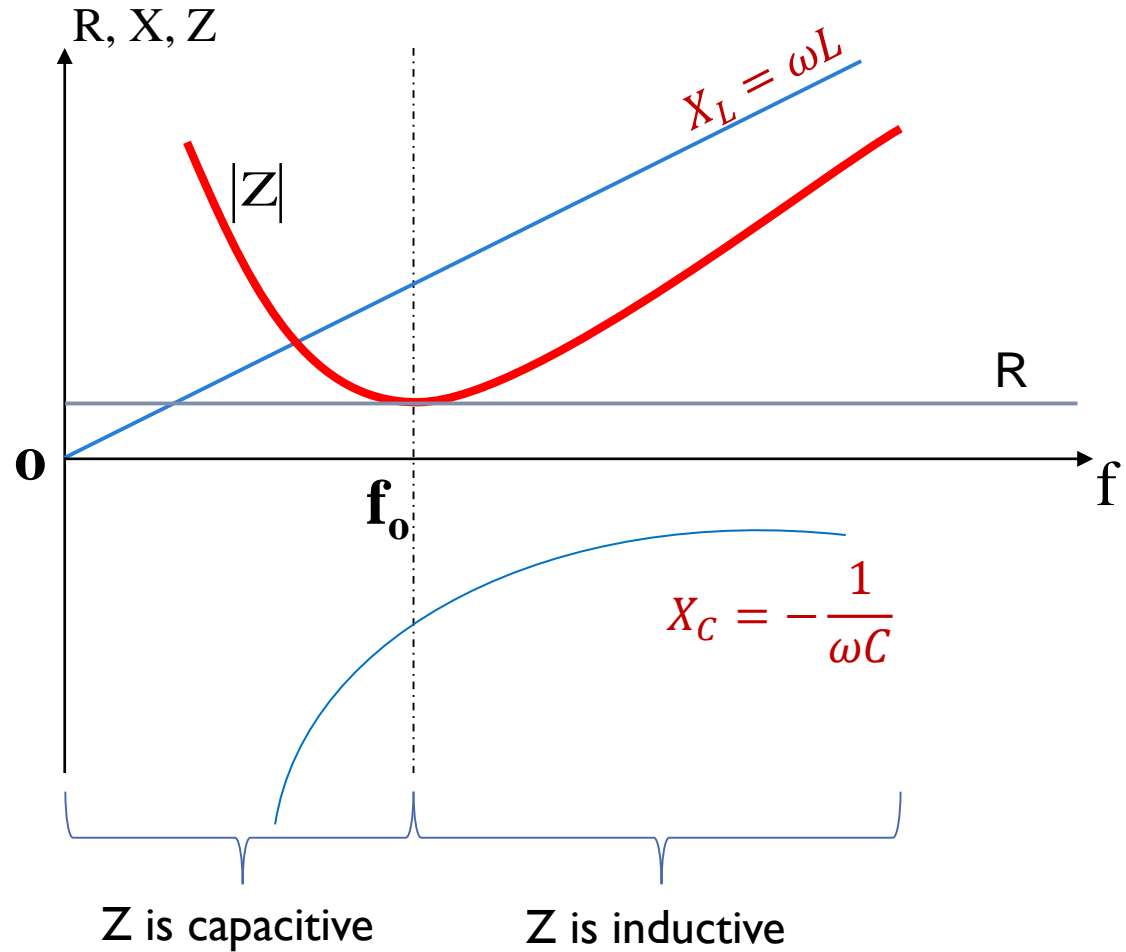

***' $f_0$  is called the resonant frequency'***



# Series Resonance


- **When series RLC circuit is at resonance,**
  - Current is in phase with voltage
  - Circuit power factor is unity
  - $X_L = X_C$
  - $Z = R$
- **Resonant frequency for a series RLC circuit is obtained as follows:**

*Imaginary part of  $Z_{eq} = 0$*

$$X_L = X_C$$

$$\omega_0 L = \frac{1}{\omega_0 C}$$
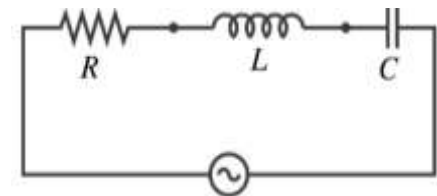
$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ hertz}$$




$v(t)$ , variable frequency

$$Z = R + j(X_L \sim X_C)$$



# Current vs. Frequency in RLC Series Circuit

Variation of current with frequency

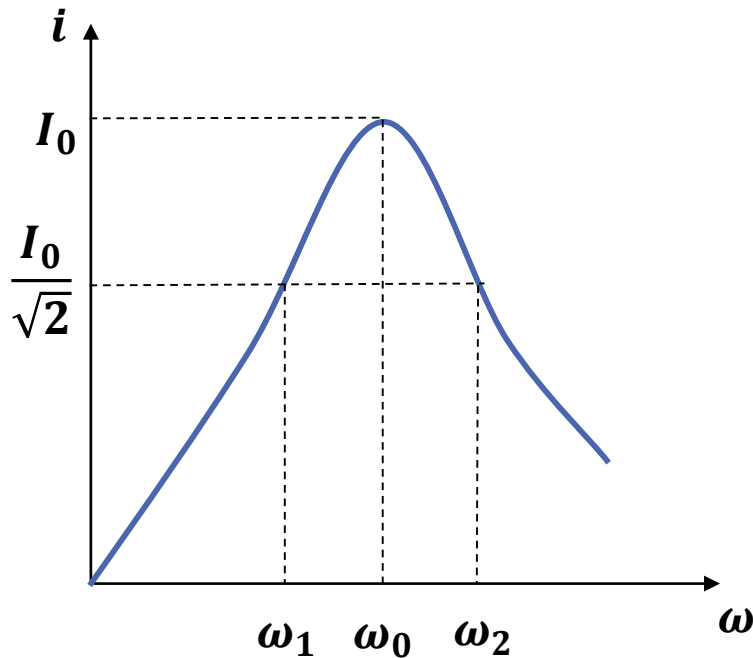

$$I_0 = I_{max} = \frac{V_{rms}}{R}$$

- **Half Power Frequency**

*'Frequency at which the power is half of the power at resonant frequency'*

$$Power = \frac{1}{2} I_0^2 R = \left( \frac{I_0}{\sqrt{2}} \right)^2 R$$

$$At \omega_1 \text{ and } \omega_2, I = \frac{I_0}{\sqrt{2}}$$

$\omega_1$  = Lower half power frequency

$\omega_2$  = Upper half power frequency

$$\text{Bandwidth} = \omega_2 - \omega_1$$

*In practice the curve of  $|I|$  against  $\omega$  is not symmetrical about the resonant frequency*



# Half Power Frequency

$$\text{Impedance at } \omega_1 \text{ and } \omega_2, |Z| = \frac{V_0}{\frac{I_0}{\sqrt{2}}} = \sqrt{2}R$$

Below Resonant frequency  $\omega_0$ ,  $|X_C| > |X_L|$

At  $\omega_1$ ,

$$\sqrt{R^2 + (X_C - X_L)^2} = \sqrt{2}R$$

$$X_C - X_L = R$$

$$\frac{1}{\omega_1 C} - \omega_1 L = R$$

$$\omega_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Above Resonant frequency  $\omega_0$ ,  $|X_L| > |X_C|$

At  $\omega_2$ ,

$$\sqrt{R^2 + (X_L - X_C)^2} = \sqrt{2}R$$

$$X_L - X_C = R$$

$$\omega_2 L - \frac{1}{\omega_2 C} = R$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 \omega_1 = \frac{1}{LC} = \omega_0^2$$

$$\omega_2 - \omega_1 = \frac{R}{L}$$



# Quality Factor for series circuit

- At resonance,  $V_C$  and  $V_L$  can be very much greater than applied voltage

$$|V_C| = |I|X_C = \frac{V \cdot X_C}{\sqrt{R^2 + (X_L - X_C)^2}}$$

At resonance,  $X_L = X_C$

$$V_C = \frac{V}{R} X_C$$

$$V_C = \frac{V}{\omega_0 CR} = QV$$

$$Q = \frac{\text{Resonant frequency}}{\text{Bandwidth}}$$

$$Q = \frac{1}{\omega_0 CR} = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

*Q is termed the Q factor or voltage magnification*

- High value of Q can lead to component damage
- Careful design necessary
- Larger the value of Q, more symmetrical the curve appears about the resonant frequency



# Illustration I

A circuit having a resistance of  $4\Omega$  and inductance of  $0.5H$  and a variable capacitance in series, is connected across a  $100V, 50Hz$  supply. Calculate:

- a) The capacitance to give resonance
- b) The voltages across the inductor and the capacitor
- c) The  $Q$  factor of the circuit

Ans:

$$C = 20.3\mu F$$

$$V_C = V_L = 3930V$$

$$Q = 39.3$$





# Illustration 2

The bandwidth of a series resonant circuit is **500 Hz**. If the resonant frequency is **6000 Hz**, what is the value of  $Q$ ? If  $R = 10 \Omega$ , what is the value of the inductive reactance at resonance? Calculate the inductance and capacitance of the circuit

Ans:




$$Q = 12$$

$$X_L = 120 \Omega$$

$$L = 3.18 \text{mH}; C = 0.22 \mu\text{F}$$



# Resonance in parallel circuits

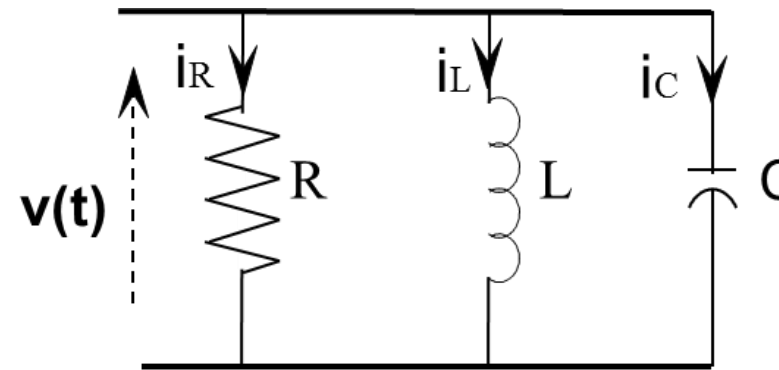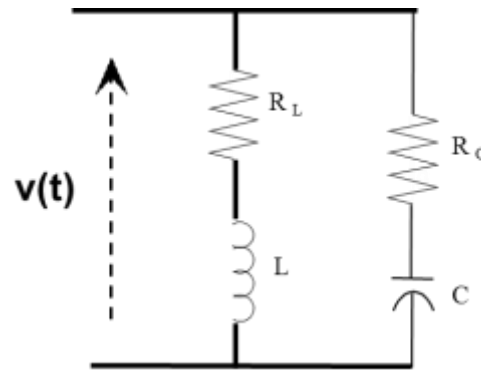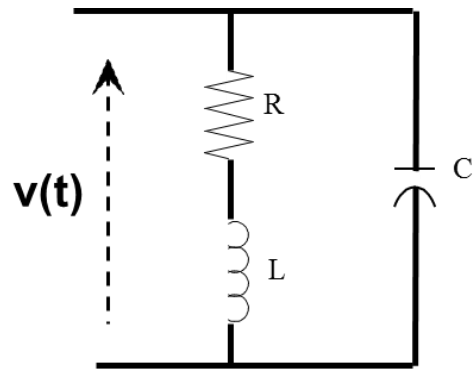


## Steps to obtain the expression of resonant frequency in parallel circuits

- Obtain the net admittance of the circuit
- Equate the imaginary part (susceptance) to zero and obtain the expression of  $\omega_r$

*The expression for resonant frequency depends on circuit configuration*


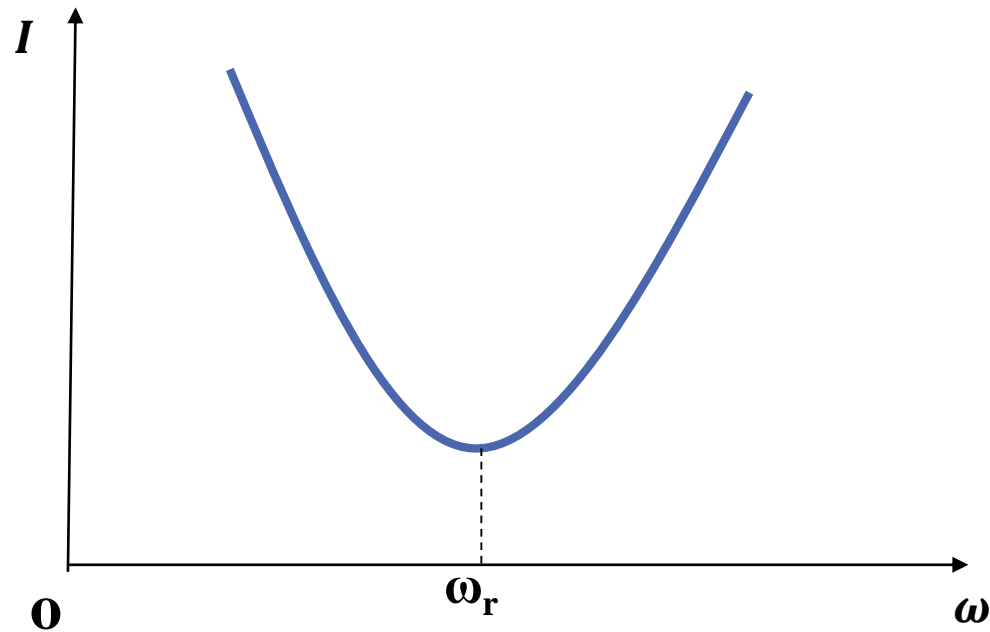
# Current vs. Frequency in parallel Circuits




- At resonance
  - Impedance is maximum
  - Resultant current minimum


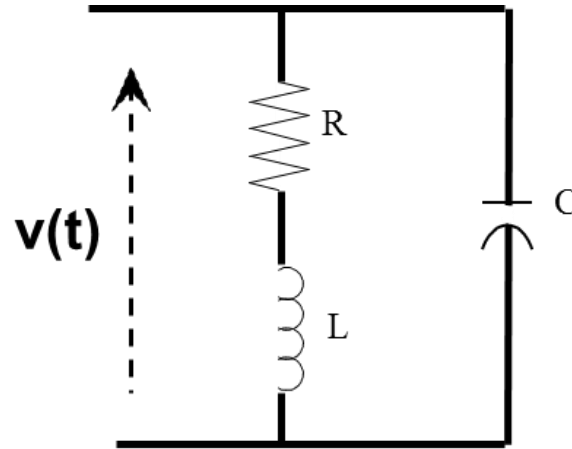
# Illustration I

Obtain the expression for resonant frequency for the given parallel circuit




$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \left(\frac{R}{L}\right)^2}$$


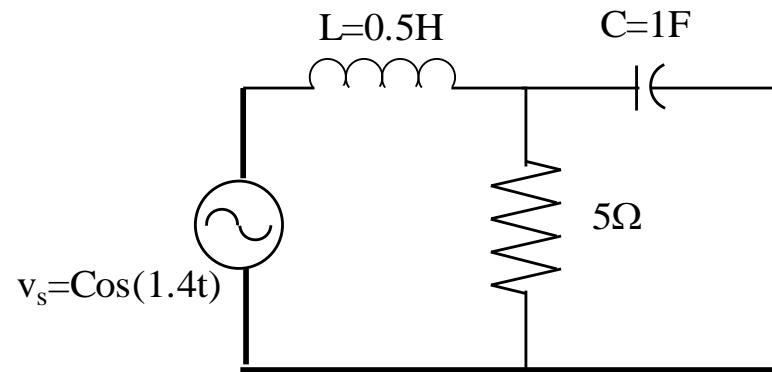
# Illustration 2

Show that circuit given in figure will be at resonance at supply frequency



$$Z = 0.099 \text{ at } \omega = 1.4 \text{ rad/sec}$$