

3 Marks

To count 0 to 4114

MSD

LSD

$\rightarrow 00H \Rightarrow 0000 \quad 0000$

1
2
3
4
5


$$A17 \Rightarrow 01000000$$
$$\boxed{142} \text{ H} \quad \boxed{1000000000}$$

ପ୍ରଥମ ପଦ୍ୟ ଦ୍ୱିତୀୟ ପଦ୍ୟ

when two digits are represented each digit has a - 4-bit representation. (0.5 marks)

for MSD: use 7490 as mod counter
LSD: use 7493 as mod counter

} Both should work together

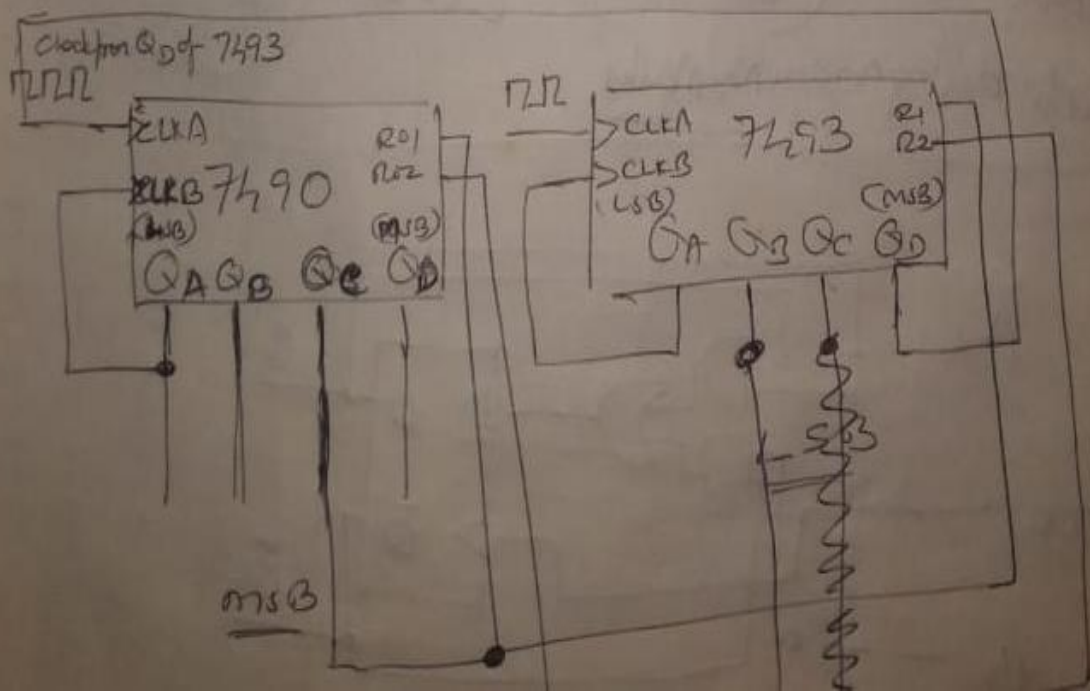

Q4. Function table defines the working of a fictitious AB flip flop. Design the AB flip flop using D flip flop and external gates. **3 Marks**

A	B	Q(t+1)	
0	0	Q'	
0	1	0	
1	0	1	
1	1	Q	

Q4.

A	B	Q(t)	Q(t+1)	D
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	1	1

1/2 marks table

BOO

A	B	Q	Q'
0	0	1	0
0	1	0	1
1	0	1	0
1	1	0	1

$D = \overline{B} \overline{Q} + A Q$

Redundant circles No marks

Correct & correct grouping

Correct

Q5. Design a JK flip flop using a basic NOR latch and gates

Q5 Function table of J-K 1/2 marks

CLK	J	K	Q(t+1)	
0	x	x	Q(t)	No change
1	0	0	Q(t)	No change
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	$\bar{Q}(t)$	Toggle

Function table of S-R Latch
NOR Circuit

Set	Reset	Q(t+1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Invalid	

Excitation Table 1/2 marks

CLK	J	K	Q(t)	Q(t+1)	Set	Reset
0	0	0	0	0	0	x
0	0	0	1	1	x	0
0	0	1	0	0	0	x
0	0	1	1	1	x	0
0	1	0	0	0	0	x
0	1	0	1	1	x	0
0	1	1	0	0	0	x
0	1	1	1	1	x	0
1	0	0	0	0	0	x
1	0	0	1	1	x	0
1	0	1	0	0	0	x
1	0	1	1	0	0	x
1	1	0	0	1	1	0
1	1	0	1	1	x	0
1	1	1	0	1	1	0
1	1	1	1	0	0	1

Table Entry 1/2 marks

Q	Q'	Q	Q'
00	00	01	01
00	01	01	00
01	00	01	01
01	01	01	00
10	00	01	01
10	01	01	00
10	10	01	01
10	11	01	00

Reset 1/2 marks

Set 1/2 marks

Reset $CLK \cdot K \cdot Q$

Set $CLK \cdot J \cdot \bar{Q}$

Circuit 1/2 marks