

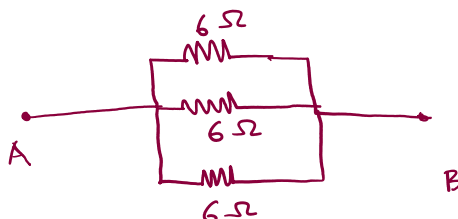


$$R_{eq} = 2.5 \Omega$$

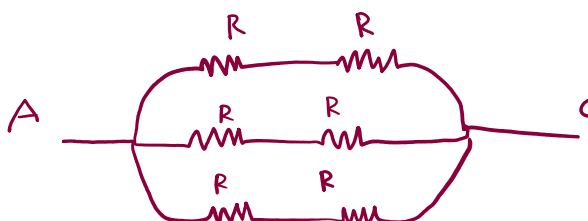

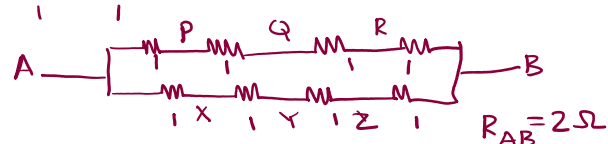
$$R_{AB} = (6 \parallel 6 \parallel 6) = 2 \Omega \quad (R \parallel R/n, R_{eq} = \frac{R}{n+1})$$




$$R_{AC} = \frac{2R}{3} \Omega$$

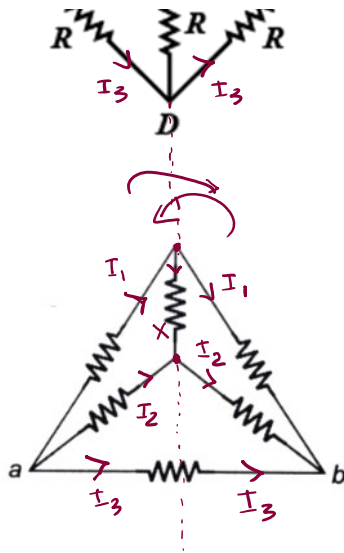- Points on VPS have the same potential
- Branches which are mirror image about the VPS have the same current



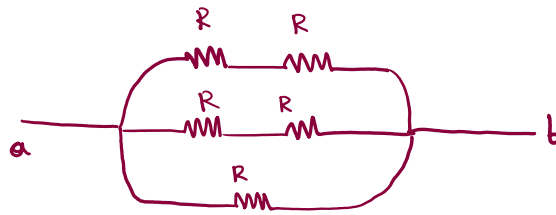Vertical Plane of Symmetry (VPS) or Left-Right Symmetry/Folding
 - Points on VPS have the same potential
 - Branches which are mirror image about the VPS have the same current



$$R_{ab} = \frac{R}{2} \Omega$$

Q1 of Quiz

An inductor and a resistor opposes _____ & _____ respectively


- a) flow of current, rate of change of current
- b) rate of change of current, flow of current ✓
- c) rate of change of current, rate of change of current
- d) flow of current, flow of current

Q2 of Quiz

The source voltage is ____

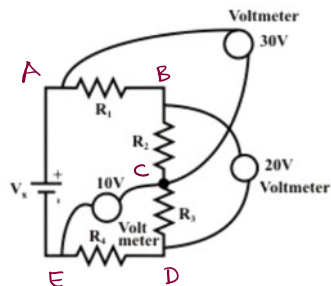- a) 10 V
- b) 20 V
- c) 30 V
- d) 40 V ✓

$$\begin{aligned} V_s &= (V_{AB} + V_{BC}) + (V_{CD} + V_{DE}) \\ &= 30 + 10 \\ &= 40 \text{ V} \end{aligned}$$



Q3 of Quiz

Two incandescent bulbs of 40 W and 60 W ratings are connected in series across the mains. Assuming the voltage rating of both the bulbs to be same, which of the following statement(s) is (are) correct?

- a) The bulbs together will consume 100 W
- b) The bulbs together will consume 50 W
- c) The 60 W bulb glows brighter
- d) The 40 W bulb glows brighter ✓

$$R_{40W} = \frac{V^2}{40} > R_{60W} = \frac{V^2}{60} \text{ as Power} = \frac{\text{Voltage}^2}{\text{Resistance}}$$

When connected in series current flowing through each element is same.



$$\text{Then, } P_{40W} = I^2 R_{40W} > P_{60W} = I^2 R_{60W}$$

So, 40 W bulb will glow brighter.

Q4 of Quiz

Resistors in the following circuit are connected in

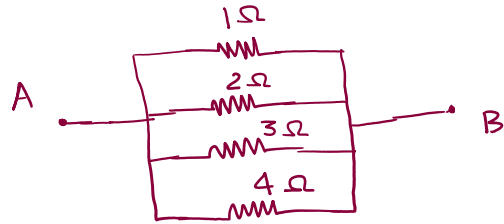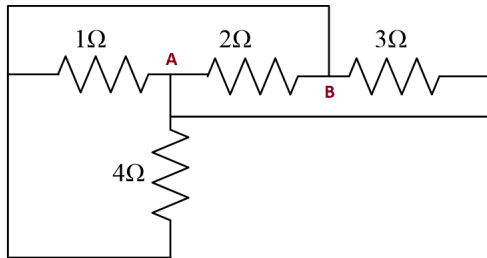- a) Series
- b) Parallel ✓
- c) Combination of series and parallel
- d) None of the above



$$R_{AB} = \frac{1}{\frac{1}{1} + \frac{1}{2} + \frac{1}{3} + \frac{1}{4}}$$

$$R_{AB} = \frac{12}{25} = 0.48 \Omega$$

(Total resistance is less than the least one)