



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)



Basic Electrical Technology

Class 8 – 17 November 2021

- Network Theorems 1

Terminologies Used


- **Linear element:** V-I characteristics is linear. E.g: R, L, C
- **Non-linear element:** V-I characteristics is non-linear. E.g: Diode
- **Bi-lateral element:** Property does not change with direction of operation. E.g: R, L, C
- **Unilateral element:** Property changes with the direction of operation. E.g: Diode
- **Linear Circuit:** Circuit with linear elements only
- **Bi-lateral circuit:** Circuit with bi-lateral elements only.
- **Response:** The output of the network. E.g: current, voltage

Procedure to apply Superposition theorem to solve a DC Circuit

1. Draw the circuit with passive elements only.
2. Place one of the sources in its position.
3. Replace the other sources by their internal resistances.
 - a. Ideal **voltage** source by **short** circuit,
 - b. Ideal **current** source by **open** circuit.
4. Find the response using one of the methods, i.e., network reduction, mesh current, node voltage methods.
5. Repeat the procedure for all the sources.
6. Add the responses due to individual sources.

Illustration 1

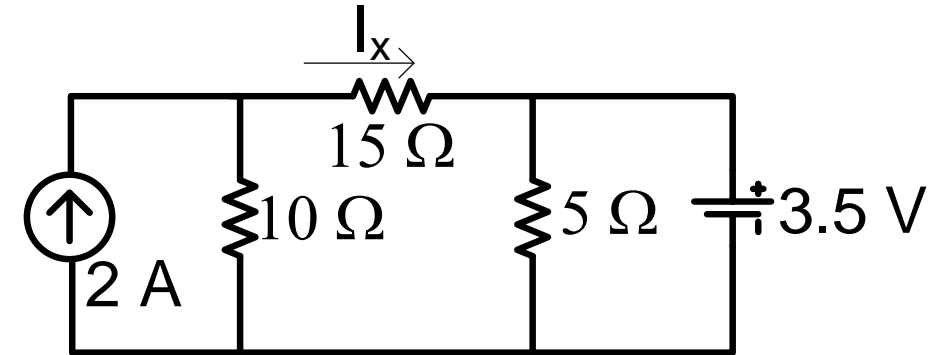
Find the current I_x using Superposition theorem



Ans: $I_x = 660$ mA

Illustration 2

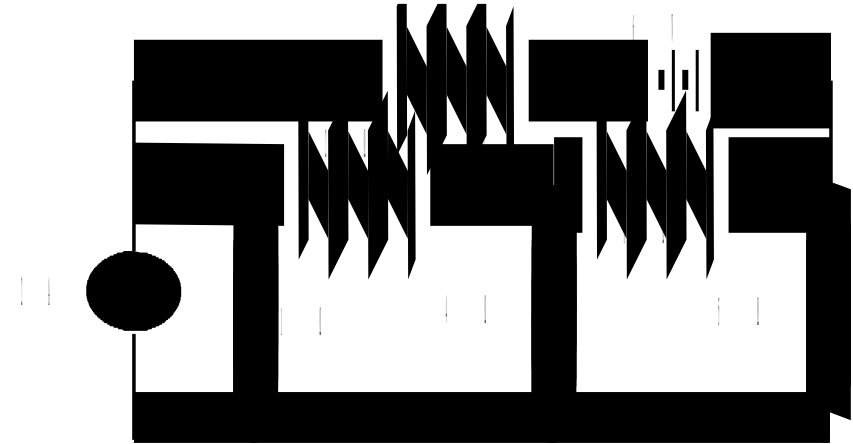Find the current I_0 using Superposition theorem



Ans: $I_0 = -105.078\text{mA}$

Limitations of superposition Theorem

- **Doesn't work for power calculation**

- Involves product of voltage and current,
- the square of current or
- the square of the voltage,
- which are **non-linear** operations

- **cannot be applied for nonlinear circuit**