

# **HARDWIRED APPROACH**

- Control logic is a clocked sequential ckt.
- So conventional sequential ckt design procedure can be applied to build CU.
- Final circuit is obtained by physically connecting gates and flip flops.
- Cost of control logic increases with system complexity.

# 10 steps for hardwired control

- 1) Define task to be performed.
- 2) Propose a trial processing section.
- 3) Provide a reg tx descr algo based on processing section outlined.
- 4) Validate the algo by using trial data.
- 5) Describe the basic char of the HW elements to be used in the processing section.
- 6) Complete the design of the processing section by establishing necessary control points.
- 7) Propose the block diagram of the controller.
- 8) Specify state diagram of controller.
- 9) Specify the char of the HW elements to be used in the controller.
- 10) Complete the controller design and draw a logic diagram of final circuit.


## Step 1: Task definition.

Design a Booth's multiplier to multiply two 4-bit signed numbers.
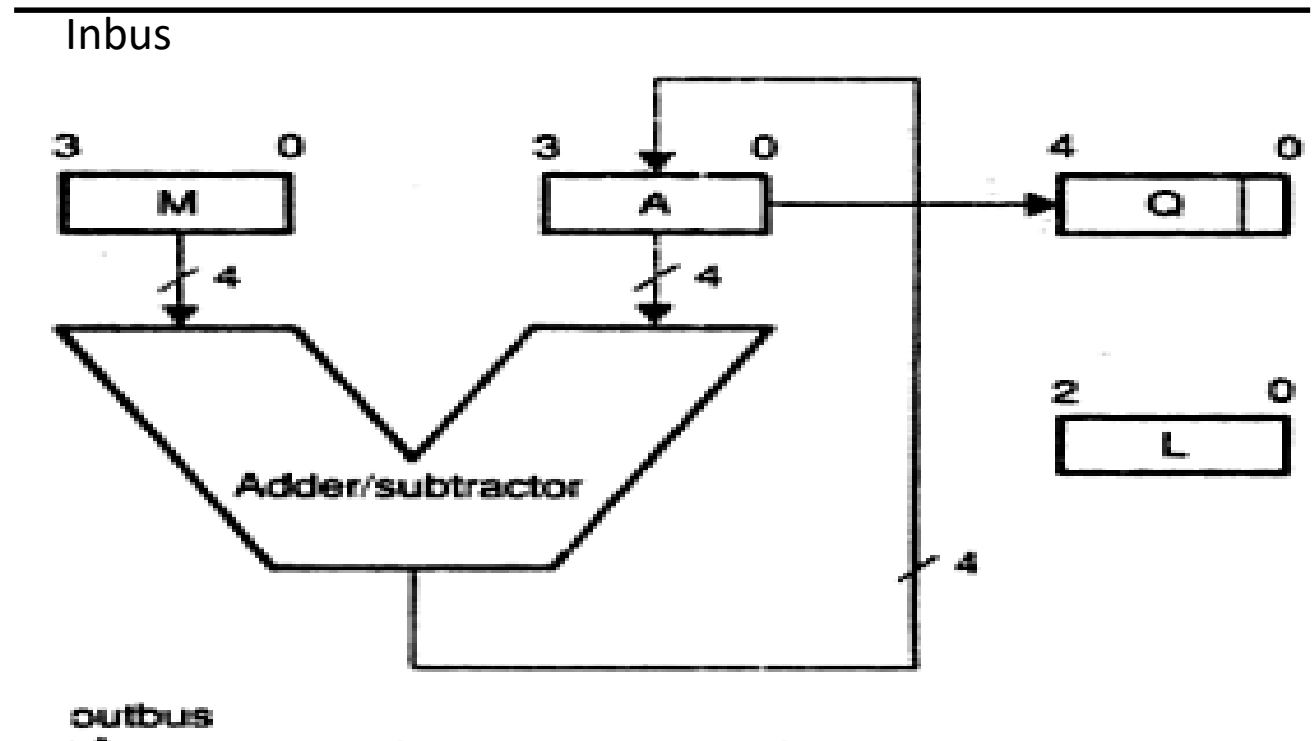
## Step 2: trial processing section.

$q_1 \ q_0$

0 0  $\rightarrow$  none  
0 1  $\rightarrow$  add M  
1 0  $\rightarrow$  sub M  
1 1  $\rightarrow$  None



**Step 3: register transfer description of Booth's multiplier procedure based on the processing section outlined in the previous step.**

## Declare registers A[4], M[4], Q[5], L[3]

## Declare buses Inbus[4], outbus[4]

Start:     $A \leftarrow 0, M \leftarrow \text{inbus}, L \leftarrow 4;$                       clear A and transfer M  
             $Q[4:1] \leftarrow \text{inbus}, Q[0] \leftarrow 0;$                       transfer Q

```

Loop:  if Q[1:0]= 01, then go to ADD
       if Q[1:0]=10, then go to SUB;
       go to Rshift;

```

```
ADD:  A ← A + M;  
      goto Rshift;
```


SUB:  $A \leftarrow A - M;$

```
Rshift:  ASR(AQ), L←L-1;
         if L>0, then go to loop
         outbus =A;
         outbus=Q[4:1];
         go to halt
```

## Step 4: Validate the algo by using trial data.


A	Q	Q <sub>-1</sub>	M	Initial Values		
0000	0011	0	0111			
1001	0011	0	0111	A	A - M	} First Cycle
1100	1001	1	0111	Shift		
1110	0100	1	0111	Shift		} Second Cycle
0101	0100	1	0111	A	A + M	
0010	1010	0	0111	Shift		} Third Cycle
0001	0101	0	0111	Shift		
						} Fourth Cycle
 
## Step 5: Processing section includes GPRs, 4-bit adder / subtractor, Tristate buffers




C	L	R	D	Clock	Action
1	0	0	0	↓	Clear
0	1	0	0	↓	Load external data
0	0	1	0	↓	Right shift
0	0	0	1	↓	Decrement by one
0	0	0	0	↓	No change

a. Storage Register

 

b. Adder-subtractor

Control input	F
1	$l + r$
0	$l - r$

 


c. Tri-state Buffer

Control input	Y
1	X
0	High Z

**Figure 4.17** Characteristics of the Component Parts Used in the Processing Section of the Booth's Multiplier

**Step 6:** The complete design of processing section establishing control points.

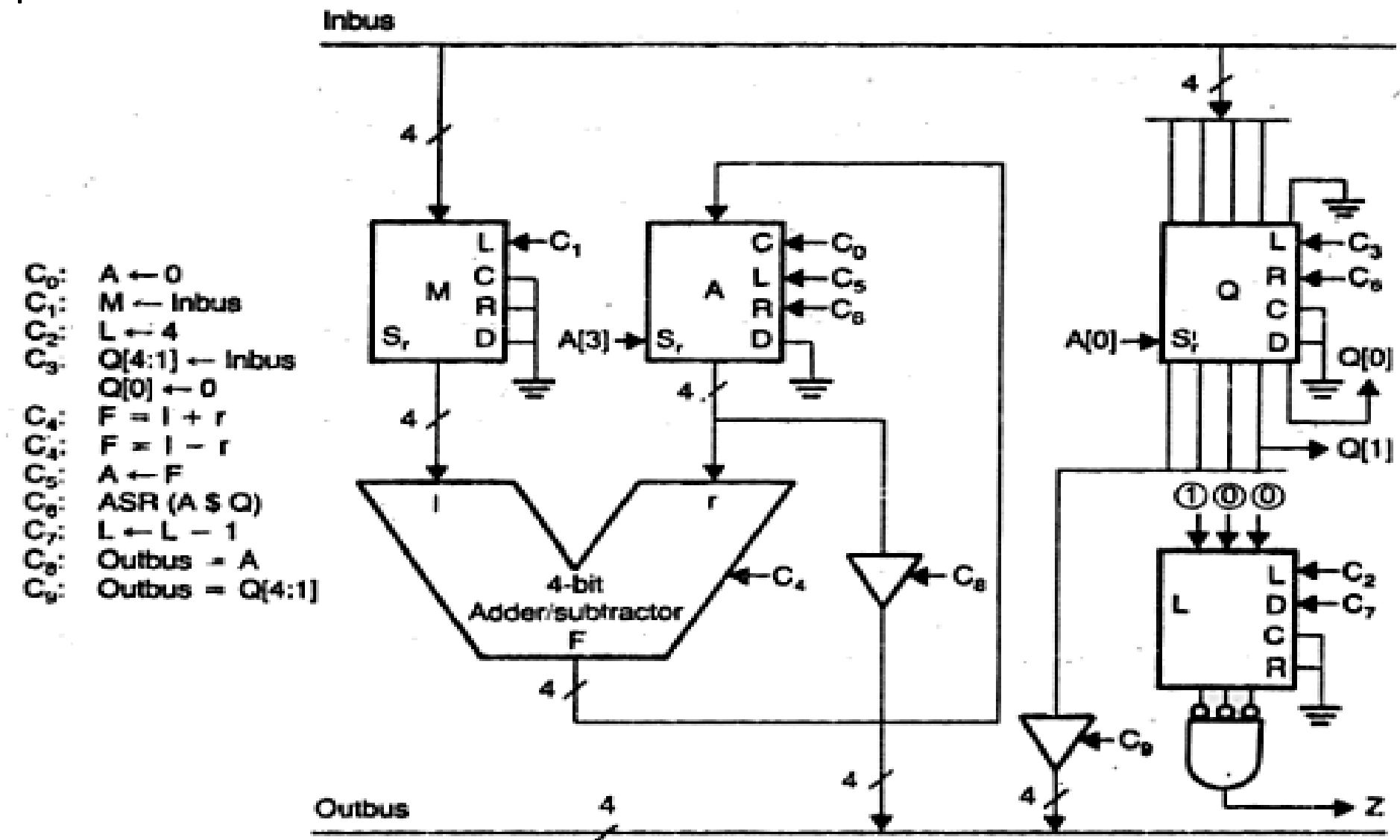


**Figure 4.18** Processing Section of the Booth's Multiplier

## Step 7: Block diagram of controller:

will have 5 i/ps and 10 o/ps.


RESET i/p is used to reset the controller so a new computation can begin.

 CLK is used to synch the controller action for trailing edge of clock pulse.




 
## Step 8: The state diagram of Booth's multiplier controller




a. State Diagram

CONTROL STATE	OPERATION PERFORMED	CONTROL SIGNALS TO BE ACTIVATED
$T_0$	$A \leftarrow 0, L \leftarrow 4, M \leftarrow \text{Inbus}$	$C_0, C_1, C_2$
$T_1$	$Q[4:1] \leftarrow \text{Inbus}, Q[0] \leftarrow 0$	$C_3$
$T_2$	None	None
$T_3$	$A \leftarrow A + M$	$C_4, C_5$
$T_4$	$A \leftarrow A - M$	$C_5$ ( $C_4 = 0$ )
$T_5$	ASR (ASQ), $L \leftarrow L - 1$	$C_6, C_7$
$T_6$	Outbus = A	$C_8$
$T_7$	Outbus = $Q[4:1]$	$C_9$
$T_8$	None	None

 b. Controller Action

**Step 9:** The controller includes a mod -16 counter, a 4: 16 decoder, a sequence controller (SC).

**Step 9:** The controller includes a mod -16 counter, a 4: 16 decoder, a sequence controller (SC).



**a. Block Diagram**


C	L	E	Clock	Action
1	X	X	X	Clear
0	1	X	↓	Load external data
0	0	1	↓	Count up
0	0	0	↓	No operation

**Figure 4.22** Characteristics of the Counter Used in the Controller Design

SC HW, which sequences the controller according to state diagram.

Hence TT for SC must be derived from the controller's state diagram.

**Step 10:** The multiplier controller with its logic diagram

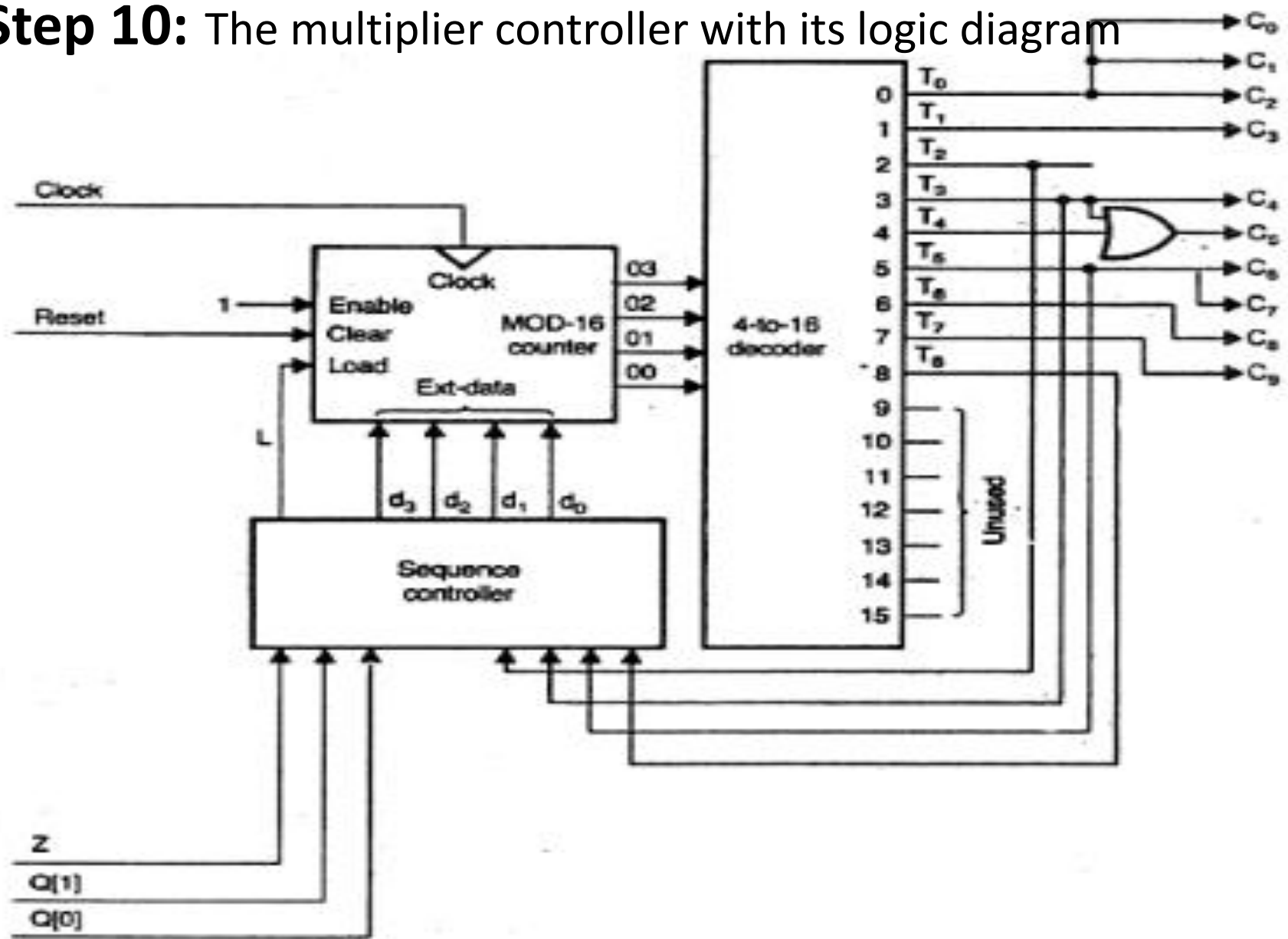

**Figure 4.23** Logic Diagram of the Booth's Multiplier Controller

Z	Q [1]	Q [0]	T <sub>2</sub>	T <sub>1</sub>	T <sub>0</sub>	T <sub>-1</sub>	L	External-data			
								d3	d2	d1	d0
X	0	0	1	X	X	X	1	0	1	0	1
X	1	1	1	X	X	X	1	0	1	0	1
X	1	0	1	X	X	X	1	0	1	0	0
X	X	X	X	1	X	X	1	0	1	0	1
0	X	X	X	X	1	X	1	0	0	1	0
X	X	X	X	X	X	1	1	1	0	0	0

## Implementing SC using PLA:

$$P_0 = Q[1]' Q[0]' T_2$$


$$P_1 = Q[1] Q[0] T_2$$

$$P_2 = Q[1] Q[0]' T_2$$

$$P_3 = T_3$$

$$P_4 = Z' T_5$$

$$P_5 = T_8$$

 

b. PLA Implementation

Figure 4.24 Sequence Controller Design

The PLA o/ps are summerized as

$$L = P0 + P1 + P2 + P3 + P4 + P5$$

$$d3 = P5$$

$$d2 = P0 + P1 + P2 + P3$$

$$d1 = P4$$

$$d0 = P0 + P1 + P3$$

The controller design is completed by relating the control unit (T0-T8) with control i/ps C0-C9 as below:

$$C0 = C1 = C2 = T0$$

$$C3 = T1$$

$$C4 = T3$$

$$C5 = T3 + T4$$

$$C6 = C7 = T5$$

$$C8 = T6$$

$$C9 = T7$$



# CU design using a PLA and D F/Fs


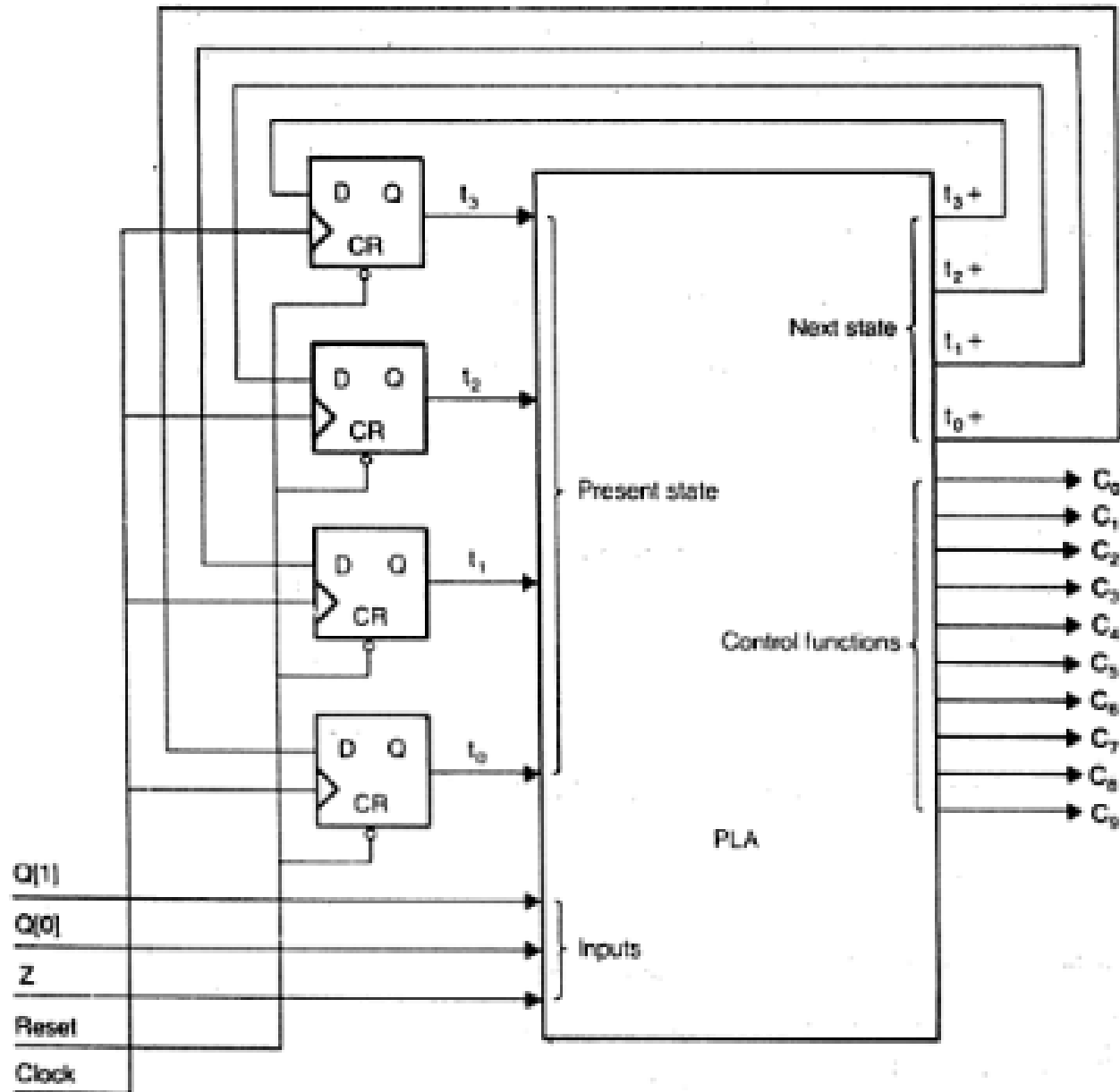


Figure 4.25 Organization of the PLA Control Unit for the Booth's Multiplier

Present state is	PLA Input							PLA Output													
	Present state in binary				Inputs			Next state (in binary)				Control functions									
	$t_3$	$t_2$	$t_1$	$t_0$	Q [1]	Q [0]	Z	$t_3^+$	$t_2^+$	$t_1^+$	$t_0^+$	$C_0$	$C_1$	$C_2$	$C_3$	$C_4$	$C_5$	$C_6$	$C_7$	$C_8$	$C_9$
T <sub>0</sub>	0	0	0	0	X	X	X	0	0	0	1	1	1	1	0	0	0	0	0	0	0
T <sub>1</sub>	0	0	0	1	X	X	X	0	0	1	0	0	0	0	1	0	0	0	0	0	0
T <sub>2</sub>	0	0	1	0	0	1	X	0	0	1	1	0	0	0	0	0	0	0	0	0	0
T <sub>3</sub>	0	0	1	0	0	0	X	0	1	0	1	0	0	0	0	0	0	0	0	0	0
T <sub>4</sub>	0	0	1	0	1	1	X	0	1	0	1	0	0	0	0	0	0	0	0	0	0
T <sub>5</sub>	0	0	1	0	1	0	X	0	1	0	0	0	0	0	0	0	0	0	0	0	0
T <sub>6</sub>	0	0	1	1	X	X	X	0	1	0	1	0	0	0	0	1	1	0	0	0	0
T <sub>7</sub>	0	1	0	0	X	X	X	0	1	0	1	0	0	0	0	0	1	0	0	0	0
T <sub>8</sub>	0	1	0	1	X	X	0	0	0	1	0	0	0	0	0	0	0	1	1	0	0
T <sub>9</sub>	0	1	0	1	X	X	1	0	1	1	0	0	0	0	0	0	0	1	1	0	0
T <sub>10</sub>	0	1	1	0	X	X	X	0	1	1	1	0	0	0	0	0	0	0	0	1	0
T <sub>11</sub>	0	1	1	1	X	X	X	1	0	0	0	0	0	0	0	0	0	0	0	0	1
T <sub>12</sub>	1	0	0	0	X	X	X	1	0	0	0	0	0	0	0	0	0	0	0	0	0

Controller's state table

Figure 4.36 PLA Table

 

**Figure 4.27 PLA Contents**

# Microprogrammed control unit:

Control word: all control signals that can be simultaneously activated are grouped to form the CW.

Micro operation:  $A \leftarrow 0$ ,  $\text{outbus} = A$ , etc..

Each CW contains signals to activate one or more micro operations.

Control memory:

- Control words are held in separate memory called control memory (CM).
- Control words are fetched from CM and individual control fields are routed to various functional units to achieve desired task.


All microinstructions have 2 important fields:

- Control field
- Next address field

Purpose of control field is to indicate which control lines are to be activated.

Purpose of Next address field is to specify the address of the next microinstruction to be executed.
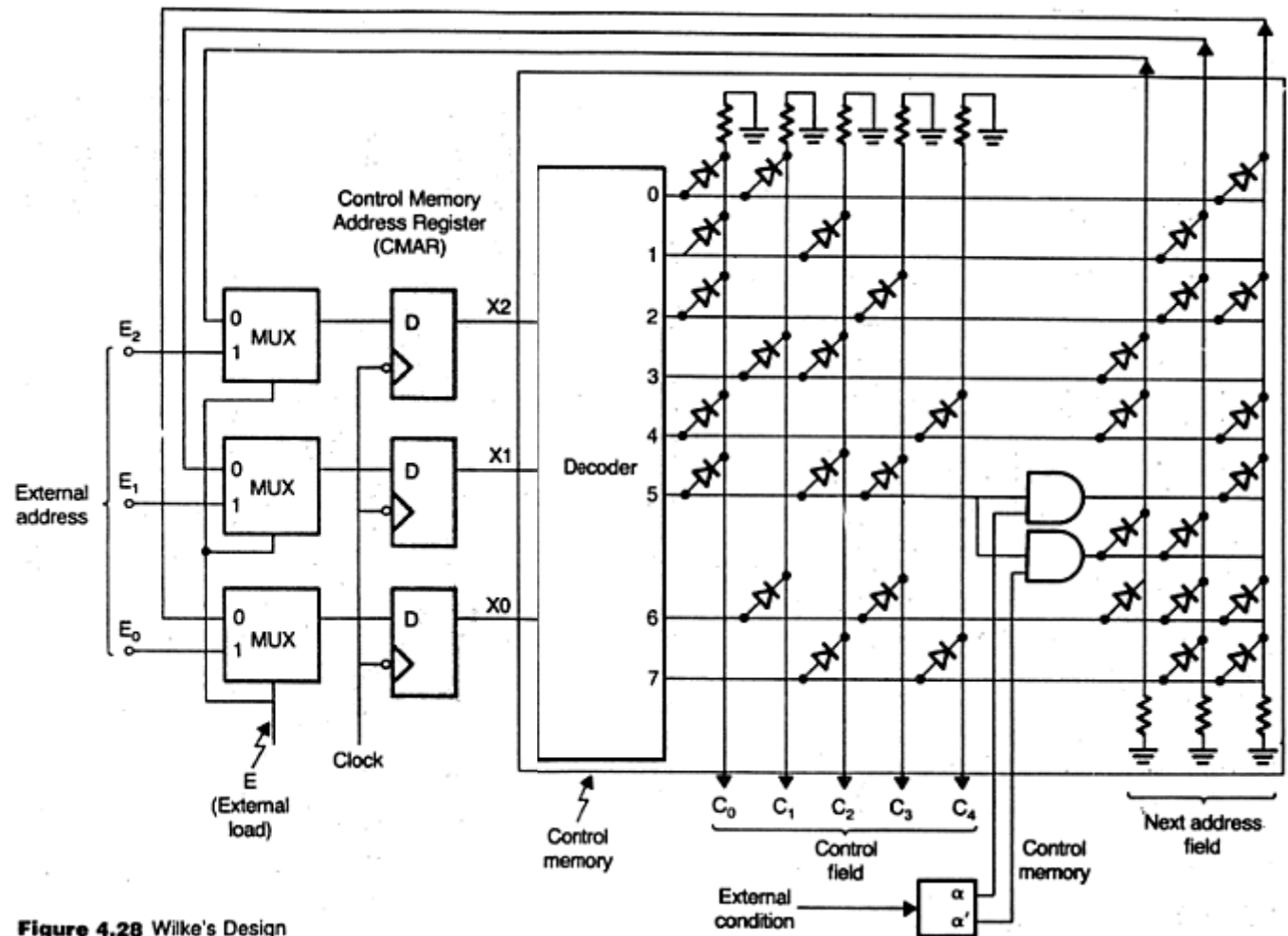
# Wilke's design of microprogrammed control unit



The length of the  $\mu$ instruction is dependent on factors:

- How many  $\mu$ operations will have to be activated simultaneously.
- The method by which the address of next  $\mu$ instruction is specified.

All  $\mu$ operations executed in parallel can be specified in a single  $\mu$ instruction.

This allows short  $\mu$ programs to be written.

If the degree of parallelism increases, then the length of  $\mu$ instruction increases.

Ilrly short  $\mu$ instructions have limited capability in expressing parallelism. The overall length of  $\mu$ program will increase.

Various ways of organizing the control information:

Consider A, B, C, D each communicates with the outbus

C0: outbus=A;

C1: outbus=B;

C2: outbus=C;

C3: outbus=D;




C0	C1	C2	C3
----	----	----	----

C0	C1	C2	C3	
1	0	0	0	Outbus=A
0	1	0	0	Outbus=B
0	0	1	0	Outbus=C
0	0	0	1	Outbus=D
0	0	0	0	NO operation

Here there is no need of decoding the control field.  
This method is known as unencoded format.

The above valid 5 binary patterns also can be represented as

E2	E1	E0	
0	0	0	No operation
0	0	1	Outbus=A
0	1	0	Outbus=B
0	1	1	Outbus=C
1	0	0	Outbus=D

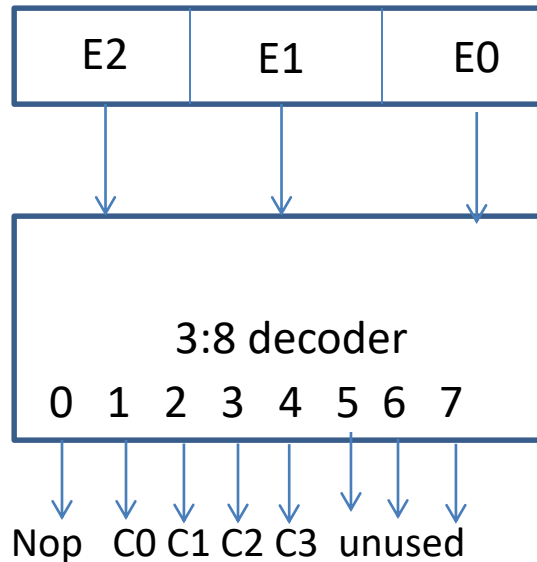

HW: How a 15 control lines can be specified in unencoded and encoded format? What variations you can have?

What is Horizontal and vertical  $\mu$ instr?  
Features?

## **Hardwired approach v/s microprogrammed CU:**


1. Microprogrammed approach is more expensive.
2. Control memory may reduce the overall speed of the machine, since microinstructions retrieval process takes significant amount of time.
3. Microprogramming provides a well structured control organization.
4. With Microprogramming, many additions and changes are made by simply changing the microprogram in Control memory, where as a small change in hardwired approach may lead to redesign the entire system.
5. Microprogrammed approach offers greater flexibility than hardwired since it provides an easy means for altering the contents of CM.

# Architecture of modern microprogrammed control unit:


Next address field from the  $\mu$ instruction can be eliminated. This pointer is referred as microprogram counter (MPC).

MPC is functionally identical to PC.

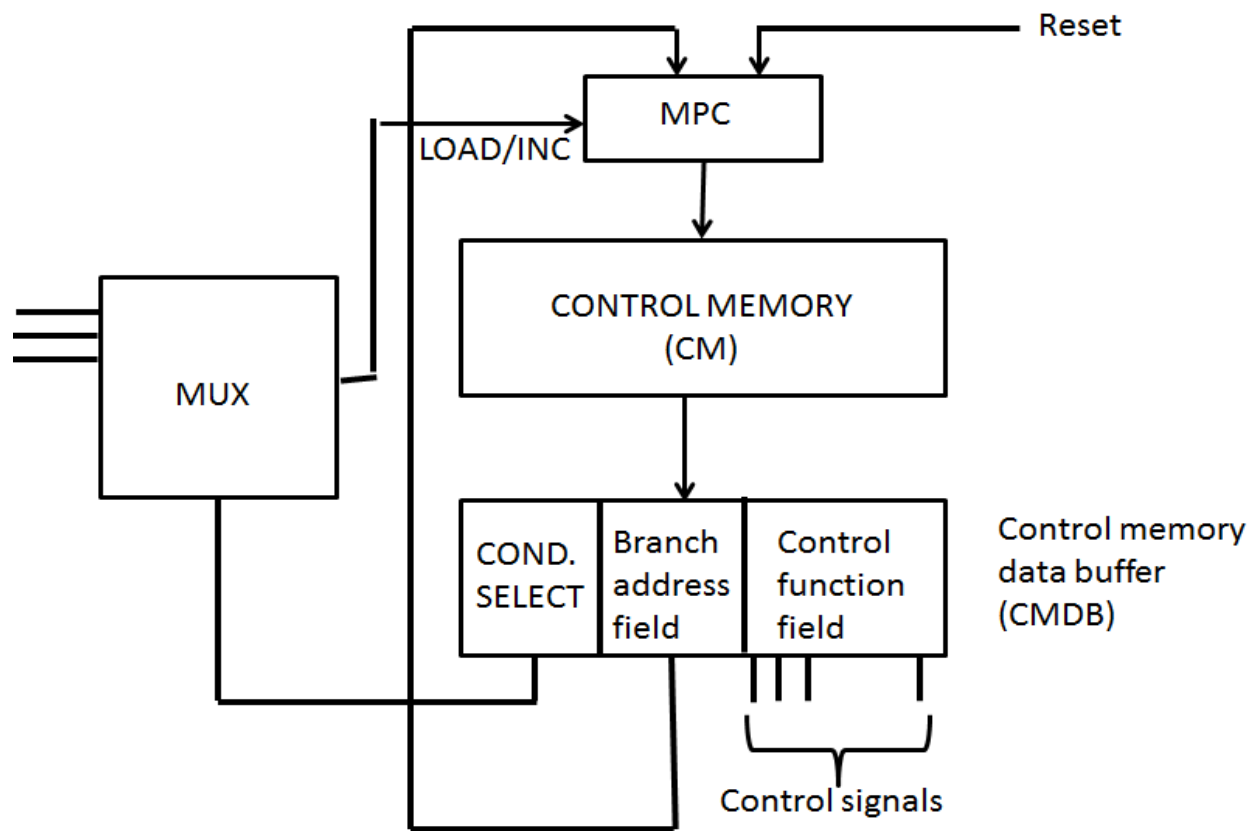
It points to the  $\mu$ instruction to be executed next and incremented after each  $\mu$ instruction fetch.



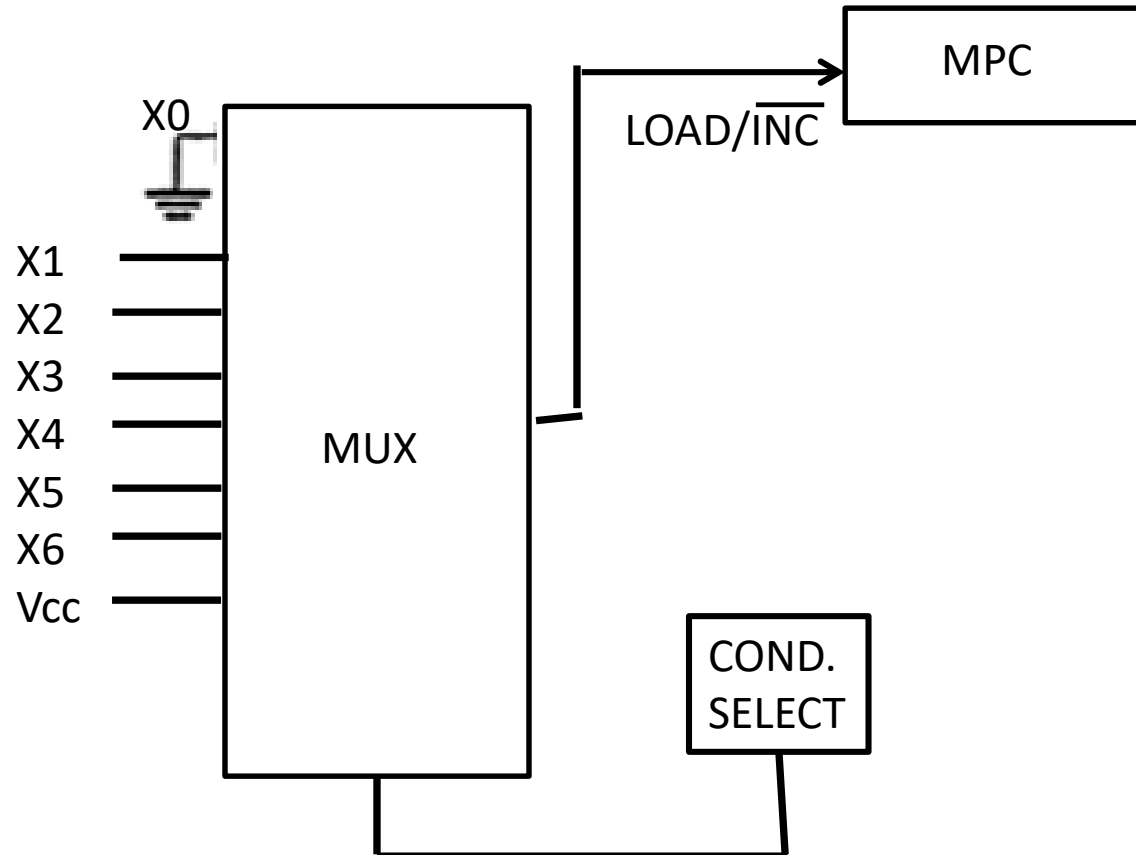Suppose 6 external conditions X1, X2, X3, ..X6 are to be tested. Cond select field and MUX can be organized as:  
If cond sel 000 then MUX o/p 0. MPC incremented. No branch.  
If cond sel 111 MUX o/p 1. Unconditional branching.  
If cond sel 001 MUX o/p is same as value of X1. Now MPC will be loaded with branch addr when X1=1 else it is incremented.



 Writing  $\mu$ program is ltr to writing ALP.  
 $\mu$ programmer must have more thorough knowledge about system archi  
To speedup the development of  $\mu$ code,  $\rightarrow$   $\mu$ assembly language.



These  $\mu$ codes are held in CM.



# Design of $\mu$ programmed CU for 4 X 4 Booth's Multiplier:

STEP1: Write  $\mu$ program in a symbolic form.

Control Mem Addr	Control Word
0	START: $A \leftarrow 0, M \leftarrow \text{Inbus}, L \leftarrow 4;$
1	$Q[4:1] \leftarrow \text{Inbus}, Q[0] \leftarrow 0;$
2	LOOP: If $Q[1:0]=01$ then goto ADD;
3	If $Q[1:0]=10$ then goto SUB;
4	Goto RSHIFT;
5	ADD: $A \leftarrow A+M;$
6	Goto RSHIFT;
7	SUB: $A \leftarrow A-M;$
8	RSHIFT: $\text{ASR}(A\$Q), L \leftarrow L-1;$
9	If $Z=0$ then goto LOOP
10	outbus=A;
11	outbus= $Q[4:1];$
12	HALT: Goto HALT

CM holds 13 words, requiring a 4-bit branch address field.

STEP2:  $Q[1]Q[0]=01$

$Q[1]Q[0]=10$  and  $Z=0$  are checked. These cond are applied as i/ps to cond sel MUX.

MUX must have atleast 5 data i/ps and 8:1 data selector.

3-bit cond sel field is used to encode 5 diff cond:

### Cond Select Field

0 0 0

0 0 1

0 1 0

0 1 1

1 0 0

### Action Taken

No branching

Branch if  $Q[1]Q[0]=01$

Branch if  $Q[1]Q[0]=10$


Branch if  $Z=0$

Unconditional branch

Size of CW is

$$\begin{aligned} &= \text{Size of Cond sel field} + \text{Size of branch field} + \text{No of functions} \\ &= 3 + 4 + 10 \\ &= 17 \text{ bits} \end{aligned}$$

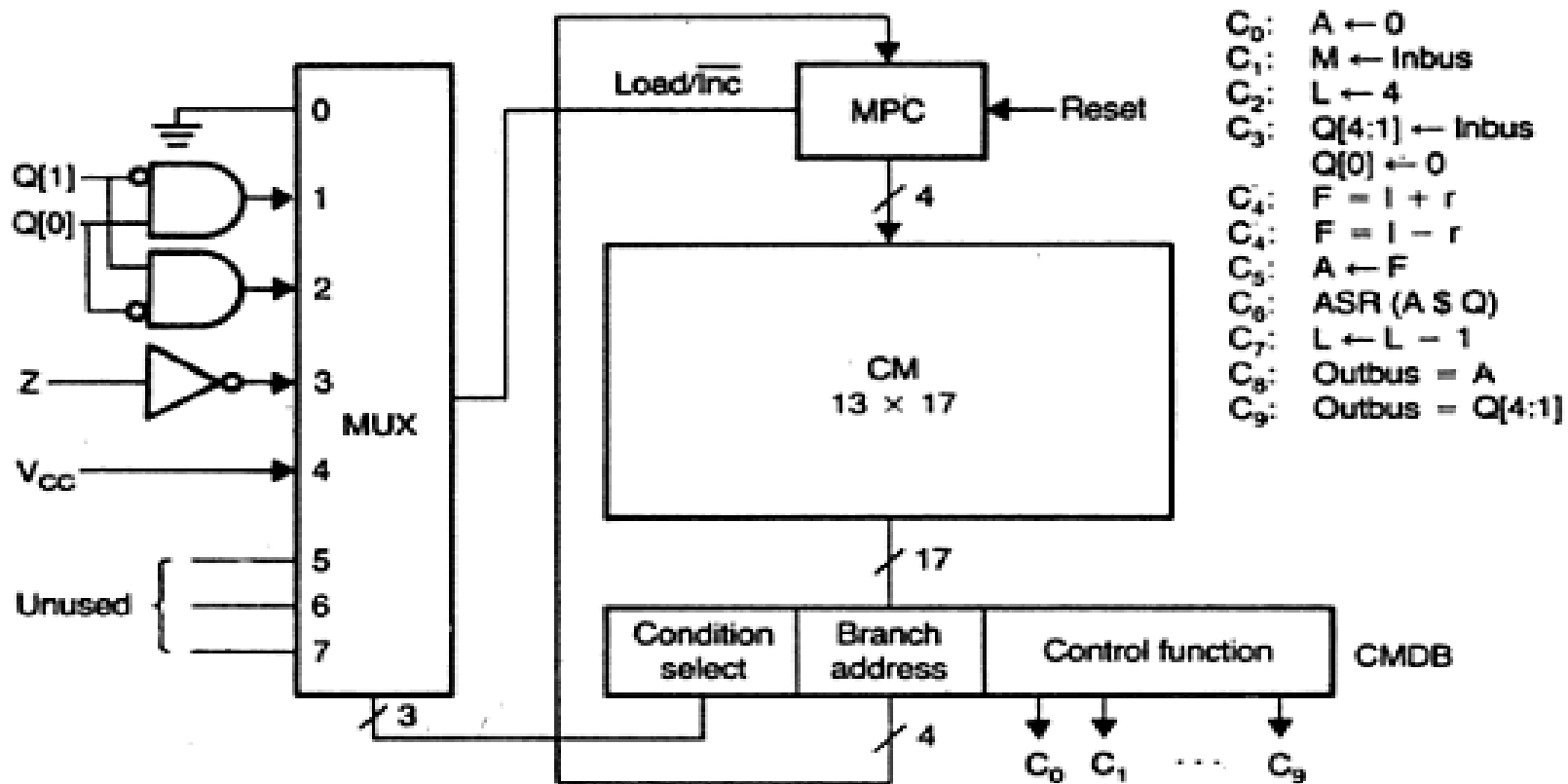Size of CMDB is 17 bits and CM is  $13 \times 17 = 221$ bits



ROM ADDRESS		CONTROL WORD											
In Dec	In Binary	COND SELECT	BRANCH ADDRESS	CONTROL FUNCTION									
				C0	C1	C2	C3	C4	C5	C6	C7	C8	C9
0	0 0 0 0	0 0 0	0 0 0 0	1	1	1	0	0	0	0	0	0	0
1	0 0 0 1	0 0 0	0 0 0 0	0	0	0	1	0	0	0	0	0	0
2	0 0 1 0	0 0 1	0 1 0 1	0	0	0	0	0	0	0	0	0	0
3	0 0 1 1	0 1 0	0 1 1 1	0	0	0	0	0	0	0	0	0	0
4	0 1 0 0	1 0 0	1 0 0 0	0	0	0	0	0	0	0	0	0	0
5	0 1 0 1	0 0 0	0 0 0 0	0	0	0	0	1	1	0	0	0	0
6	0 1 1 0	1 0 0	1 0 0 0	0	0	0	0	0	0	0	0	0	0
7	0 1 1 1	0 0 0	0 0 0 0	0	0	0	0	0	1	0	0	0	0
8	1 0 0 0	0 0 0	0 0 0 0	0	0	0	0	0	0	1	1	0	0
9	1 0 0 1	0 1 1	0 0 1 0	0	0	0	0	0	0	0	0	0	0
10	1 0 1 0	0 0 0	0 0 0 0	0	0	0	0	0	0	0	0	1	0
11	1 0 1 1	0 0 0	0 0 0 0	0	0	0	0	0	0	0	0	0	1
12	1 1 0 0	1 0 0	1 1 0 0	0	0	0	0	0	0	0	0	0	0

Binary listing of  $\mu$ program for 4 X 4 Booth's Multiplier